

ESERCIZIO 1

$$A(f) = -\frac{1}{j2\pi fRC}$$

$$|A(f)| = k \Rightarrow \frac{1}{2\pi f_0 RC} = k \Rightarrow B = \frac{1}{2\pi k f_0 C}$$

ESERCIZIO 2


$$A(f) = -A_1 \frac{j \frac{f}{f_{P1}} \left(1 + j \frac{f}{f_2}\right)}{\left(1 + j \frac{f}{f_{P1}}\right) \left(1 + j \frac{f}{f_2}\right)}$$

$$A_1 = 1 + \frac{R_2}{R} \quad (A_0 = -1)$$

$$f_{P1} = \frac{1}{2\pi R_1 C_1}$$

$$f_2 = \frac{1}{2\pi R_2 C_2}$$
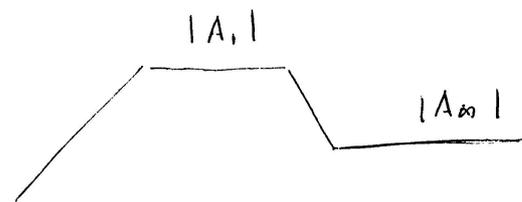
$$f_2 = \frac{1}{2\pi C_2 (R_2 \parallel R)}$$



3/1

$$I_C \approx I_C + I_B = \frac{V^+}{2R_C}$$

$$V_{CE} = V^+ - (R_C + R_E) I_C =$$

$$I_B = \text{(della corrente)} = I_D$$

$$V_{GS} = \sqrt{\frac{2I_D}{\beta}} + V_T$$

$$R_2 = (R_1 + R_2) \frac{V_{GS}}{V^+}$$

$$R_1 = R_T - R_2 =$$


$$V_{DS} = V_{CE} - V_f > V_{GS} - V_T$$

$$g_m = \beta (V_{GS} - V_T) =$$

$$h_{fe} =$$

$$h_{re} = r_{bb'} + \frac{V_T}{I_C} h_{fe}$$

$$R_G = R_1 \parallel R_2$$

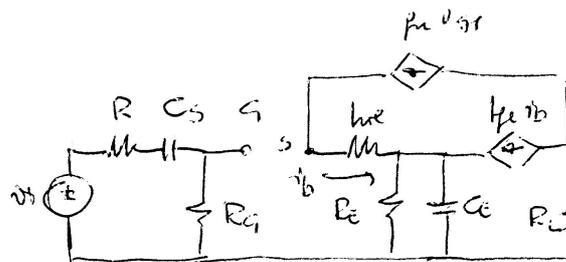

3/2

$$v_u = -R_c (h_{fe} + 1) i_b = -R_c (h_{fe} + 1) g_m v_{gs}$$

$$v_{gs} = \frac{R_B}{R + R_B} v_i - [h_{re} + R_E (h_{fe} + 1)] g_m v_{gs}$$

$$v_{gs} \left[1 + g_m [h_{re} + R_E (h_{fe} + 1)] \right] = \frac{R_B}{R + R_B} v_i$$

$$\left. \frac{v_u}{v_i} \right|_{C_E \rightarrow \text{short}} = - \frac{R_B}{R + R_B} \frac{R_c (h_{fe} + 1) g_m}{1 + g_m [h_{re} + R_E (h_{fe} + 1)]} =$$

$$\left. \frac{v_u}{v_i} \right|_{C_E \text{ disconnected}} = - \frac{R_B}{R + R_B} \frac{R_c (h_{fe} + 1) g_m}{1 + g_m h_{re}} =$$

$$f_{P_{C_E}} = \frac{1}{2\pi C_E (R + R_E)} =$$

$$R_{i_{C_E}} = R_E \parallel \frac{h_{re} + \frac{1}{g_m}}{(h_{fe} + 1)} =$$

$$f_{P_{C_E}} = \frac{1}{2\pi C_E R_{i_{C_E}}} =$$

$$f_{2_{C_E}} = \frac{1}{2\pi R_E C_E} =$$

3/3

$$A(\omega) = A_{CB} \frac{j \frac{\omega}{f} \left(1 + j \frac{\omega}{f_2} \right)}{\left(1 + j \frac{\omega}{f_{p1}} \right) \left(1 + j \frac{\omega}{f_{p2}} \right)}$$

$$|A(\omega)| = \frac{|A_{CB}|}{\sqrt{2}} \Rightarrow \frac{1}{2} = \frac{\left(\frac{\omega}{f} \right)^2 \left(1 + \frac{\omega^2}{f_2^2} \right)}{\left(1 + \frac{\omega^2}{f_{p1}^2} \right) \left(1 + \frac{\omega^2}{f_{p2}^2} \right)}$$

$$\Rightarrow \omega^4 \left(\frac{1}{f_{p1}^2 f_{p2}^2} - \frac{2}{f^2 f_2^2} \right) + \omega^2 \left(\frac{1}{f_{p1}^2} + \frac{1}{f_{p2}^2} - \frac{2}{f^2} \right) + 1 = 0$$

da cui le soluzioni

$$0) \quad R_{VCL} = R_C \Rightarrow f_H = \frac{1}{2\pi R_C C_L} \Rightarrow C_L = \frac{1}{2\pi R_C f_H}$$

$$1) \quad R_{VCR} = (R \parallel R_0) + R_D \left[\left(\frac{1}{\mu+1} \right) \frac{g_m (R \parallel R_0)}{1 + g_m R_D} + 1 \right]$$

(CR fornisce anche una via)

ESERCIZIO 4

ok

R

$$A_1 = + \frac{h_{fe} R_c}{h_{ie} + R_B} \frac{R_E \parallel \frac{h_{ie} + R_c}{h_{fe} + 1}}{R_i + \left(R_E \parallel \frac{h_{ie} + R_c}{h_{fe} + 1} \right)}$$

$$A_2 = \frac{-h_{fe} R_c}{R_o + h_{ie} + (R_E \parallel R_i)(h_{fe} + 1)}$$

$$A_c = A_1 + A_2 =$$

$$A_d = 0.5 (A_1 - A_2) =$$

$$|K| = \left| \frac{A_d}{A_c} \right| \quad (\text{dB})$$