
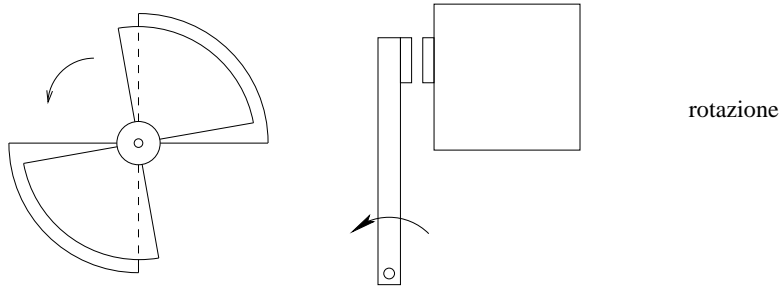


Sensori e trasduttori - figure e formule matematiche.
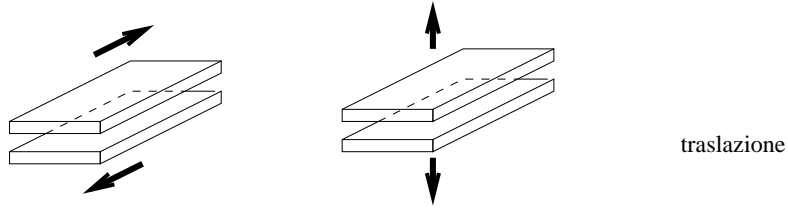
$$C = \varepsilon \frac{A}{d} \quad (1)$$



variazione di A

variazione di d

Figura 3.1

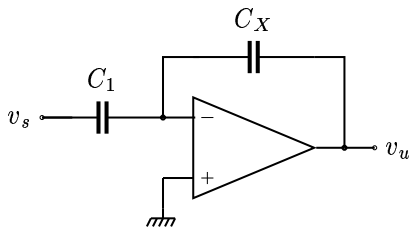


Figura 3.2

$$v_u = -\frac{Z_X}{Z_1} v_s = -\frac{C_1}{C_X} v_s \quad (2)$$

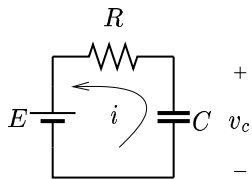


Figura 3.3

$$q = C v_C = \varepsilon \frac{A}{x} v_C \quad (3)$$

$$q \simeq q_0 + \left. \frac{\delta q}{\delta x} \right|_{x_0, v_{C0}} \Delta x + \left. \frac{\delta q}{\delta v_C} \right|_{x_0, v_{C0}} \Delta v_C \quad (4)$$

con

$$q_0 = \varepsilon \frac{A}{x_0} E, \quad \left. \frac{\delta q}{\delta x} \right|_{x_0, v_{C0}} = -\varepsilon \frac{A}{x_0^2} E \quad \text{e} \quad \left. \frac{\delta q}{\delta v_C} \right|_{x_0, v_{C0}} = \varepsilon \frac{A}{x_0}. \quad (4')$$

$$q \simeq \varepsilon \frac{A}{x_0} E + \varepsilon \frac{A}{x_0} \left(\Delta v_C - \frac{E}{x_0} \Delta x \right) \quad (5)$$

$$i = \frac{dq}{dt} = \varepsilon \frac{A}{x_0} \left(\frac{dv_C}{dt} - \frac{E}{x_0} \cdot \frac{dx}{dt} \right). \quad (6)$$

Essendo, per le variazioni, $Ri = -v_c$,

$$i = \varepsilon \frac{A}{x_0} \left(-R \frac{di}{dt} - \frac{E}{x_0} \cdot \frac{dx}{dt} \right) \quad (6')$$

$$I(s) \left(1 + R\varepsilon \frac{A}{x_0} s \right) = -\varepsilon \frac{A}{x_0^2} E s X(s) \quad (7)$$

$$W(s) = R \frac{I(s)}{X(s)} = -\frac{\varepsilon \frac{A}{x_0^2} E s}{1 + R\varepsilon \frac{A}{x_0} s} = -\frac{ks}{1 + \tau s} \quad (8)$$

con

$$k = \varepsilon \frac{A}{x_0^2} E, \quad \tau = R\varepsilon \frac{A}{x_0} \quad \left(f_p = \frac{1}{2\pi\tau} \right).$$

$$W(s) \simeq -ks \quad (8')$$

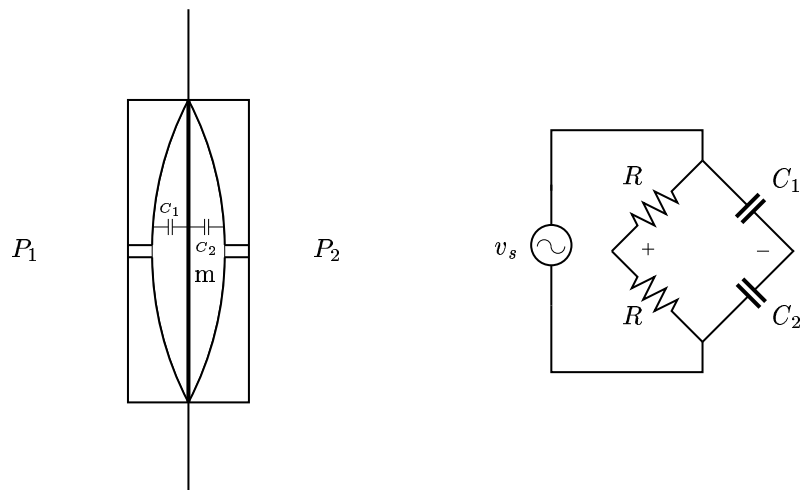


Figura 3.4

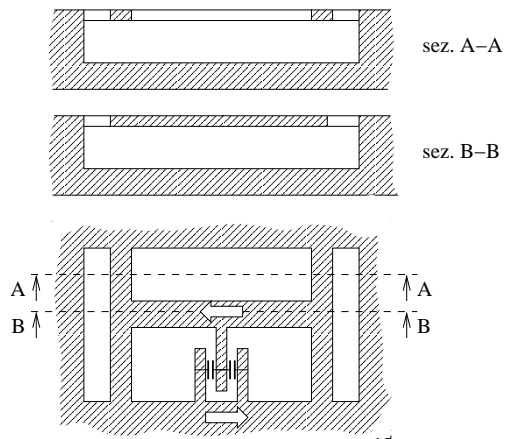


Figura 3.5

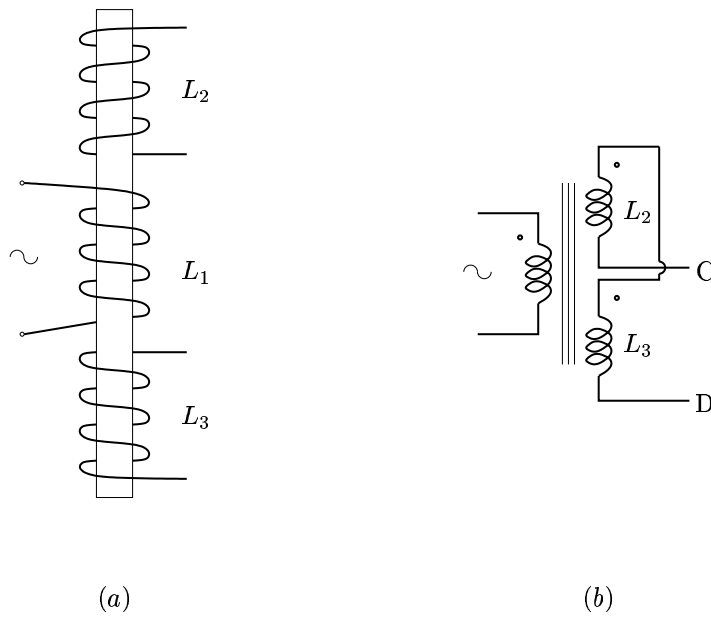


Figura 3.6

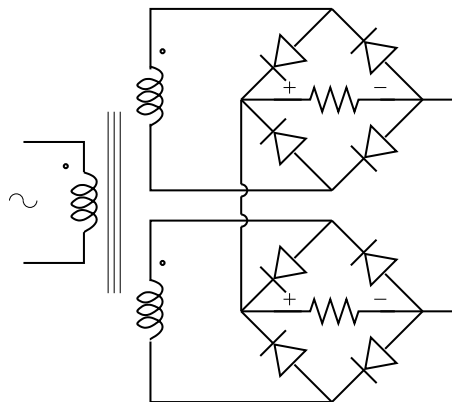


Figura 3.7

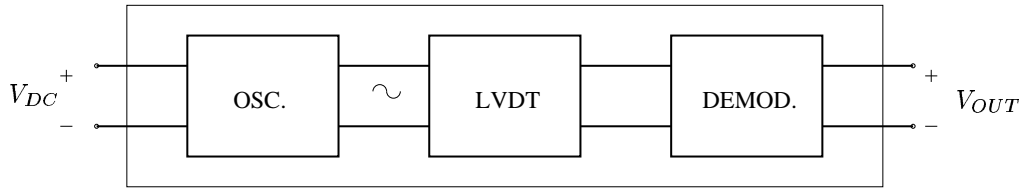


Figura 3.8

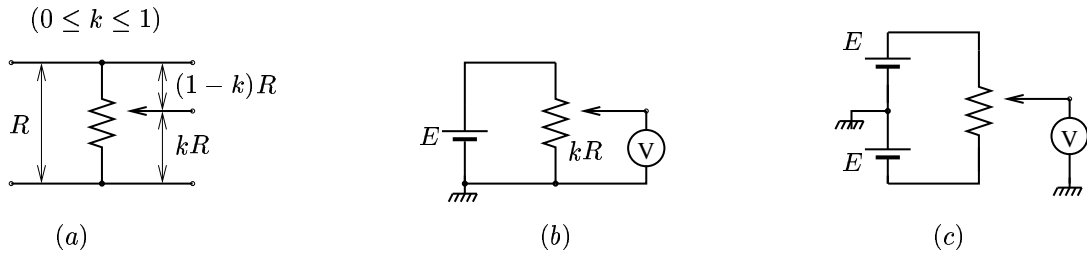


Figura 3.20

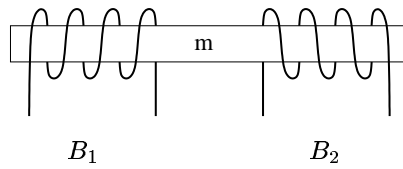


Figura 3.21

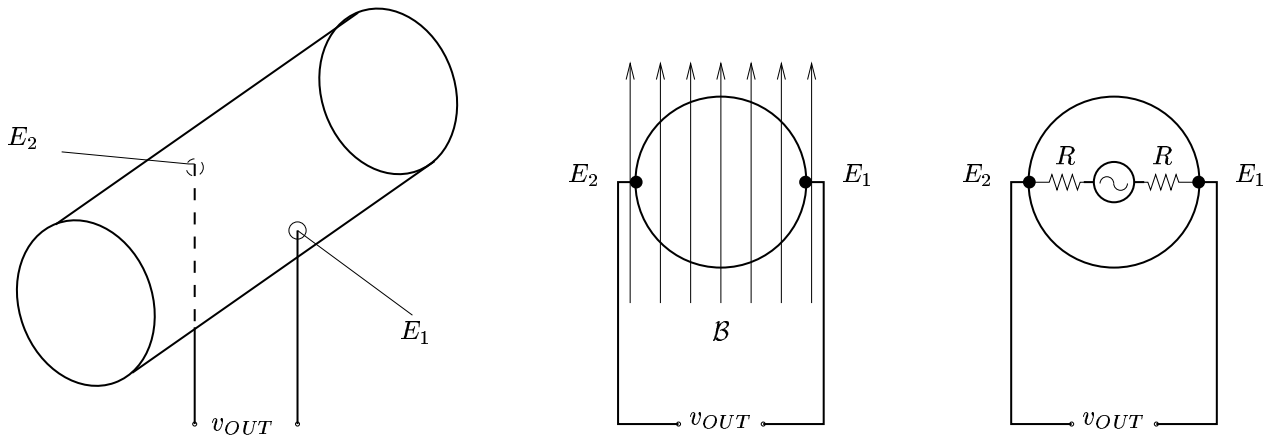


Figura 3.22

$$R = \rho \frac{l}{S} \quad (9)$$

$$V = lS = \pi l \frac{d^2}{4} \quad (10)$$

$$\Delta V = \frac{\pi}{4} (d^2 \Delta l + 2ld \Delta d) = 0 \quad (11)$$

$$\frac{\Delta l}{l} = -2 \frac{\Delta d}{d} \quad (12)$$

$$R = \frac{4\rho l}{\pi d^2} \quad (13)$$

$$\Delta R = 4\frac{\rho}{\pi} \left(\frac{\Delta l}{d^2} - \frac{2dl\Delta d}{d^4} \right) \quad (14)$$

$$\Delta R = 4\frac{\rho}{\pi d^2} \left(\Delta l - \frac{2l\Delta d}{d} \right) = 2\frac{R}{l}\Delta l \Rightarrow \frac{\Delta R}{R} = 2\frac{\Delta l}{l} = 2\varepsilon \quad (15)$$

$$\frac{\Delta R}{R} = F\varepsilon \quad (16)$$

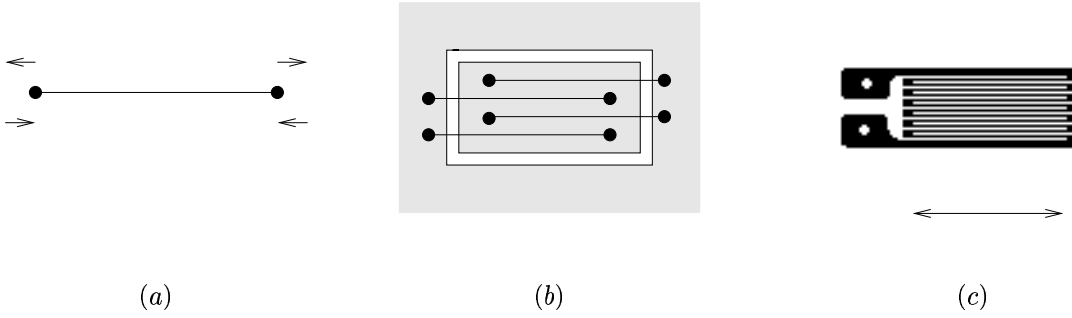


Figura 3.23

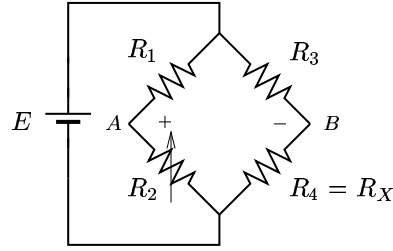


Figura 3.24

$$V_{AB} = E \left(\frac{R_X}{R_3 + R_X} - \frac{R_2}{R_1 + R_2} \right) = 0 \quad (31)$$

$$\frac{R_X}{R_3 + R_X} = \frac{R_2}{R_1 + R_2} \quad (32)$$

$$V_{AB} = E \left(\frac{R_X + \Delta R_X}{R_X + \Delta R_X + R_3} - \frac{R_2}{R_1 + R_2} \right) \quad (33)$$

$$\begin{aligned} \frac{V_{AB}}{E} &= \left(\frac{R_X + \Delta R_X}{R_X + \Delta R_X + R_3} - \frac{R_X}{R_3 + R_X} \right) = \left(\frac{1 + \Delta R_X/R_X}{1 + \Delta R_X/R_X + R_3/R_X} - \frac{1}{1 + R_3/R_X} \right) \\ &= \frac{\frac{\Delta R_X}{R_X} \frac{R_3}{R_X}}{\left(1 + \frac{R_3}{R_X}\right) \left(1 + \frac{\Delta R_X}{R_X} + \frac{R_3}{R_X}\right)} \end{aligned} \quad (34)$$

$$\frac{V_{AB}}{E} \simeq \frac{\frac{\Delta R_X}{R_X}}{2\left(2 + \frac{\Delta R_X}{R_X}\right)} = \frac{\frac{\Delta R_X}{R_X}}{4\left(1 + \frac{\Delta R_X}{2R_X}\right)} = \frac{\frac{\Delta R_X}{R_X}}{4\left(1 + \frac{F\varepsilon}{2}\right)} \quad (35)$$

$$\simeq \frac{F\varepsilon}{4\left(1 + \frac{F\varepsilon}{2}\right)} \simeq \frac{F\varepsilon}{4} \quad \text{se } F\varepsilon/2 \ll 1 \quad \left(\frac{\Delta R_X}{2R_X} \ll 1\right)$$

$$\frac{V_{AB}}{E} = \left(\frac{R_X + \Delta R_X}{2R_X} - \frac{1}{2}\right) = \frac{\Delta R_X}{2R_X} = \frac{F\varepsilon}{2} \quad (36)$$

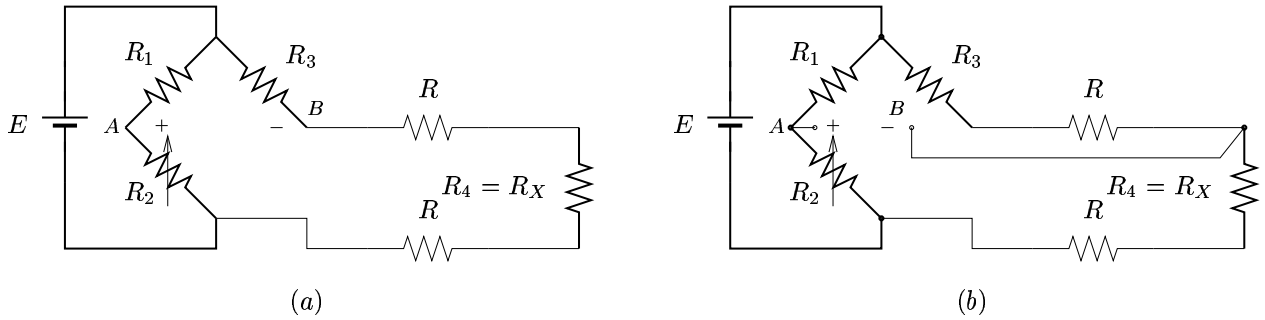


Figura 3.25

$$R(T) = R_0 \left\{ 1 + \alpha \left[T + \delta \left(1 - \frac{T}{100} \right) \frac{T}{100} + \beta \left(1 - \frac{T}{100} \right) \left(\frac{T}{100} \right)^3 \right] \right\} \quad (41)$$

con

$$\alpha = 0.00385 \text{ } ^\circ\text{C}^{-1}$$

$$\beta : \text{ costante di Van Dusen} \quad \begin{array}{ll} \beta = 0 & T > 0 \\ \beta \neq 0 & T < 0 \end{array}$$

$$\delta = 1.491$$

$$R_0 = R(0 \text{ } ^\circ\text{C})$$

$$R(T) = R_0(1 + \alpha T) \quad (42)$$

$$\ln(R) = a_0 + \frac{a_1}{T} + \frac{a_2}{T^2} + \frac{a_3}{T^3} \quad (43)$$

$$\ln(R) = a_0 + \frac{a_1}{T} \quad (44)$$

$$R(T) = R_0 \exp \left[\beta \left(\frac{1}{T} - \frac{1}{T_0} \right) \right] \quad (45)$$

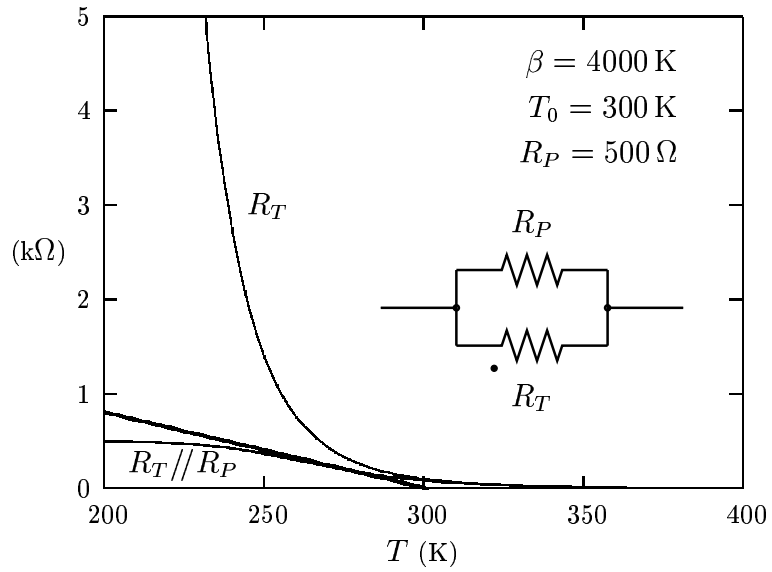


Figura 3.26

$$E^2 = A + B\sqrt{v} \quad (+Cv) \tag{46}$$

$$E = C_1(T_1 - T_2) + C_2(T_1^2 - T_2^2) \tag{47}$$

$$\alpha = \frac{dE}{dT_1} = C_1 + 2C_2T_1 \tag{48}$$

$$V_U = -R_3(I_2 - I_1) = \alpha R_3(T_1 - T_2) \tag{49}$$

$$V_U = -R_3(I_2 - I_1 + I_3) = \alpha R_3(T_1 - T_2 + T_3) \quad \text{con} \quad I_3 = \alpha T_3 \tag{50}$$

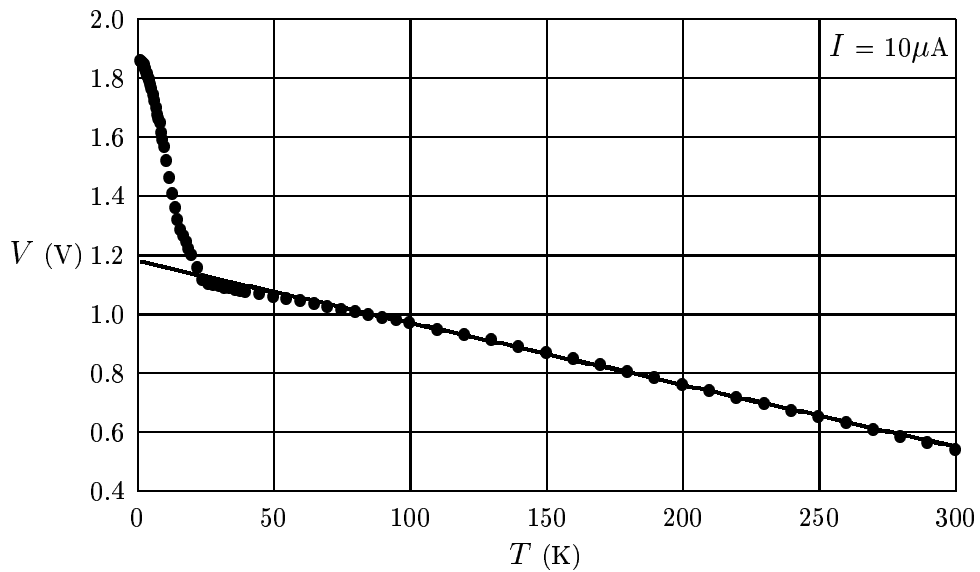


Figura 3.27

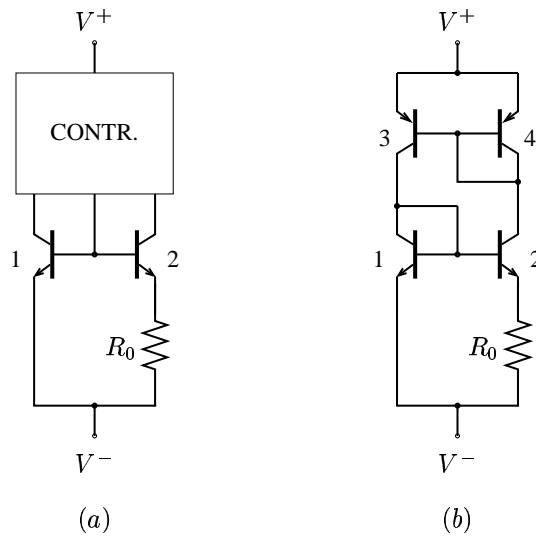


Figura 3.28



$$I_{E1} \simeq I_{C1} \simeq \alpha_{F1} I_{ES1} e^{\frac{V_{BE1}}{\eta V_T}} \quad \text{e} \quad I_{E2} \simeq I_{C2} \simeq \alpha_{F2} I_{ES2} e^{\frac{V_{BE2}}{\eta V_T}} \quad (51)$$

$$\frac{I_{C1}}{I_{C2}} = H = e^{\frac{V_{BE1} - V_{BE2}}{\eta V_T}} \quad (52)$$


$$\log \frac{1}{H} = \frac{V_{BE1} - V_{BE2}}{\eta V_T} \quad (53)$$

$$V_{BE1} - V_{BE2} = \eta V_T \log \frac{1}{H} = \eta \frac{kT}{q} \log \frac{1}{H} \propto T \quad (54)$$
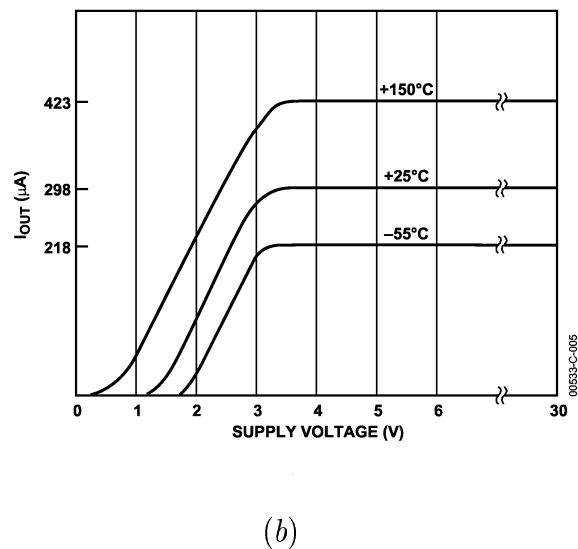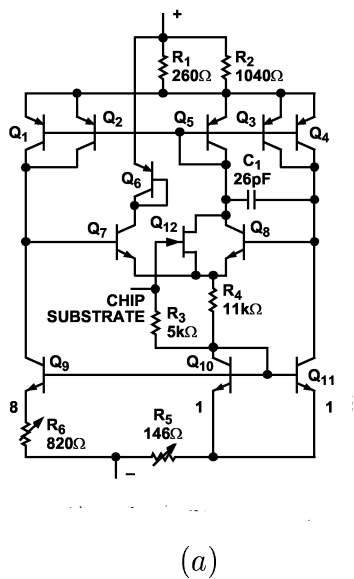
$$V_{BE1} - V_{BE2} = R_0 I_{C2} \propto T \quad (55)$$



(da www.analog.com)
Figura 3.29

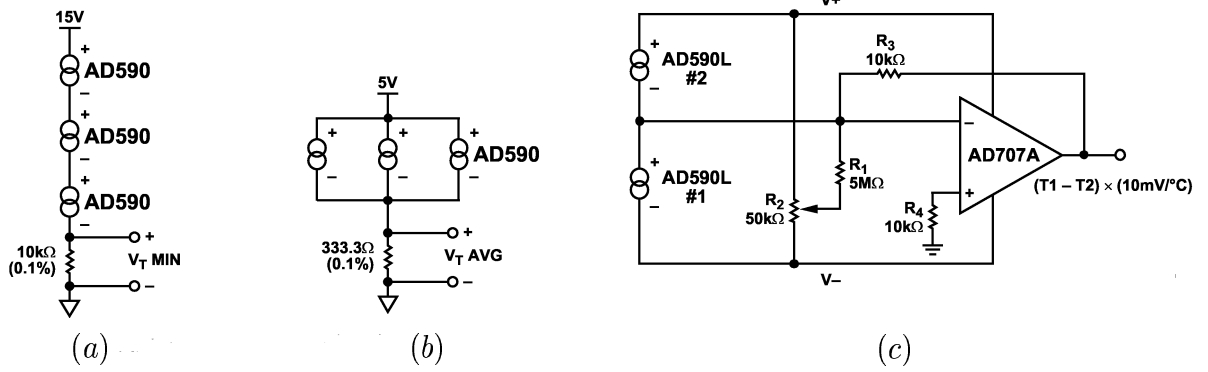

(da www.analog.com)

Figura 3.30

$$V_U = -R_3(I_2 - I_1) = -\alpha R_3(T_2 - T_1) = \alpha R_3(T_1 - T_2) \quad (56)$$

$$V_U = -R_3(I_2 - I_1 + I_3) = -\alpha R_3(T_2 - T_1 + T_R) = \alpha R_3(T_1 - T_2 - T_R) \quad (57)$$

$$\text{con } I_R = \alpha T_R$$