


Analog Filter Design

Part. 3: Time Continuous Filter Implementation

Sect. 3-a:

- General considerations
- Passive filters

Design approaches

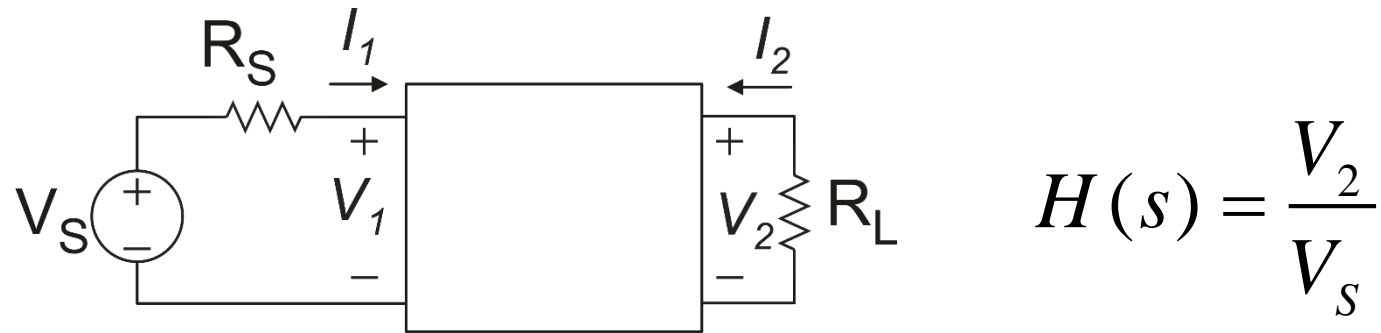

- Passive LC (R) ladder filters
- Cascade of Biquadratic (Biquad) and Bilinear cells
- State Variable Filters
- Simulation of LC filters with active RC networks

Filter Parameters

- For a given transfer function $H(s)$, a particular implementation is characterized by several FOMs (Figures Of Merit). The most frequently used are:

➤ Dynamic Range: $DR = \frac{\max(V_{out})}{v_{n-out}}$ v_{n-out} = output noise


➤ Sensitivity to component variations

➤ Component value spread, e.g. $\frac{C_{max}}{C_{min}}$

$$\left\{ \begin{array}{l} S_x^{\omega_0} = \frac{d\omega_0 / \omega_0}{dx / x} = \frac{x}{\omega_0} \frac{d\omega_0}{dx} \\ S_x^Q = \frac{x}{Q} \frac{dQ}{dx} \end{array} \right.$$

LC passive filters: "The Prototype filter"

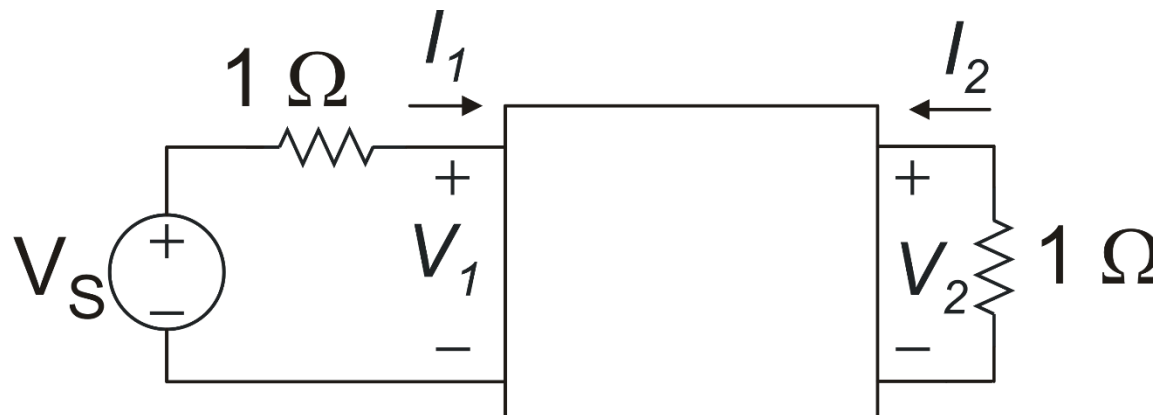
- LC ladder filters are synthesized in normalized (1 rad/s, 1 Ω) and low-pass form (prototype filter)
- Transformation rules are used to derive the required filter function (e.g. band-pass) and parameters (e.g. actual operating frequencies) from the prototype filter



$$H_N(s) = \frac{V_2}{V_S}$$

Normalized Low-Pass
Function


Passive Lossless Ladder Filters

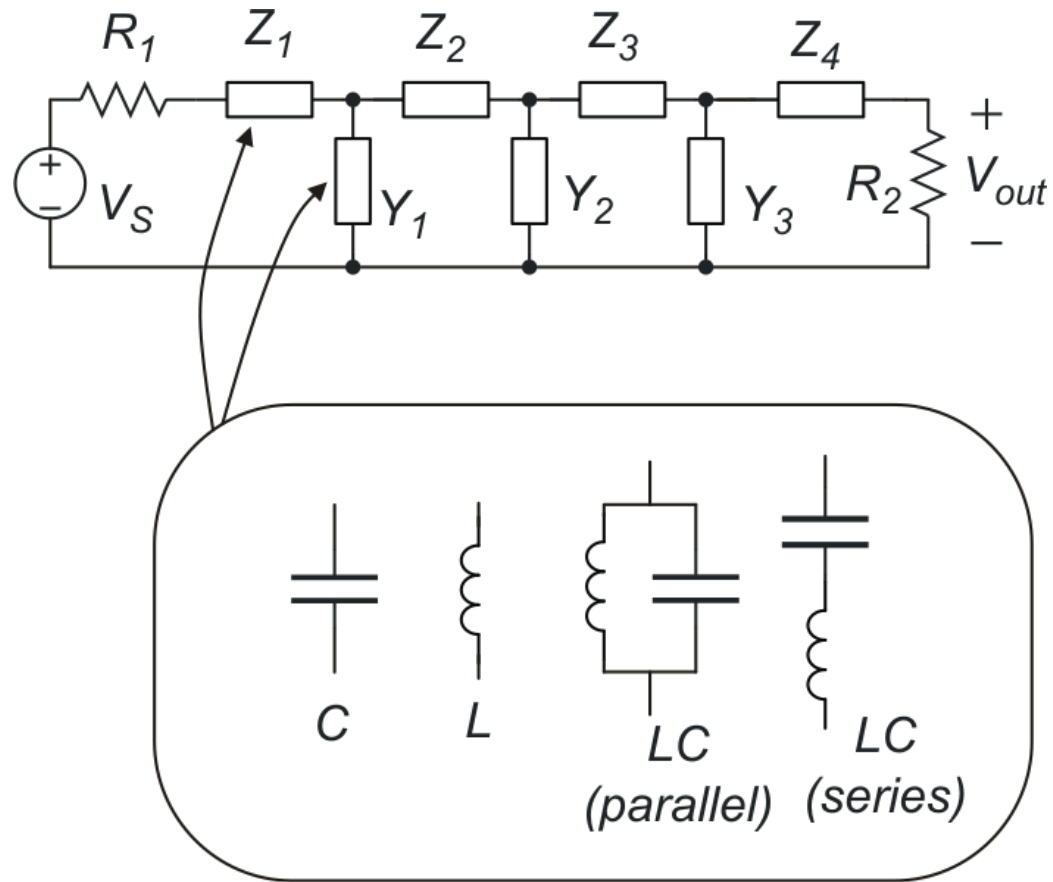

- Doubly terminated LC ladder network
- Advantages: **minimum sensitivity** to component variation in the pass-band
- **The lowest sensitivity is achieved with equally terminated networks ($R_1=R_2$).**
- Can be used as starting point for the synthesis of active RC filters
- Drawback: tuning requires change of all components.

order (N) = number of capacitors + number of inductors

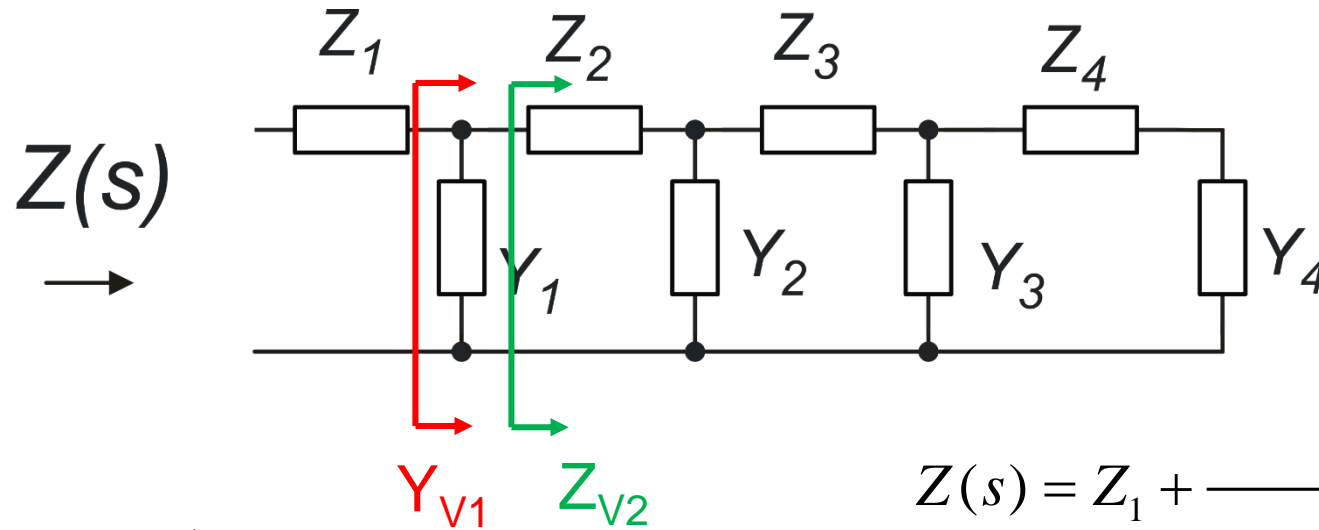Ladder networks: driving point impedance (d.p.i.)



- Driving point impedances (or d.p. admittances)
- Transfer impedances (or t. admittances)

$$Z(s) = Z_1 + \frac{1}{Y_{V1}}$$

$$Z(s) = Z_1 + \frac{1}{Y_1 + \frac{1}{Z_{V2}}}$$

• • •

$$Z(s) = Z_1 + \frac{1}{Y_1 + \frac{1}{Z_2 + \frac{1}{Y_2 + \frac{1}{Z_3 + \frac{1}{Y_3 + \frac{1}{Z_4 + \frac{1}{Y_4}}}}}}}$$

"Continued fraction"

Cauer synthesis approach for d.p.i.

$$Z(s) = \frac{s^4 + 4s^2 + 3}{s^3 + 2s}$$

$$Z(s) = s + \frac{2s^2 + 3}{s^3 + 2s}$$



$$Z_1 = s$$

$$\frac{1}{Y_{V1}} = \frac{2s^2 + 3}{s^3 + 2s}$$

$$Y_{V1} = \frac{s^3 + 2s}{2s^2 + 3} = \frac{s}{2} + \frac{s/2}{2s^2 + 3}$$


In the end
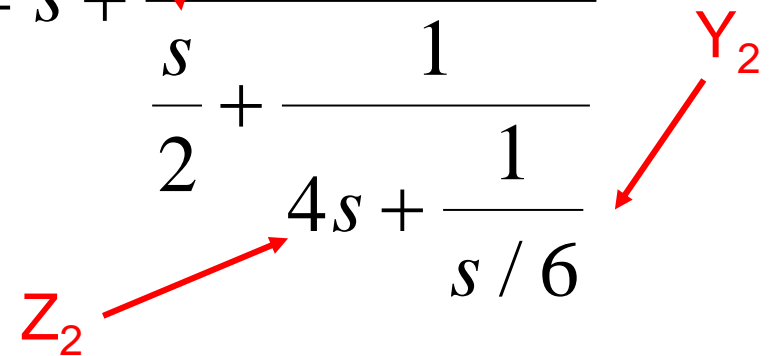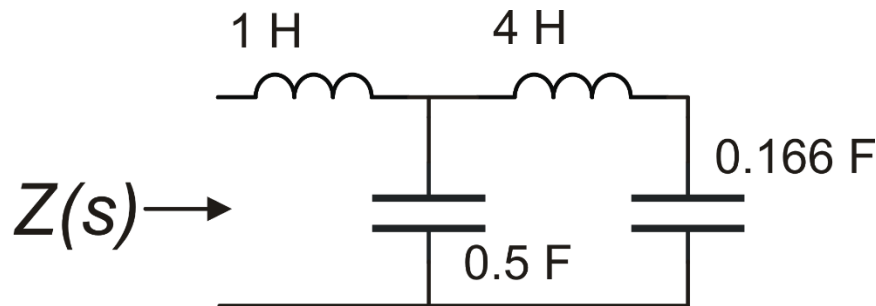
$$Z(s) = s + \frac{1}{\frac{s}{2} + \frac{1}{4s + \frac{1}{s/6}}}$$




Prototype Filter Configurations (all poles)

$N=2M+1$ (odd order)

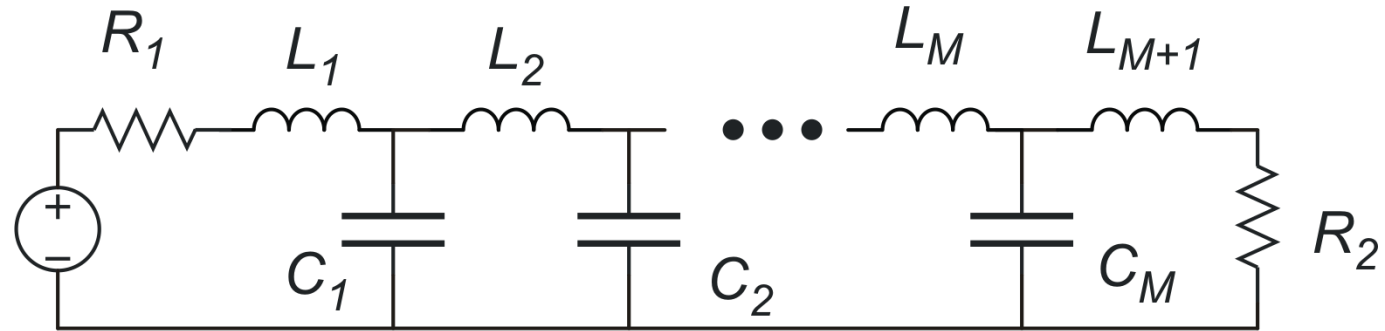


$N=2M$ (even order)

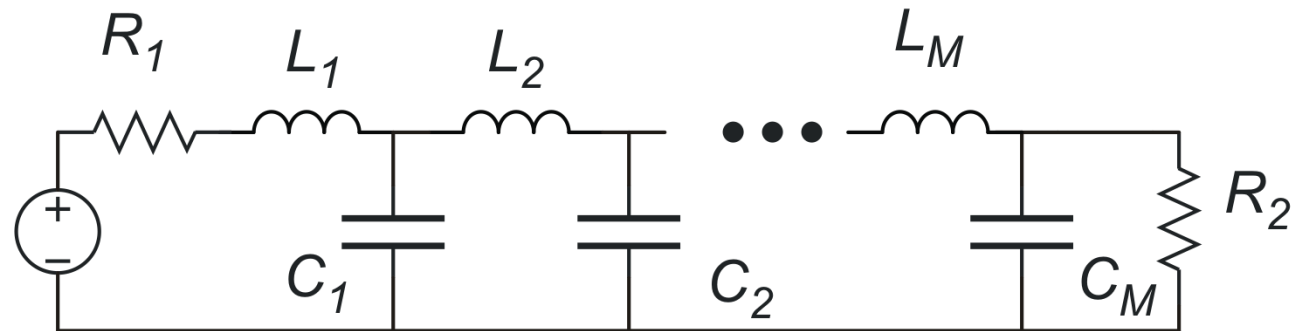


Pass-band gain: $k = \frac{R_2}{R_1 + R_2} < 1$ (0.5 for equally terminated networks)

Alternate solution (all poles)

$N=2M+1$ (odd order)


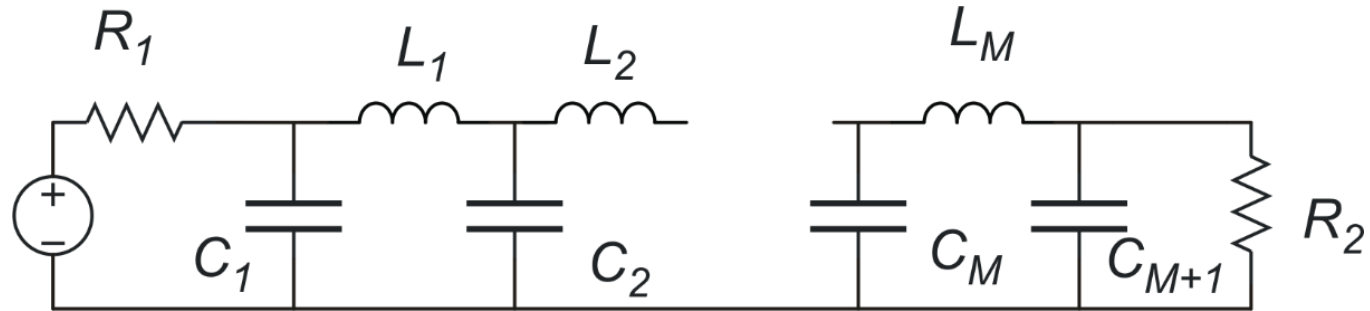


$N=2M$ (even order)

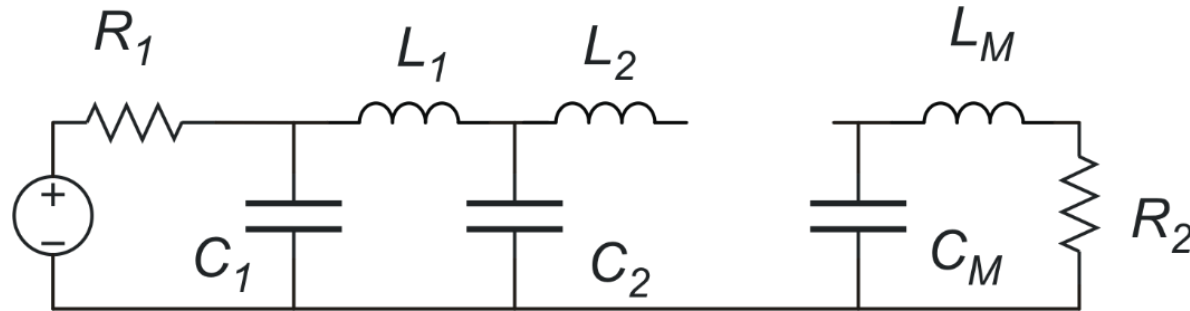

Pass-band gain: $k = \frac{R_2}{R_1 + R_2} < 1$ (0.5 for equally terminated networks)

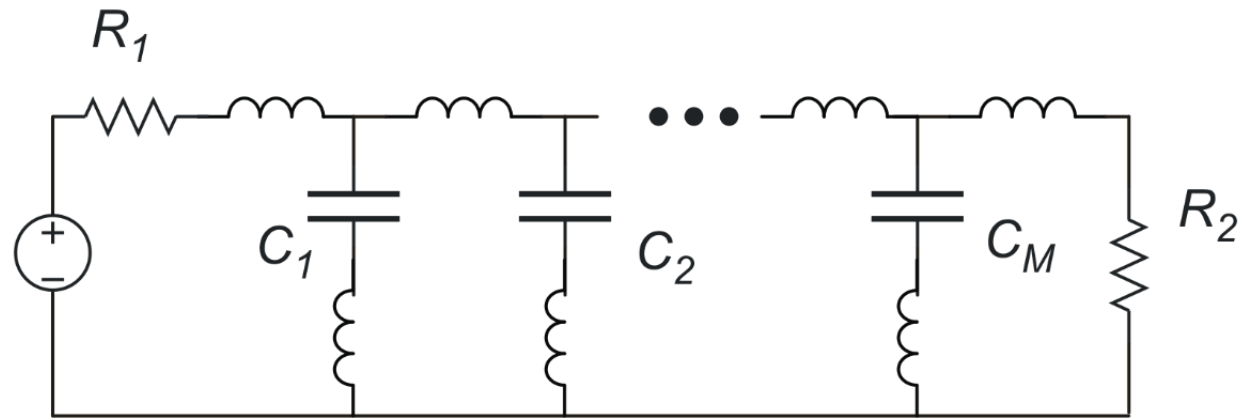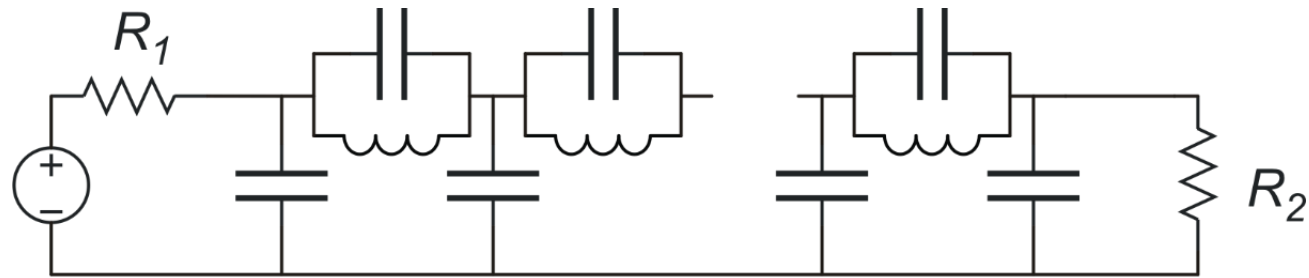LC ladder network for TF with imaginary zeros (e.g. Inverse Chebyshev and Cauer Elliptic filters)



Frequency scaling rules

- Frequency scaling allows to change the normalization frequency, allowing transformation of the characteristic frequencies of the filter

$$s_n \rightarrow \frac{s}{\omega_N}$$
$$\frac{1}{s_n C} \rightarrow \frac{\omega_N}{sC} \Rightarrow C \rightarrow \frac{C}{\omega_N} \quad \text{---||---}$$
$$s_n L \rightarrow s \frac{L}{\omega_N} \Rightarrow L \rightarrow \frac{L}{\omega_N} \quad \text{---}\omega\text{---}$$
$$R \rightarrow R \quad \text{---}\omega\text{---}$$

Impedance Scaling Rule

- Impedance scaling is used to change component values leaving the transfer function unaltered. The target is finding feasible component values for the chosen technology

If the network includes only:

- Two terminal impedances (L,R,C components)
- Voltage Controlled Voltage Sources (VCVS) i.e Ideal voltage amplifiers.
- Current Controlled Current Sources (CCCS) i.e. ideal current amplifiers

Then: the V_{out}/V_S transfer function is unchanged when all the impedances are multiplied by the same function $f(s)$

Impedance scaling: component transformation

An important case is when the function $f(s)$ is a constant factor K :

$$\frac{1}{s_n C} \rightarrow K \frac{1}{sC} \Rightarrow C \rightarrow \frac{C}{K}$$



$$sL \rightarrow KsL \Rightarrow L \rightarrow KL$$



$$R \rightarrow KR$$



Element transformations

- **Goal:** to change the filter response from low-pass to the other three possibilities (high-pass, etc.) and perform frequency scaling at the same time.

Let us recall the following transformations:

From Low-Pass to:

High-Pass

$$s_n \rightarrow \frac{\omega_N}{s}$$

Band-Pass

$$s_n \rightarrow \frac{\omega_0}{B} \left(\frac{s}{\omega_0} + \frac{\omega_0}{s} \right)$$

Band -Stop


$$s_n \rightarrow \left[\frac{\omega_0}{B} \left(\frac{s}{\omega_0} + \frac{\omega_0}{s} \right) \right]^{-1}$$

Element Transformation


Low-pass to High-pass

$$s_n \rightarrow \frac{\omega_N}{s}$$

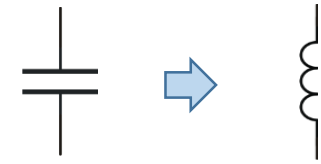
$$\frac{1}{s_n C} \rightarrow \frac{s}{\omega_N C} \Rightarrow C \rightarrow L = \frac{1}{\omega_N C}$$


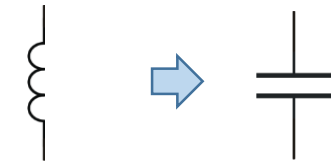
$$s_n L \rightarrow \frac{\omega_N}{s} L \Rightarrow L \rightarrow C = \frac{1}{\omega_N L}$$



$$R \rightarrow R$$

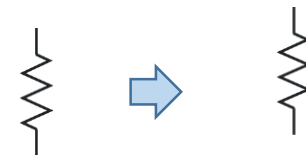

Element Transformation


Low-pass to Band-pass

$$s_n \rightarrow \frac{\omega_0}{B} \left(\frac{s}{\omega_0} + \frac{\omega_0}{s} \right)$$


$$s_n \rightarrow \frac{s}{B} + \frac{\omega_0^2}{sB}$$

$$\frac{1}{s_n C} \rightarrow \frac{1}{\frac{sC}{B} + \frac{\omega_0^2 C}{sB}} = \frac{1}{sC_P + \frac{1}{sL_P}}$$
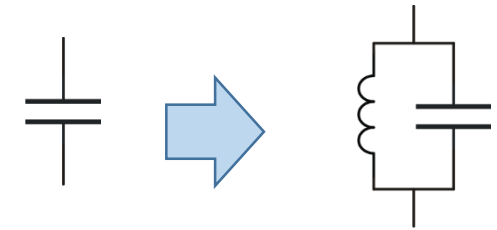
$$s_n L \rightarrow L \frac{s}{B} + L \frac{\omega_0^2}{sB} = sL_S + \frac{1}{sC_S}$$



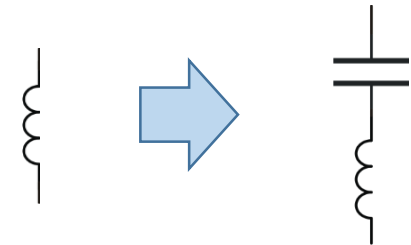
$$C_P = \frac{C}{B} \quad L_P = \frac{B}{\omega_0^2 C}$$




$$C_S = \frac{B}{\omega_0^2 L} \quad L_S = \frac{L}{B}$$

Element Transformation

Low-pass to Band-stop
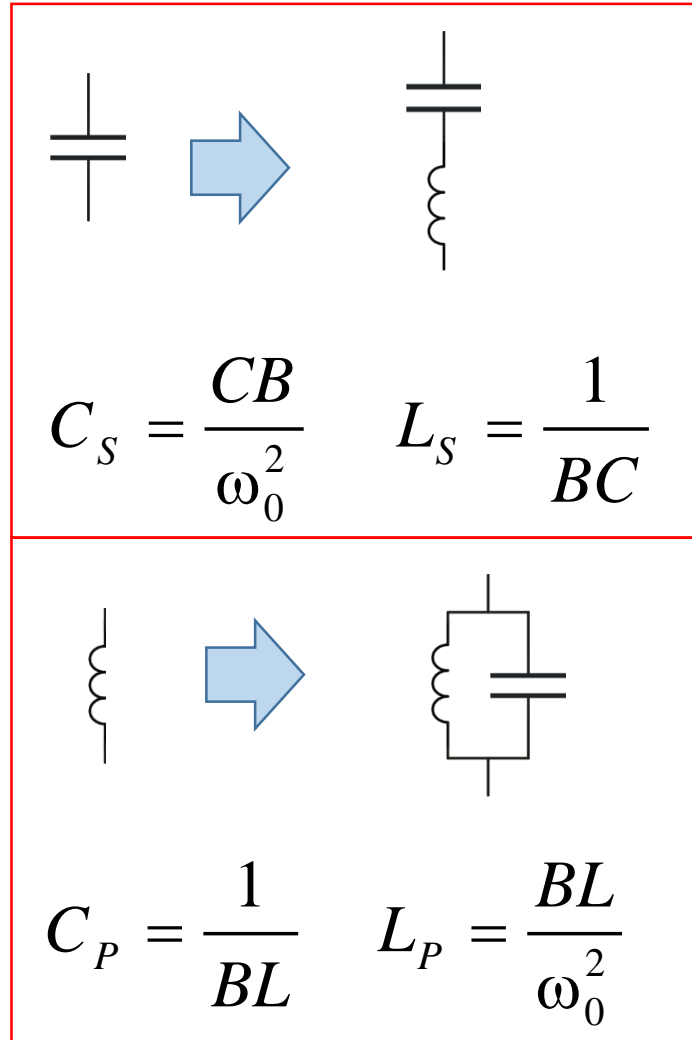
$$s_n \rightarrow \left[\frac{\omega_0}{B} \left(\frac{s}{\omega_0} + \frac{\omega_0}{s} \right) \right]^{-1}$$




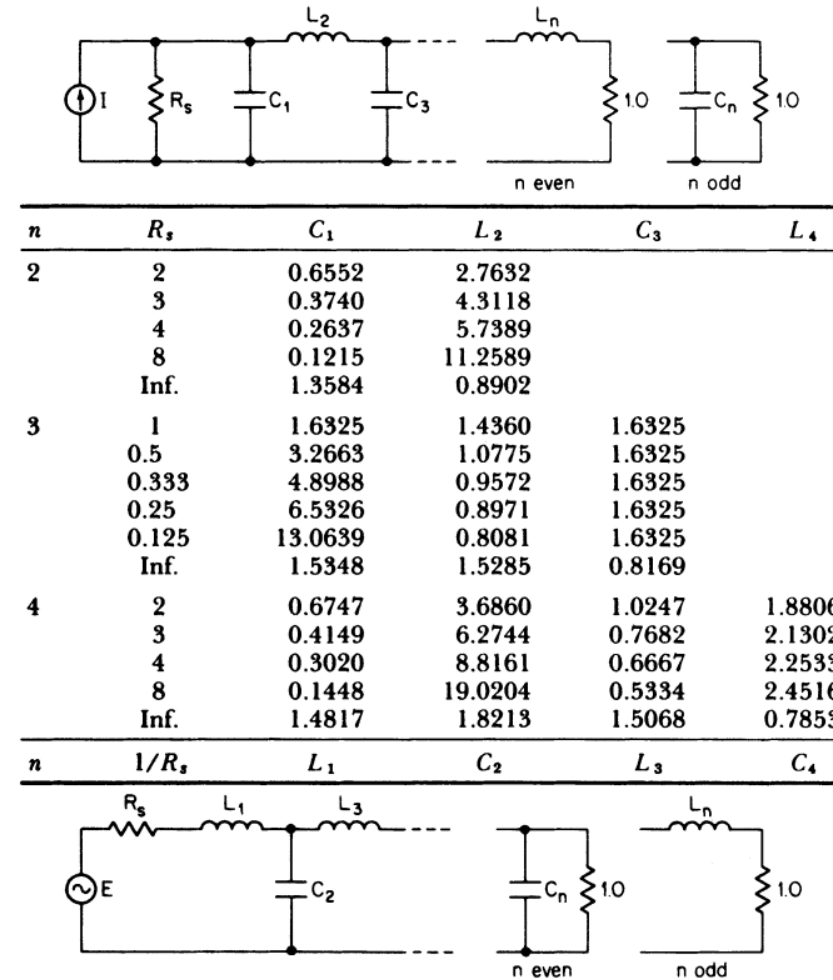
Design of LC ladder passive filters

- A procedure that allows designing an arbitrary transfer function with a ladder structure does not exist.
- All-pole functions (e.g. Butterworth, Chebyshev I, Bessel) can be designed with a standard approach, where the branches of the ladder (Z and Y elements) are pure capacitors or inductors. Given a class of networks, not all functions are feasible.
- The rigorous design of Cauer (elliptic) filters is less straightforward.
- **Tables** are available for the most frequently used ladder topologies and transfer functions. Several **CAD design tools** are also available.



Table example

Williams & Taylor
 «Electronic Filter Design
 Handbook»
 2006, McGraw-Hill

TABLE 11-29 0.25-dB Chebyshev LC Element Values



Example: Butterworth Prototype Filter

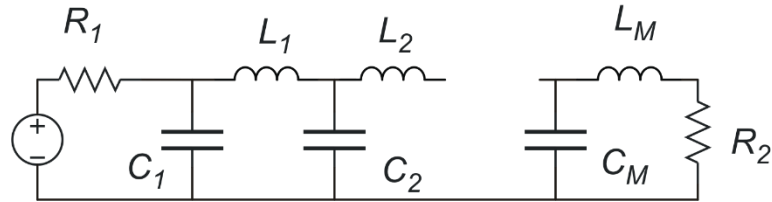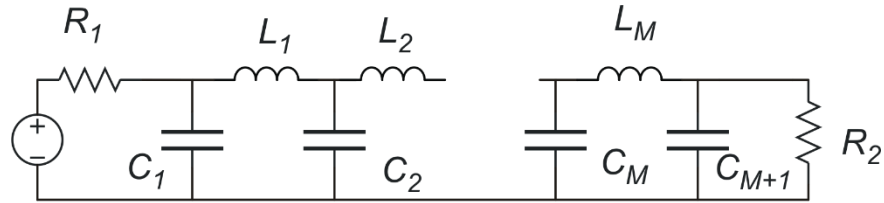


radians - per - seconds


$\omega=1$

N	C1	L1	C2	L2	C3	L3	C4	L4	C5	L5
2	1.4142	1.4142								
3	1.0000	2.0000	1.0000				Butterworth (1 rps passband)			
4	0.7654	1.8478	1.8478	0.7654						
5	0.6180	1.6180	2.0000	1.6180	0.6180					
6	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2740	0.4450			
8	0.3902	1.1111	1.6629	1.9616	1.9616	1.6629	1.1111	0.3902		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129

Chebyshev 1 dB ripple

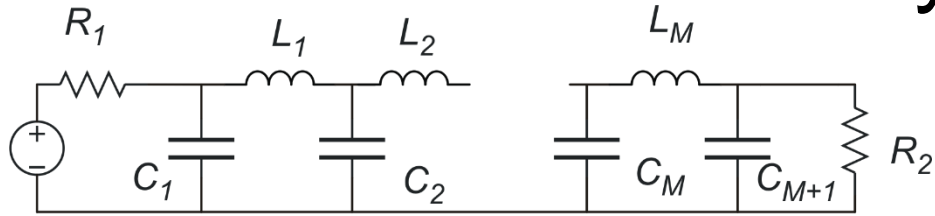

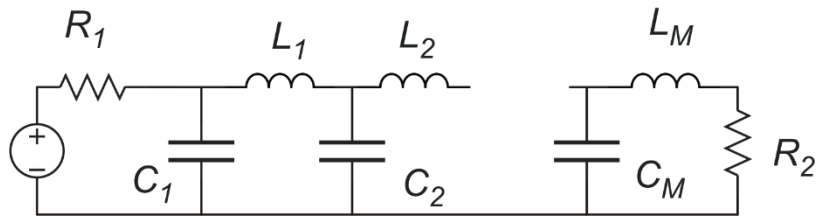Note: In these tables, generally $\omega=1$ is the **-3 dB angular frequency**, regardless of ripple (and A_p)
 e.g. Williams & Taylor «Electronic Filter Design Handbook»



n	C1	L1	C2	L2	C3	L3	C7
2	0.572	3.132					
3	2.216	1.088	2.216				
4	0.653	4.411	0.814	2.535			
5	2.207	1.128	3.103	1.128	2.207		
6	0.679	3.873	0.771	4.711	0.969	2.406	
7	2.204	1.131	3.147	1.194	3.147	1.131	2.204

Example

- Design a LC ladder Chebyshev filter with the following characteristics:

$f_{\text{pass}} = 10$ kHz, Maximum Pass-band attenuation 1 dB


$f_{\text{stop}} = 20$ kHz Minimum Stop-Band Attenuation: 40 dB

Python: cheb1ord: Order=5, $\omega_p = 62.8$ krad/s

But: tables are normalized to $\omega_{-3\text{dB}}$. From the magnitude plot:

$$f_{-3\text{dB}} \cong 10.34 \text{ kHz} \quad \omega'_N = \omega_{-3\text{dB}} \cong 65 \text{ krad/s}$$

LC Filter design using Tables

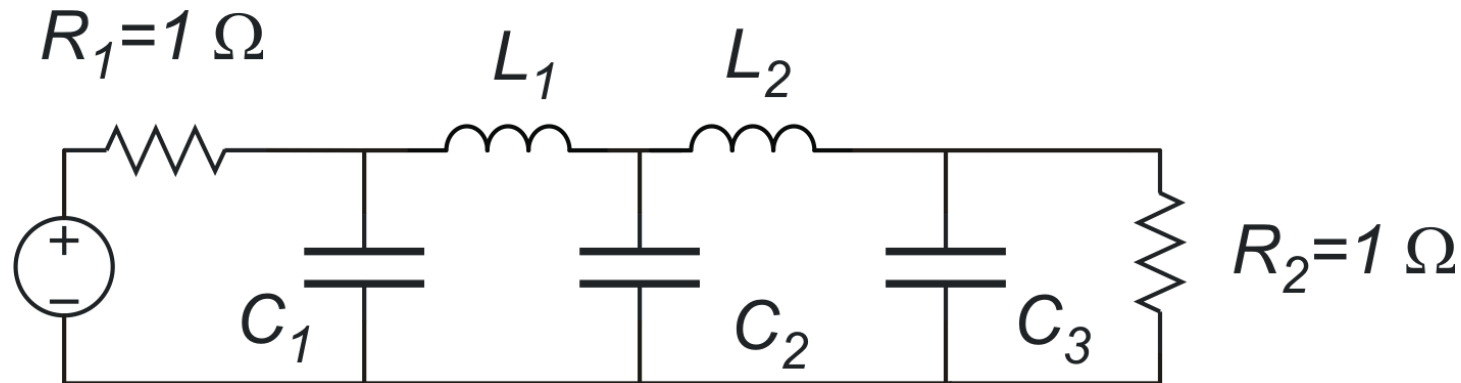

From table: prototype filter

$$\omega'_N = \omega_{-3dB} = 1 \text{ rad/s}$$

$$C_1 = 2.207 \text{ F}$$

$$L_1 = 1.128 \text{ H}$$

$$C_2 = 3.103 \text{ F}$$

$$L_2 = 1.128 \text{ H}$$

$$C_3 = 2.207 \text{ F}$$

$$C \rightarrow \frac{C}{\omega'_N}$$

$$L \rightarrow \frac{L}{\omega'_N}$$

$$\omega_{-3dB} = 65 \text{ krad/s}$$

$$C_1 = 33.9 \mu\text{F}$$

$$L_1 = 17.35 \mu\text{H}$$

$$C_2 = 47.7 \mu\text{F}$$

$$L_2 = 17.35 \mu\text{H}$$

$$C_3 = 33.9 \mu\text{F}$$

Frequency
scaled
filter