

Analog Filter Design

Part. 3: Time Continuous (TC) Filter Implementation

Sect. 3-a: Active Filters

Motivations

- Inductors are generally difficult to miniaturize
 - $L \sim (\text{coil area}) \times (\text{number of coils})^2 \times (\text{magnetic permeability})$
 - Integrated inductors limited to a few nH (max)
 - Stray magnetic field cause unwanted coupling
- Resistors and capacitors can be easily integrated: feasible ranges are much wider than for inductors
- Active Filters Target: Synthesis of arbitrary transfer functions using only resistors, capacitors and active elements.

Design approaches for active TC filters

System-level architectures

- Cascade of Biquadratic (Biquad) and Bilinear cells
- State Variable Filters (MLF: Multiple Loop Feedback circuits)
- Simulation of LC filters with active RC networks



Circuit-level architectures

- Op-amp based
- OTA (Operational transconductance amplifier) – based

Cascade of Biquad (Bilinear) functions

➤ Biquad Transfer Function

$$H_{BQ}(f) = \frac{c_2 s^2 + c_1 s + c_0}{s^2 + d_1 s + d_0} = H_0 \frac{b_2 s^2 + b_1 \frac{\omega_z}{Q_z} s + b_0 \omega_z^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2} \quad \begin{array}{l} b_2, b_0 : 0, 1 \\ b_1 : 0, \pm 1 \end{array}$$

➤ Bilinear Transfer Function

$$H_{BL}(f) = H_0 \frac{b_1 s + b_0 \omega_z}{s + \omega_p} \quad \begin{array}{l} b_1 : 0, 1 \\ b_0 : 0, \pm 1 \end{array}$$


“Bits” b_2, b_1, b_0 determine which terms are present in the numerator

Poles vs. Biquad coefficients

For a 2nd order polynomial with complex roots:

$$(s - s_p)(s - s_p^*) = s^2 + (s_p + s_p^*)s + s_p s_p^* = s^2 + 2 \operatorname{Re}(s_p)s + |s_p|^2$$

$$\omega_p = |s_p| \quad Q_P = \frac{|s_p|}{2 \operatorname{Re}(s_p)}$$

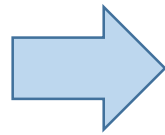

Biquads can be easily extracted from "zpk" output of python or Matlab filter synthesis functions

For the zeroes, identical rules apply, with the exception of :

- Zeros in the origin, s^2 or s term only ($b_0=0$)
- Zeros to infinity, only constant term is present ($b_1, b_2=0$)

Notable cases

$$\frac{\omega_p^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

Low pass

$$\frac{s^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

High pass

$$\frac{\frac{\omega_p}{Q_p} s}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

Band pass

$$\frac{s^2 + \omega_p^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$


Band Stop

$$\frac{s^2 - \frac{\omega_p}{Q_p} s + \omega_p^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

All pass
(phase equalizer)

All these biquads have unity gain in their respective pass-bands

Sequencing criteria for biquad cascades

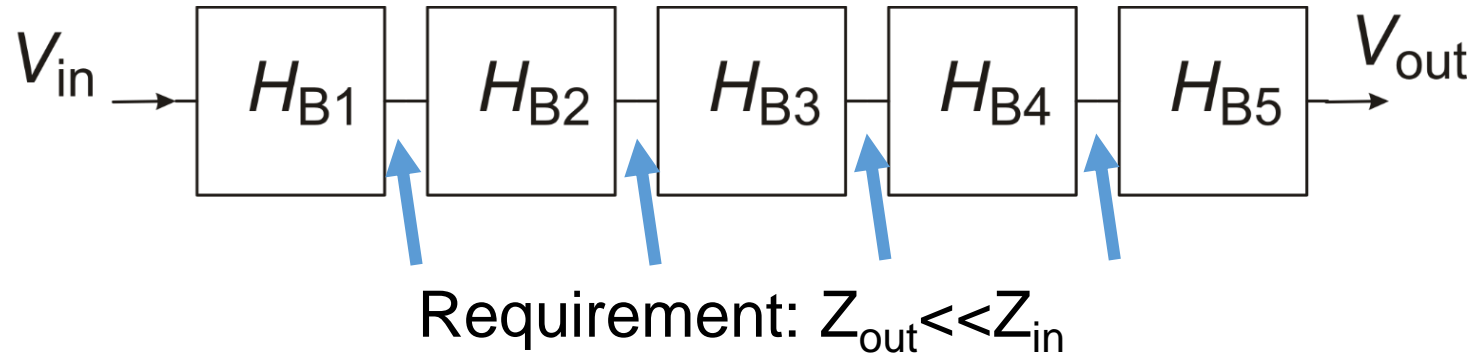

Degrees of Freedom:

- Poles – Zeroes pairing (when zeroes are present)
- Physical position of each biquad in the cascade
- Pass-Band gain of each individual element of the cascade

Sequencing criteria: Targets and Rules of Thumb

Targets

- Maximize the Dynamic Range (DR)
- Minimize the transmission sensitivity (to component variations)
- Minimize the pass-band attenuation

Rules


- **Pairing:** couple together poles and zeroes which are closer in the s-plane (flatter response, less component spread)
- **Position:** Place the biquads with lower Q closer to the inputs
Keep biquads with similar frequency of maximum as far away as possible
If possible, place LP Biquads first and HP or BP Biquads last
- **Gain distribution:** balance the signal amplitude over the various biquads

Biquad implementations

- Op-amp Based:
 - SAB (Single Opamp Biquad)
 - Finite Gain SABs – positive feedback**
 - Finite Gain SABs – negative feedback
 - Infinite Gain SABs**
 - Multiple op-amp Biquads (e.g. MFL)
- OTA based (Gm-C filters)

SABs


Finite gain

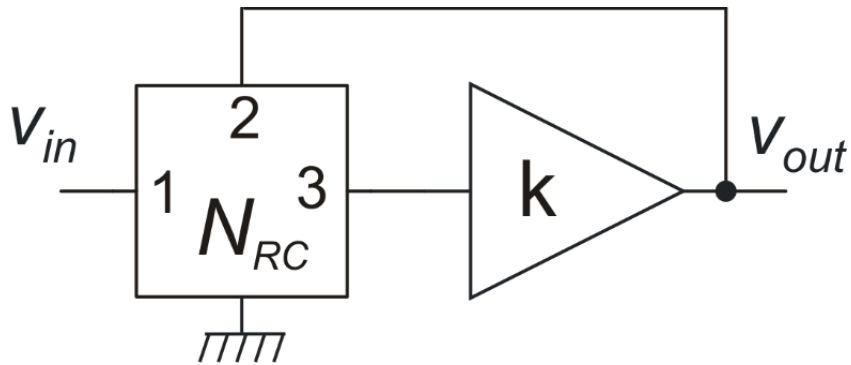

$$\begin{cases} I_3 = y_{13}V_1 + y_{23}V_2 + y_{33}V_3 = 0 \\ V_3 = V_2 / k \end{cases}$$

$$\frac{V_{out}}{V_{in}} = \frac{V_2}{V_1} = \frac{-y_{13}}{y_{23} + y_{33}/k}$$

Infinite gain

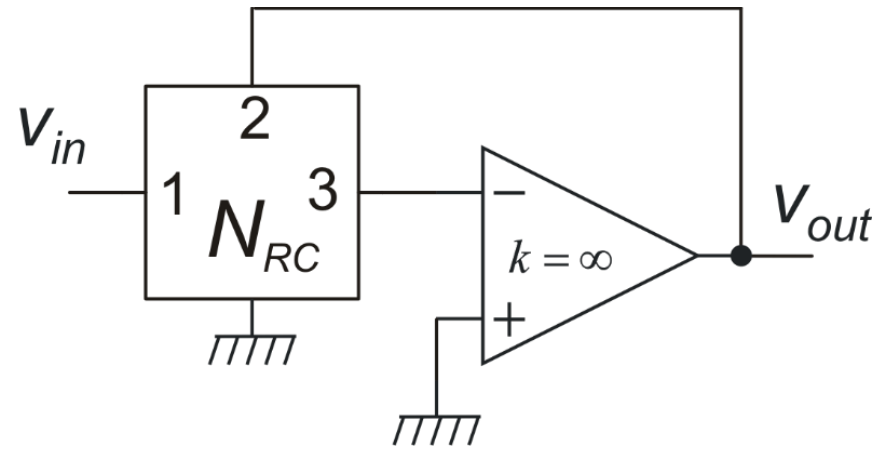


$$I_3 = y_{13}V_1 + y_{23}V_2 = 0$$


$$\frac{V_{out}}{V_{in}} = \frac{V_2}{V_1} = \frac{-y_{13}}{y_{23}}$$

Example: Sallen-Key Biquads

(R.P. Sallen, E.L. Key – MIT Labs, 1955)

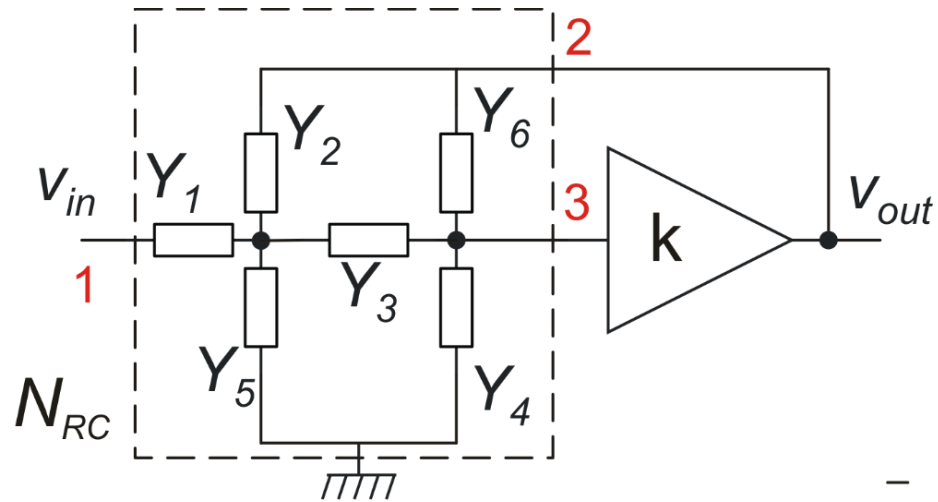


SK General configuration

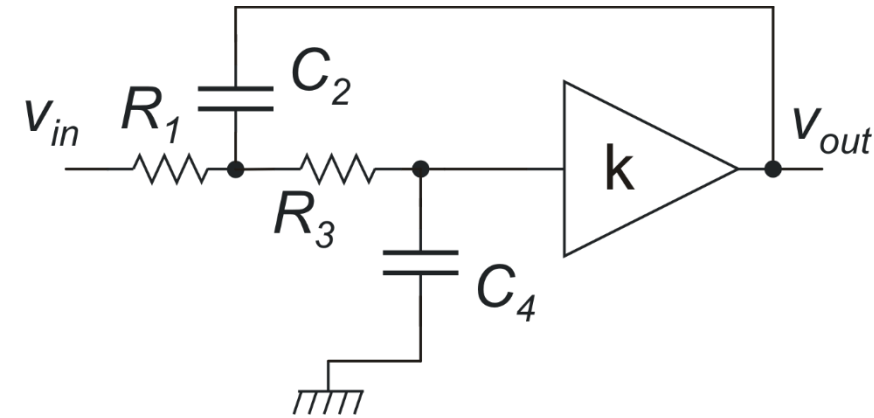


SK- Low pass filter

$$\frac{V_{out}}{V_{in}} = \frac{KY_1 Y_3}{(Y_1 + Y_2 + Y_5)(Y_3 + Y_4 + Y_6) + Y_3(Y_4 + Y_6) - K\{Y_6(Y_1 + Y_2 + Y_3 + Y_5) + Y_2 Y_3\}}$$

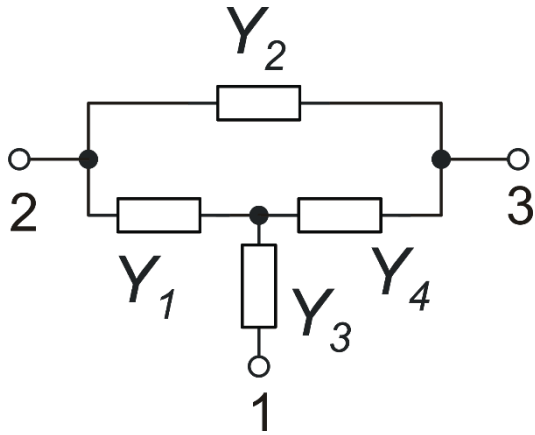Example II: SAB with infinite amplifier gain and "bridged-T" network



Bridged -T network



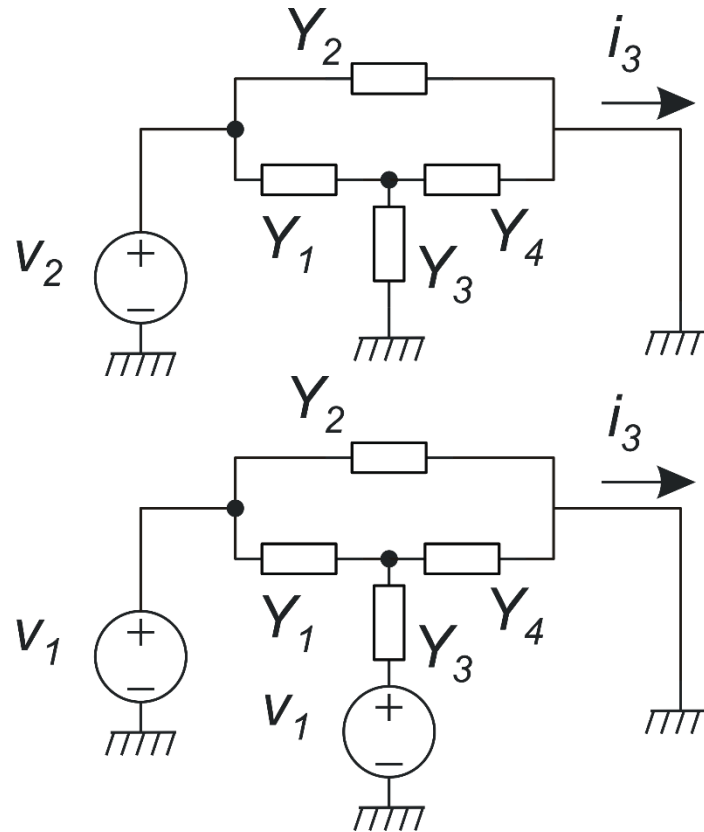


$$-y_{23} = \frac{i_3}{v_2} = \frac{Y_2 (Y_1 + Y_3 + Y_4) + Y_1 Y_4}{(Y_1 + Y_3 + Y_4)}$$

$$-y_{13} = \frac{i_1}{v_2} = \frac{Y_3 Y_4}{(Y_1 + Y_3 + Y_4)}$$

For infinite (negative) amplifier gain: $\rightarrow H = \frac{-y_{13}}{y_{23}} = \frac{-Y_3 Y_4}{Y_2 (Y_1 + Y_3 + Y_4) + Y_1 Y_4}$

Band-pass Delyannis-Friend Biquad

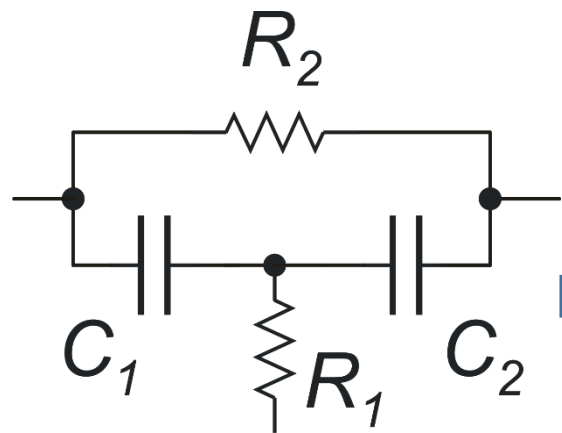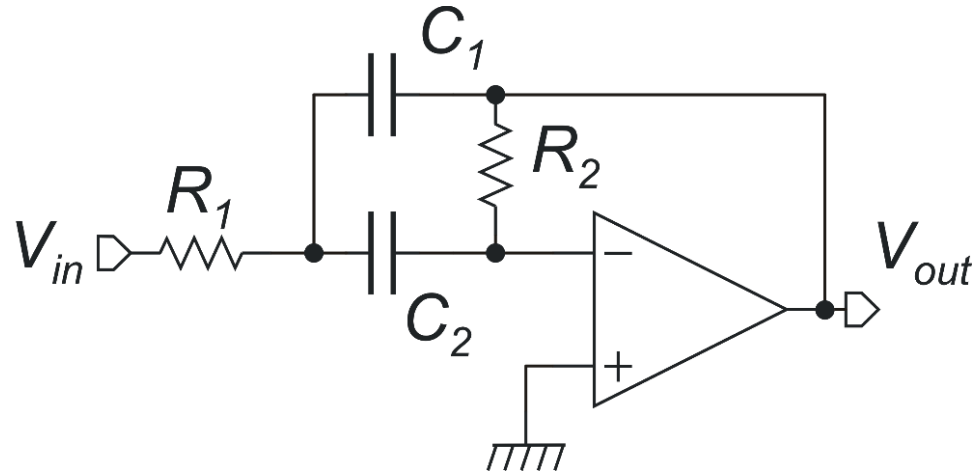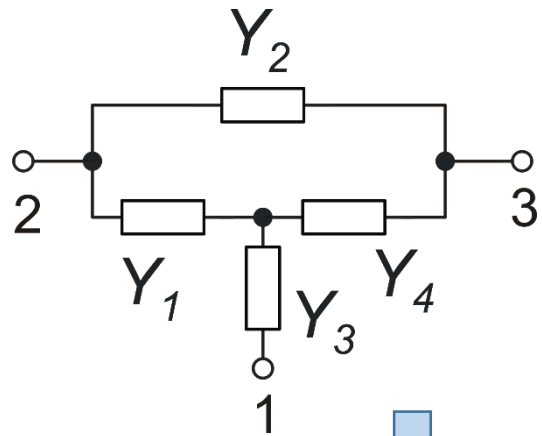


$$\begin{aligned}
 Y_1 &= sC_1 \\
 Y_2 &= 1/R_2 \\
 Y_3 &= 1/R_1 \\
 Y_4 &= sC_2
 \end{aligned}$$

Band-pass
Biquad

$$H(s) = \frac{\frac{s}{R_1 C_2}}{s^2 + \frac{1}{R_2 C_1} s + \frac{1}{R_1 R_2 C_1 C_2}}$$

Multiple Feedback Loop Filters

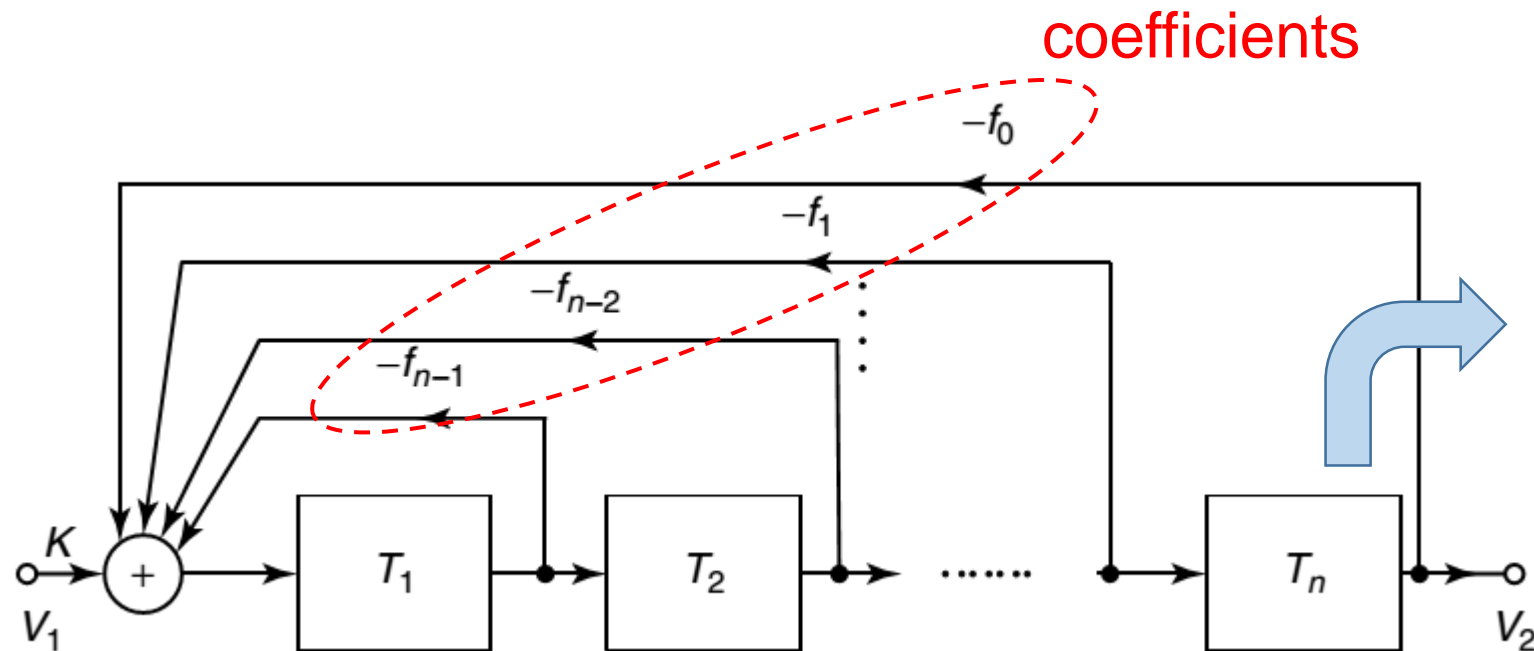- Cascaded Biquads: Feedback exist only inside blocks
 - MFL Filters: Feedback involve all stages together
- ➔ More Interaction: less sensitivity to component variations



- $T_i(s)$ can be:
- Integrators
 - Lossy Integrators
 - Biquads

“Follow the Leader Filter” (FLF) architecture”


Integral representation of transfer functions

$$\frac{V_2}{V_1} = \frac{a_n s^n + a_{n-1} s^{n-1} \dots + a_1 s + a_0}{s^n + b_{n-1} s^{n-1} \dots + b_1 s + b_0}$$

generic rational
transfer function


divide
by s^n

$$(s^n + b_{n-1} s^{n-1} \dots + b_1 s + b_0) V_2 = (a_n s^n + a_{n-1} s^{n-1} \dots + a_1 s + a_0) V_1$$

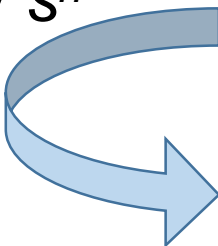
$$\left(1 + b_{n-1} \frac{1}{s}, \dots, +b_1 \frac{1}{s^{n-1}} + b_0 \frac{1}{s^n}\right) V_2 = \left(a_n + a_{n-1} \frac{1}{s}, \dots, +a_1 \frac{1}{s^{n-1}} + a_0 \frac{1}{s^n}\right) V_1$$

$$V_2 = \left(-b_{n-1} \frac{1}{s}, \dots, -b_1 \frac{1}{s^{n-1}} - b_0 \frac{1}{s^n}\right) V_2 + \left(a_n + a_{n-1} \frac{1}{s}, \dots, +a_1 \frac{1}{s^{n-1}} + a_0 \frac{1}{s^n}\right) V_1$$

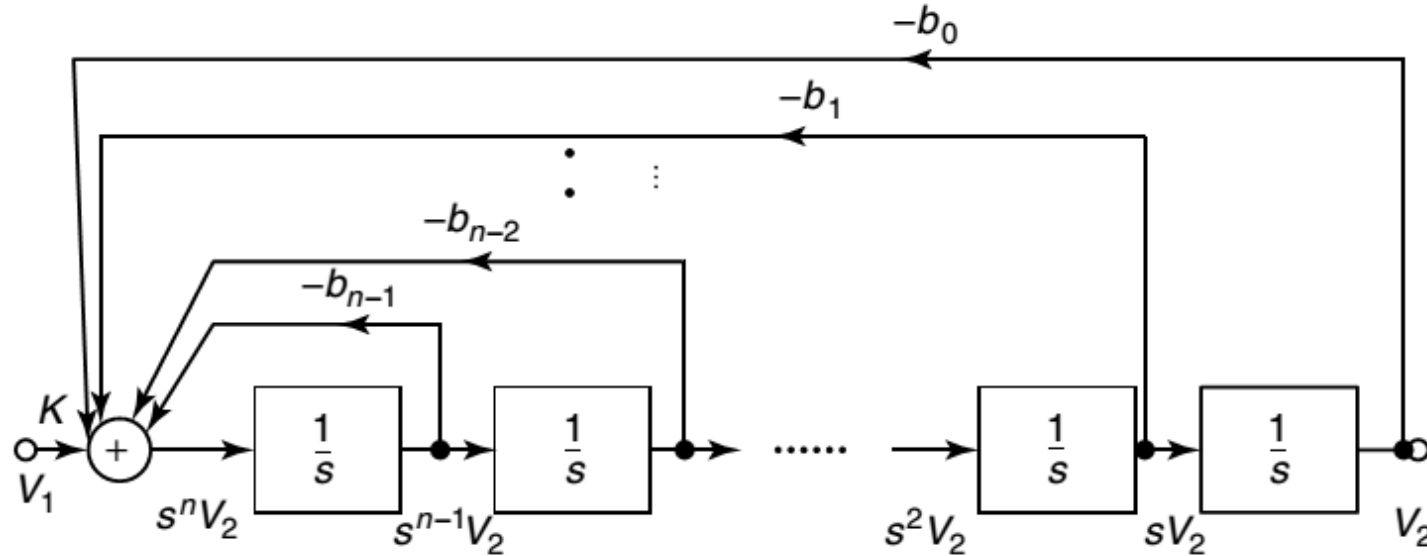State variable filters (MFL filters based on Integrators)




$$V_2 = V_1 \left(\frac{1}{s} \right)^n - b_0 \left(\frac{1}{s} \right)^n V_2 - b_1 \left(\frac{1}{s} \right)^{n-1} V_2 \dots - b_{n-1} \left(\frac{1}{s} \right) V_2$$

$$\frac{V_2}{V_1} = \frac{K}{s^n + b_{n-1} s^{n-1} \dots + b_1 s + b_0}$$



Low pass, all poles filters

Multi Feedback – Multi Feed Forward

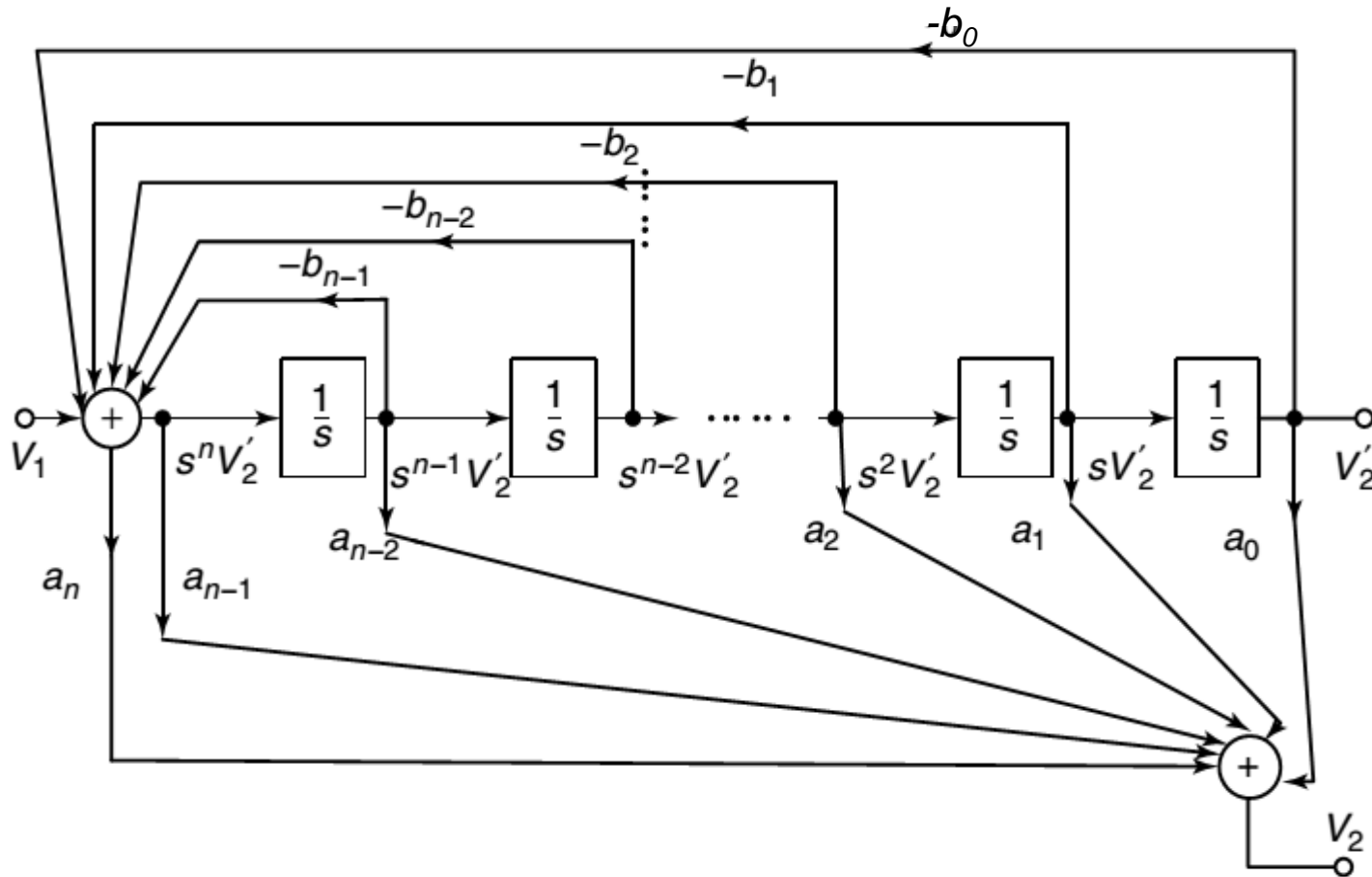


$$\frac{V_2'}{V_1} = \frac{1}{s^n + b_{n-1}s^{n-1} \dots + b_1s + b_0}$$

$$\frac{V_2}{V_1} = \frac{a_n s^n + a_{n-1} s^{n-1} \dots + a_1 s + a_0}{s^n + b_{n-1} s^{n-1} \dots + b_1 s + b_0}$$

Arbitrary Functions
(poles and zeros)


Integrators: Op-amp based solution

Integrator (inverting)

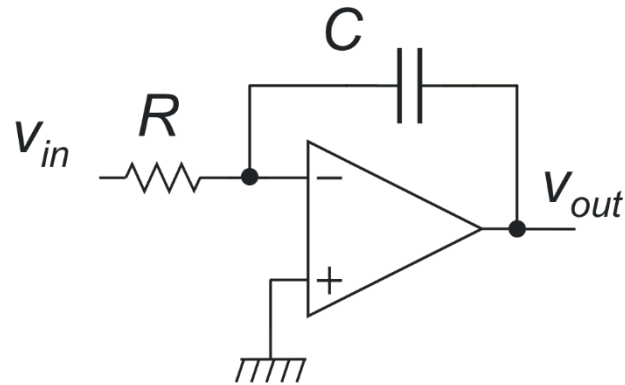


$$\frac{v_{out}}{v_{in}} = -\frac{1}{RC} \frac{1}{s}$$

Lossy Integrator (inverting)

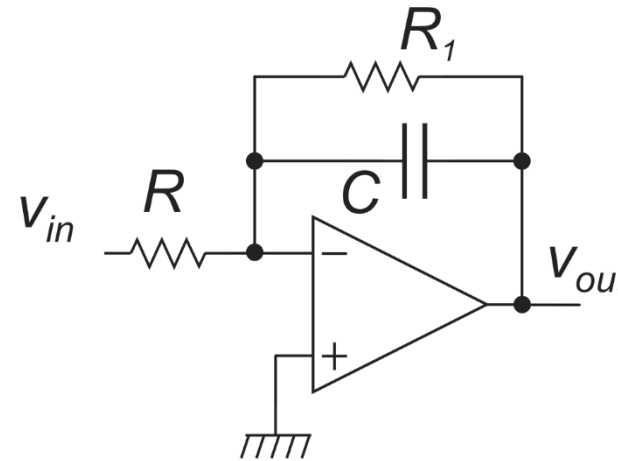

$$\frac{v_{out}}{v_{in}} = -\frac{R_1}{R} \left(\frac{\frac{1}{R_1 C}}{s + \frac{1}{R_1 C}} \right)$$

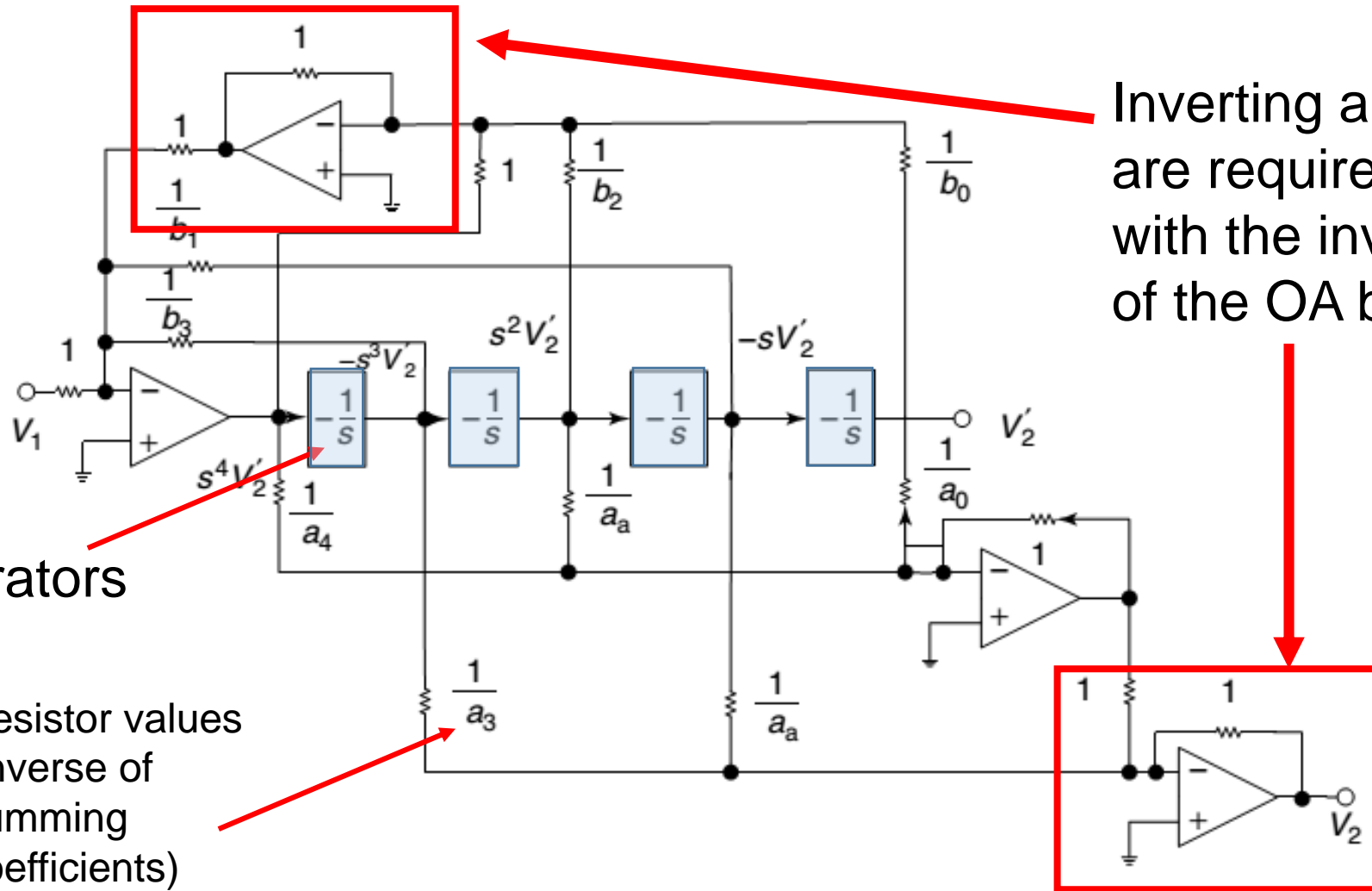Example: State variable Filter with Op-amp Integrators




Inverting amplifiers are required to cope with the inverting function of the OA based Integrators

Opamp integrators (inverting)

Resistor values (inverse of summing coefficients)


MLF: Example Universal 2nd order Filter

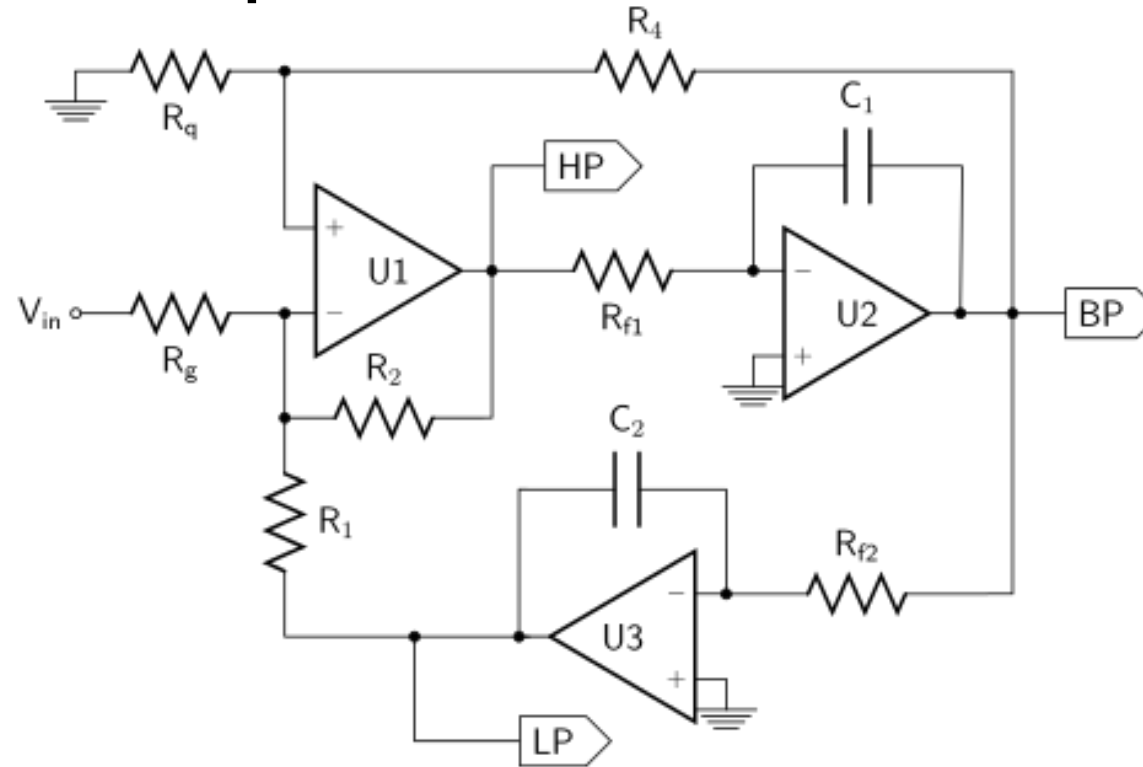

Kerwin-Huelsman-Newcomb (KHN) filter
(Produces LP, BP and HP outputs: Single Input – Multiple Output)

OTA: definitions and basic circuits


OTA (Transconductor)

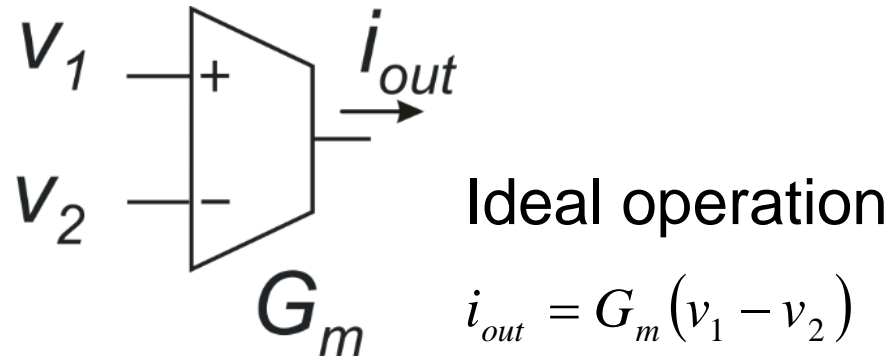


Typical non-idealities:

- Finite Rout
- Input Capacitance
- Frequency dependence of Gm
- Input/Output ranges


OTA-C (Gm-C) Integrator

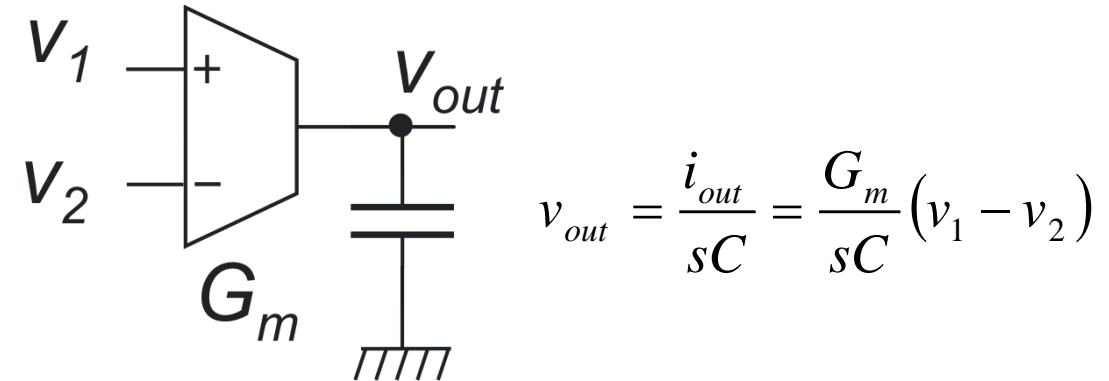

OTA-C (Gm-C) Eq. Resistor

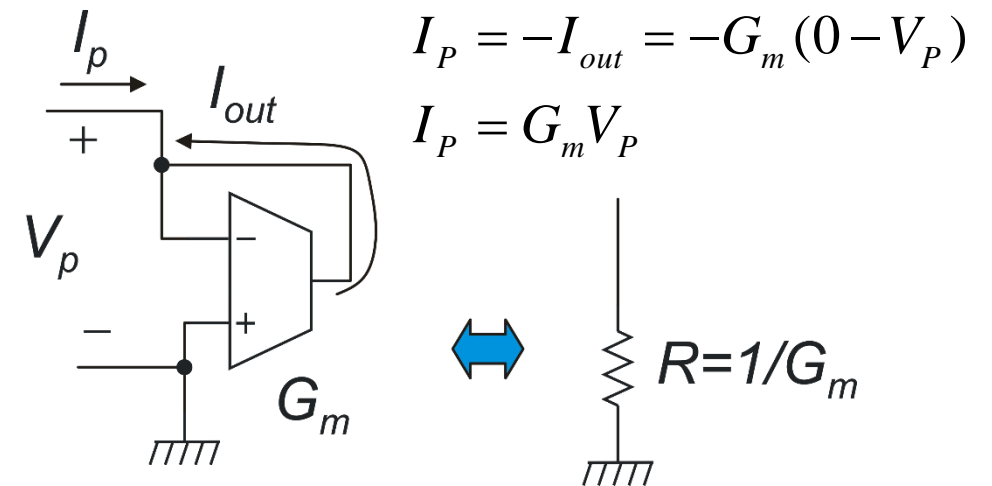


Ota-Based summing circuits

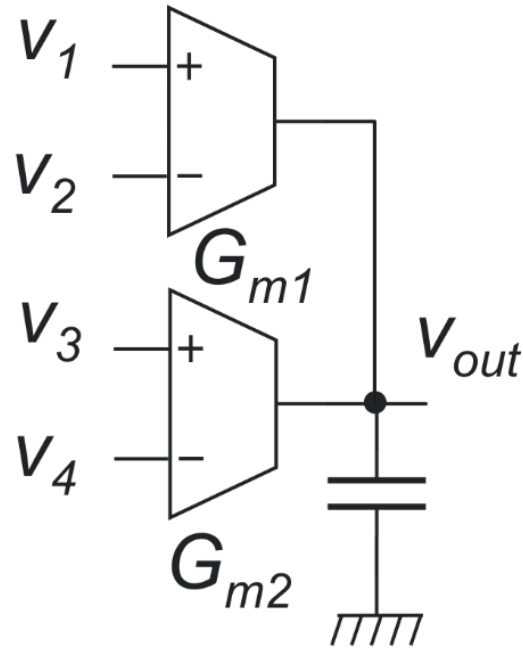

Summing Integrator
(inverting / non-inverting)

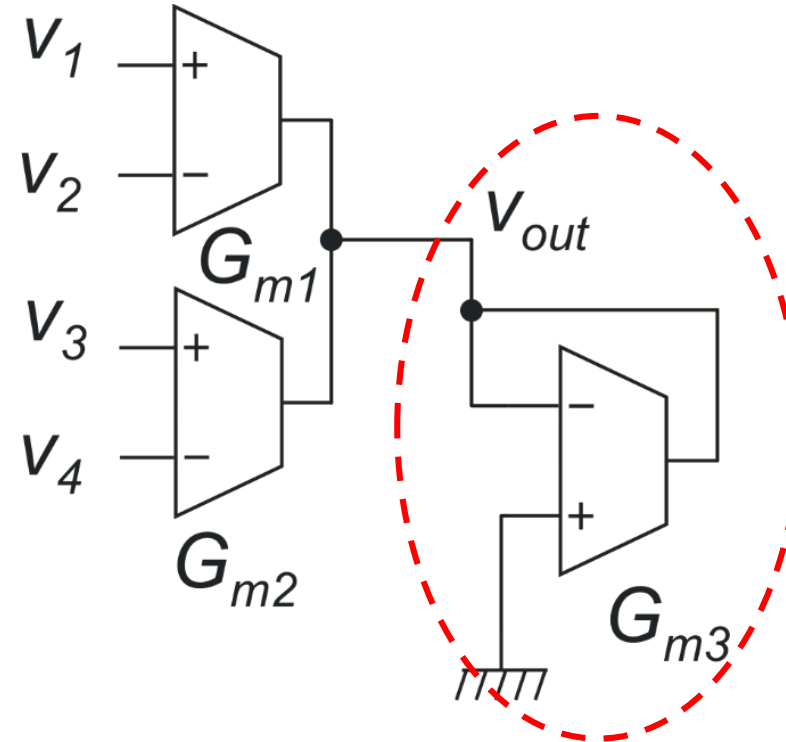
$$v_{out} = \frac{G_{m1}}{sC} \left[(v_1 - v_2) + \frac{G_{m2}}{G_{m1}} (v_3 - v_4) \right]$$



Summing amplifier
(inverting / non-inverting)

$$v_{out} = \frac{G_{m1}}{G_{m3}} (v_1 - v_2) + \frac{G_{m2}}{G_{m3}} (v_3 - v_4)$$



Gm-C integrator with feed-forward input

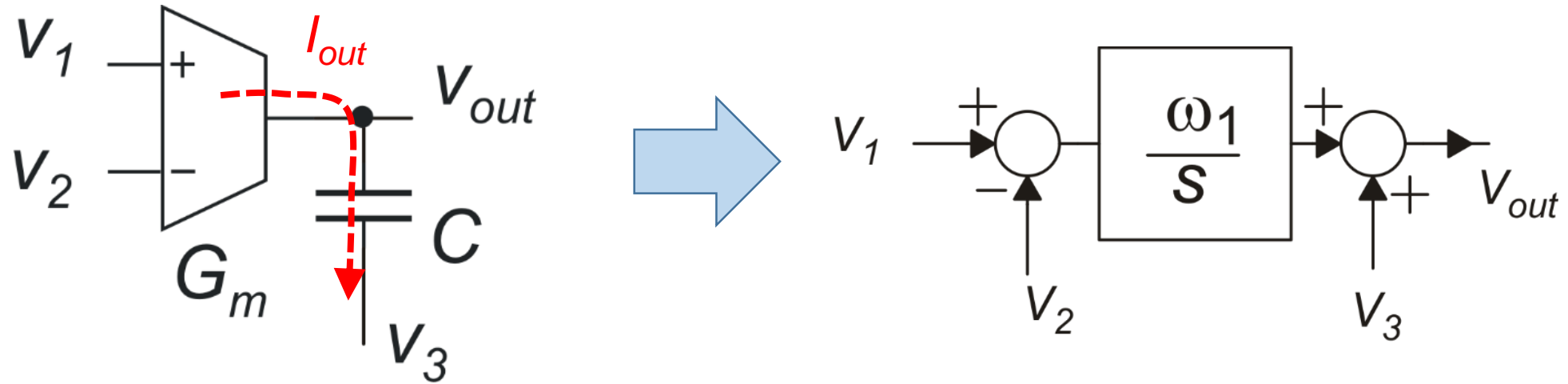


$$v_{out} = \frac{G_m}{sC} (v_1 - v_2) + v_3$$

$$\omega_1 = \frac{G_m}{C}$$

Gm-C integrator cascade

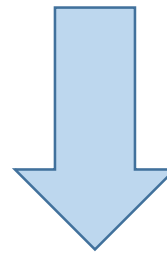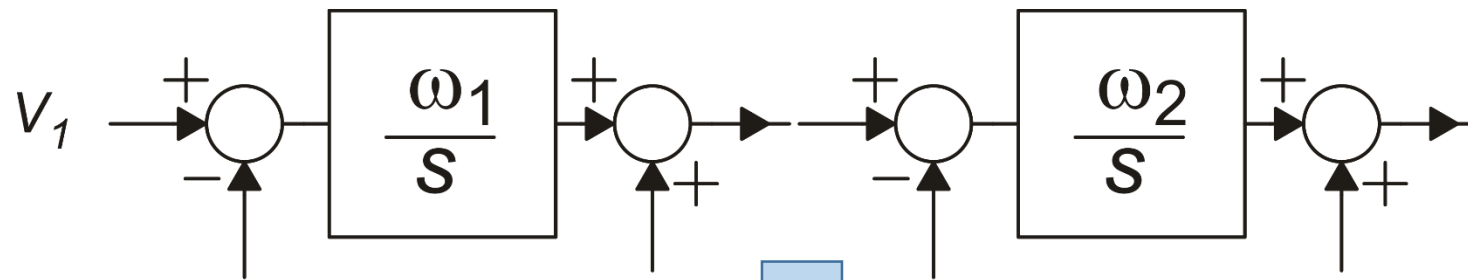


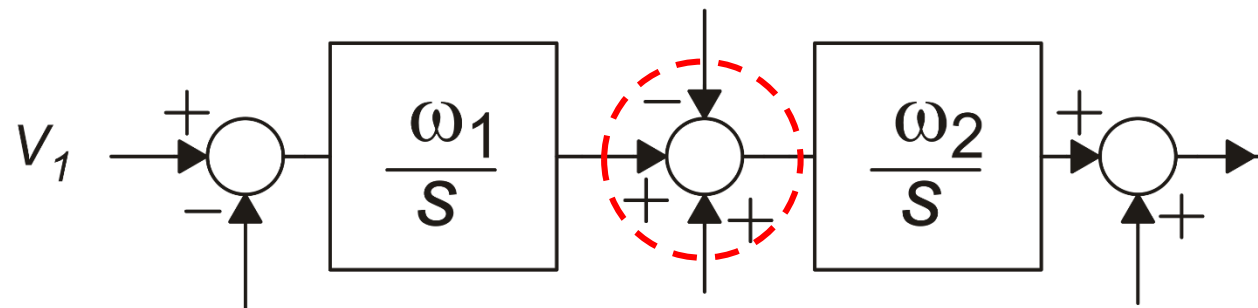Two signals with opposite signs can be added at each internal node of the cascade



Gm-C state variable filter: coefficients
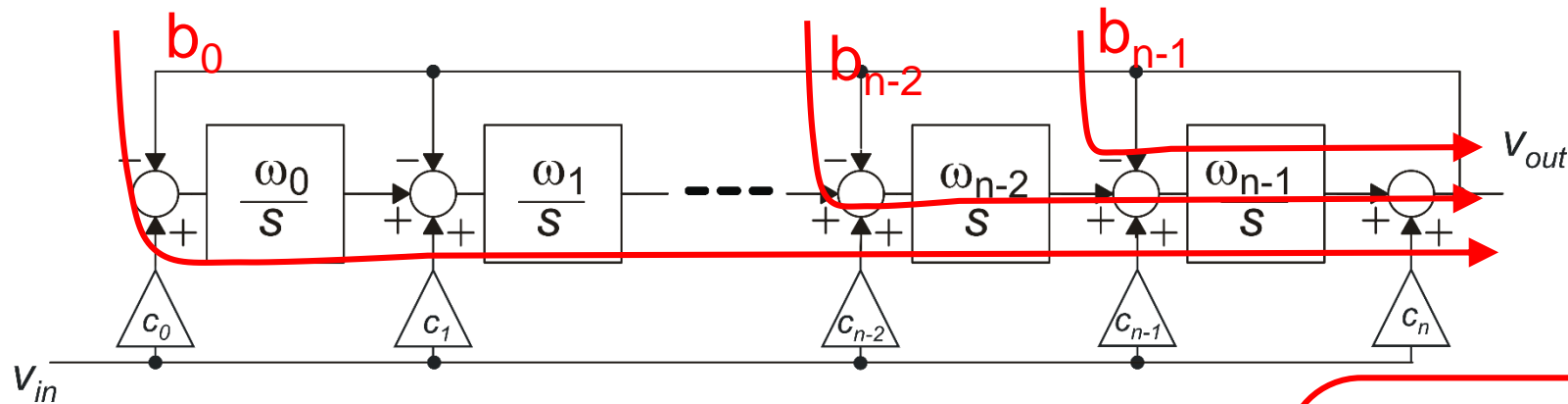
$$V_{out} = \left(-b_{n-1} \frac{1}{s}, \dots, -b_1 \frac{1}{s^{n-1}} - b_0 \frac{1}{s^n} \right) V_{out} + \left(a_n + a_{n-1} \frac{1}{s}, \dots, +a_1 \frac{1}{s^{n-1}} + a_0 \frac{1}{s^n} \right) V_{in}$$



$$b_{n-1} = \omega_{n-1}$$

$$b_{n-2} = \omega_{n-1} \omega_{n-2}$$

⋮

$$b_0 = \omega_{n-1} \omega_{n-2} \dots \omega_0$$

$$a_n = c_n$$

$$a_{n-1} = c_{n-1} b_{n-1}$$

$$a_{n-2} = c_{n-2} b_{n-2}$$




⋮

$$a_0 = c_0 b_0$$

Example: First order high pass / low pass filters

$$H(s) = \frac{\omega_p}{s + \omega_p}$$




low pass

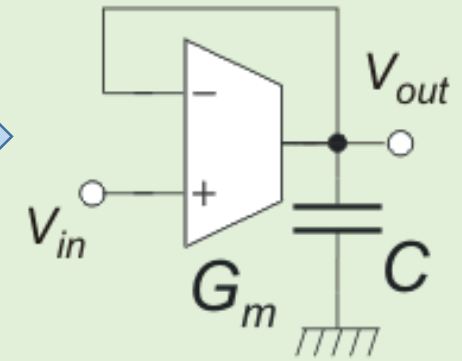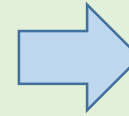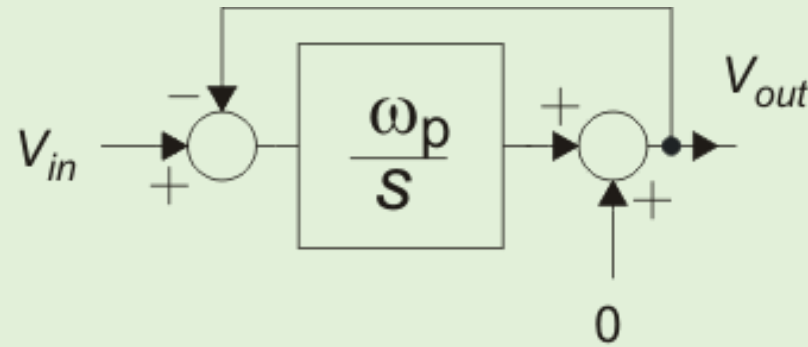


$$\omega_p = \frac{G_m}{C}$$

high pass

$$H(s) = \frac{s}{s + \omega_p}$$

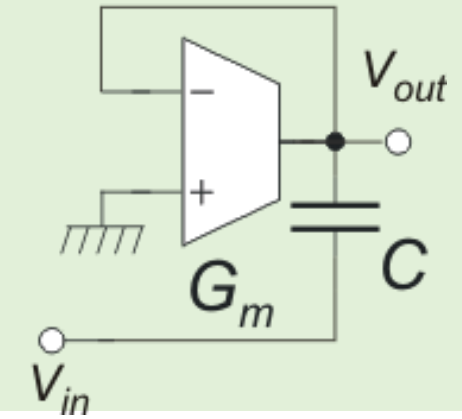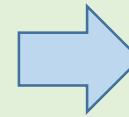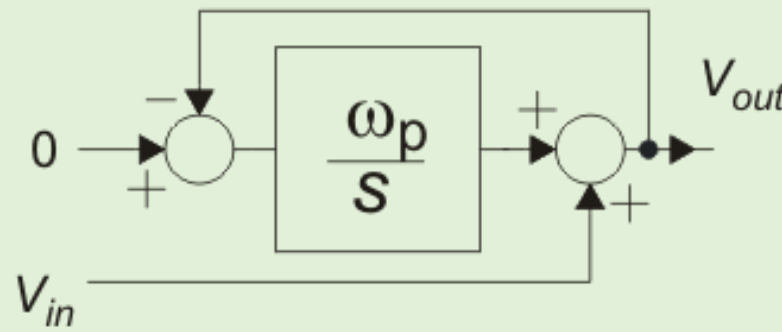

Example: State variable Gm-C biquad

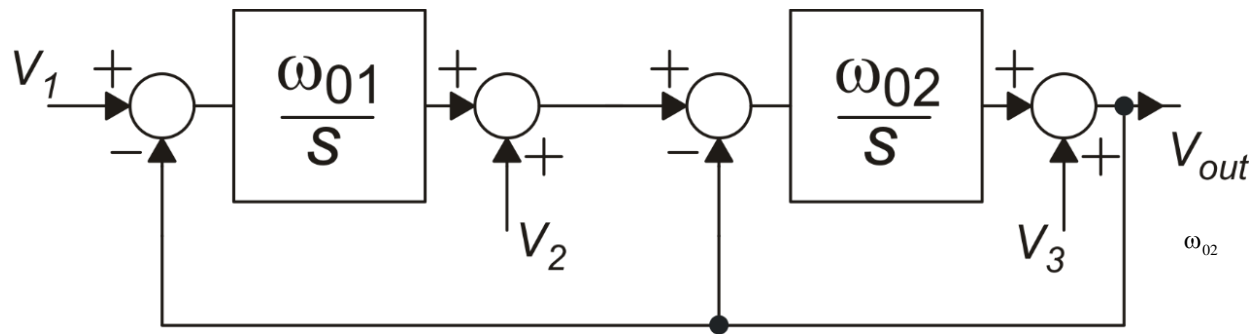

$$H(s) = \frac{B_2 s^2 + B_1 \frac{\omega_p}{Q_p} s + B_0 \omega_p^2}{s^2 + \frac{\omega_p}{Q_p} s + \omega_p^2}$$

$$v_1 = B_0 v_{in} \quad B_0, B_1, B_2 = \{0, 1\}$$


$$v_2 = B_1 v_{in}$$

$$v_3 = B_2 v_{in} \quad \text{Flexible Biquad}$$

$$\omega_p = \sqrt{\omega_{01} \omega_{02}}$$

$$Q_p = \sqrt{\frac{\omega_{01}}{\omega_{02}}}$$

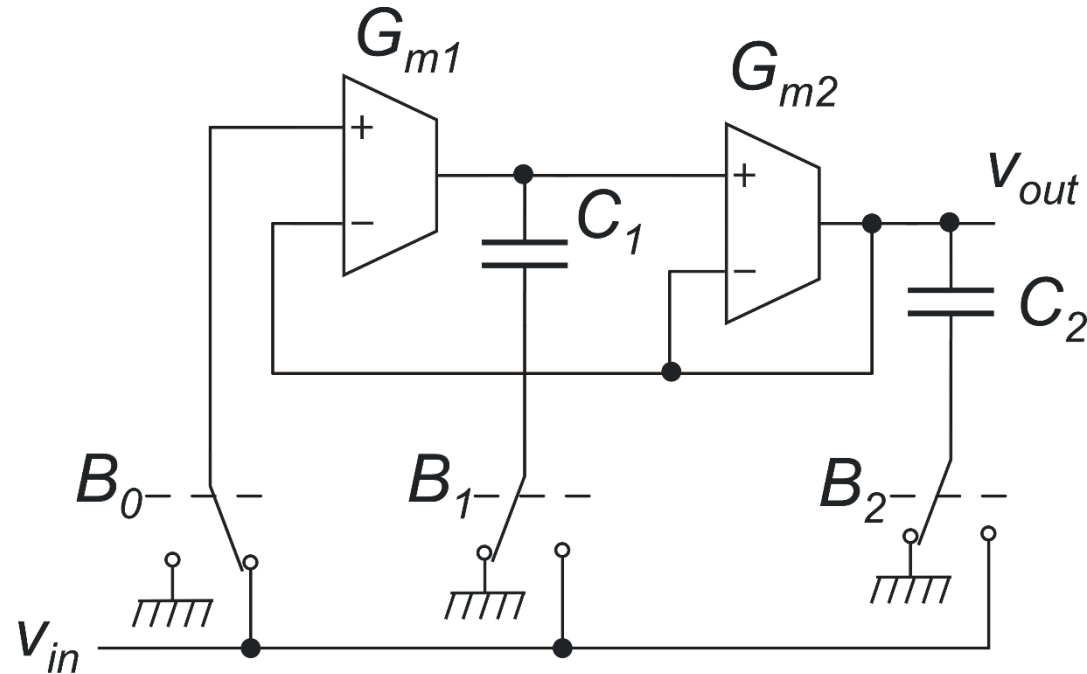State variable Flexible Biquad – OTA implementation



$$\omega_{01} = \frac{G_{m1}}{C_1} \quad \omega_{02} = \frac{G_{m2}}{C_2}$$




$$\omega_p = \sqrt{\frac{G_{m1}}{C_1} \frac{G_{m2}}{C_2}} \quad Q_P = \sqrt{\frac{G_{m1}}{G_{m2}} \frac{C_2}{C_1}}$$

Function	B0	B1	B2
Low pass	1	0	0
High pass	0	0	1
Band-Pass	0	1	0
Notch	1	0	1

Simulation of Ladder Filters with OTAs


- **Simulation of the inductor: application of the OTA based Gyrator**
- **Simulation of the nodal equations by means of OTAs (signal flow path)** May require inductor simulation, depending on the transfer function to synthesize and/or architecture

Gyrator


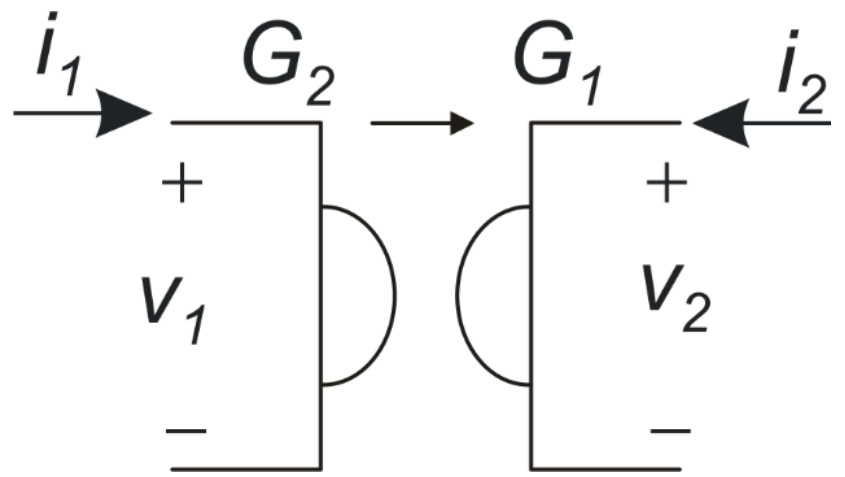


$$i_2 = -G_1 v_1$$

$$i_1 = G_2 v_2$$

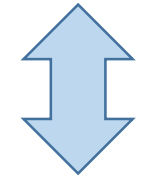

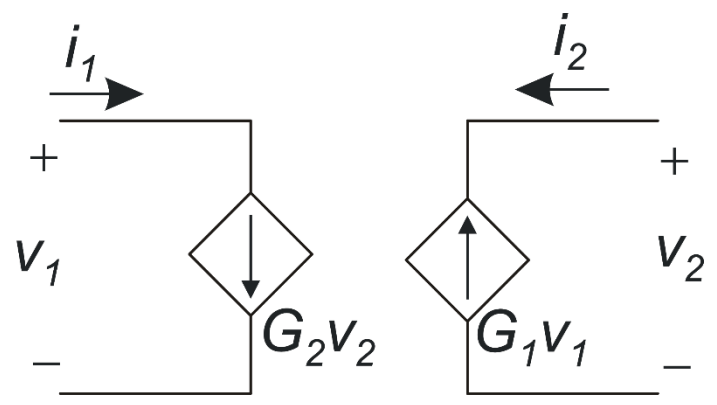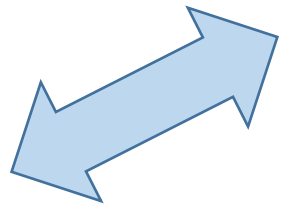
$$Y = \begin{pmatrix} 0 & G_2 \\ -G_1 & 0 \end{pmatrix}$$



Y-parameters equivalent circuit

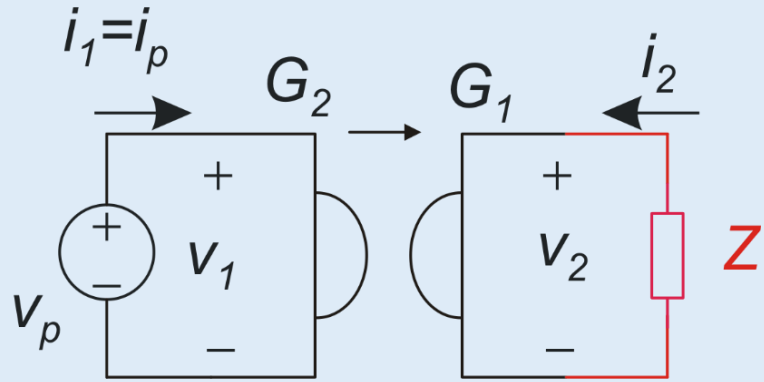Inductance simulation by means of a gyrator and a capacitor.




Generic Impedance Inversion

$$Z_V = \frac{v_P}{i_P} = \frac{v_P}{G_2 v_2} \quad v_2 = -i_2 Z = G_1 v_p Z$$


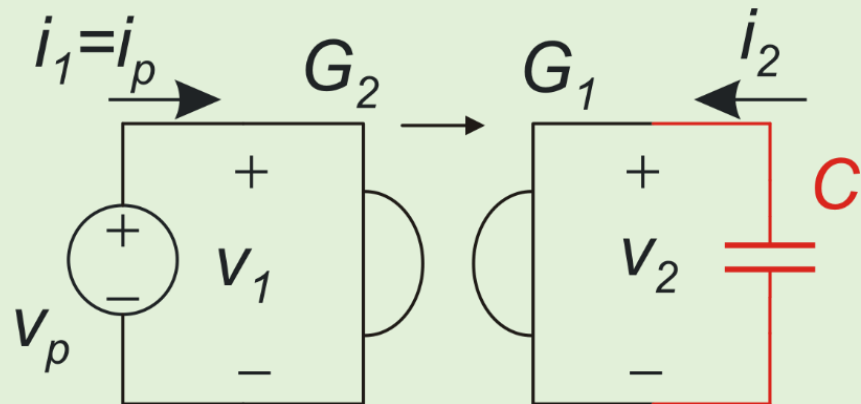
$$Z_V = \frac{v_P}{i_P} = \frac{v_P}{G_2 G_1 v_P Z} = \frac{1}{G_1 G_2 Z}$$






Inductor Synthesis


$$Z = \frac{1}{C_s} \Rightarrow Z_V = \frac{C_s}{G_1 G_2}$$

$$L_{EQ} = \frac{C}{G_1 G_2}$$

OTA Based Gyration

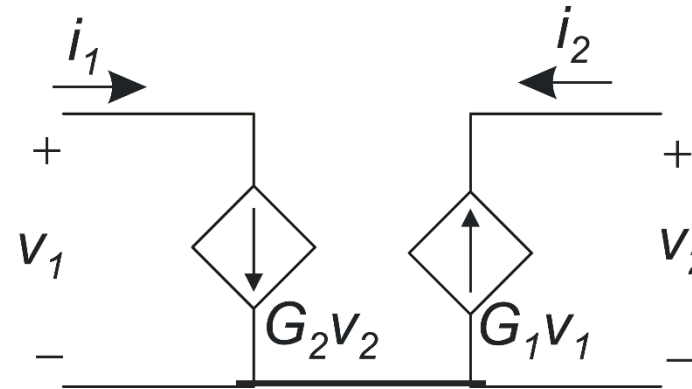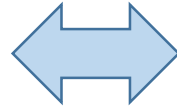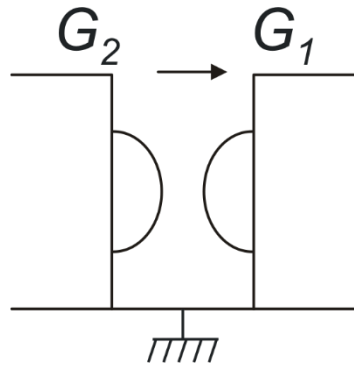


Grounded gyrator

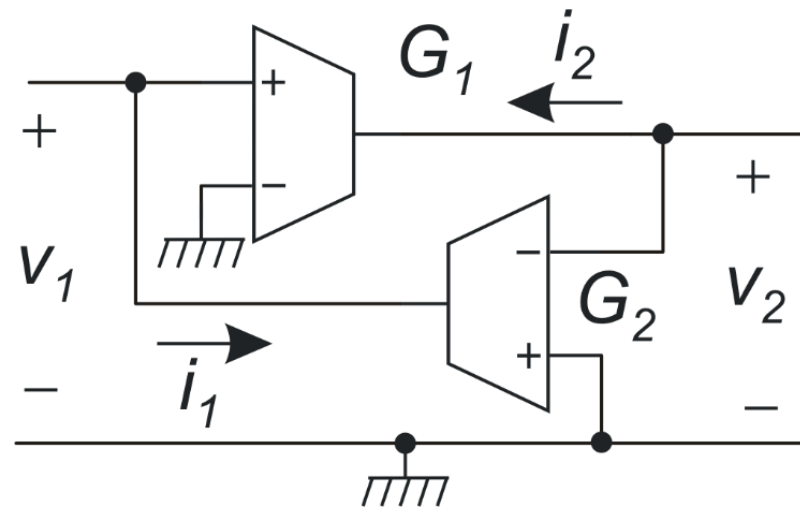

$$i_2 = -G_1 v_1$$


$$i_1 = G_2 v_2$$

Inductor simulation with OTAs

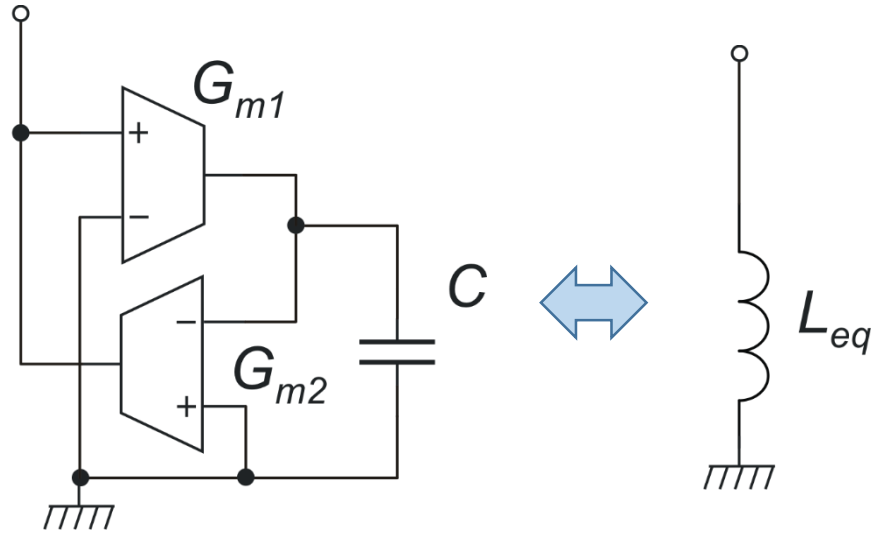

Grounded Inductor

$$L_{EQ} = \frac{C}{G_{m1} G_{m2}}$$

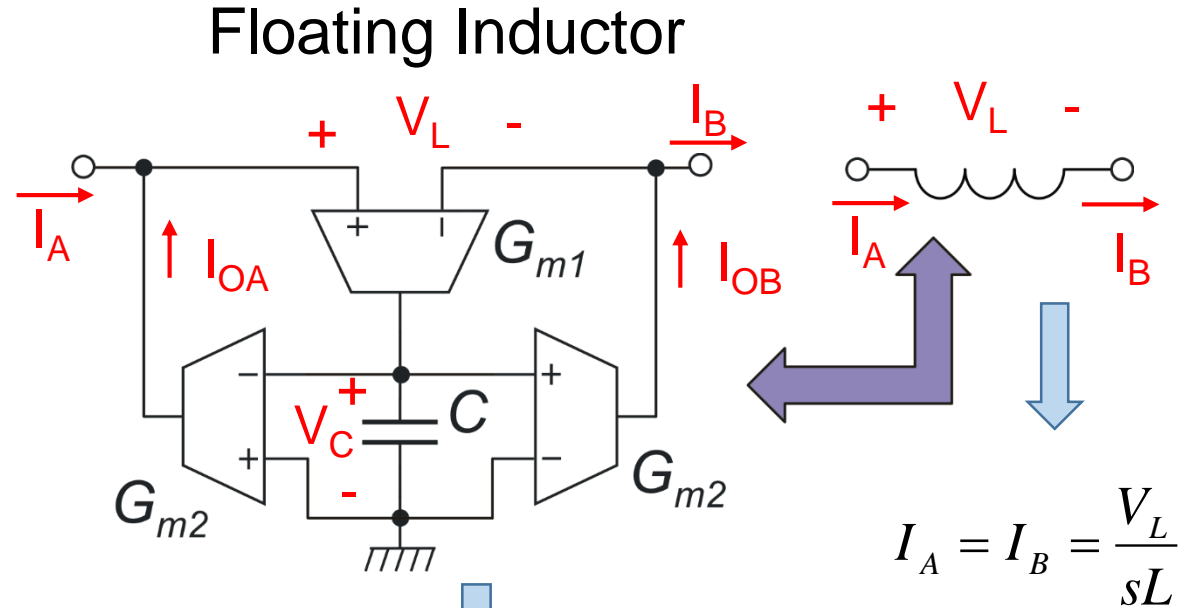

Floating Inductor

$$I_A = I_B = \frac{V_L}{sL}$$

$$V_C = \frac{1}{sC} G_{m1} V_L ;$$


$$I_A = -I_{OA} = G_{m2} V_C ; I_B = I_{OB} = G_{m2} V_C$$

$$I_A = I_B = \frac{G_{m2} G_{m1}}{sC} V_L$$

$$L_{EQ} = \frac{C}{G_{m1} G_{m2}}$$

Inductor simulation with OTAs - Example

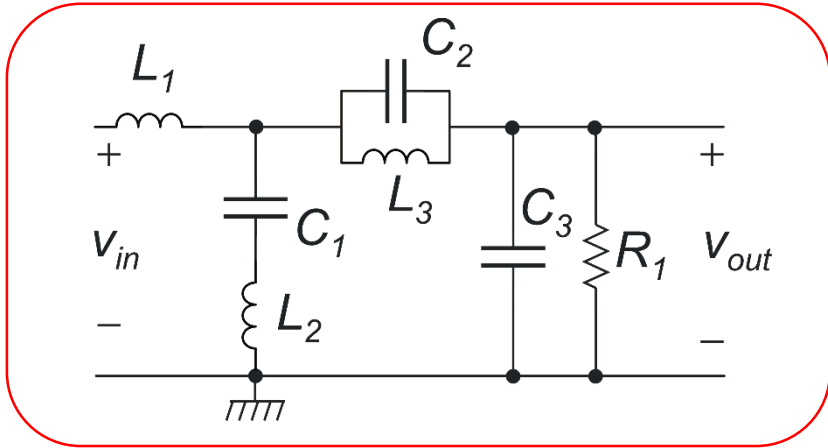L_1, L_3 : floating inductors
 L_2 : grounded inductor




Initial passive filter

$$C_{L1} = L_1 G_m^2$$


$$C_{L2} = L_2 G_m^2$$

$$C_{L3} = L_3 G_m^2$$

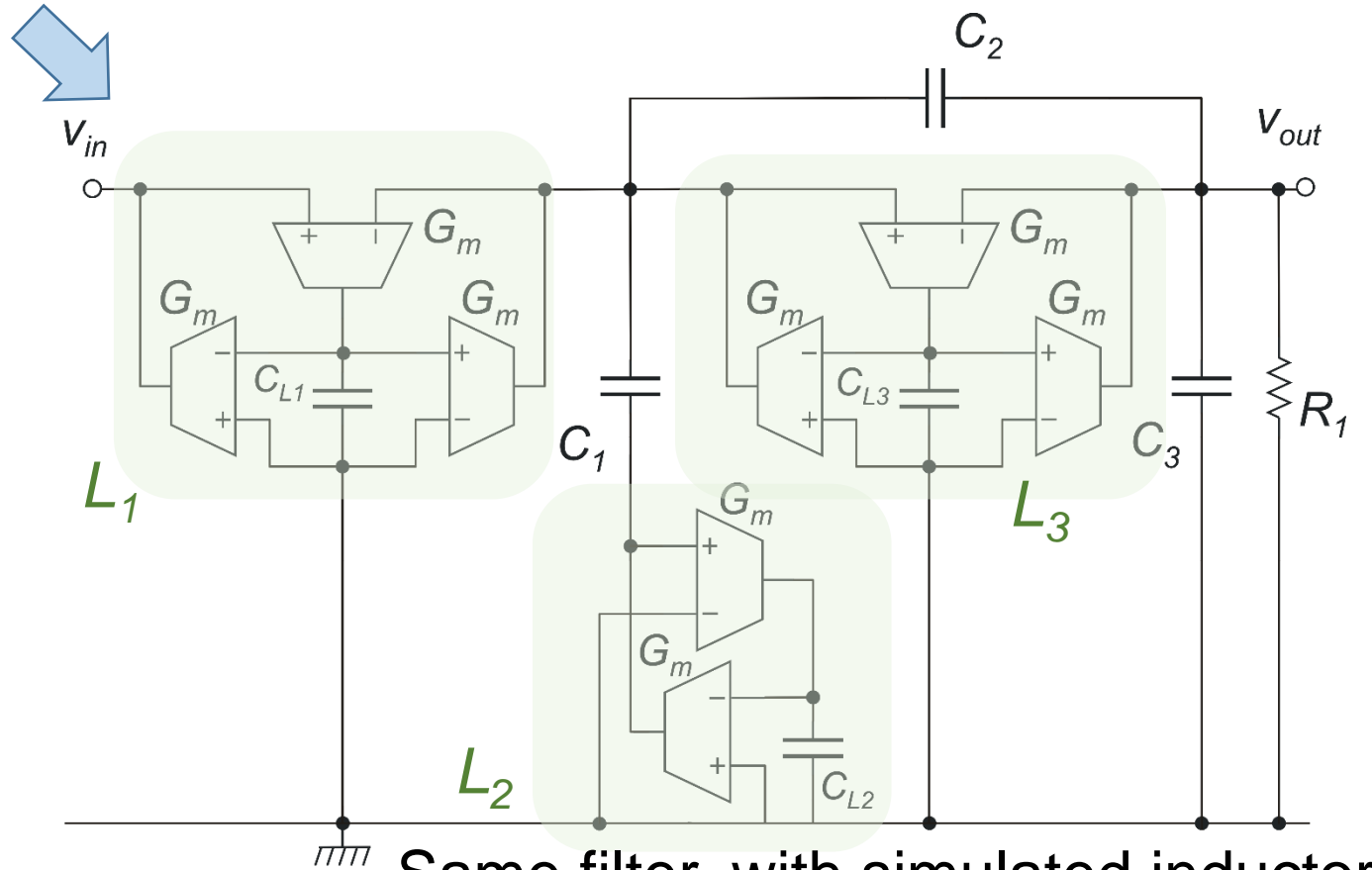

Same filter, with simulated inductors

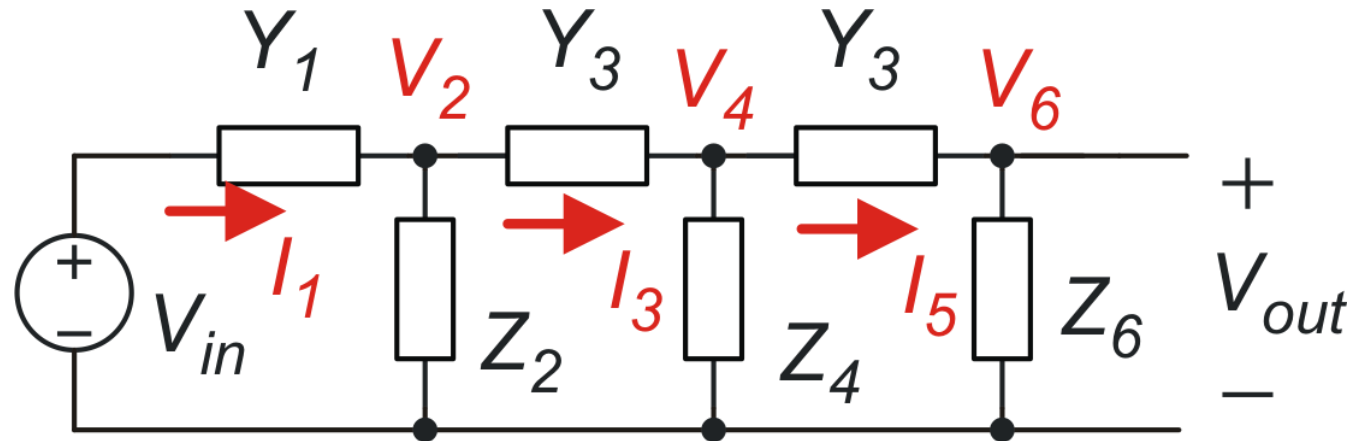Signal flow simulation of ladder (LC) networks with OTAs



Network Equations

$$I_1 = Y_1(V_{in} - V_2)$$

$$V_2 = Z_2(I_1 - I_3)$$

$$I_3 = Y_3(V_2 - V_4)$$

$$V_4 = Z_4(I_3 - I_5)$$


$$I_5 = Y_5(V_4 - V_6)$$

$$V_6 = Z_6 I_5$$


Variable transformations

Target: Transform current variables (I_1, I_3, I_5)
into voltage variables
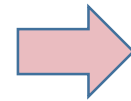
$$V_1 = \frac{1}{g} I_1 \quad V_3 = \frac{1}{g} I_3 \quad V_5 = \frac{1}{g} I_5$$



Homogeneous
equivalent
equations

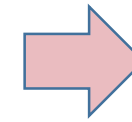

$$V_1 = \frac{Y_1}{g} (V_{in} - V_2)$$

$$V_2 = gZ_2 (V_1 - V_3)$$


$$V_3 = \frac{Y_3}{g} (V_2 - V_4)$$

$$V_4 = gZ_4 (V_3 - V_5)$$

$$V_5 = \frac{Y_5}{g} (V_4 - V_6)$$

$$V_6 = gZ_6 V_5$$

Leap-Frog architecture

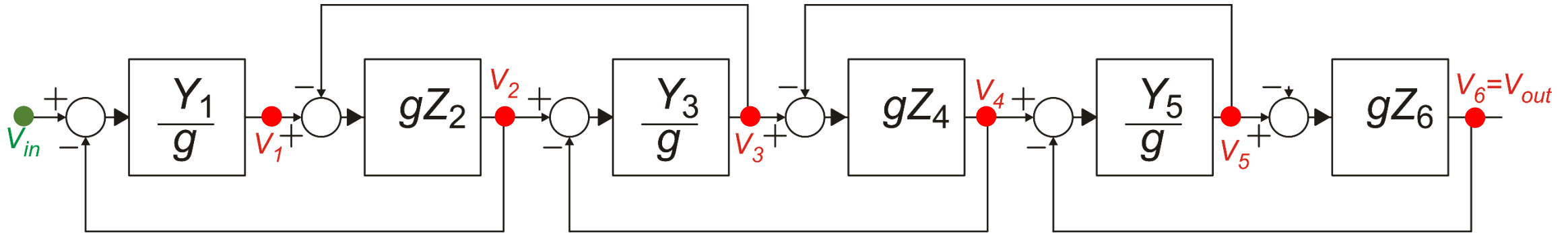


Homogeneous equivalent equations

$$V_1 = \frac{Y_1}{g} (V_{in} - V_2) \quad V_4 = gZ_4 (V_3 - V_5)$$

$$V_2 = gZ_2 (V_1 - V_3) \quad V_5 = \frac{Y_5}{g} (V_4 - V_6)$$

$$V_3 = \frac{Y_3}{g} (V_2 - V_4) \quad V_6 = gZ_6 V_5$$

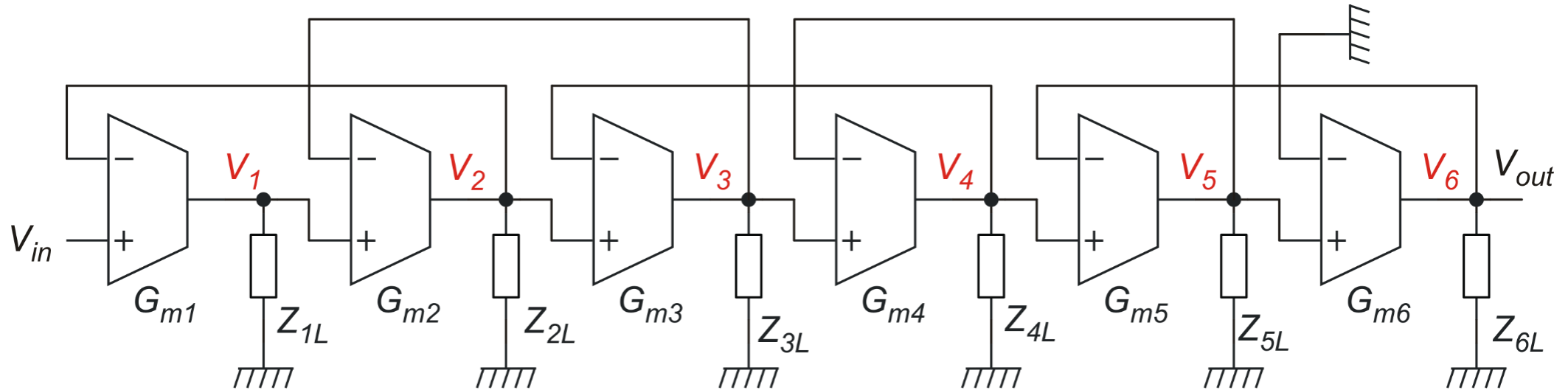OTA implementation of the Leap-Frog structure



$$V_1 = \frac{Y_1}{g} (V_{in} - V_2)$$

$$V_2 = gZ_2 (V_1 - V_3)$$

$$V_1 = Z_{1L} G_{m1} (V_{in} - V_2)$$

$$V_2 = Z_{2L} G_{m2} (V_1 - V_3)$$

$$Z_{1L} = \frac{Y_1}{gG_{m1}}$$


$$Z_{2L} = \frac{gZ_2}{G_{m2}}$$

same for all
odd indexes

same for all
even indexes

Example: 5th Order Chebyshev Filter

$f_p = 10 \text{ kHz}$

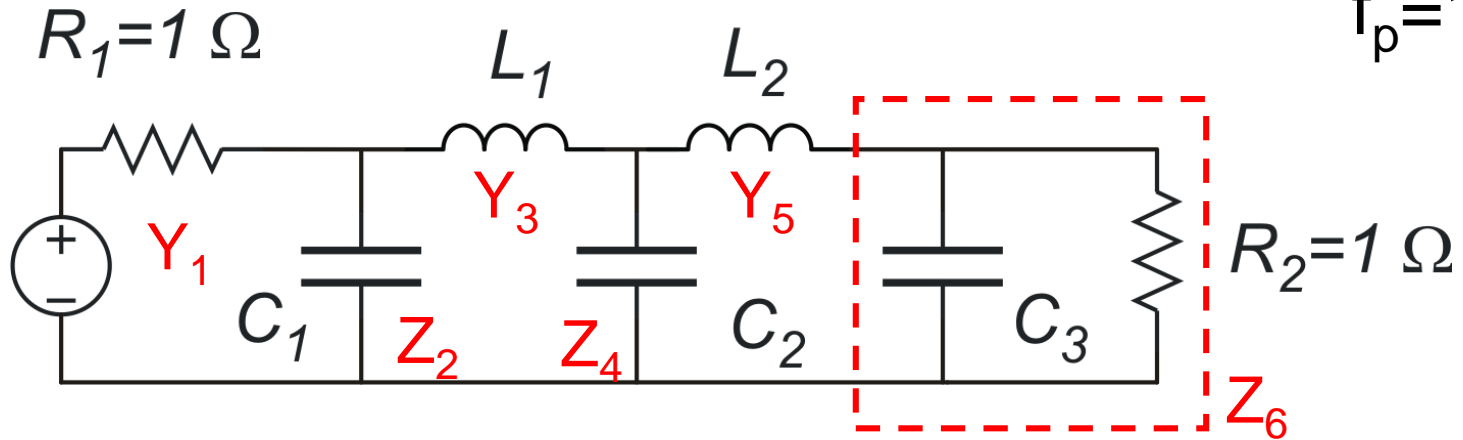

$C_1 = 33.9 \mu\text{F}$
 $L_1 = 17.35 \mu\text{H}$
 $C_2 = 47.7 \mu\text{F}$
 $L_2 = 17.35 \mu\text{H}$
 $C_3 = 33.9 \mu\text{F}$

$$Z_{1L} = \frac{1}{R_1} \frac{1}{gG_{m1}} \quad g = 1 \text{ S} \quad R_1 = 1 \Omega \quad Z_{1L} = \frac{1}{G_{m1}} \quad Z_{1L} = 1 \text{ k}\Omega \Rightarrow G_{m1} = 1 \text{ mS}$$

$$Z_{2L} = \frac{gZ_2}{G_{m2}} = \frac{g}{sC_1G_{m2}} \Rightarrow Z_{2L} = \frac{1}{sC_{2L}} \quad C_{2L} = \frac{G_{m2}}{g} C_1 \quad g = 1 \text{ S} \quad C_{2L} = 339 \text{ pF} \quad G_{m2} = 10 \mu\text{S}$$

Example: 5th Order Chebyshev Filter


$$Z_{3L} = \frac{Y_3}{gG_{m1}} \quad Y_3 = \frac{1}{sL_1} \quad \Rightarrow \quad Z_{3L} = \frac{1}{sL_1 gG_{m1}} = \frac{1}{sC_{3L}} \quad \Rightarrow \quad C_{3L} = L_1 gG_{m1}$$

$$g = 1 \text{ S} \quad \Rightarrow \quad C_{3L} = 173.5 \text{ pF}$$

$$G_{m3} = 10 \text{ } \mu\text{S}$$

Z_{4L}, Z_{5L}
Same procedure

Z_{6L}

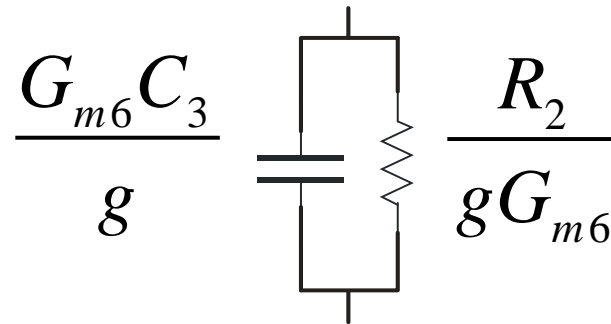

$$Z_{6L} = \frac{gZ_6}{G_{m6}} = \frac{g}{G_{m6}} \frac{1}{\frac{1}{R_2} + sC_3} = g \frac{1}{\frac{G_{m6}}{R_2} + sG_{m6}C_3}$$

- $R_{1L} = 1 \text{ k}\Omega$
- $C_{2L} = 339 \text{ pF}$
- $C_{3L} = 173.5 \text{ pF}$
- $C_{4L} = 47.7 \text{ pF}$
- $C_{5L} = 173.5 \text{ pF}$
- $Z_{6L} = 100 \text{ k}\Omega \parallel 339 \text{ pF}$
- $G_{m1} = 1 \text{ mS}$
- $G_{m2-6} = 10 \text{ } \mu\text{S}$

Frequent choices in active ladder filters

- Inductor synthesis :

 - HP filters (ideal for all-grounded inductors)

 - BP filters

 - LP – filters with zeroes


- Leapfrog architectures:

 - LP all – pole filters

 - BP filters (resonant groups simulated by biquads)


Self-Tuning of OTA Filters

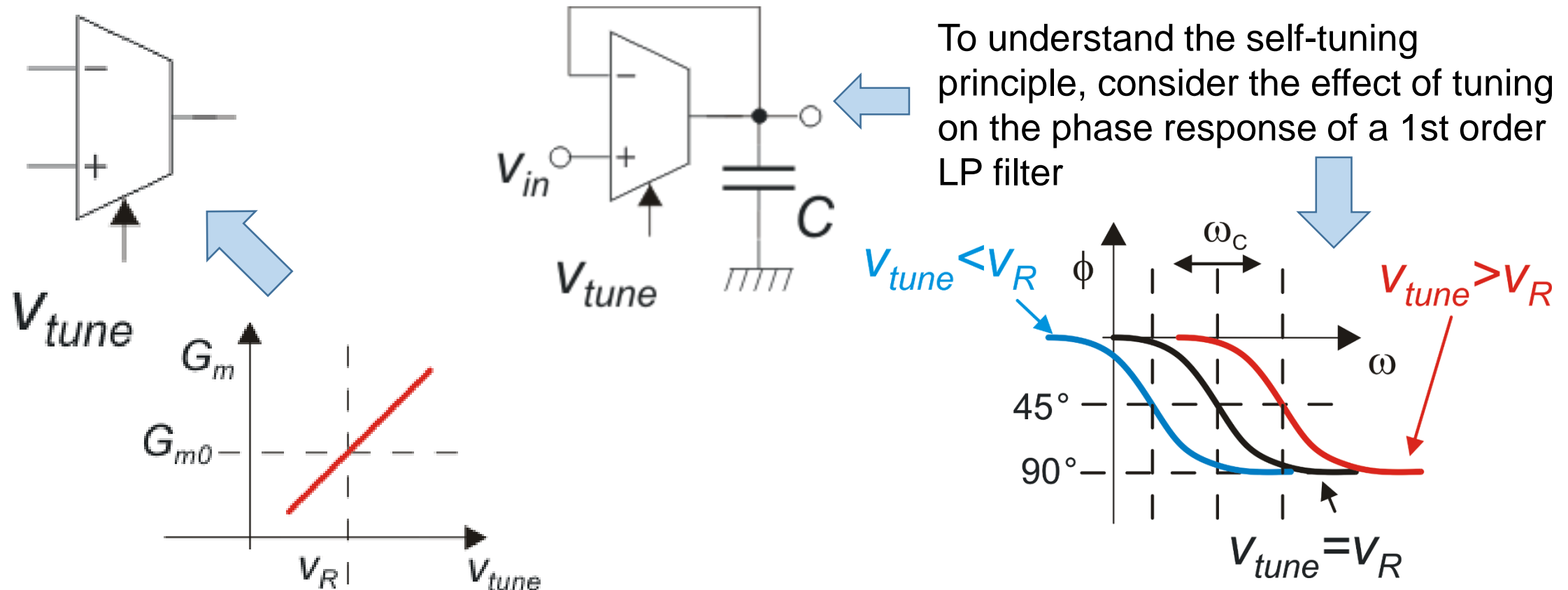In integrated circuits, G_m 's and capacitances are strongly affected by PVT variations (up to $\pm 30\%$ variations). For these reasons, in most OTAs the G_m can be controlled by means of a voltage applied to a proper terminal (V_{tune}). In this way self-tuning of the filter can be accomplished.



Self-Tuning of OTA Filters: master slave approach

Reference frequency source

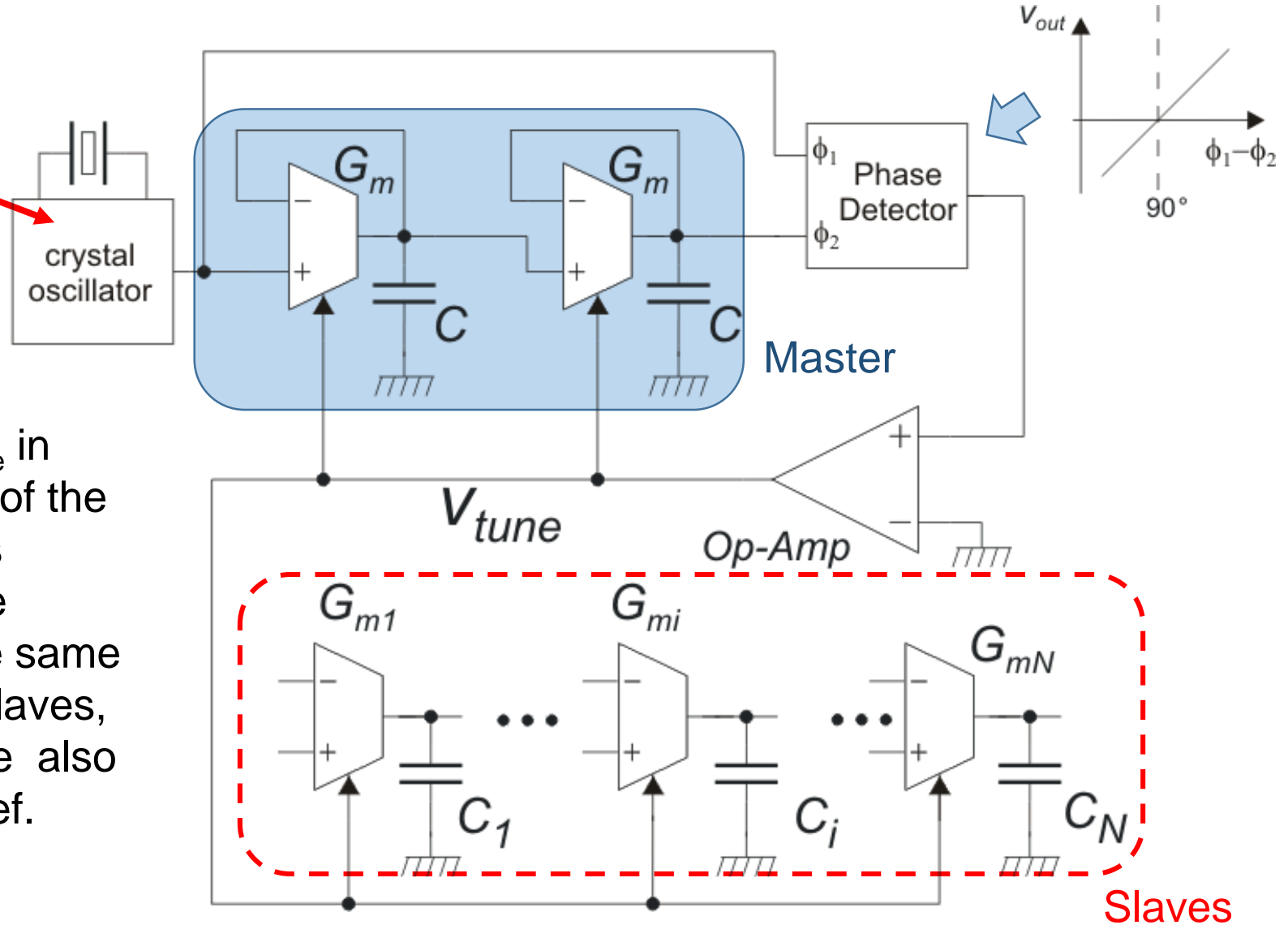

The loop varies V_{tune} in such a way that ωC of the two master LP filters equals the reference frequency. Since the same V_{tune} is fed to the slaves, their G_m/C ratios are also proportional to the ref. frequency.