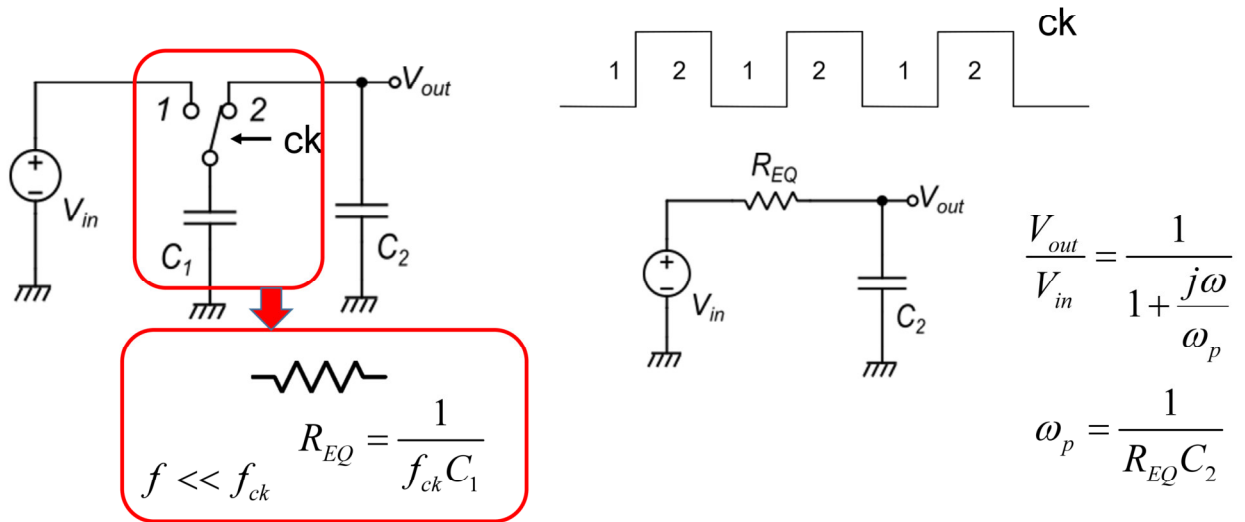




# Switched Capacitor (SC) circuits: general considerations

The SC equivalent resistance



# Switched Capacitor (SC) circuits: general considerations

The discrete time nature of SC circuits

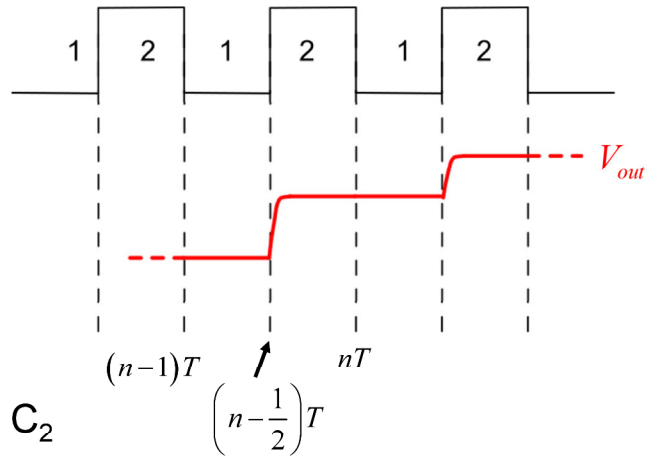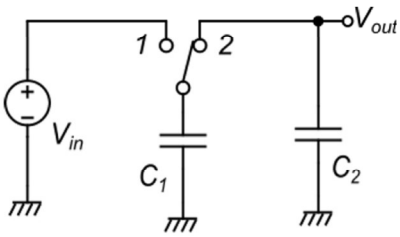

Phase 1:  $V_{out}$  holds,  $V_{C1} = V_{IN}$

Phase 2:  $C_1$  **samples**  $V_{IN}$  and discharges into  $C_2$

$$V_{out}(nT) = \frac{C_1 V_{in} \left( \left( n - \frac{1}{2} \right) T \right) + C_2 V_{out} \left( (n-1)T \right)}{C_1 + C_2}$$

← This discrete-time equation is valid at any frequency

$$f \ll f_{ck}$$


# Non-idealities in (SC) circuits

Sampling of a voltage on a capacitor: errors

- $kT/C$  noise
- Charge injection

## The $kT/C$ noise:


a simple example

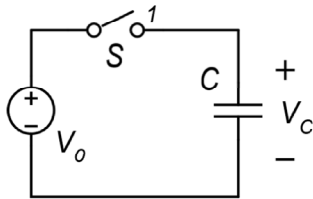

Phase 1: track

Phase 2: hold

Simple example:  
 $V_0$  is constant


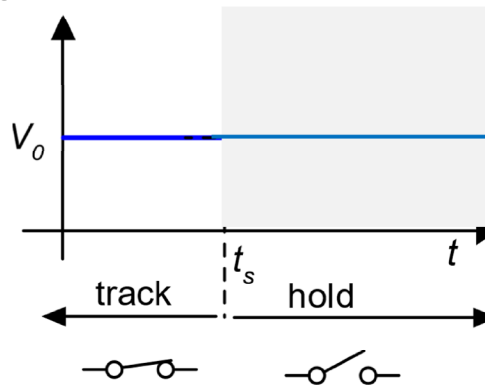


$V_\epsilon$  is present even if the switch is perfectly ideal

What is the origin of  $V_\epsilon$  ?
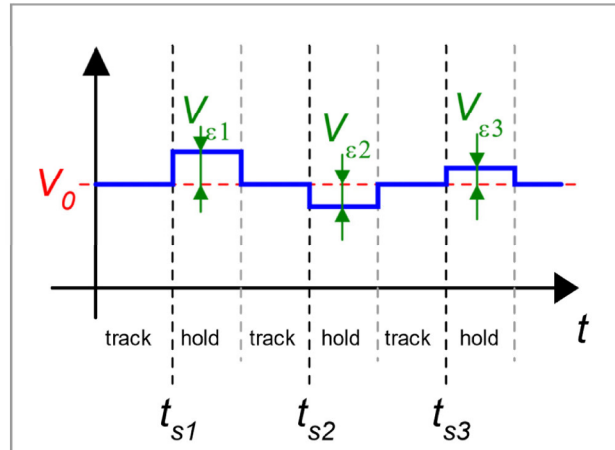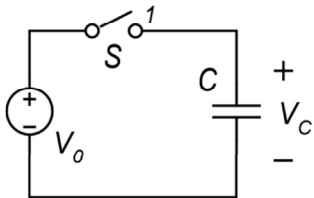
## Random nature of $V_\epsilon$

Repeating the sampling operation several time, the error is everytime different both in terms of magnitude and sign: it is a **random process**




Its mean square value is determined only by:

- capacitor value
- temperature

$$\langle v_\epsilon^2 \rangle = \frac{kT}{C}$$



## Origin of the $kT/C$ noise

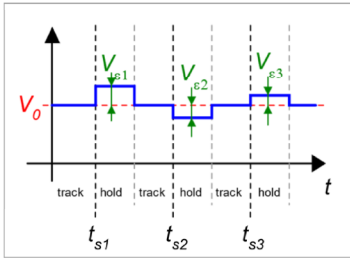


$$\langle v_{\epsilon}^2 \rangle = \frac{kT}{C}$$

Now it is clearer: voltage  $V_C$  was already fluctuating due to the noise of the resistor and we simply sample  $V_0$  together with the noise sampled at  $t_s$

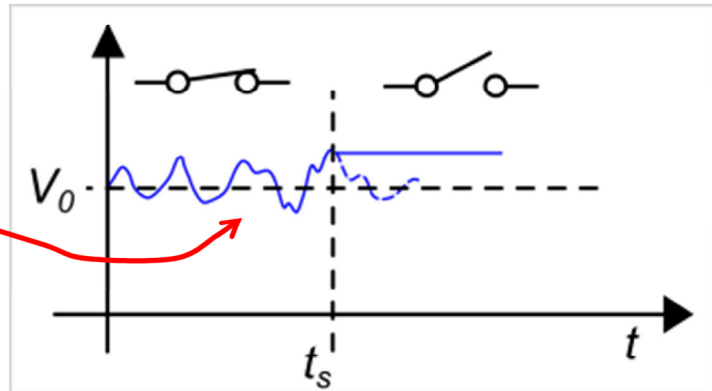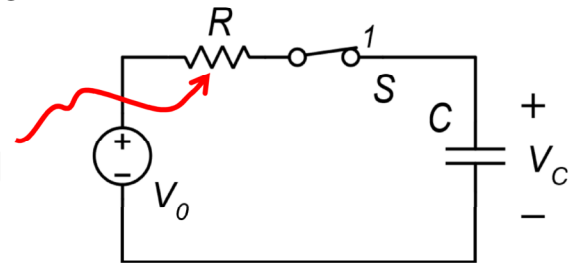Let us add a series resistance: it can be due to the switch on-resistance and to the equivalent resistance of voltage source  $V_0$ .




## Origin of the $kT/C$ noise

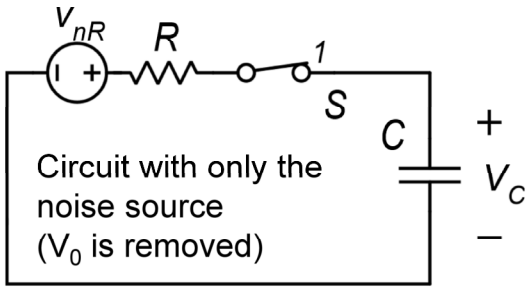

$$S_{VC} = 4kTR \frac{1}{1 + \left(\frac{f}{f_p}\right)^2} \quad f_p = \frac{1}{2\pi RC}$$


$$\langle v_{nc}^2 \rangle = \int_0^\infty S_{VC}(f) df = \frac{kT}{C}$$

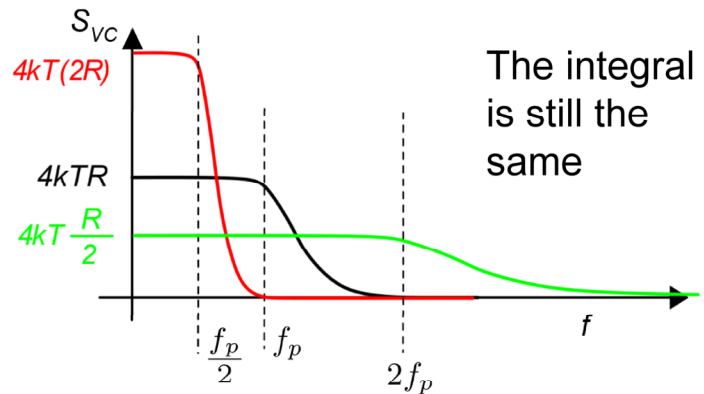$R \rightarrow 2R$      $R \rightarrow R/2$



The ideal case ( $R=0$ ) represents a limit where  $4kTR$  tends to zero and  $f_p$  tends to infinity. Again, the integral is still the same
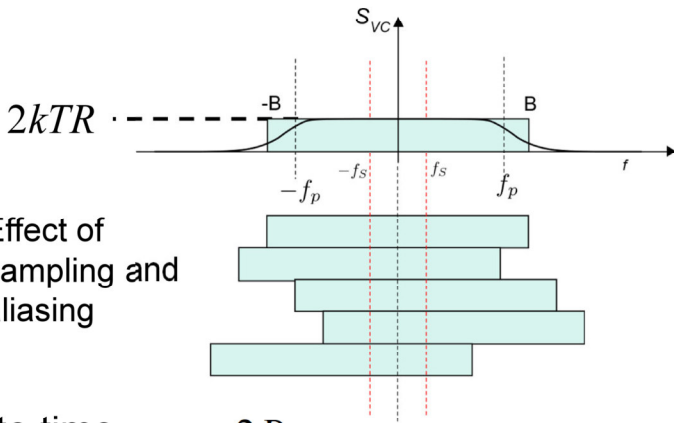
# kT/C noise as a result of continuous time noise sampling



Two-sided spectral density of voltage  $V_C$

The green rectangle is a simplified representation of the PSD

For the integral (i.e. mean square voltage of  $V_C$ ) to be the same,  $B$  must be the effective noise BW:


Discrete time PSD

if  $\frac{2B}{f_s} \gg 1$

$$B = f_p \frac{\pi}{2}$$

$$S_{n-KTC} = \left(1 + \frac{2B}{f_s}\right) 2kTR \cong \left(2 \cdot \frac{1}{2\pi RC} \frac{\pi}{2} \frac{1}{f_s}\right) 2kTR = \frac{kT}{C} \frac{1}{f_s}$$

## Changing the sampling frequency

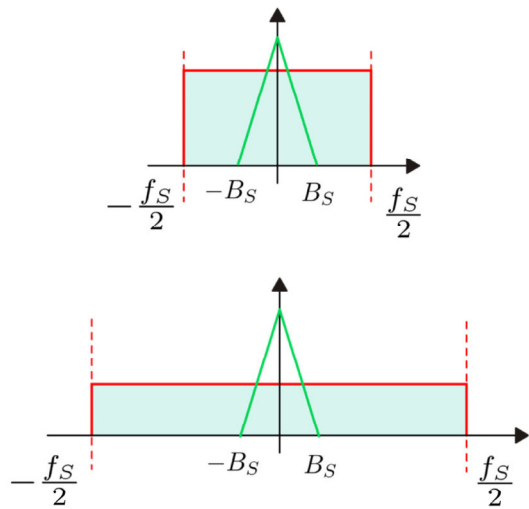

The integral of the  $kT/C$  noise PSD is equal to  $kT/C$ , independently of the sampling frequency

Increasing the sampling frequency, the PSD is reduced proportionally to maintain the integral constant

In this way, filtering the output sequence in the discrete time domain (either by digital or analog processing), we get less noise in the signal bandwidth



## $kT/C$ noise in summary


- $kT/C$  noise is always present when we sample a voltage on a capacitor. The mean-square voltage of the samples is equal to  $kT/C$  and is independent of the series resistances of the switch, voltage source and capacitor.
- The result of sampling with a uniform sampling period produces a discrete time sequence affected by  $kT/C$  noise.
- If the sampling frequency  $f_S$  is  $\ll f_p$ , (i.e.  $B \gg f_S$ ), then the PSD of the  $kT/C$  noise is constant over the DT-frequency interval  $-f_S/2, f_S/2$ .
- Sometimes it is convenient to refer to the noise in terms of charge accumulated into the capacitor. In this case:

$$Q_\varepsilon = V_\varepsilon C \qquad \langle Q_\varepsilon^2 \rangle = \langle V_\varepsilon^2 \rangle C^2 = \frac{kT}{C} C^2 = kTC$$

The **charge injection** phenomenon: a systematic error in SC circuits




Differently from the  $kT/C$  noise, charge injection is due to switch **non-idealities**

The n-MOS switch

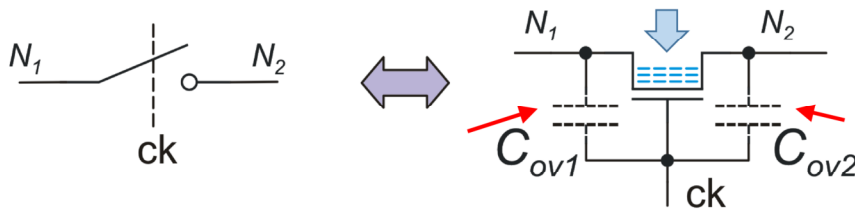


- Presence of overlap capacitance between the switch terminals and the control voltage
- In the on-state, there is charge accumulated into the channel (the mobile charge) that have to be drawn from the drain and source where it has to be pushed back when the switch is turned off
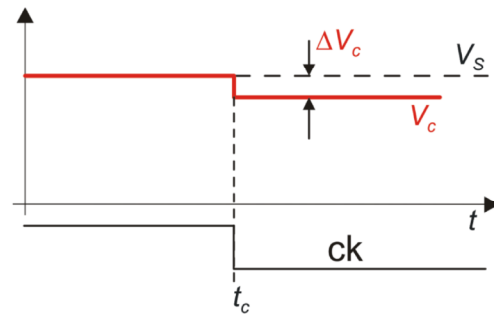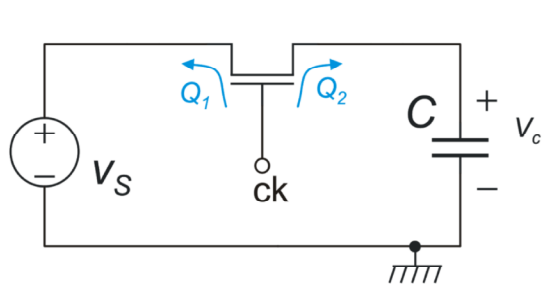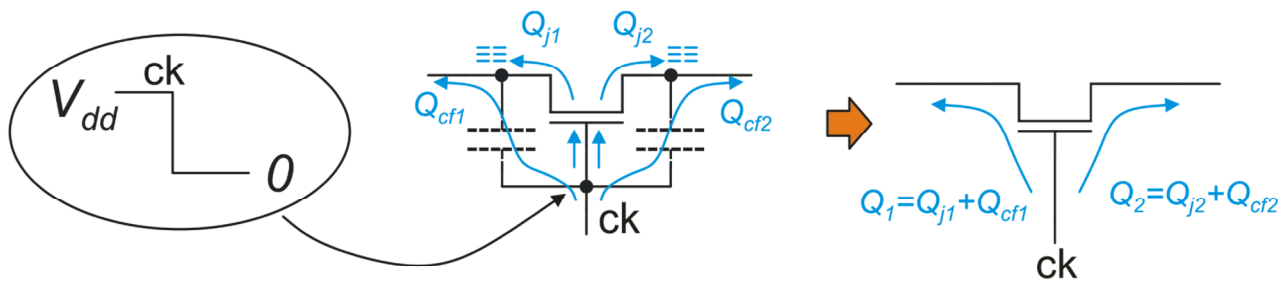
# Charge injection during the on-to-off transient





$$\Delta V_c = \frac{Q_2}{C}$$
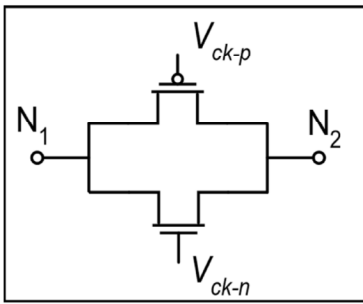
## Charge injection in the pass-gate (transmission gate)




pass gate

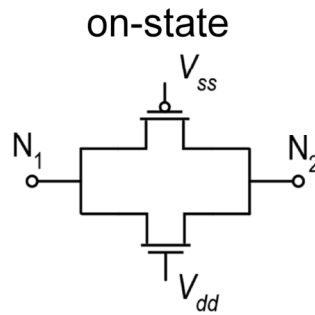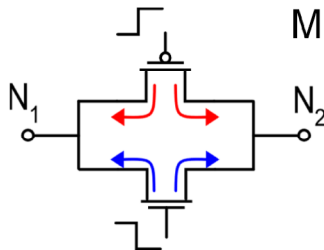


Voltage levels that are correctly transmitted by the n-MOS and p-MOS switches in the on-state

Charge injection in the on-to-off transient:

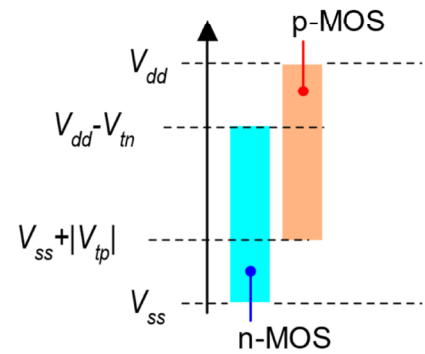charges are of opposite sign, but compensation is **imperfect** since the mobile charge depends on the  $V_{GS}$  and then on voltages at the  $N_1$ ,  $N_2$  nodes


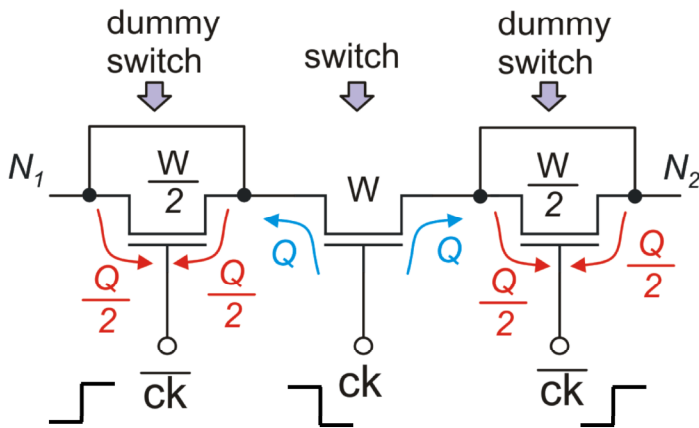
## Signal independent charge injection compensation




The dummy-switch does not affect the switching function, since it is short-circuited.

Its injected charge is opposite to that of the main switch because it is driven by the complementary control signal

- The dummy switches have the same length of the main switch but they have half the width.
- Dummy switches can be applied to both the p-mos and n-mos of a pass-gate

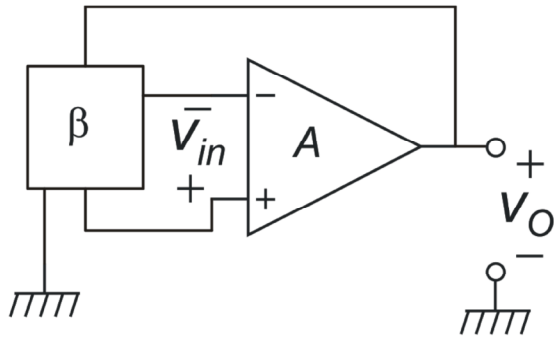The input voltage of op-amps in closed loop configuration and in presence of noise / offset



$$\text{Amplifier: } v_O = A(v_{in} - v_n)$$

$$\text{Feedback network: } v_{in} = \beta v_O + V_k$$

$$v_{in} = \beta A(v_{in} - v_n) + V_k$$

$$v_{in} (1 - \beta A) = -v_n \beta A + V_k$$

$$v_{in} = \frac{-\beta A}{1 - \beta A} v_n + \frac{V_k}{1 - \beta A}$$

The input voltage of op-amps in closed loop configuration and in presence of noise / offset

$$v_{in} = \frac{-\beta A}{1 - \beta A} v_n + \frac{V_k}{1 - \beta A} \quad \beta = -\beta_0 < 0 \quad (\beta_0 > 0, \text{ independent of } s)$$

Let us focus on the effect of noise:

$$v_{in} = \frac{\beta_0 \frac{A_0}{1 + \frac{s}{\omega_p}}}{1 + \beta_0 \frac{A_0}{1 + \frac{s}{\omega_p}}} v_n = \frac{\beta_0 A_0}{1 + \frac{s}{\omega_p} + \beta_0 A_0} v_n$$

$$A = \frac{A_0}{1 + \frac{s}{\omega_p}}$$

The fact that this term can be non-negligible is the origin of the finite gain error, We will not consider it for now.

The input voltage of op-amps in the presence of noise

$$v_{in} = \frac{\beta_0 A_0}{1 + \frac{s}{\omega_p} + \beta_0 A_0} v_n \quad v_{in} = \frac{\beta_0 A_0}{\underbrace{1 + \beta_0 A_0}_{\cong 1}} \frac{1}{1 + \frac{s}{\underbrace{\omega_p (1 + \beta_0 A_0)}_{\cong \omega_p \beta_0 A_0 \cong \beta_0 \omega_0}}} v_n$$

At the input of the op-amp we find a low-pass filtered version of the input referred noise


The cut-off frequency of the filter is nearly  $\beta_0 f_0$



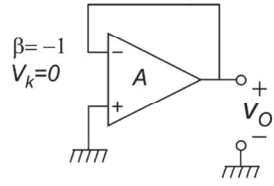
## A few examples

$$v_{in} = \beta v_O + V_k$$


$$v_{in} = \frac{-\beta A}{1 - \beta A} v_n + \frac{V_k}{1 - \beta A}$$




Unity Gain configuration

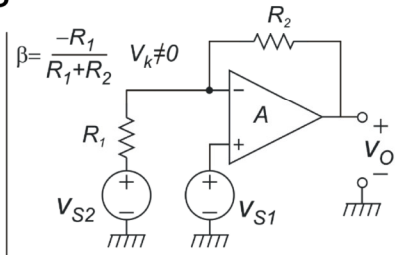

Inverting / non-Inverting Amplifier

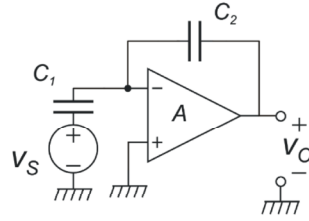

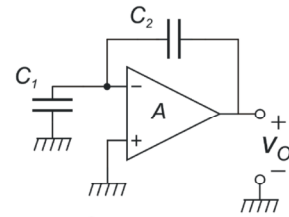Inverting Amplifier with capacitive feedback




Inverting Amplifier with capacitive feedback for  $V_S=0$
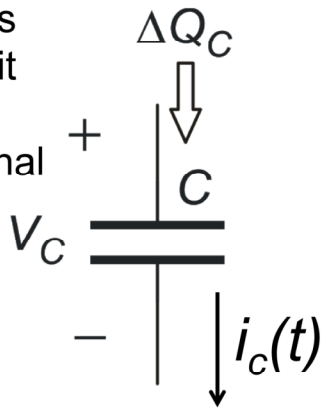
## Charges through capacitors: conventions

Conventions on signs:

A charge is positive if it enters the plus terminal



Charge that pass through the capacitor from time  $t_i$  to time  $t_f$

$$\Delta Q = \int_{t_i}^{t_f} i_c(t) dt = C [V_C(t_f) - V_C(t_i)]$$



$$V_C(t_f) = V_C(t_i) + \frac{\Delta Q}{C}$$