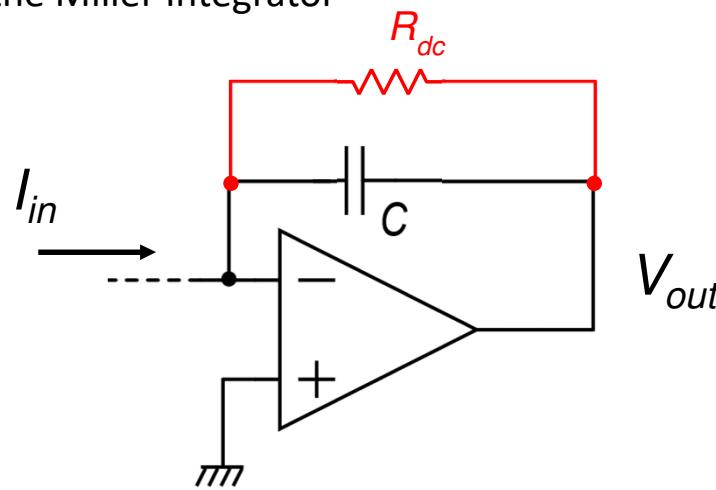


An interface for capacitive sensors based on the SC charge amplifier

Charge amplifier

Invented by Walter Kistler in 1950
It is based on the Miller Integrator



$$V_{out}(t_2) = -\frac{1}{C} \int_{t_1}^{t_2} I_{in} dt + V_{out}(t_1)$$



Charge fed to the amplifier from t_1 to t_2
 $= \Delta Q(t_2, t_1)$

This value is an uncertainty and may also cause saturation of the amplifier

The classical solution consists in placing a resistor of very high resistance (R_{dc}) in parallel with the capacitor

Unfortunately, this resistor also discharge the charge accumulated across C, imposing condition: $t_2 - t_1 \ll R_{dc}C$

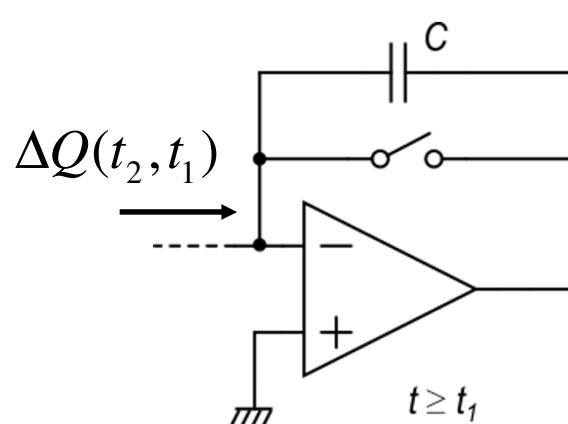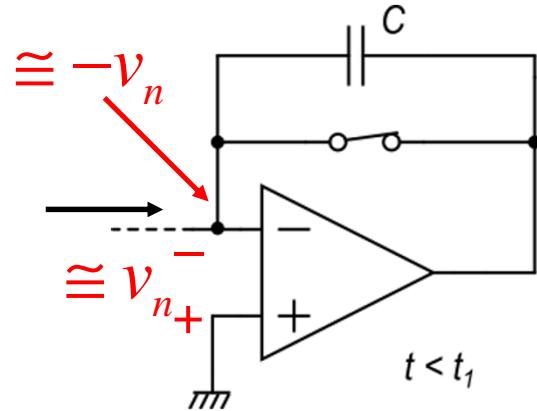A Switched Capacitor (SC) charge amplifier



Note: $v_n(t)$ includes the offset voltage, which can be quite large in CMOS circuits

$$V_{out} = 0$$

$$V_{out}(t_2) = -\frac{\Delta Q(t_2, t_1)}{C}$$


Ideal case

$$V_{out} \approx -v_n(t)$$

$$V_{out}(t_2) = \frac{-\Delta Q(t_2, t_1)}{C} - v_n(t)$$

Real case

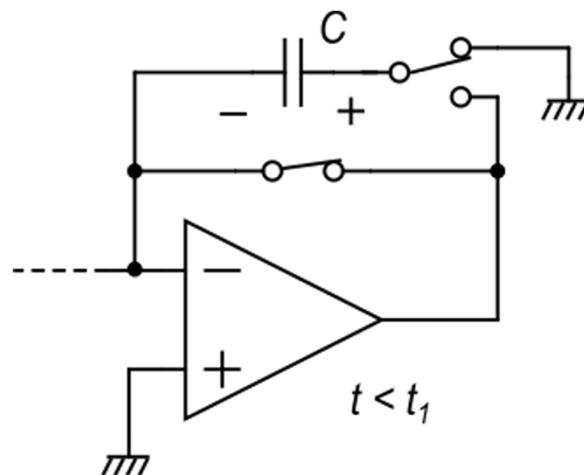
SC charge amplifier with offset cancellation



$$V_{out} \cong -v_n(t)$$

$$V_c \cong 0 - (-v_n(t)) = v_n(t)$$

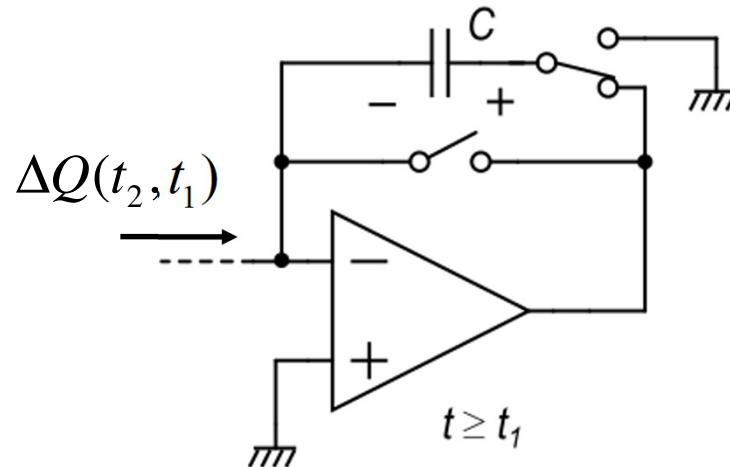
The feedback capacitor is pre-charged with $v_n(t)$




$$V_{out}(t_2) \cong -v_n(t_2) + V_C(t_2) = \underbrace{-v_n(t_2) + v_n(t_1)}_{\text{All } v_n \text{ components}} - \frac{\Delta Q(t_2, t_1)}{C}$$

All v_n components (offset, low freq. noise) that do not change across the t_1, t_2 interval are cancelled

SC interface for capacitive sensors

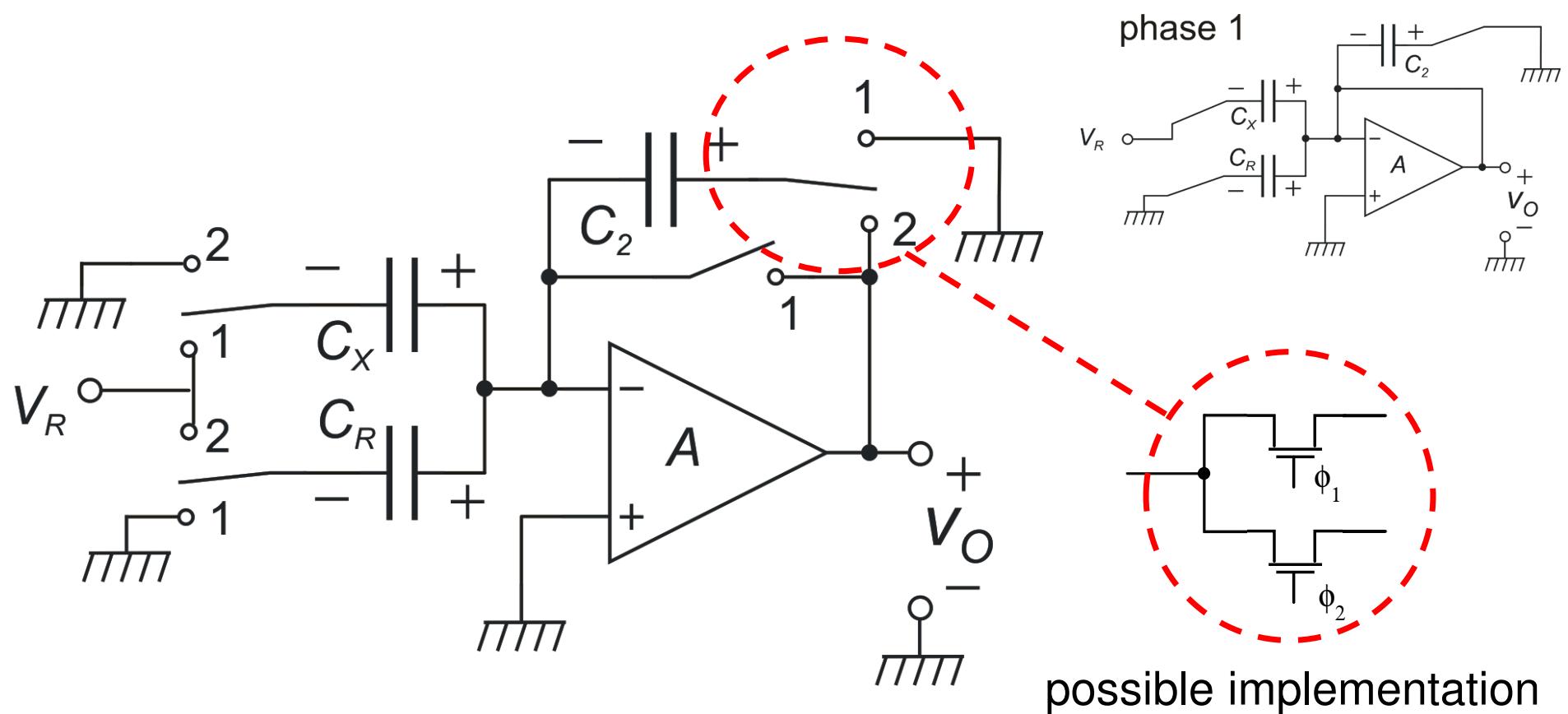

Phase 1: Capacitor voltages



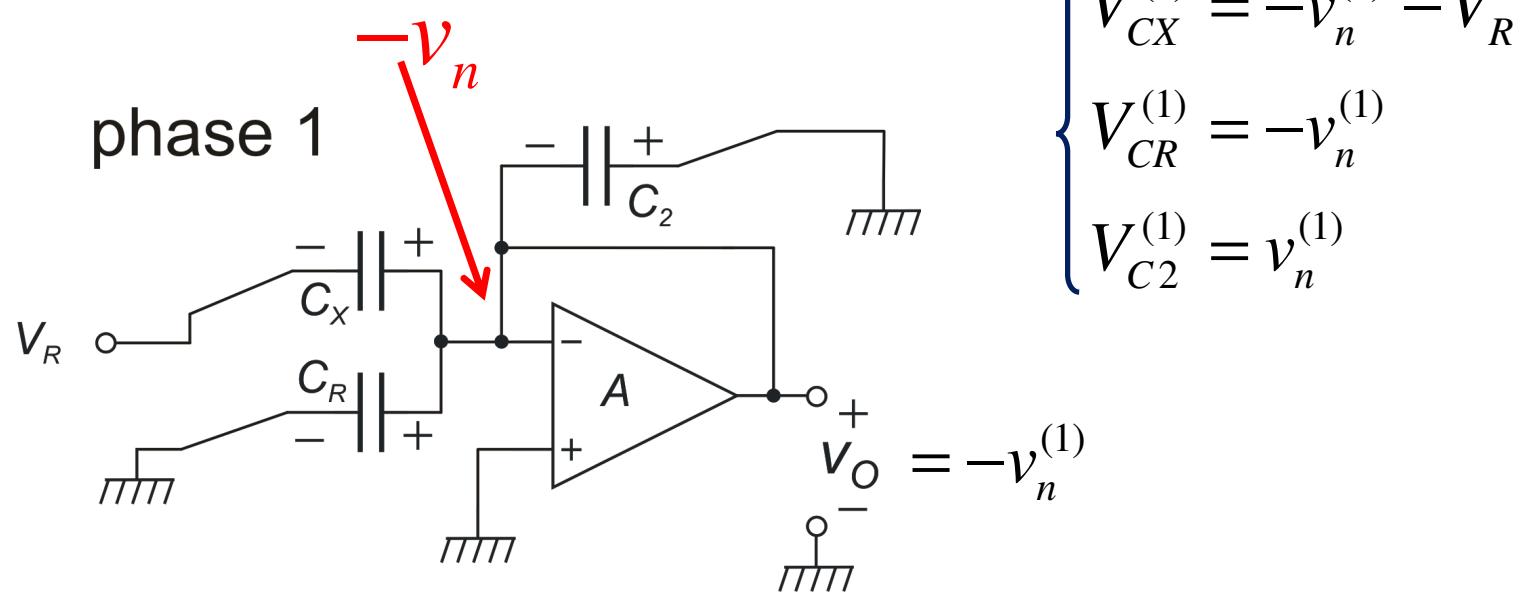


Transition to phase 2

In SC circuits, timing of the switches is critical, due to the risk to alter the charge stored into the capacitors

S_2 opens and
 C_2 samples $v_n^{(1)}$

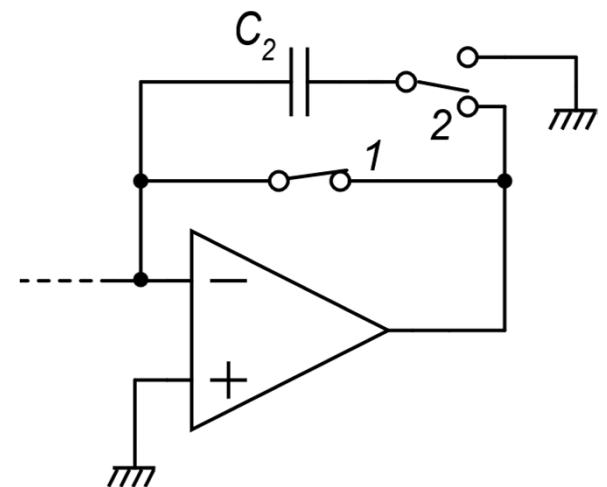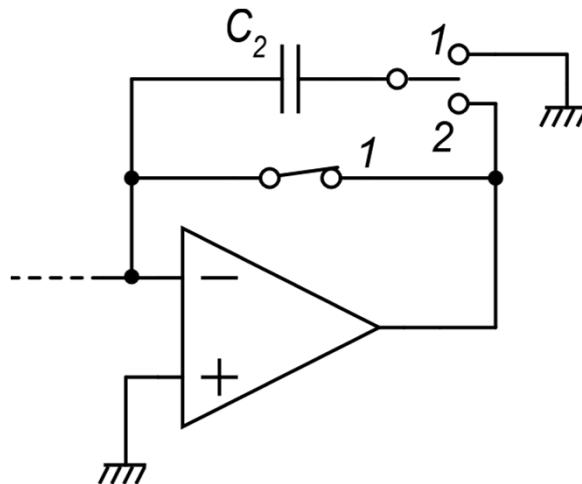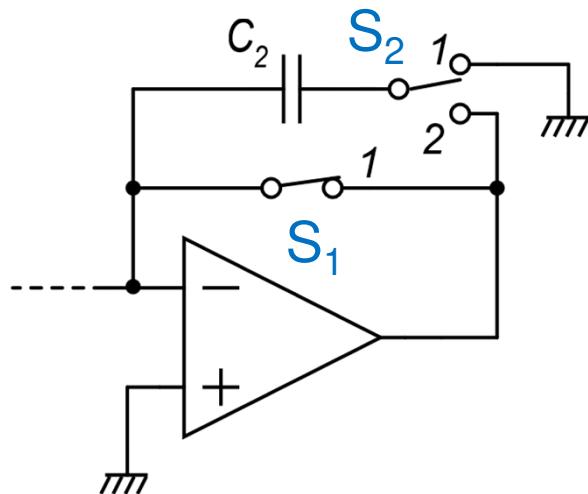
If S_1 is still closed in the previous position (phase 1), when S_2 closes to phase 2 position, C_2 is short circuited




The intermediate phase "i"

In order to avoid the occurrence of unwanted temporary short-circuits the transition from phase 1 to phase 2 occurs according the following steps:


Switches are closed
in position 1

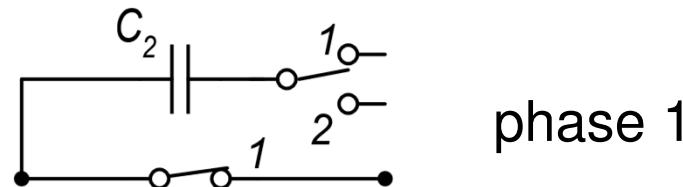

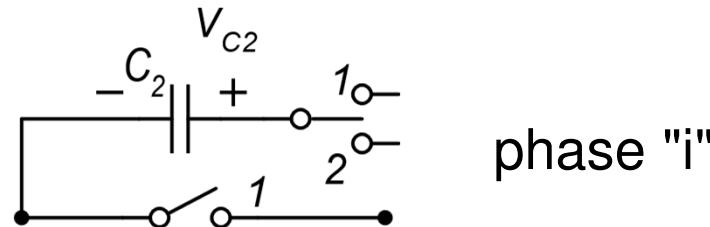All switches opens
(capacitors sample
their voltages)



Switches close
in position 2


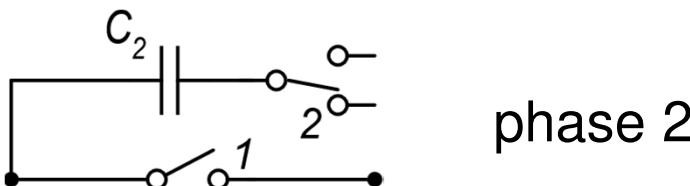


$$V_{C2}^{(i)} = v_n^{(1)} + v_\varepsilon$$

kT/C noise

Phase 1 to phase 2 transition
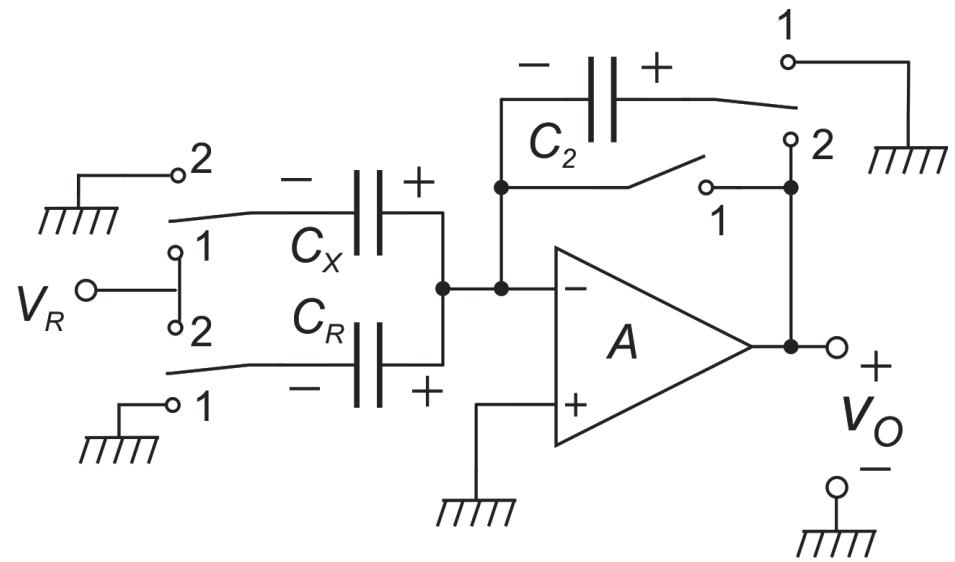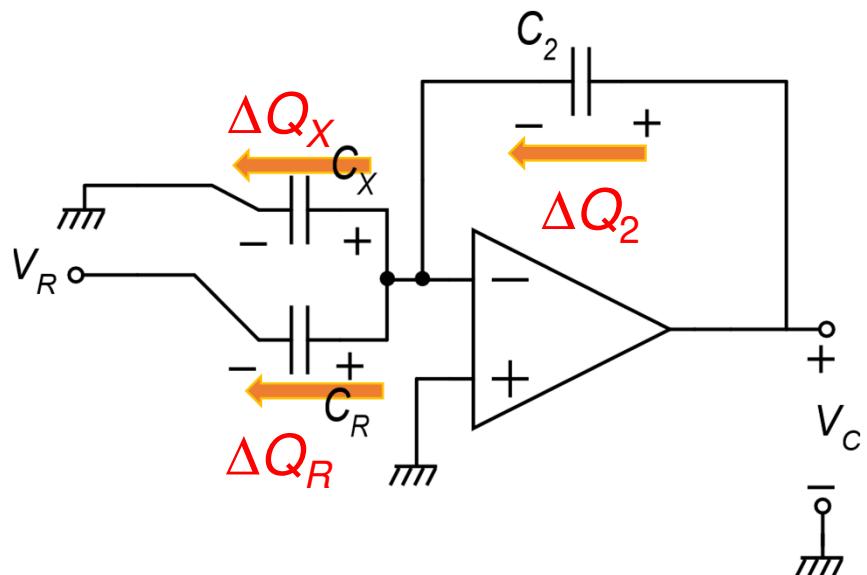
$$\begin{cases} V_{CX}^{(i)} = -v_n^{(1)} - V_R + v_{\epsilon X} \\ V_{CR}^{(i)} = -v_n^{(1)} + v_{\epsilon R} \\ V_{C2}^{(i)} = v_n^{(1)} + v_{\epsilon 2} \end{cases}$$




$$\Delta Q_X = C_X (V_{CX}^{(2)} - V_{CX}^{(i)})$$

$$\Delta Q_R = C_R (V_{CR}^{(2)} - V_{CR}^{(i)})$$

$$\Delta Q_2 = \Delta Q_X + \Delta Q_R$$

Phase 2 voltages

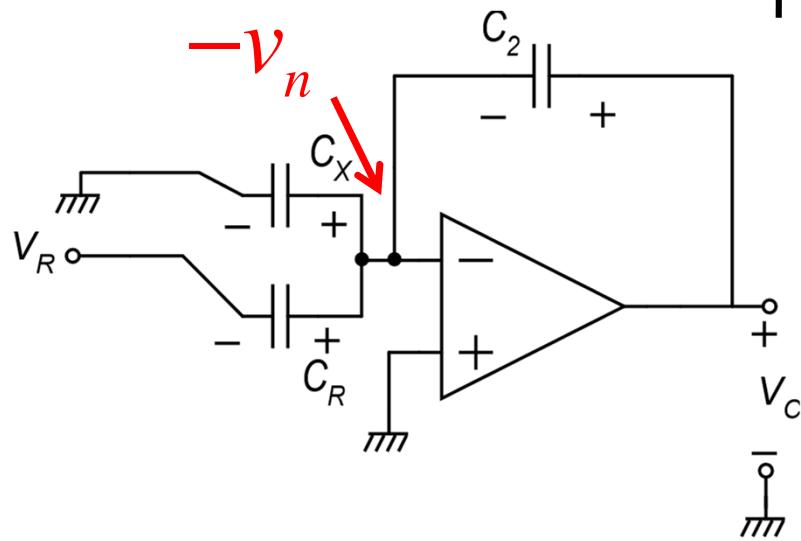

$$V_{CX}^{(2)} = -v_n^{(2)}$$

$$V_{CR}^{(2)} = -v_n^{(2)} - V_R$$

$$V_{C2}^{(2)} = V_{C2}^{(i)} + \frac{\Delta Q_2}{C_2}$$

$$V_o^{(2)} = -v_n^{(2)} + V_{C2}^{(2)}$$



$$\Delta Q_2 = \Delta Q_X + \Delta Q_R = C_X \left(V_{CX}^{(2)} - V_{CX}^{(i)} \right) + C_R \left(V_{CR}^{(2)} - V_{CR}^{(i)} \right)$$

$$V_o^{(2)} = -v_n^{(2)} + V_{C2}^{(i)} + \frac{1}{C_2} \left[C_X \left(V_{CX}^{(2)} - V_{CX}^{(i)} \right) + C_R \left(V_{CR}^{(2)} - V_{CR}^{(i)} \right) \right]$$

Phase 2 output voltage

$$V_o^{(2)} = -v_n^{(2)} + V_{C2}^{(i)} + \frac{1}{C_2} \left[C_X \left(V_{CX}^{(2)} - V_{CX}^{(i)} \right) + C_R \left(V_{CR}^{(2)} - V_{CR}^{(i)} \right) \right]$$


$$\begin{cases} V_{CX}^{(1)} = -v_n^{(1)} - V_R \\ V_{CR}^{(1)} = -v_n^{(1)} \\ V_{C2}^{(1)} = v_n^{(1)} \end{cases} \quad \begin{cases} V_{CX}^{(i)} = -v_n^{(1)} - V_R + v_{\varepsilon X} \\ V_{CR}^{(i)} = -v_n^{(1)} + v_{\varepsilon R} \\ V_{C2}^{(i)} = v_n^{(1)} + v_{\varepsilon 2} \end{cases} \quad \begin{aligned} V_{CX}^{(2)} &= -v_n^{(2)} \\ V_{CR}^{(2)} &= -v_n^{(2)} - V_R \end{aligned}$$

$$V_o^{(2)} = -v_n^{(2)} + v_n^{(1)} + v_{\varepsilon 2} + \frac{1}{C_2} \left[C_X \left(-v_n^{(2)} + v_n^{(1)} + V_R - v_{\varepsilon X} \right) + C_R \left(-v_n^{(2)} - V_R + v_n^{(1)} - v_{\varepsilon R} \right) \right]$$

$$V_o^{(2)} = \frac{C_X - C_R}{C_2} V_R + \left(-v_n^{(2)} + v_n^{(1)} \right) \left(1 + \frac{C_X}{C_2} + \frac{C_R}{C_2} \right) + v_{\varepsilon 2} - \frac{C_X}{C_2} v_{\varepsilon X} - \frac{C_R}{C_2} v_{\varepsilon R}$$

Output voltage components

$$\Delta C = C_X - C_R$$
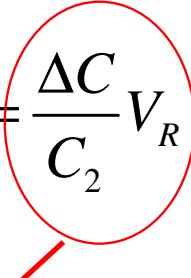
$$V_o^{(2)} = \frac{\Delta C}{C_2} V_R + \left(-v_n^{(2)} + v_n^{(1)} \right) \left(1 + \frac{C_X}{C_2} + \frac{C_R}{C_2} \right) + v_{\varepsilon 2} - \frac{C_X}{C_2} v_{\varepsilon X} - \frac{C_R}{C_2} v_{\varepsilon R}$$


useful signal
sensitivity: $\frac{V_R}{C_2}$

Amplifier noise (CDS)

kT/C noise

Referred to
the input diff.
capacitance

$$\Delta C_n^{(2)} = \frac{\left(-v_n^{(2)} + v_n^{(1)} \right)}{V_R} (C_2 + C_X + C_R) + \frac{C_2 v_{\varepsilon 2} - C_X v_{\varepsilon X} - C_R v_{\varepsilon R}}{V_R}$$

Example: DR of the SC interface considering only kT/C noise

$$\Delta C_n = \frac{C_2 v_{\varepsilon 2} - C_X v_{\varepsilon X} - C_R v_{\varepsilon R}}{V_R}$$

$$DR = \frac{\Delta C_{FS}}{\Delta C_{n-pp}} = \frac{\Delta C_{FS}}{4\Delta C_{rms}}$$

$$\Delta C_{rms} = \sqrt{\langle \Delta C_n^2 \rangle}$$

$$\langle (\Delta C_n)^2 \rangle = \frac{1}{V_R^2} \left(C_2^2 \langle (v_{\varepsilon 2})^2 \rangle + C_X^2 \langle (v_{\varepsilon X})^2 \rangle + C_R^2 \langle (v_{\varepsilon R})^2 \rangle \right)$$

$$\langle (\Delta C_n)^2 \rangle = \frac{1}{V_R^2} \left(C_2^2 \frac{kT}{C_2} + C_X^2 \frac{kT}{C_X} + C_R^2 \frac{kT}{C_R} \right) = \frac{kT}{V_R^2} (C_2 + C_X + C_R)$$

$$DR = \frac{\Delta C_{FS}}{4\sqrt{\frac{kT}{V_R^2} (C_2 + C_X + C_R)}}$$

Example: DR of the SC interface considering only kT/C noise

$$DR = \frac{\Delta C_{FS}}{4\sqrt{\frac{kT}{V_R^2}(C_2 + C_X + C_R)}}$$

$$= \frac{1}{4\sqrt{\frac{kT}{\Delta C_{FS} V_R^2} \frac{(C_2 + C_X + C_R)}{\Delta C_{FS}}}}$$

$$DR = \frac{V_R}{4\sqrt{kT / \Delta C_{FS}}} \sqrt{\frac{\Delta C_{FS}}{(C_2 + C_X + C_R)}}$$

$$DR = \frac{1}{\frac{4}{\Delta C_{FS}} \sqrt{\frac{kT}{V_R^2}(C_2 + C_X + C_R)}}$$

$$= \frac{1}{4} \sqrt{\frac{1}{\frac{kT}{\Delta C_{FS} V_R^2} \frac{(C_2 + C_X + C_R)}{\Delta C_{FS}}}}$$

rms value of the kT/C
noise associated to
 ΔC_{FS}