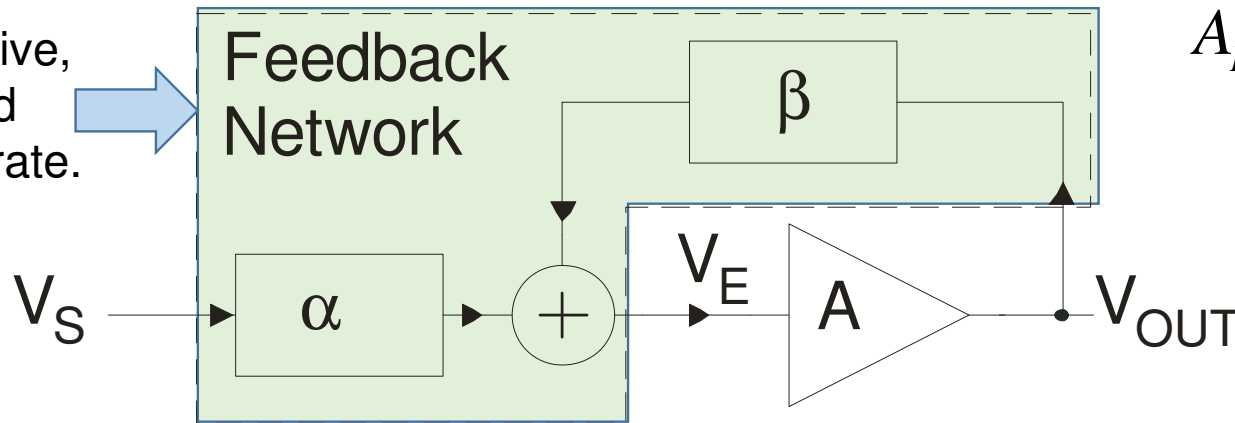


Use of Pellegrini's cut-insertion theorem for the design of feedback systems

Block diagram of a feedback system

Typically passive, then linear and possibly accurate.



$$A_L \equiv \frac{V_{OUT}}{V_S} = -\frac{\alpha}{\beta} \frac{\beta A}{\beta A - 1}$$

$$A_{L-ideal} \cong -\frac{\alpha}{\beta}$$




$$\Delta A_L = A_L - A_{L-ideal}$$

$$\Delta A_L = -\frac{\alpha}{\beta} \left(\frac{\beta A}{\beta A - 1} \right) + \frac{\alpha}{\beta} = -\frac{\alpha}{\beta} \left(\frac{\beta A}{\beta A - 1} - 1 \right) = -\frac{\alpha}{\beta} \left(\frac{1}{\beta A - 1} \right) \cong -\frac{\alpha}{\beta} \frac{1}{\beta A} \quad (|\beta A| \gg 1)$$

$$|\epsilon_{AL}| \equiv \left| \frac{\Delta A_L}{A_L} \right| \cong |\beta A|^{-1}$$

Passive network:
linear and reliable

In a real electronic network:

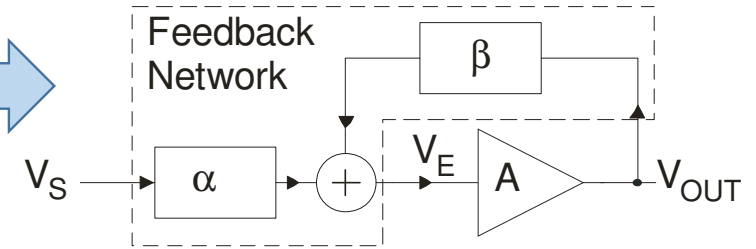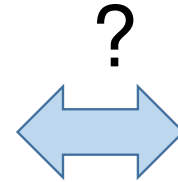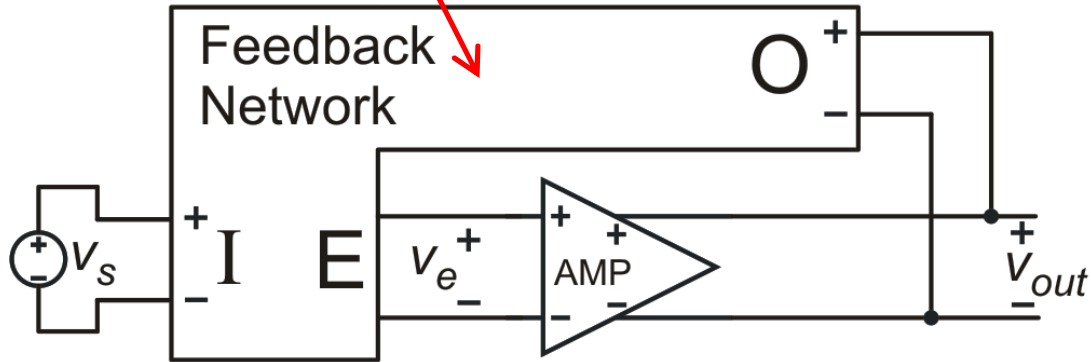


Desired correspondence

~~$$\alpha_N \rightarrow \alpha$$~~


~~$$\beta_N \rightarrow \beta$$~~

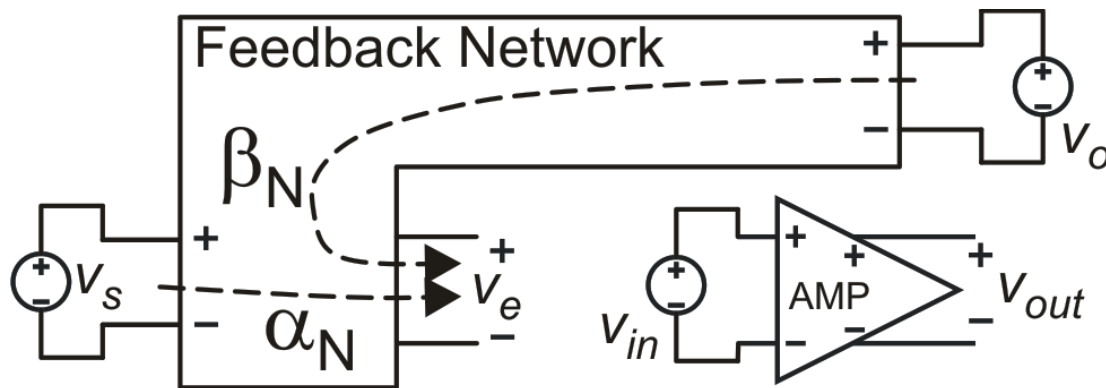~~$$A_{OL} = \frac{V_{out}}{V_{in}} \rightarrow A$$~~




Separation of feedback network and gain element (AMP)

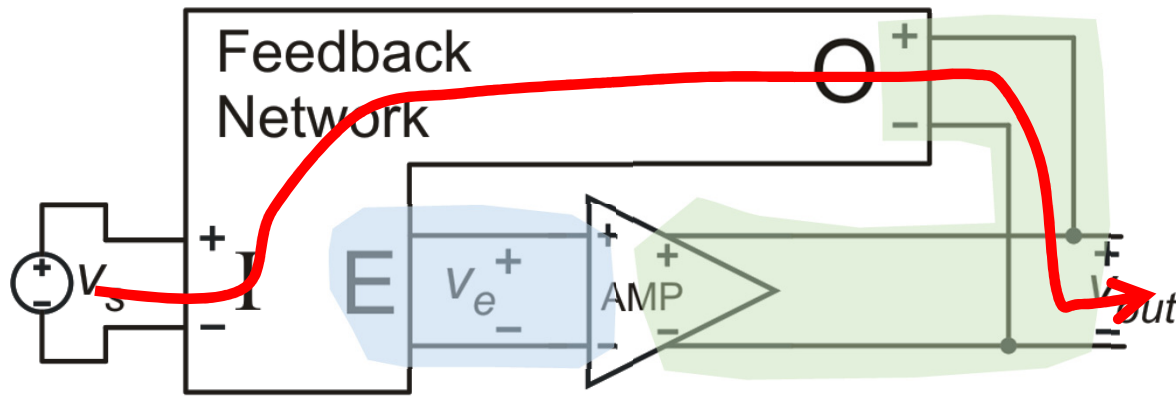Problems that prevent a direct correspondence between the electrical circuit and the simplified block diagram of a feedback system



- Loading effects of the feedback network on AMP
- Loading effect of the amplifier input impedance on the feedback network
- Direct signal path from the input signal V_s and the output voltage through the feedback network (occurs if the amplifier has a non-zero output impedance).

Pellegrini's cut-insertion theorem

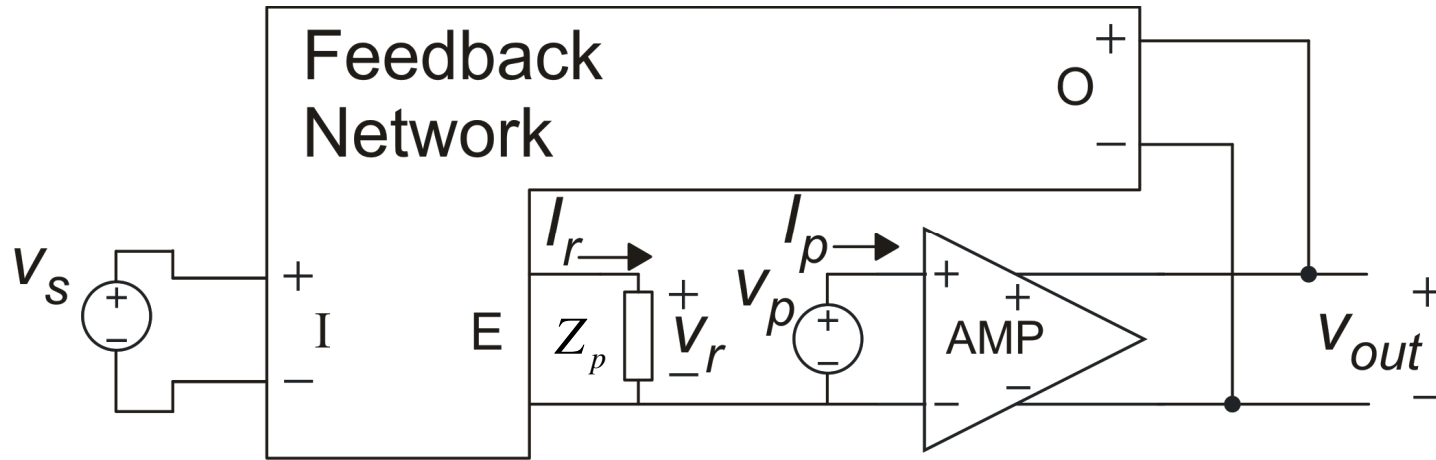

A, β, α
now are calculated
taking into account
loading effects

γ

takes into account
the feed-forward
path through the
feedback network


$$Z_i = \left(\frac{v_p}{i_p} \right)_{v_s=0} ; \underline{\beta} \equiv \left(\frac{v_r}{v_{out}} \right)_{v_s=0} ; \underline{A} = \left(\frac{v_{out}}{v_p} \right)_{v_s=0} ; \frac{1}{Z_p} = \frac{1}{Z_i} + \frac{\rho}{\alpha} (1 - \beta A)$$

$$\underline{\gamma} = \left(\frac{v_{out}}{v_s} \right)_{v_p=0} ; \underline{\alpha} \equiv \left(\frac{v_r}{v_s} \right)_{v_p=0} ; \rho = \left(\frac{i_p}{v_s} \right)_{v_p=0}$$

←
↑


ρ is zero if the op-amp is unidirectional

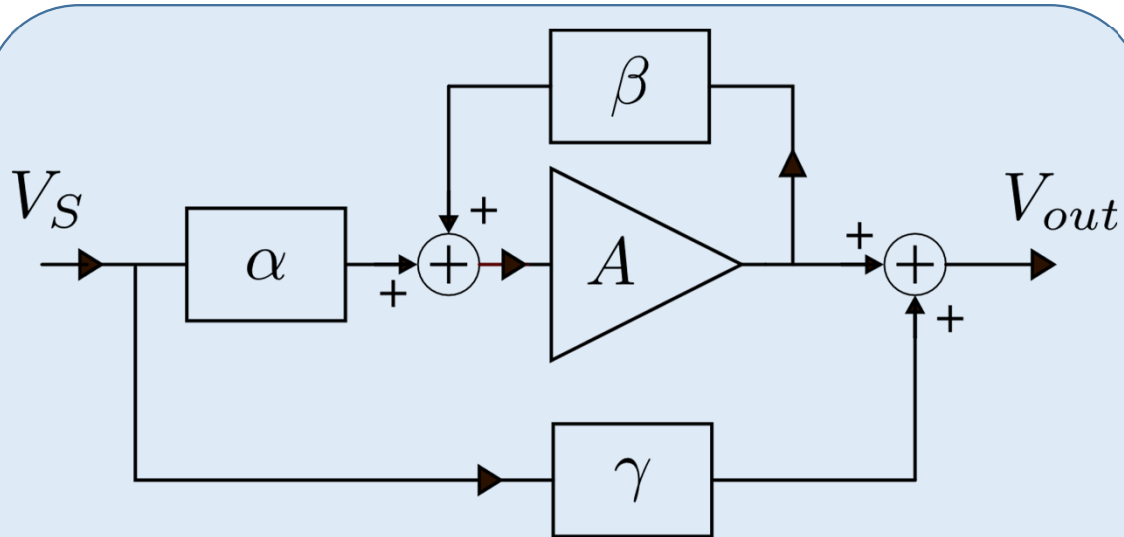Block diagram corresponding to the cut-insertion schematization



$$\frac{v_{out}}{v_s} = A_L = -\frac{\alpha \beta A}{\beta \beta A - 1} + \gamma$$

$$\lim_{|\beta A| \rightarrow \infty} A_L = -\frac{\alpha}{\beta} + \gamma$$

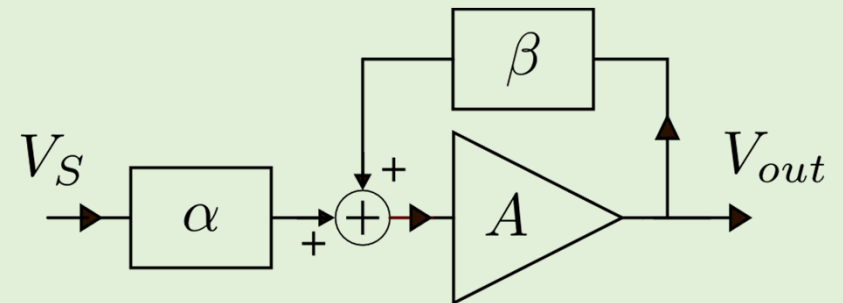

Ideal feedback system

Problems when using the cut-insertion theorem for design purposes


1. I have to design the feedback network for three transfer functions (α , β and γ) instead of only two.
2. α and γ depend on the output impedance of the amplifier, Z_{out} , which is a parameter that varies much and cannot be predicted reliably.
3. Only in the case that Z_{out} is much smaller than the typical impedances of the feedback network, we can design the network for α , β and γ with port "O" short circuited ($\gamma=0$).

Typically, this does not occur in integrated circuits.


$$\frac{v_{out}}{v_s} = -\frac{\alpha}{\beta} + \gamma$$

Configuration for

← α, γ

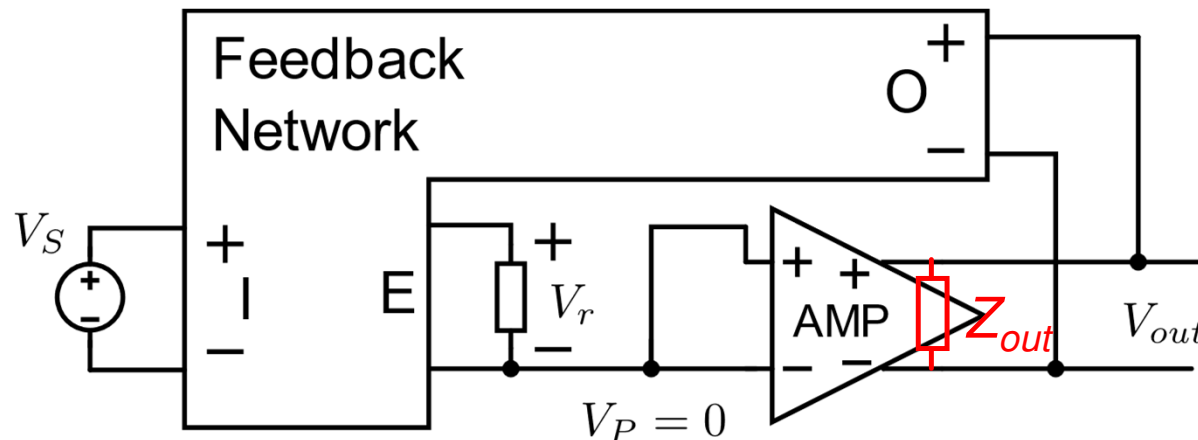

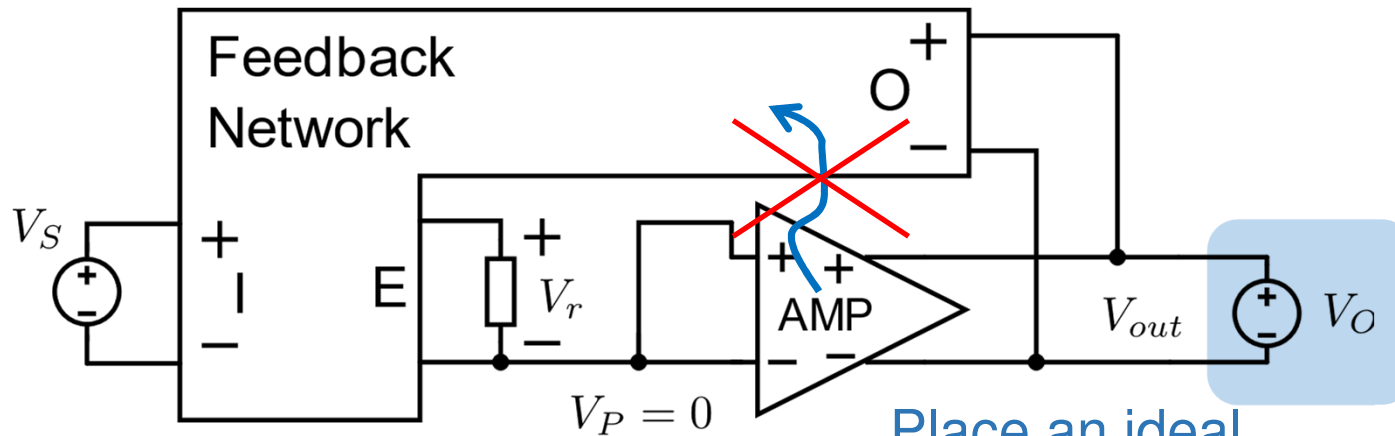Cut insertion theorem with modified definition of α (and β)



Introduce a new definition of α and β (renamed α^* and β^*)

$$\alpha^* \equiv \left(\frac{v_r}{v_s} \right)_{v_p, v_o=0} ; \beta^* \equiv \left(\frac{v_r}{v_o} \right)_{v_p, v_s=0}$$


If AMP communicates with the feedback network only through the input and output ports (no intermediate signal path exists between them)

.....
then $\beta^* = \beta$

and:

$$\frac{v_{out}}{v_s} = -\frac{\alpha^*}{\beta} \frac{\beta A}{\beta A - 1} + \frac{\gamma}{1 - \beta A}$$

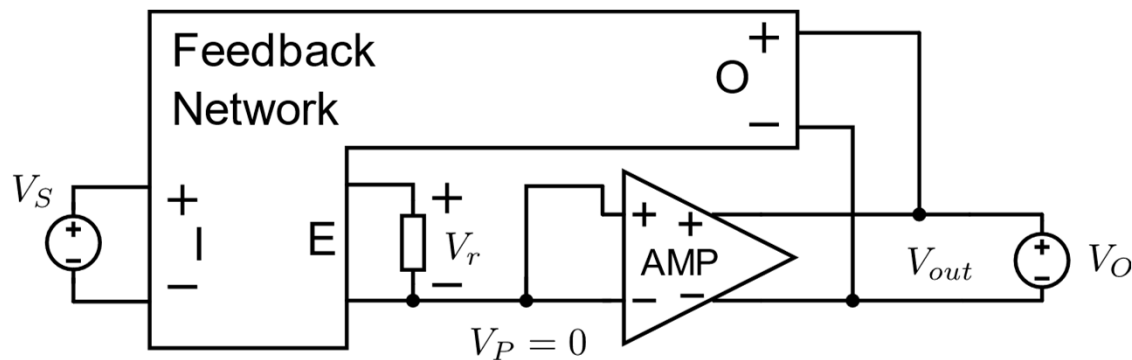Cut insertion theorem with modified definition of α



$$\frac{v_{out}}{v_s} = \frac{\alpha^*}{\beta} \frac{\beta A}{\beta A - 1} + \frac{\gamma}{1 - \beta A}$$

Now γ is divided by the loop gain βA

$$\lim_{|\beta A| \rightarrow \infty} \frac{v_{out}}{v_s} = -\frac{\alpha^*}{\beta} = -\frac{\alpha^*}{\beta^*}$$


The definition of α^* is deeply different from that of α .

Also the definition of β^* is different from that of β . but the two values coincides in most practical cases.


α^* and β^* are very similar to α_N and β_N that are the functions for which we design the feedback network

Ideal transfer function and network functions


$$\lim_{|\beta A| \rightarrow \infty} \frac{v_{out}}{v_s} = -\frac{\alpha^*}{\beta} = -\frac{\alpha^*}{\beta^*}$$

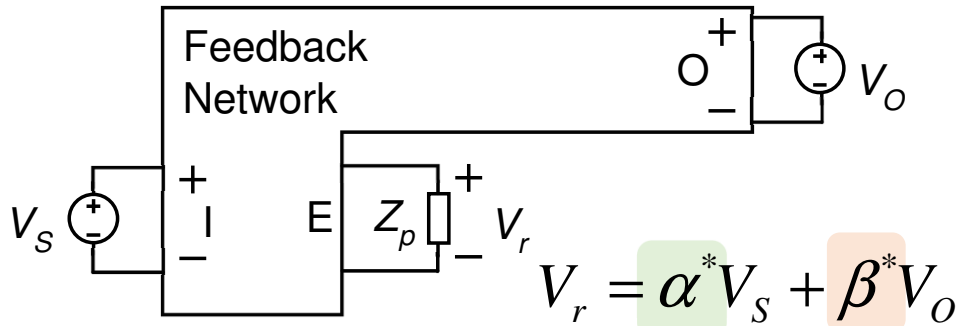

$$V_r = \alpha^* V_S + \beta^* V_O$$

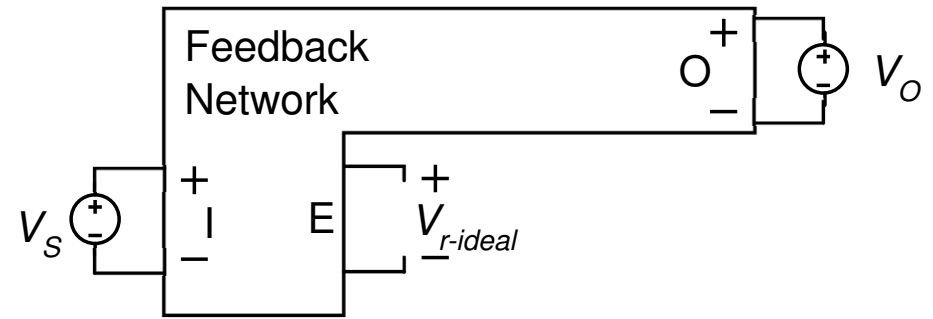
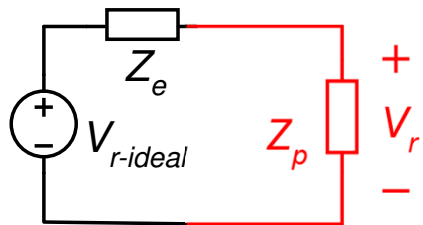
$$V_{r-ideal} = \alpha_N V_S + \beta_N V_O$$



$$V_r = (\alpha_N V_S + \beta_N V_O) \frac{Z_p}{Z_p + Z_e}$$

$$V_r = \alpha_N \frac{Z_p}{Z_p + Z_e} V_S + \beta_N \frac{Z_p}{Z_p + Z_e} V_O$$

$$\alpha^* = \alpha_N \frac{Z_p}{Z_p + Z_e}$$

$$\beta^* = \beta_N \frac{Z_p}{Z_p + Z_e}$$

$$\frac{\alpha^*}{\beta^*} = \frac{\alpha_N}{\beta_N}$$

Thevenin equivalent of port E

Finite gain error

$$A_{L-ideal} = -\frac{\alpha^*}{\beta^*} = -\frac{\alpha_N}{\beta_N}$$

$$A_L = -\frac{\alpha^*}{\beta} \frac{\beta A}{\beta A - 1} + \frac{\gamma}{1 - \beta A}$$

$$\Delta A_L = A_L - A_{L-ideal}$$

$$\Delta A_L = -\frac{\alpha^*}{\beta} \frac{\beta A}{\beta A - 1} + \frac{\gamma}{1 - \beta A} - \left(-\frac{\alpha^*}{\beta} \right)$$

$$\Delta A_L = -\frac{\alpha^*}{\beta} \left(\frac{\beta A}{\beta A - 1} - 1 \right) + \frac{\gamma}{1 - \beta A}$$

$$\Delta A_L = -\frac{\alpha^*}{\beta} \left(\frac{1}{\beta A - 1} \right) + \frac{\gamma}{1 - \beta A}$$

$$\frac{\Delta A_L}{A_{L-ideal}} = \left(\frac{1}{\beta A - 1} \right) \left(1 + \frac{\gamma}{A_{L-ideal}} \right)$$



$$e_r = \left| \frac{\Delta A_L}{A_{L-ideal}} \right| \cong \frac{1}{|\beta A|} \left| 1 + \frac{\gamma}{A_{L-ideal}} \right|$$

From the Schwarz inequality:

$$e_r \leq \frac{1}{|\beta A|} \left(1 + \left| \frac{\gamma}{A_{L-ideal}} \right| \right)$$

Final recap
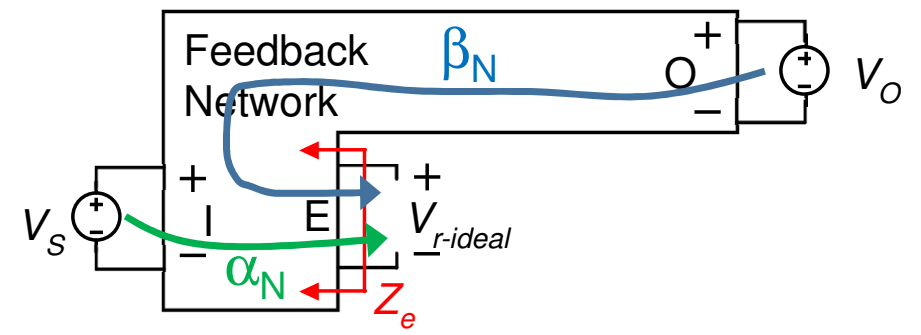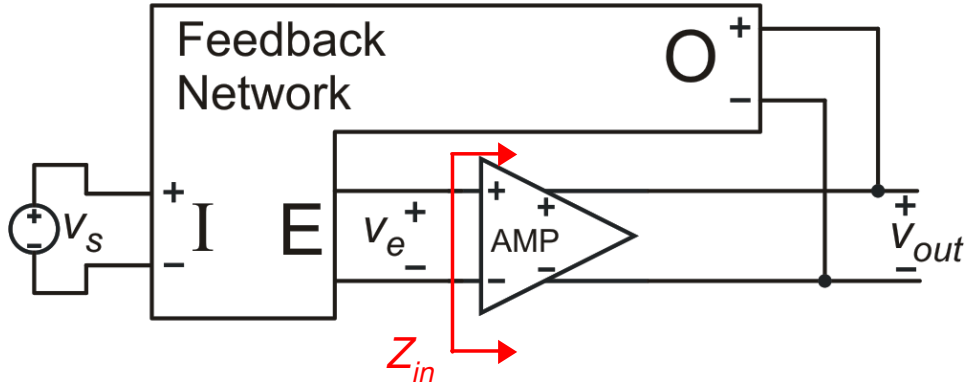
$$A_{L-ideal} = -\frac{\alpha^*}{\beta^*} = -\frac{\alpha_N}{\beta_N}$$



$$e_r \leq \frac{1}{|\beta A|} \left(1 + \left| \frac{\gamma}{A_{L-ideal}} \right| \right)$$

$$\beta = \beta^* = \beta_N \frac{Z_{in}}{Z_{in} + Z_e}$$

$$A = A_{VOL} \frac{Z_o}{Z_o + Z_{out}}$$

