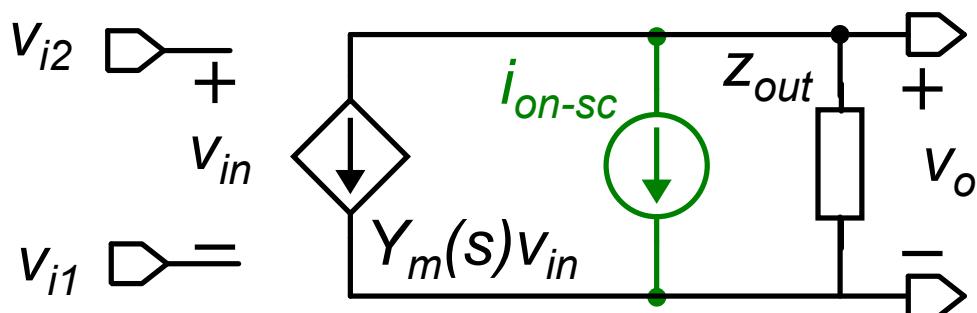


# Amplifier Norton schematization with output referred noise source



It is possible to model any amplifier (whole amplifier or single amplifier stage) with a Norton equivalent circuit of the output port and take into account noise with an additional current source  $i_{on-sc}$

$$v_o = - \left( Y_m v_{in} + i_{on-sc} \right) Z_{out} = -Y_m Z_{out} \left( v_{in} + \frac{i_{on-sc}}{Y_m} \right)$$


General input-output law of a voltage amplifier with noise/offset:  $v_o = A_V (v_{in} - v_n)$

$A_V = -Y_m Z_{out}$

**Input referred noise voltage**


$$v_n = \frac{-i_{on-sc}}{Y_m}$$
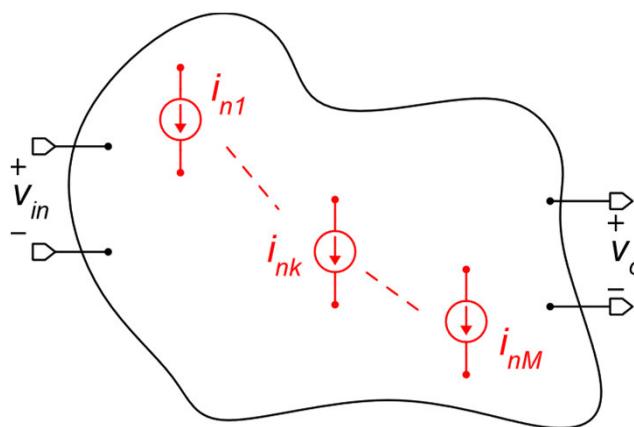
# General method to calculate the input referred noise / offset




Generic amplifier with  $M$  internal noise current sources

$$v_n = \frac{-i_{on-sc}}{Y_m}$$

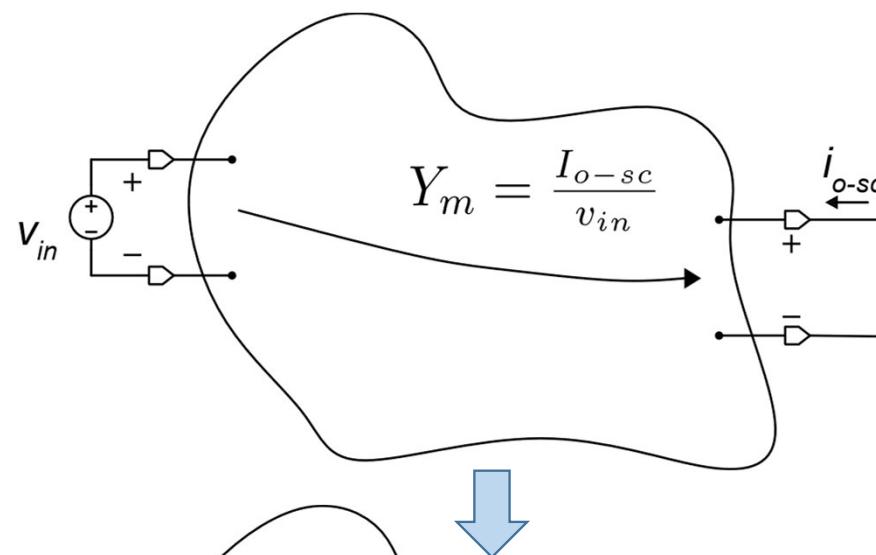

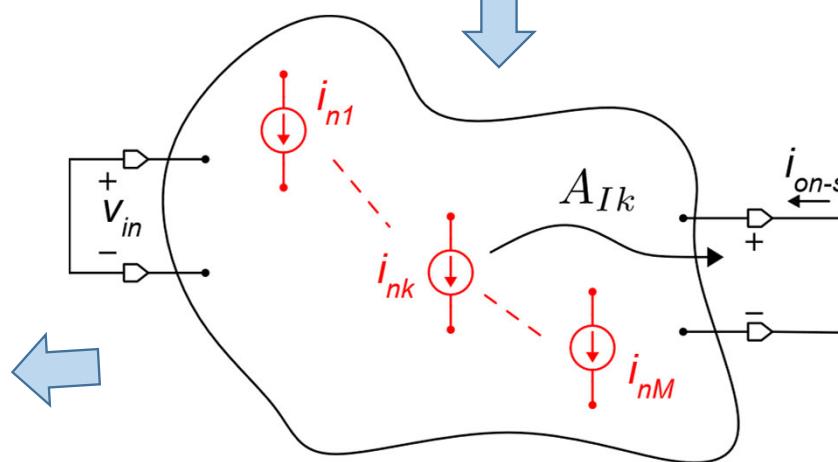**Step 1.** Noise sources off, input signal on, determine  $Y_m$





**Step. 2** Signal off, determine  $i_{on-sc}$  with the superposition theorem


$$i_{on-sc} = \sum_{k=1}^M A_{Ik} i_{nk}$$
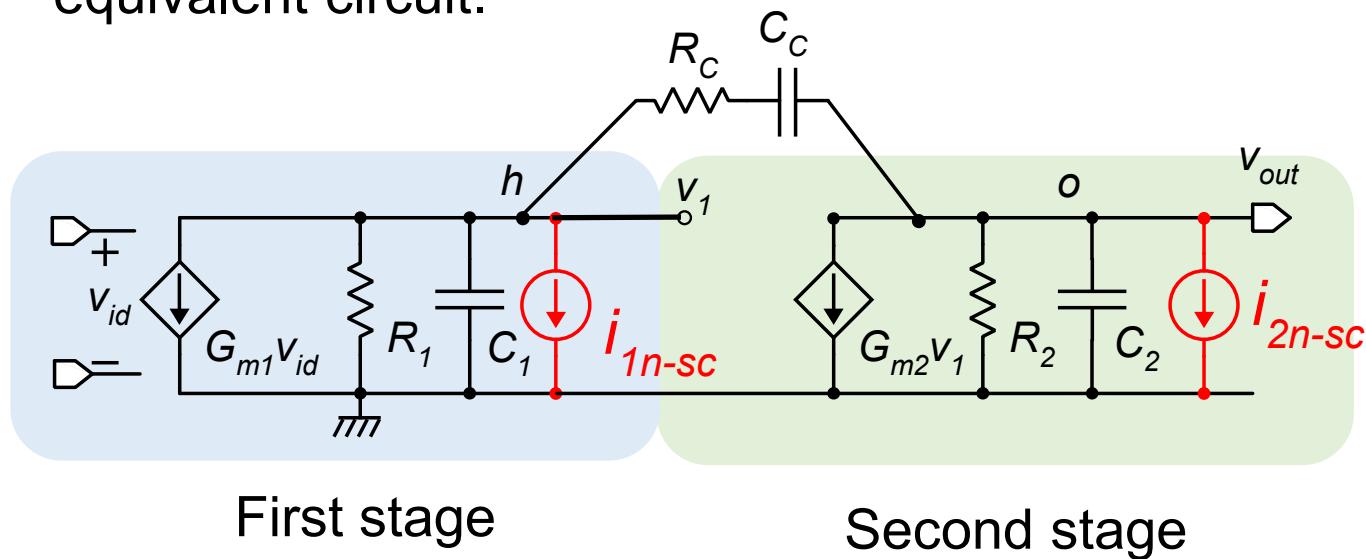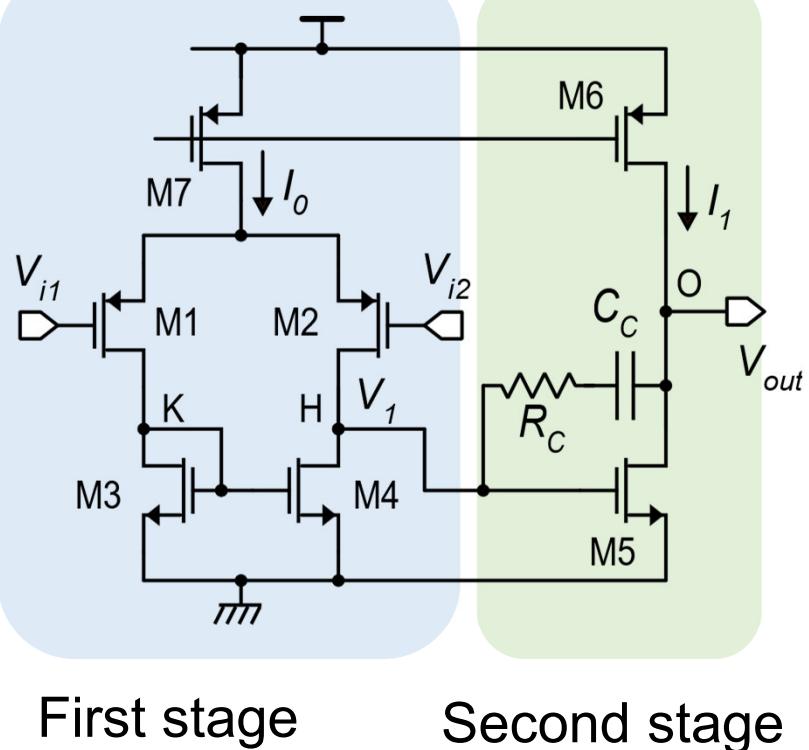
## Application of the method to the two-stage op-amp

It is convenient to calculate the equivalent output noise currents of the two stages individually, and then study the whole amplifier using the following equivalent circuit.


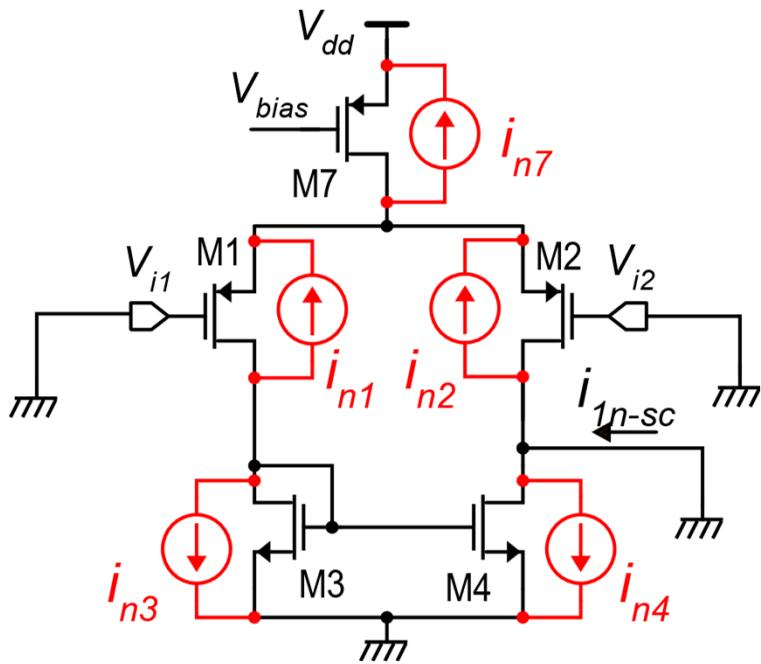
## Output noise short circuit current of the first stage




Input stage with noise current sources of all devices

In order to calculate the output noise short-circuit current, we need to calculate the current gains  $A_{Ik}$ , from each one of the MOSFET noise sources to the output short circuit current.

## Effect of $i_{n3}$ , $i_{n4}$

**$i_{n4}$**  is directly connected to the output port, then it flows directly into the output short circuit:


$$A_{I_4} = 1$$

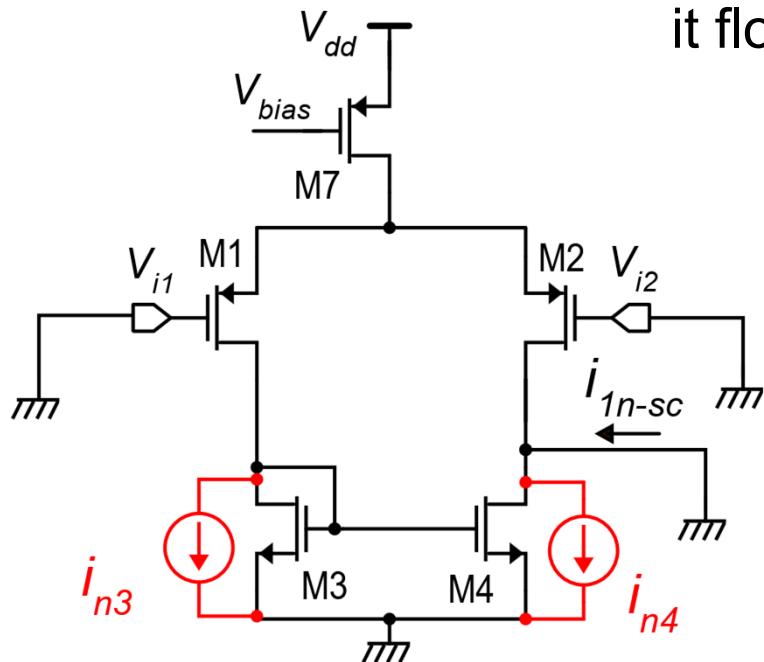

**$i_{n3}$**  is directly connected to the input of the current mirror. It sees a low resistance towards the mirror and high resistance towards M1 ( $2r_{d1}$ ). Then it flows almost completely into the mirror and reaches the output port after an inversion (caused by the mirror).

$$A_{I_3} \cong -1$$

## Effect of $i_{n7}$

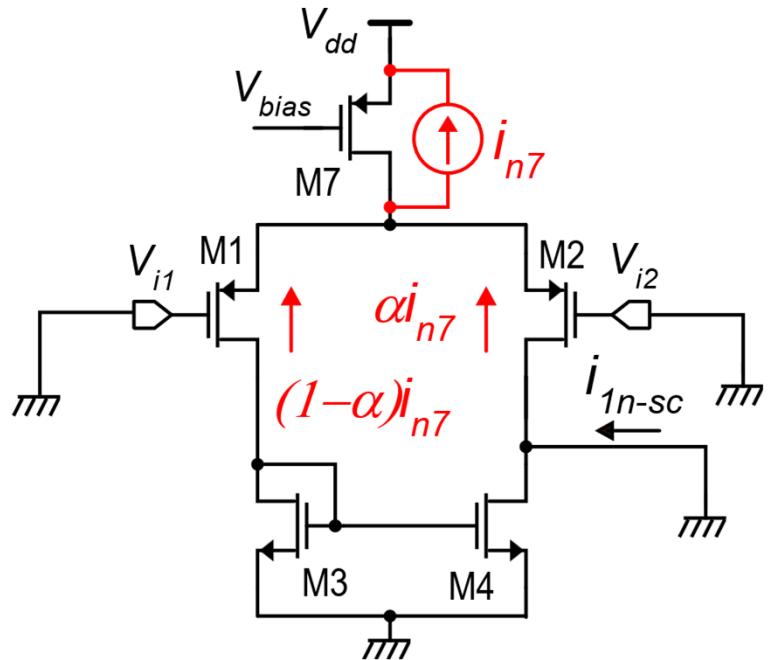

$$i_{on-cc}(i_{n7}) \approx i_{n7} [\alpha - (1 - \alpha)] = i_{n7} [2\alpha - 1]$$


In the case of perfect symmetry and zero input differential voltage ( $V_{id}=0$ ), which is the case that we are analyzing:

$$\alpha = \frac{1}{2} \Rightarrow i_{1n-sc}(i_{n7}) \approx 0 \quad A_{I7} \approx 0$$


If a relatively large input differential voltage is present,  $\alpha$  can be significantly different from 0.5 and the effect of  $i_{n7}$  is no more negligible.

In the following part of this analysis, we will consider  $\alpha=0.5$

## Effect of $i_{n1}$ , $i_{n2}$

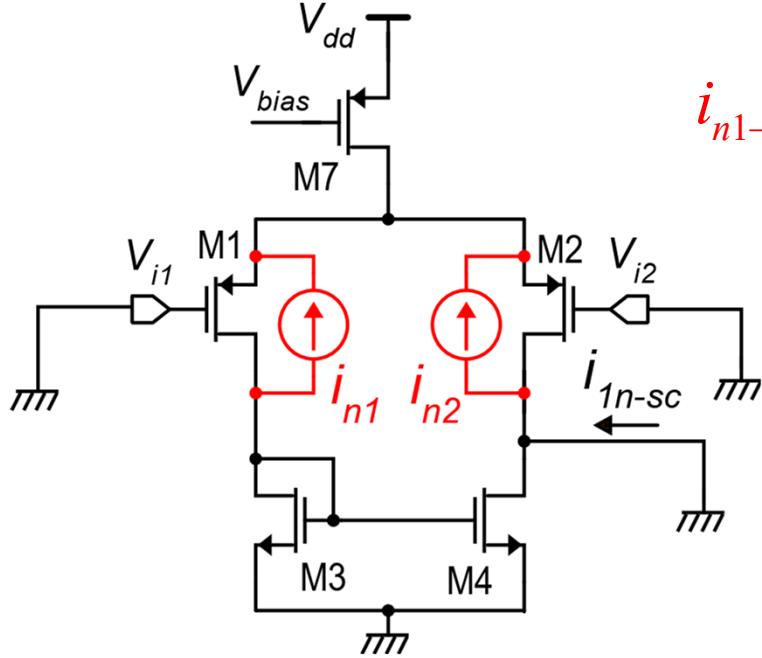

$$i_{n1-a} = i_{n1-b} = i_{n1}$$

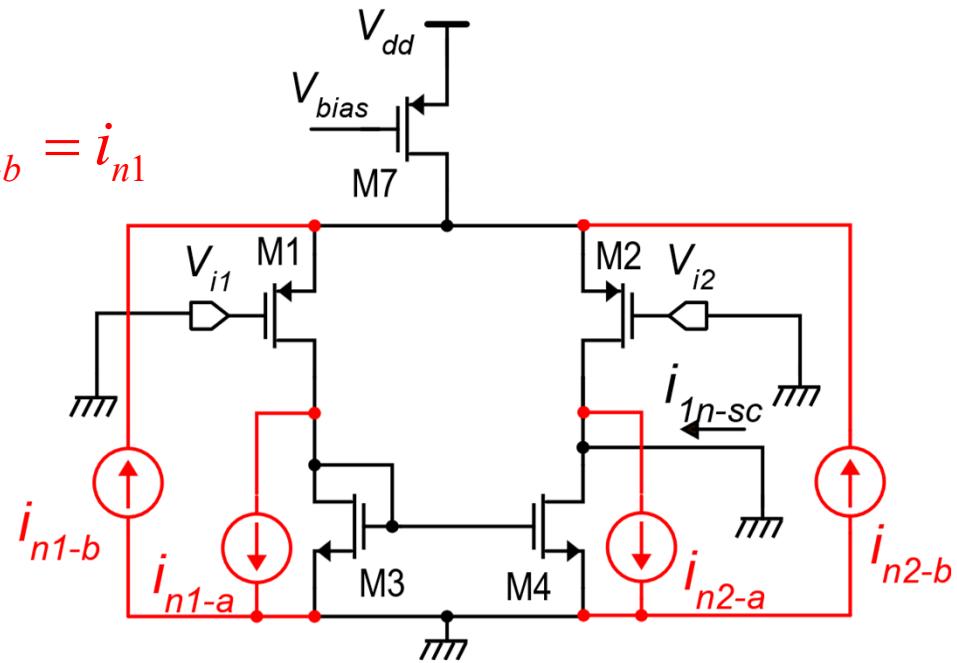


Since  $i_{n1}$  and  $i_{n2}$  are floating, we can split them into two sources with a terminal at *gnd*.


$i_{n1-a}$ : same effect as  $i_{n3}$ :  $A_{I1-a} \approx -1$   
 $i_{n1-b}$ : same effect as  $i_{n7}$ :  $A_{I1-b} \approx 0$        $A_{I1} \approx -1$

Repeating the procedure for  $i_{n2}$        $A_{I2} \approx 1$

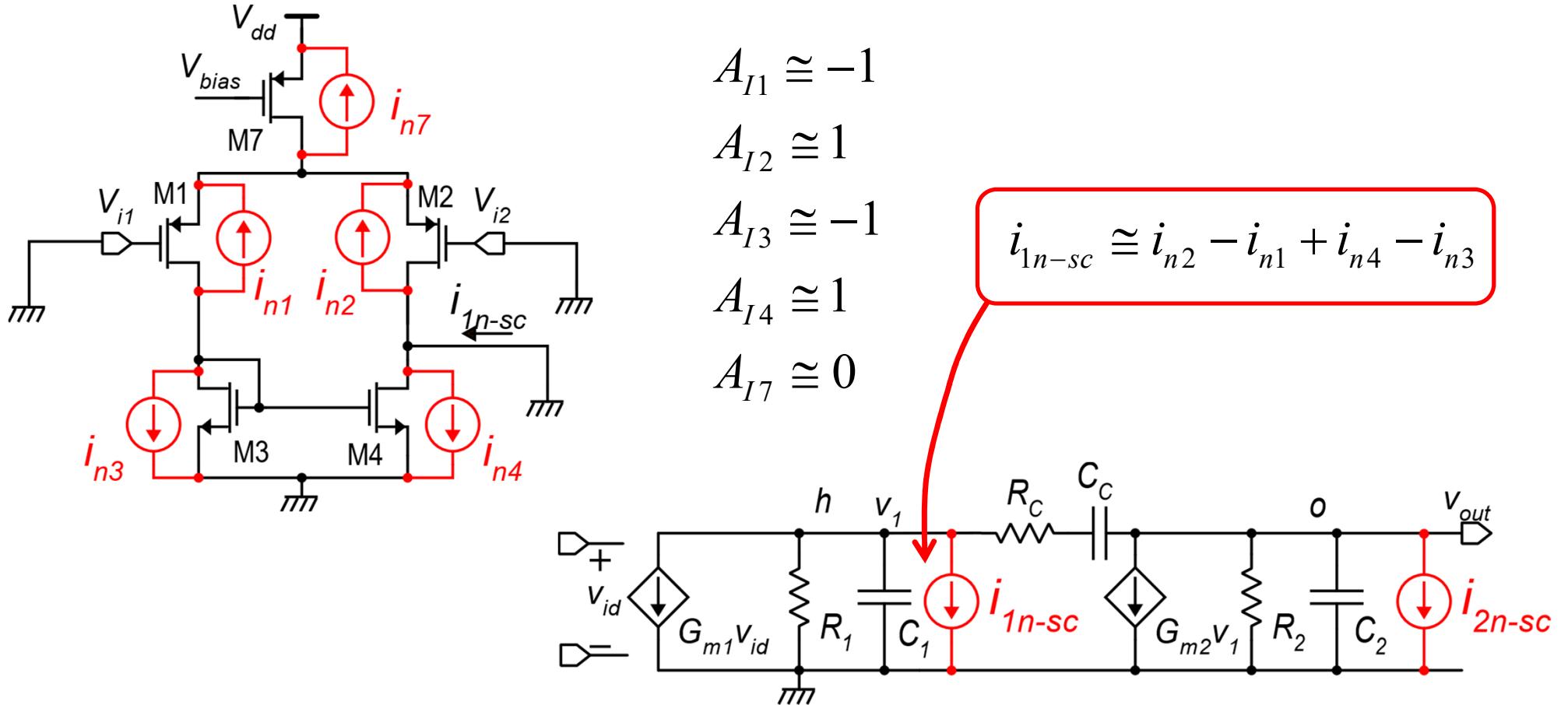
Putting all contribution together for the first stage:


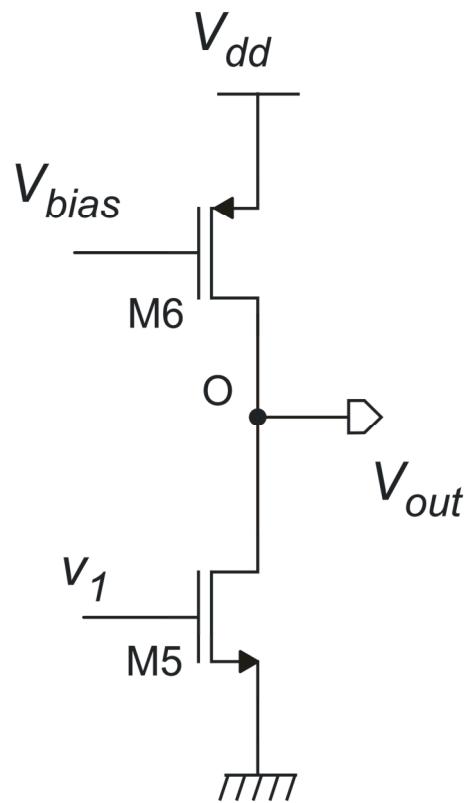
## Equivalent output noise current of the second stage



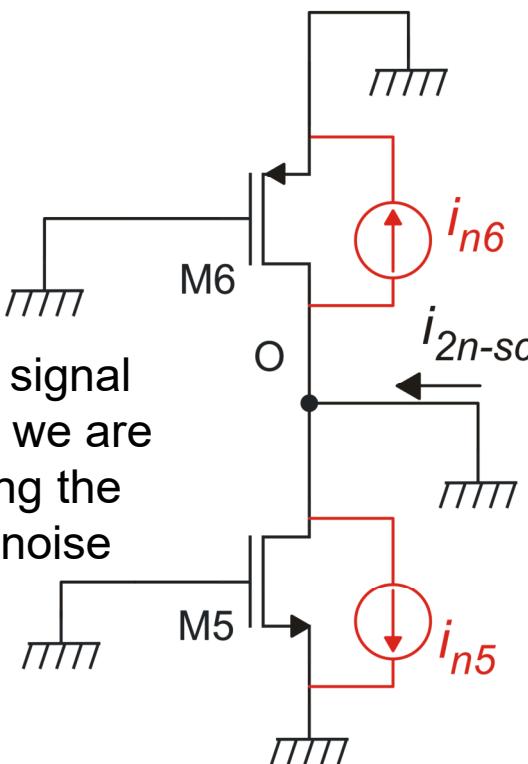
No input signal  
because we are  
calculating the  
effect of noise



$$i_{2n-sc} \cong i_{n5} + i_{n6}$$

Equivalent small signal circuit  
with current sources

## Putting the two stages together

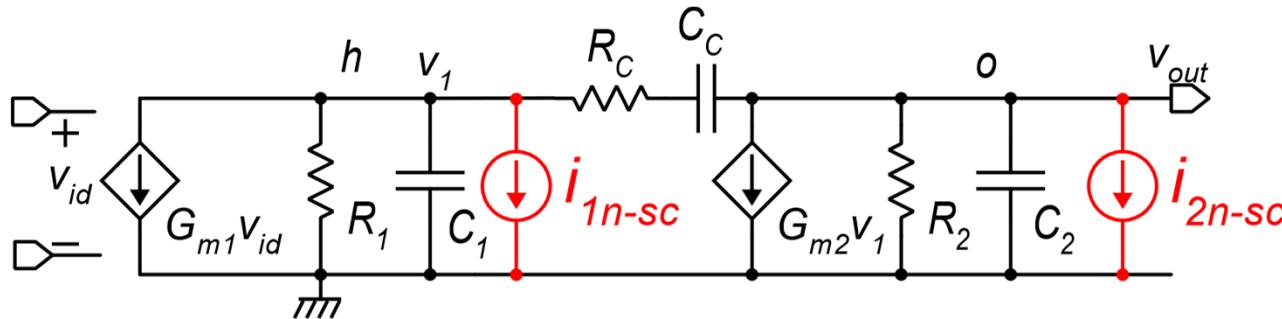


Step 1. Calculate the  $Y_m$  of the op-amp

$$i_{o-sc} = G_{m1}v_{id} \cdot A_{Ih}$$


$$A_{Ih} = \frac{i_{o-sc}}{i_h}$$
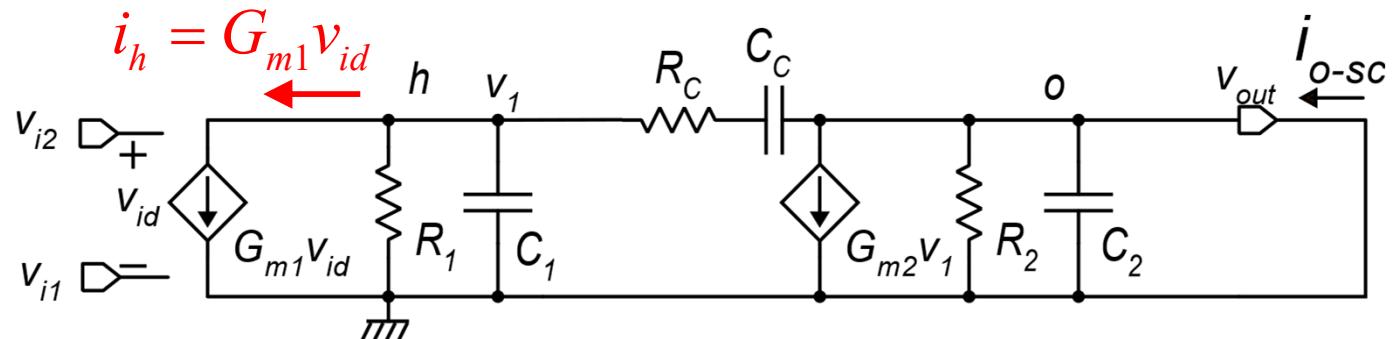
$$Y_m = \frac{i_{o-sc}}{v_{id}} = G_{m1}A_{Ih}$$



$A_{Ih}$  is the transfer function (current gain) from a current source connected between node  $h$  and gnd to the output short circuit current

## Calculation of $A_{Ih}$

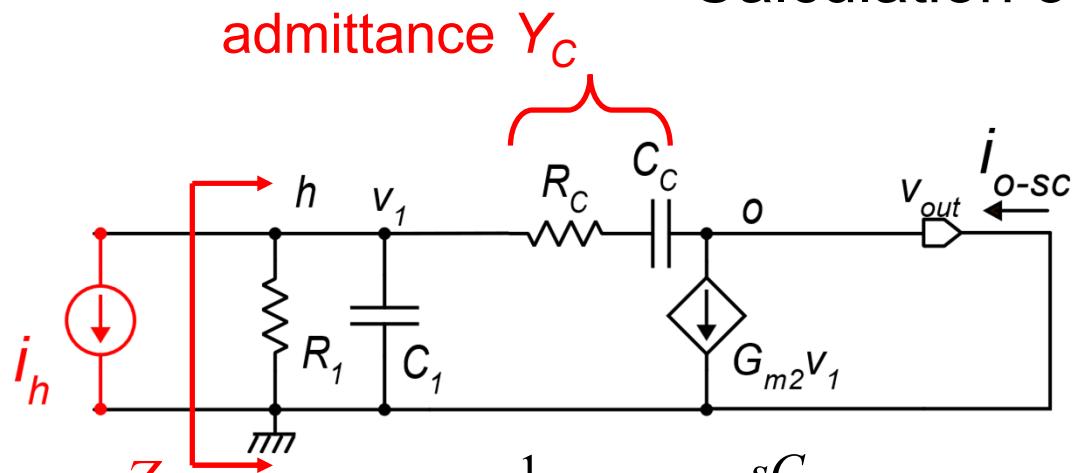

$$Z_A = \frac{1}{Y_C + \frac{1}{sC_C}} = \frac{sC_C}{1 + sR_C C_C}$$

$$Z_A = \frac{1}{Y_C + \frac{1}{R_1} + sC_1}$$

$$G_{m2} - Y_C = \left( G_{m2} - \frac{sC_C}{1 + sR_C C_C} \right) = \frac{G_{m2} - sC_C (1 - G_{m2} R_C)}{1 + sR_C C_C}$$

$$\text{since we set } R_C = \frac{1}{G_{m2}} \Rightarrow G_{m2} - Y_C = \frac{G_{m2}}{1 + sR_C C_C}$$

$$i_{o-sc} = v_1 G_{m2} - v_1 Y_C = v_1 (G_{m2} - Y_C)$$

$$v_1 = -Z_A i_h \rightarrow i_{o-sc} = -Z_A i_h (G_{m2} - Y_C)$$

$$A_{Ih} = \frac{i_{o-sc}}{i_h} = -Z_A (G_{m2} - Y_C)$$

## Calculation of $A_{Ih}$


$$Z_A = \frac{1}{\frac{sC_C}{1+sC_C R_C} + \frac{1}{R_1} + sC_1} = \frac{R_1(1+sC_C R_C)}{1+s(C_C R_1 + C_C R_C + C_1 R_1) + s^2 R_C C_C R_1 C_1}$$

$$G_{m2} - Y_C = \frac{G_{m2}}{1+sR_C C_C}$$

$$A_{Ih} = -Z_A (G_{m2} - Y_C) = \frac{-G_{m2} R_1}{1+s(C_C R_1 + C_C R_C + C_1 R_1) + s^2 R_C C_C R_1 C_1}$$


dc value:  $A_{Ih}(0) = -G_{m2} R_1$   
 $|A_{Ih}(0)| \gg 1$

qualitative frequency dependence

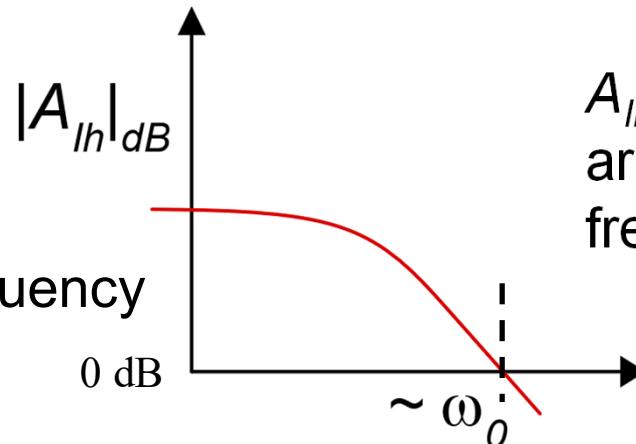

$A_{Ih}$  drops below 1 (0 dB) around the unity-gain frequency of the op-amp:

Let us come back to the noise

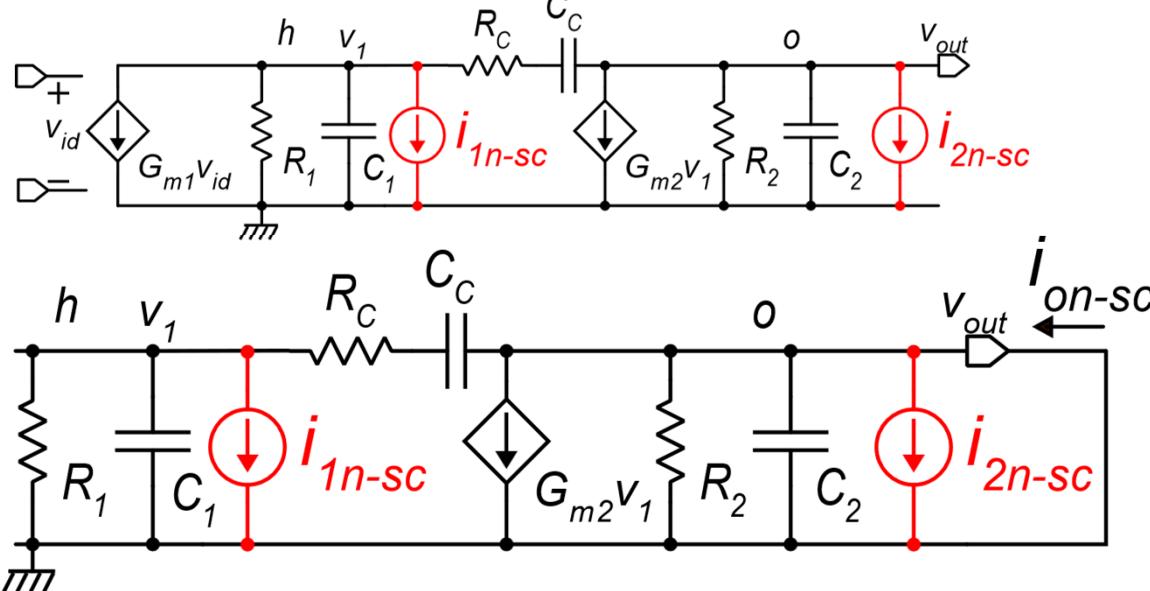

Circuit for calculation of the total output noise current

$$v_n = -\frac{1}{G_{m1}} \left( i_{1n-sc} + \frac{i_{2n-sc}}{A_{ih}} \right)$$

up to frequencies where  $|A_{ih}| \gg 1 \Rightarrow v_n \cong \frac{-i_{1n-sc}}{G_{m1}}$


$$Y_m = \frac{i_{o-sc}}{v_{id}} = G_{m1} A_{ih}$$

$$v_n = \frac{-i_{on-sc}}{Y_m}$$

$$i_{on-sc} = i_{2n-sc} + A_{ih} i_{1n-sc}$$

$$v_n = -\frac{i_{2n-sc}}{G_{m1} A_{ih}} - \frac{i_{1n-sc}}{G_{m1}}$$

## In the simple 2-stage op-amp

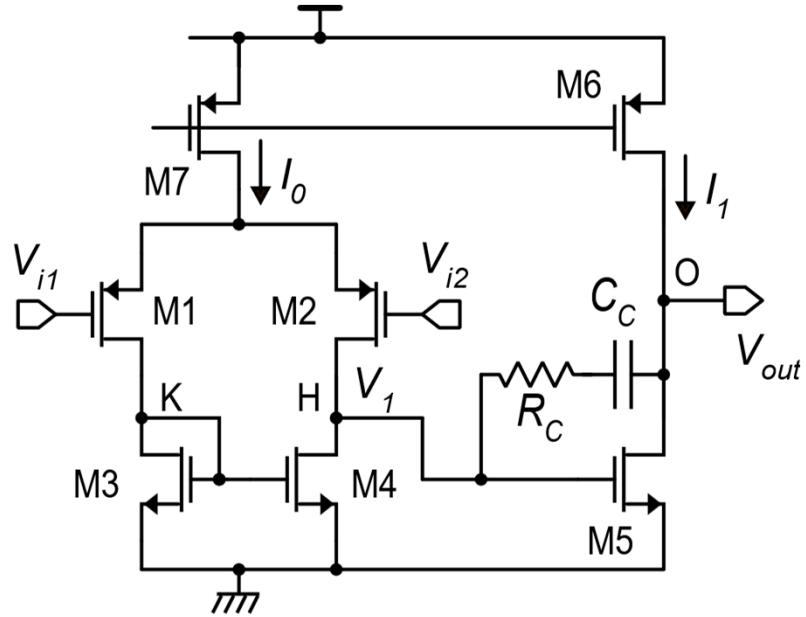

$$v_n \cong \frac{-i_{1n-sc}}{G_{m1}} = \frac{i_{n1} - i_{n2} + i_{n3} - i_{n4}}{g_{m1}}$$


$$S_{vn}(f) = \frac{S_{I1} + S_{I2} + S_{I3} + S_{I4}}{g_{m1}^2}$$

$$S_{vn}(f) = 2 \frac{S_{I1} + S_{I3}}{g_{m1}^2}$$

$$S_{In} = g_m^2 S_{Vn}$$

$$S_{vn}(f) = 2 \frac{g_{m1}^2 S_{v1} + g_{m3}^2 S_{v3}}{g_{m1}^2} = 2 \left( S_{v1} + \frac{g_{m3}^2}{g_{m1}^2} S_{v3} \right)$$

## Input noise density of the op-amp

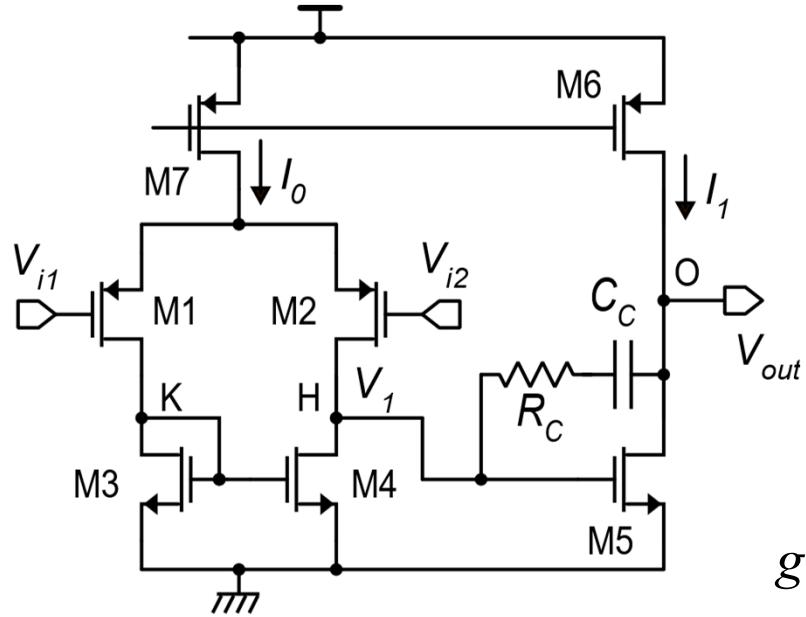

$$S_{vn}(f) = 2 \left( S_{v1} + \frac{g_{m3}^2}{g_{m1}^2} S_{v3} \right)$$

$$\underline{S_{vn}(f) = 2(S_{v1} + F^2 S_{v3})}$$


$$F = \frac{g_{m3}}{g_{m1}}$$

$$g_m = \frac{I_D}{V_{TE}} \quad \Rightarrow \quad F = \frac{I_{D3}}{V_{TE3}} \frac{V_{TE1}}{I_{D1}}$$

$$\underline{F = \frac{I_{D3}}{I_{D1}} \frac{V_{TE1}}{V_{TE3}}}$$

For this amplifier  $I_{D3}=I_{D1}$ , then:  $F = \frac{V_{TE1}}{V_{TE3}}$

## Thermal noise

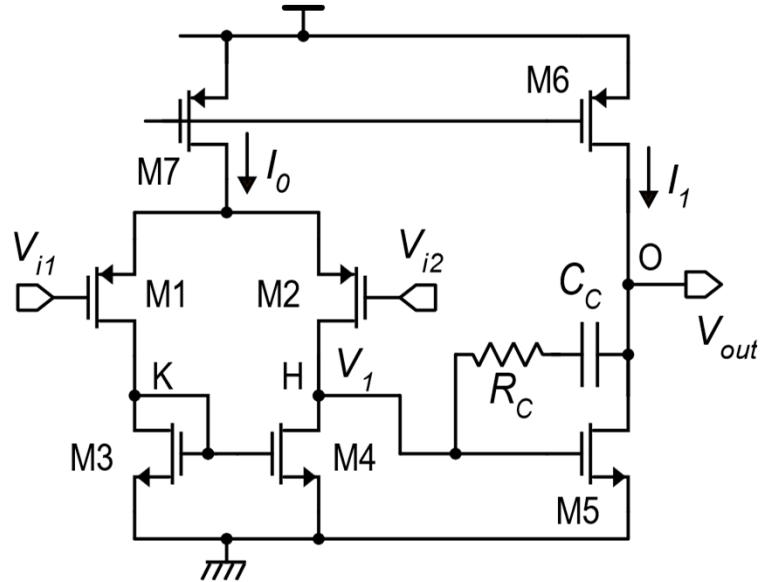

$$S_{vn}(f) = 2(S_{v1} + F^2 S_{v3})$$

using:  $S_v(f) = \frac{8}{3} kT \frac{1}{g_m}$


$$S_{vn-th}(f) = 2 \left( \frac{8}{3} kT \frac{1}{g_{m1}} + F^2 \frac{8}{3} kT \frac{1}{g_{m3}} \right)$$

$$S_{vn-th}(f) = 2 \cdot \frac{8}{3} kT \frac{1}{g_{m1}} \left( 1 + F^2 \frac{g_{m1}}{g_{m3}} \right)$$

$$F = \frac{g_{m3}}{g_{m1}}$$

$$S_{vn-th}(f) = 2 \cdot \frac{8}{3} kT \frac{1}{g_{m1}} (1 + F)$$

## Flicker noise

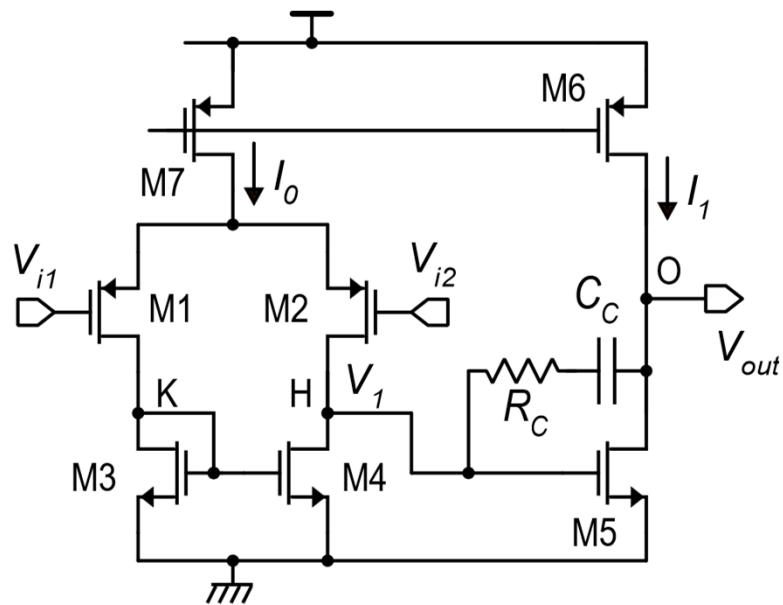


$$S_{vn}(f) = 2(S_{v1} + F^2 S_{v3})$$

using:  $S_v(f) = \frac{N_f}{WL} \frac{1}{f}$


p-MOS  $\Rightarrow N_{fp}$

n-MOS  $\Rightarrow N_{fn}$

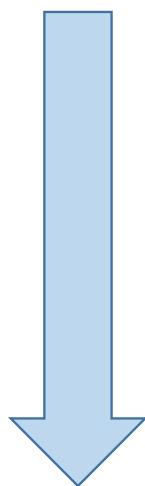

$$S_{vn-F}(f) = 2 \left( \frac{N_{fp}}{W_1 L_1} + F^2 \frac{N_{fn}}{W_3 L_3} \right) \frac{1}{f}$$
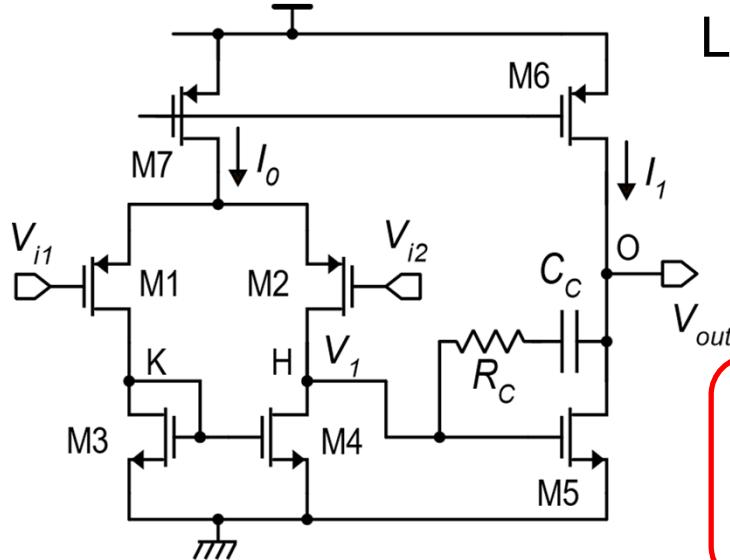
## General considerations about the op-amp noise:



Let us recall the thermal noise and use:  $g_{m1} = I_{D1}/V_{TE1}$ )

$$S_{vn-th}(f) = 2 \cdot \frac{8}{3} kT \frac{1}{g_{m1}} (1+F) = 2 \cdot \frac{8}{3} kT \frac{V_{TE1}}{I_{D1}} (1+F)$$


Thermal

$$S_{vn-F}(f) = 2 \left( \frac{N_{fp}}{W_1 L_1} + F^2 \frac{N_{fn}}{W_3 L_3} \right) \frac{1}{f}$$

Flicker

- For both the thermal and flicker noise, it is convenient to set  $F \ll 1$  ( $V_{TE1} \ll V_{TE3}$ )
- The larger  $I_{D1}$ , the lower the input thermal noise voltage density
- A small  $V_{TE1}$  helps obtaining small thermal noise densities with lower current
- A small flicker noise density can be obtained using large M1 and M3 areas

## Input offset voltage of the op-amp

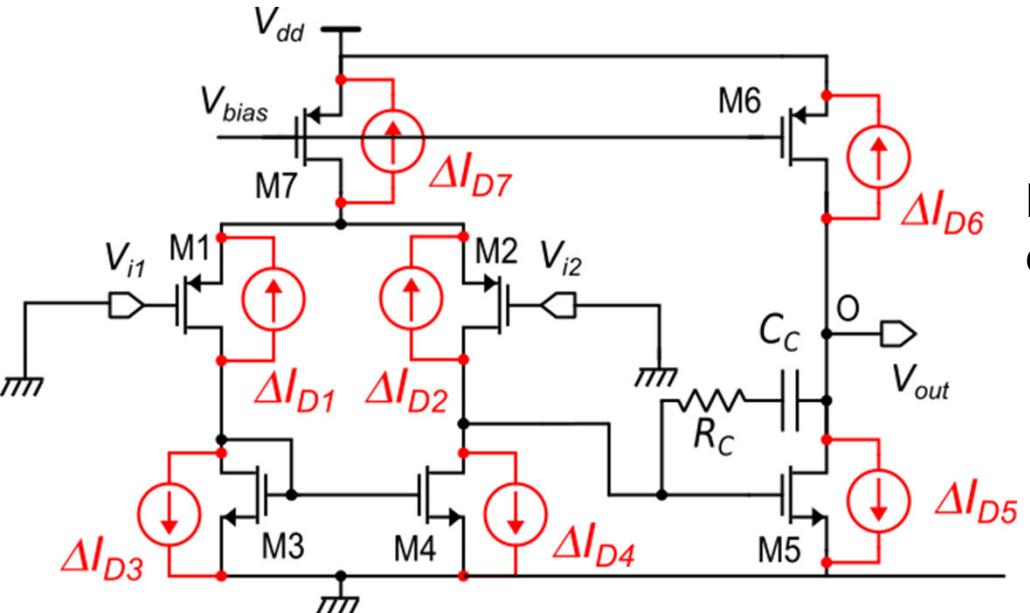

Op-amp with the equivalent current sources that takes into account parameter variations

$$v_n \approx \frac{-i_{1n-sc}}{G_{m1}} = \frac{i_{n1} - i_{n2} + i_{n3} - i_{n4}}{g_{m1}}$$

Let us just replace the noise current sources with the equivalent current sources of parameter variations

$$v_{io} \approx \frac{\Delta I_{D1} - \Delta I_{D2} + \Delta I_{D3} - \Delta I_{D4}}{g_{m1}}$$

Note that M1,M2 and M3,M4 form pairs of matched devices.

Then, we can group their parameter variation sources into single contributions that contain only matching errors

$$v_{io} \approx \frac{\Delta I_{D1,2} + \Delta I_{D3,4}}{g_{m1}}$$

## Input offset voltage of the op-amp

$$v_{io} \cong \frac{\Delta I_{D1,2} + \Delta I_{D3,4}}{g_{m1}} = \frac{I_{D1} \left[ \frac{\Delta \beta_{1,2}}{\beta_1} - \frac{2\Delta V_{t1,2}}{|V_{GS} - V_t|_1} \right] + I_{D3} \left[ \frac{\Delta \beta_{3,4}}{\beta_3} - \frac{2\Delta V_{t3,4}}{(V_{GS} - V_t)_3} \right]}{g_{m1}}$$

$$v_{io} \cong \frac{I_{D1}}{g_{m1}} \left\{ \left[ \frac{\Delta \beta_{1,2}}{\beta_1} - \frac{2\Delta V_{t1,2}}{|V_{GS} - V_t|_1} \right] + \frac{I_{D3}}{I_{D1}} \left[ \frac{\Delta \beta_{3,4}}{\beta_3} - \frac{2\Delta V_{t3,4}}{(V_{GS} - V_t)_3} \right] \right\}$$

in strong inversion



$$\frac{I_{D1}}{g_{m1}} = V_{TE1} = \frac{|V_{GS} - V_t|_1}{2}$$

$$v_{io} \cong \frac{|V_{GS} - V_t|_1}{2} \frac{\Delta \beta_{1,2}}{\beta_1} - \Delta V_{t1,2} + \\ + \frac{|V_{GS} - V_t|_1}{2} \frac{I_{D3}}{I_{D1}} \frac{\Delta \beta_{3,4}}{\beta_3} - \frac{I_{D3}}{I_{D1}} \frac{|V_{GS} - V_t|_1}{(V_{GS} - V_t)_3} \Delta V_{t3,4}$$

## Input offset voltage of the op-amp

$$v_{io} \cong \frac{|V_{GS} - V_t|_1}{2} \frac{\Delta\beta_{1,2}}{\beta_1} - \Delta V_{t1,2} + \frac{|V_{GS} - V_t|_1}{2} \frac{I_{D3}}{I_{D1}} \frac{\Delta\beta_{3,4}}{\beta_3} - \boxed{\frac{I_{D3}}{I_{D1}} \frac{|V_{GS} - V_t|_1}{(V_{GS} - V_t)_3} \Delta V_{t3,4}}$$


$F$

$$F = \frac{g_{m3}}{g_{m1}} = \frac{I_{D3}}{I_{D1}} \frac{V_{TE1}}{V_{TE3}}$$

in strong inversion:  $V_{TE1} = \frac{|V_{GS} - V_t|_1}{2}$ ,  $V_{TE3} = \frac{(V_{GS} - V_t)_3}{2}$

$$v_{io} \cong \underbrace{\frac{|V_{GS} - V_t|_1}{2} \frac{\Delta\beta_{1,2}}{\beta_1} - \Delta V_{t1,2}}_{\text{Contribution of the input pair devices}} + \underbrace{\left( \frac{I_{D3}}{I_{D1}} \right) \frac{|V_{GS} - V_t|_1}{2} \frac{\Delta\beta_{3,4}}{\beta_3} - F \Delta V_{t3,4}}_{\text{Contribution of the mirror devices}}$$
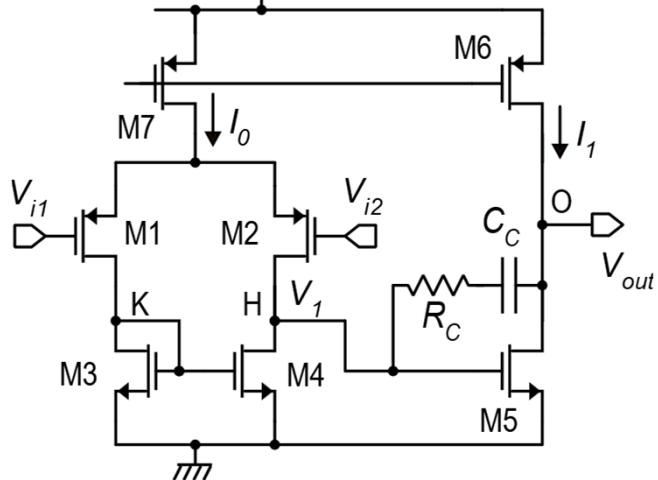
# Input offset voltage of the op-amp: standard deviation



$$v_{io} \cong \frac{|V_{GS} - V_t|_1}{2} \frac{\Delta\beta_{1,2}}{\beta_1} - \Delta V_{t1,2} + \left( \frac{I_{D3}}{I_{D1}} \right) \frac{|V_{GS} - V_t|_1}{2} \frac{\Delta\beta_{3,4}}{\beta_3} - F \Delta V_{t3,4}$$

$$I_{D1} = I_{D3}$$

$$v_{io} \cong \frac{|V_{GS} - V_t|_1}{2} \frac{\Delta\beta_{1,2}}{\beta_1} - \Delta V_{t1,2} + \frac{|V_{GS} - V_t|_1}{2} \frac{\Delta\beta_{3,4}}{\beta_3} - F \Delta V_{t3,4}$$


$$\sigma_{vio}^2 \cong \frac{(V_{GS} - V_t)_1^2}{4} \sigma_{\frac{\Delta\beta_{1,2}}{\beta_1}}^2 + \sigma_{\Delta V_{t1,2}}^2 + \frac{(V_{GS} - V_t)_1^2}{4} \sigma_{\frac{\Delta\beta_{3,4}}{\beta_3}}^2 + F^2 \sigma_{\Delta V_{t3,4}}^2$$

$$\sigma_{vio}^2 \cong \frac{(V_{GS} - V_t)_1^2}{4} \frac{C_{\beta p}^2}{W_1 L_1} + \frac{C_{Vtp}^2}{W_1 L_1} + \frac{(V_{GS} - V_t)_1^2}{4} \frac{C_{\beta n}^2}{W_3 L_3} + F^2 \frac{C_{Vtn}^2}{W_3 L_3}$$

$$\sigma_{\Delta V_t} = \frac{C_{Vt}}{\sqrt{WL}}$$

$$\sigma_{\frac{\Delta\beta}{\beta}} = \frac{C_\beta}{\sqrt{WL}}$$

## Design for input offset voltage

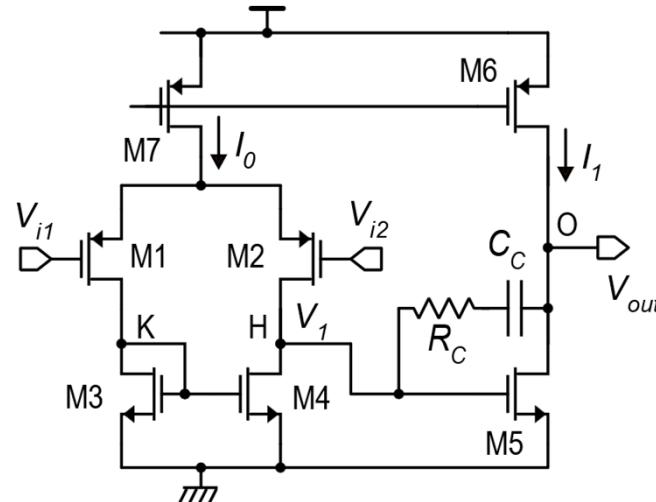

$$\sigma_{vio}^2 \cong \frac{(V_{GS} - V_t)_1^2}{4} \frac{C_{\beta p}^2}{W_1 L_1} + \frac{C_{Vtp}^2}{W_1 L_1} + \frac{(V_{GS} - V_t)_1^2}{4} \frac{C_{\beta n}^2}{W_3 L_3} + F^2 \frac{C_{Vtn}^2}{W_3 L_3}$$

$$\sigma_{vio}^2 \cong \frac{A}{W_1 L_1} + \frac{B}{W_3 L_3}$$

$$A = \frac{(V_{GS} - V_t)_1^2}{4} C_{\beta p}^2 + C_{Vtp}^2 ; \quad B = \frac{(V_{GS} - V_t)_1^2}{4} C_{\beta n}^2 + F^2 C_{Vtn}^2$$

Total gate area of the input pair and mirror:

$$S = 2(W_1 L_1 + W_3 L_3)$$

## Offset voltage: area optimization procedure

$$\sigma_{vio}^2 \cong \frac{A}{W_1 L_1} + \frac{B}{W_3 L_3}$$

$$W_3 L_3 = a \cdot W_1 L_1$$

$$S = 2(W_1 L_1 + W_3 L_3)$$

Example: if  $a=1$ , we are assigning the same area to the input pair and to the mirror

Optimization problem: find the value of  $a$  that allows obtaining the required  $\sigma_{vio}$  with the minimum area occupation.

$$\sigma_{vio}^2 \cong \frac{A}{W_1 L_1} + \frac{B}{a W_1 L_1} = \frac{1}{W_1 L_1} \left( A + \frac{B}{a} \right)$$

$$W_1 L_1 = \frac{1}{\sigma_{vio}^2} \left( A + \frac{B}{a} \right)$$

$$S = 2(W_1 L_1 + a W_1 L_1) = 2 W_1 L_1 (1 + a)$$


$$S = 2 \frac{1}{\sigma_{vio}^2} \left( A + \frac{B}{a} \right) (1 + a)$$

We need to find the minimum of this function of  $a$
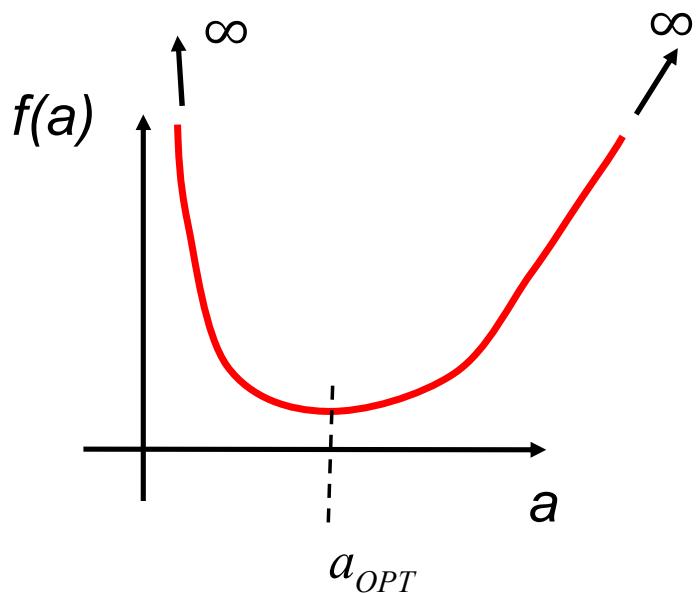
## Offset voltage: area optimization procedure

$$S = 2 \frac{1}{\sigma_{vio}^2} \left( A + \frac{B}{a} \right) (1+a) = 2 \frac{1}{\sigma_{vio}^2} \left( A + aA + \underbrace{\frac{B}{a} + B}_{a} \right)$$

$$\sigma_{vio}^2 \cong \frac{A}{W_1 L_1} + \frac{B}{W_3 L_3}$$



only these two terms depend on  $a$ . then we have to find the minimum of:

$$f(a) = aA + \frac{B}{a} \quad \frac{df(a)}{da} = A - \frac{B}{a^2} = 0$$


$$a_{OPT} = \sqrt{\frac{B}{A}} \quad (a > 0)$$

$$\begin{cases} W_1 L_1 = \frac{1}{\sigma_{vio}^2} \left( A + \frac{B}{a_{OPT}} \right) \\ W_3 L_3 = a \cdot W_1 L_1 \end{cases}$$

## Current consumption of the op-amp

- In this section, we will consider the main factors that affect the current consumption of the operational amplifier.
- We have already found an expression that ties the current consumption with the GBW specification
- Here, we will review that expression, introducing also the role of the " $F$ " parameter that comes from the noise and offset analysis
- After that, we will find an expression of the current consumption that highlights the relationship with the thermal noise specification
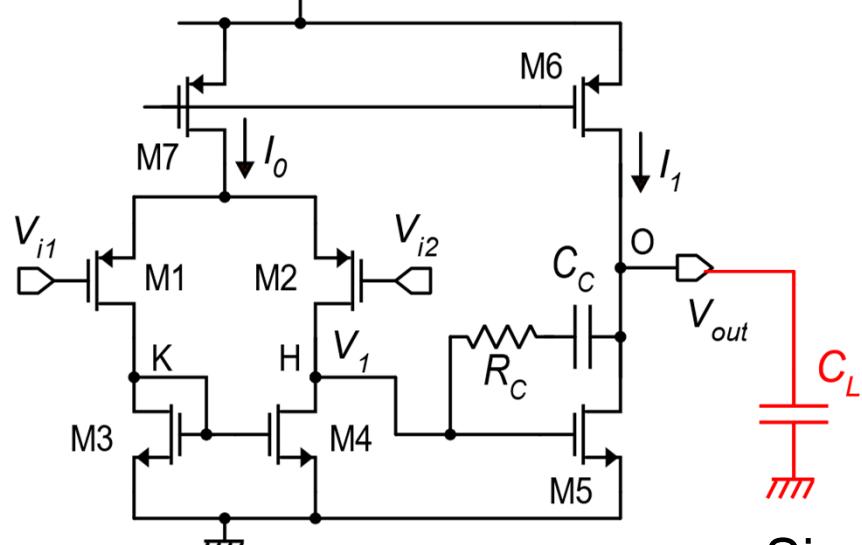
## $GBW$ and supply current (from the $GBW$ and $\varphi_m$ design procedure)



$$I_{supply} = 2\pi\sigma \cdot GBW \cdot C_L \cdot \left( V_{TE5} + 2 \frac{g_{m1}}{g_{m5}} V_{TE1} \right)$$

$$I_{supply} = 2\pi\sigma \cdot GBW \cdot C_L \cdot V_{TE5} \left( 1 + 2 \frac{g_{m1}}{g_{m5}} \frac{V_{TE1}}{V_{TE5}} \right)$$

define:  $\frac{g_{m1}}{g_{m5}} = \frac{1}{\sigma} \frac{C_C}{C_L} = r_{gm}$

Since  $V_{GS5} = V_{GS3}$      $V_{TE5} = V_{TE3}$


$$\frac{V_{TE1}}{V_{TE5}} = \frac{V_{TE1}}{V_{TE3}} = F$$

$$I_{supply} = 2\pi\sigma \cdot GBW \cdot C_L \cdot V_{TE5} \left( 1 + 2Fr_{gm} \right)$$

Fraction due to  
the second stage

Fraction due to  
the first stage
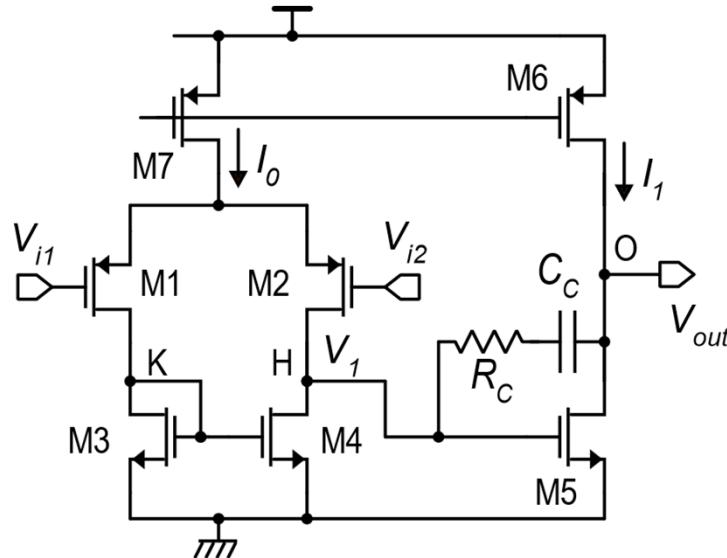
## Current consumption of the op-amp - role of the thermal noise spec



If the "dominant" specification is the thermal noise PSD ( $S_{vn-th}$ ), we can use a different expression

Let us start again from the general formula:

$$I_{supply} = 2g_{m1}V_{TE1} + g_{m5}V_{TE5}$$

We need to highlight  
the role of  $g_{m1}$

$$S_{vn-th} = 2 \cdot \frac{8}{3} kT \frac{1}{g_{m1}} (1 + F) \rightarrow g_{m1} = 2 \cdot \frac{8}{3} kT \frac{1}{S_{vn-th}} (1 + F)$$

## Current consumption of the op-amp

$$I_{supply} = 2g_{m1}V_{TE1} + g_{m5}V_{TE5} = 2g_{m1}V_{TE1} \left( 1 + \frac{1}{2} \frac{g_{m5}}{g_{m1}} \frac{V_{TE5}}{V_{TE1}} \right) = 2g_{m1}V_{TE1} \left( 1 + \frac{1}{2r_{gm}F} \right)$$

$$g_{m1} = 2 \cdot \frac{8}{3} kT \frac{1}{S_{vn-th}} (1+F)$$

$$\frac{1}{r_{gm}} \quad \frac{1}{F}$$

$$I_{supply} = 2 \cdot 2 \cdot \frac{8}{3} kT \frac{1}{S_{vn-th}} (1+F) V_{TE1} \left( 1 + \frac{1}{2r_{gm}F} \right)$$

Note: F and 1/F appear: an optimum F value can be calculated

Note:  $I_{supply} \propto \frac{1}{S_{vn-th}}$

low thermal noise ( $S_{vn-th}$ ) means high current consumption

$$I_{supply} = \frac{32}{3} kT (1+F) \frac{V_{TE1}}{S_{vn-th}} \left( 1 + \frac{1}{2r_{gm}F} \right)$$

The diagram shows the term  $\frac{1}{2r_{gm}F}$  from the original equation split into two fractions:  $\frac{1}{2r_{gm}}$  and  $\frac{1}{F}$ . A blue bracket groups  $\frac{1}{2r_{gm}}$  and  $F$ , with a blue arrow pointing to it from the text "calculated". Red arrows point from the text "Fraction due to the first stage" to  $\frac{1}{2r_{gm}}$  and from the text "Fraction due to the second stage" to  $F$ .

## Examples

Case 1:  $GBW = 10\text{MHz}$ ,  $C_{L-\max} = 10\text{pF}$ ,  $\sigma = 3$   $V_{TE5} = 150\text{ mV}$ ,  $V_{TE1} = 50\text{mV}$ ,  $C_C = C_L$

$$F = \frac{V_{TE1}}{V_{TE3}} = \frac{V_{TE1}}{V_{TE5}} = \frac{1}{3} \quad r_{gm} = \frac{g_{m1}}{g_{m5}} = \frac{1}{\sigma} \frac{C_C}{C_L} = \frac{1}{3} \quad I_{supply} = 2\pi\sigma \cdot GBW \cdot C_L \cdot V_{TE5} \left( 1 + 2Fr_{gm} \right)$$

$$I_{supply} = 2\pi\sigma \cdot GBW \cdot C_L \cdot V_{TE5} \left( 1 + \frac{2}{9} \right) = 6.28 \cdot 3 \cdot 10 \times 10^6 \cdot 10 \times 10^{-12} \cdot 0.15 \cdot \frac{11}{9} = 345 \mu\text{A}$$

Case 2: as above, but the GBW specification is replaced by noise specs:

$$\sqrt{S_{vn-th}} = 1 \text{ nV} / \sqrt{\text{Hz}} \Rightarrow S_{vn-th} = 10^{-18} \text{ V}^2 / \text{Hz}$$

$$I_{supply} = \frac{32}{3} kT (1+F) \frac{V_{TE1}}{S_{vn-th}} \left( 1 + \frac{1}{2r_{gm}F} \right) = \frac{32}{3} 4 \times 10^{-21} \frac{4}{3} \frac{0.05}{10^{-18}} \left( 1 + \frac{9}{2} \right) = 15.6 \text{ mA}$$


## Consistent and contrasting specifications

As we have seen in previous example, the GBW specification and thermal noise density specification are consistent, since for both the following rule holds: the stricter the specification, the higher the required supply-current.

If the design include both specifications, then one of them is likely to be dominant. In the previous example, the noise specification dominates: the minimum supply current required to meet the required noise specification is much larger the current required for the given GBW- $C_L$  combination. Then, if we design the amplifier for the noise density, we certainly meet the GBW requirement.

Other specification pairs are likely to be contrasting: thermal noise and speed are in contrast with the supply current specification. The same can be said about flicker noise and area.

## Action of various specifications:

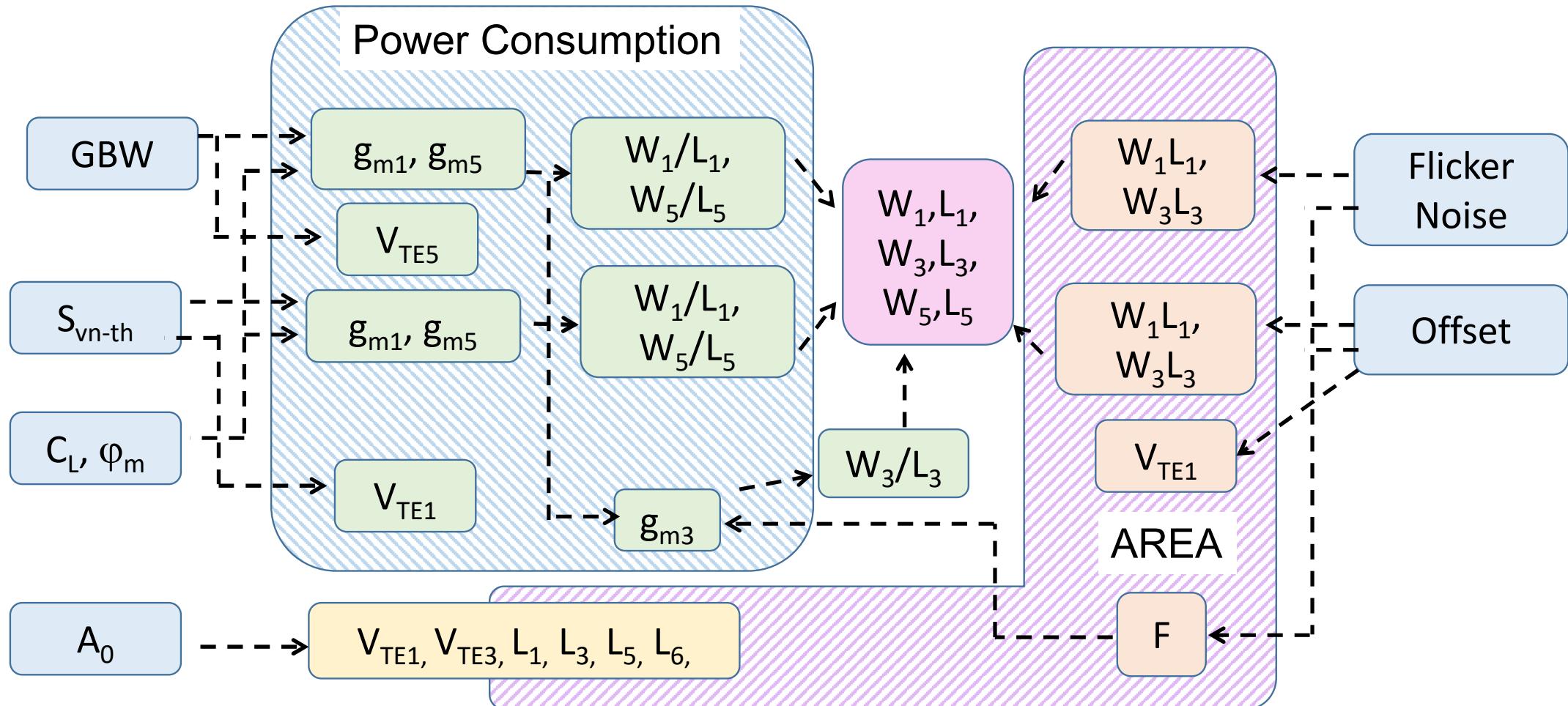

Commercial products: high speed - low thermal noise CMOS op-amp



Burr-Brown Products  
from Texas Instruments



OPA300, OPA2300  
OPA301, OPA2301

SBOS271D - MAY 2003 - REVISED JUNE 2007

---

## Low-Noise, High-Speed, 16-Bit Accurate, CMOS OPERATIONAL AMPLIFIER

---

### FEATURES

- High Bandwidth: 150MHz
- 16-Bit Settling in 150ns
- Low Noise:  $3\text{nV}/\sqrt{\text{Hz}}$
- Low Distortion: 0.003%
- Low Power: 9.5mA (typ) on 5.5V
- Shutdown to 5 $\mu\text{A}$
- Unity-Gain Stable
- Excellent Output Swing:  
(V+) – 100mV to (V-) + 100mV
- Single Supply: +2.7V to +5.5V
- Tiny Packages: MSOP and SOT23

### APPLICATIONS

- 16-Bit ADC Input Drivers
- Low-Noise Preamplifiers
- IF/RF Amplifiers
- Active Filtering

### DESCRIPTION

The OPA300 and OPA301 series high-speed, voltage-feedback, CMOS operational amplifiers are designed for 16-bit resolution systems. The OPA300/OPA301 series are unity-gain stable and feature excellent settling and harmonic distortion specifications. Low power applications benefit from low quiescent current. The OPA300 and OPA2300 feature a digital shutdown (Enable) function to provide additional power savings during idle periods. Optimized for single-supply operation, the OPA300/OPA301 series offer superior output swing and excellent common-mode range.

The OPA300 and OPA301 series op amps have 150MHz of unity-gain bandwidth, low  $3\text{nV}/\sqrt{\text{Hz}}$  voltage noise, and 0.1% settling within 30ns. Single-supply operation from 2.7V ( $\pm 1.35\text{V}$ ) to 5.5V ( $\pm 2.75\text{V}$ ) and an available shutdown function that reduces supply current to 5 $\mu\text{A}$  are useful for portable low-power applications. The OPA300 and OPA301 are available in

low power? →

# Commercial product: low power op-amp



## 1 $\mu$ A Micropower CMOS Operational Amplifiers AD8502/AD8504

### FEATURES

- Supply current: 1  $\mu$ A maximum/amplifier
- Offset voltage: 3 mV maximum
- Single-supply or dual-supply operation
- Rail-to-rail input and output
- No phase reversal
- Unity gain stable

### PIN CONFIGURATIONS



Figure 1. 8-Lead SOT-23

| DYNAMIC PERFORMANCE                                 | SR<br>GBP<br>$\emptyset_o$ | $-40^\circ\text{C} < T_A < +125^\circ\text{C}$<br>$R_{\text{LOAD}} = 1 \text{ M}\Omega$ | 2                | $\mu\text{A}$                |
|---|----------------------------|---|------------------|------------------------------|
| Slew Rate<br>Gain Bandwidth Product<br>Phase Margin |                            |   | 0.004<br>7<br>60 | V/ $\mu$ s<br>kHz<br>Degrees |

| Parameter         | Symbol | Conditions | Min | Typ | Max | Unit  |
|-------------------|--------|------------|-----|-----|-----|---|
| NOISE PERFORMANCE |        |            | 6   | 190 | 0.1 | $\mu\text{V p-p}$<br>$\text{nV}/\sqrt{\text{Hz}}$<br>$\text{pA}/\sqrt{\text{Hz}}$ |