

# Introducing myself


Michele Dei: [michele.dei@unipi.it](mailto:michele.dei@unipi.it)

Teaching during this year:  
~20 hours

Topics:  
Comparators, ADCs, DACs, Integrated Filters

New here!  
My hope is to maintain the high standards of this teaching

# Comparators

 


Symbol (differential input kind)

1) **Detect** the sign of a differential analog signal.

Sometimes S/E input case:

$V_{i2}$  is derived from an internal voltage reference

$$V_d = V_{i1} - V_{i2}$$

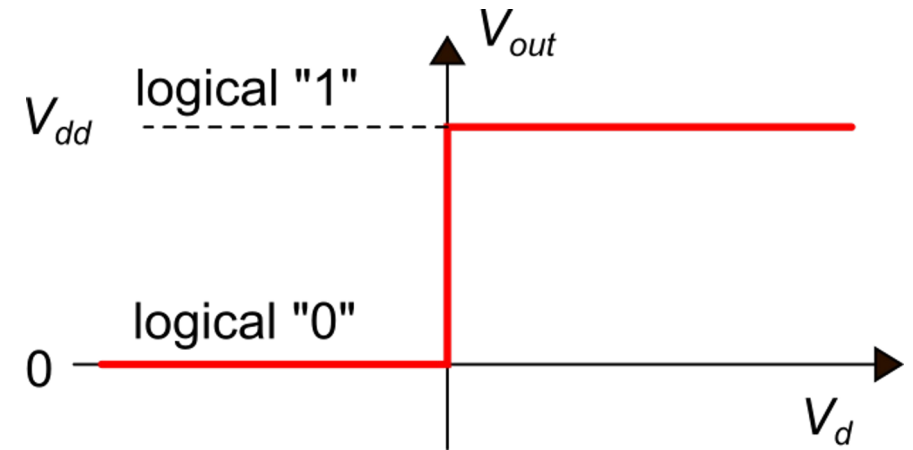

2) **Codify** the outcome in digital domain

$$V_{out} = \begin{cases} "0" & \text{if } V_d \leq 0 \\ "1" & \text{if } V_d > 0 \end{cases}$$

# Applications

## Building block in:



- Mixed-signal front-ends:  
sensors AFEs;  
signal-processing (ADCs, DACs)
- Signal-and-function generation
- Digital communication (symbol recognition in a noisy channel)
- Artificial neural networks (perceptron: linear binary classification)

# Continuous-time vs dynamic comparator
 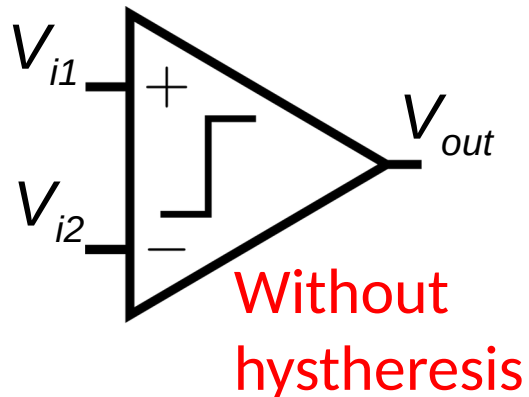
## Continuous-time (CT) comparator:

Used in level-crossing event-driven circuits


- ✗ Static power consumption
- Can be designed in order to embed hysteresis
- ✓ Output always valid


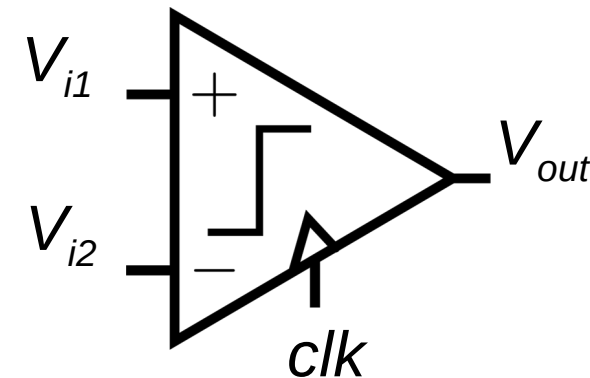
## Dynamic comparator (or latched comparator):

Used in clock-synchronous circuits (as the comparator needs a driving clock signal)

- ✓ No static power consumption (in basic single-stage configuration)
- No hysteresis
- ✗ Sometimes: output valid only during half clock period




# CT Comparators: amplifier-based implementations

A high-gain amplifier can be used as a comparator:

Op-amp topologies can be used in open loop or even positive feedback:

 Speed is prime: no frequency compensation (no stability issues)




✗ **Accuracy loss:** a region exists where the logical level is undefined

✗ In several applications this may lead to unwanted stable or metastable states (→)
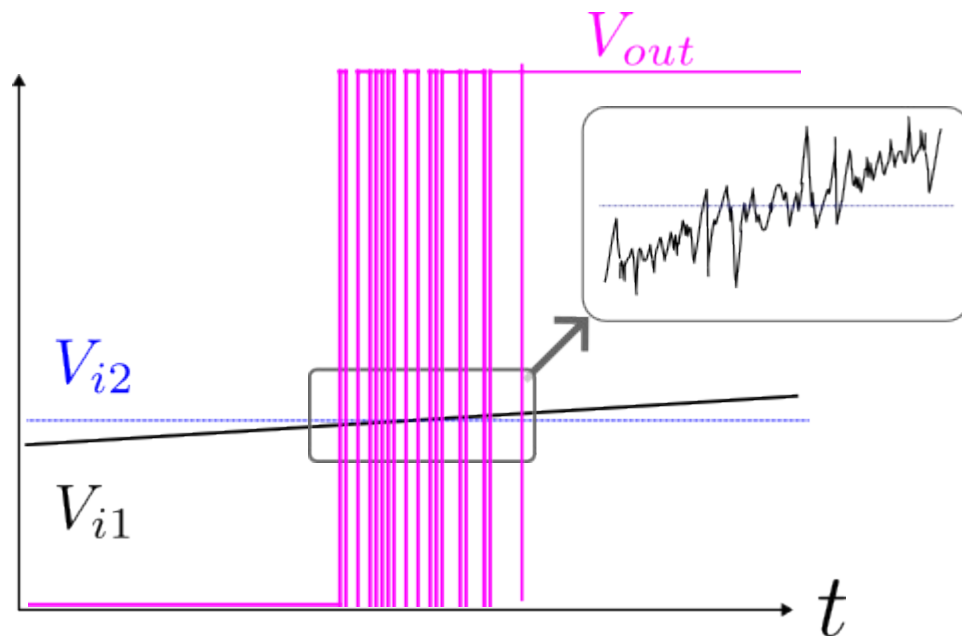
# CT Comparators: amplifier-based implementations

Transient behaviour:  
(RTI noise on  $V_{i1}$  port)




## Glitches for slow varying input

common issue to all CT comparators without hysteresis

If level crossing is used as trigger in a complex system with feed back: time uncertainty and/or stability issues


If the comparator is interfaced with a synchronous digital FSM:  $T_{hold}$ ,  $T_{setup}$  violation (need for synchronizer circuit otherwise data are loss)

# Regenerative comparators: hysteresis

 

Thanks to the hysteresis, the comparator produces a **valid output** level across the whole input range. Use of positive feedback: “**vertical**” edges.

 The hysteresis introduces an **uncertainty band** that reduces the accuracy but helps rejecting noise when the input differential voltage is close to zero.



Possible regenerative comparator:  
Op-amp-based Schmitt trigger.

## Drawbacks

- Over-sized solution for integrated cells
- Low impedance on the non-inverting input

# Off-the-shelf devices



TLV9022, TLV9032, TLV9024, TLV9034  
SNOSDA3B – JUNE 2020 – REVISED NOVEMBER 2020

## TLV902x and TLV903x High-Precision Dual and Quad Comparators

- Rail-to-Rail input with fault-tolerance
- 100ns Typ propagation delay


 


Figure 5-1. D, DGK, PW, DDF Packages  
8-Pin SOIC, VSSOP, TSSOP, SOT-23-8  
Top View

 No built-in hysteresis.  
Datasheet suggests Schmitt trigger configuration



**ANALOG DEVICES** Fast, Rail-to-Rail, Low Power, 2.5 V to 5.5 V, Single-Supply TTL/CMOS Comparator

Data Sheet AD8469

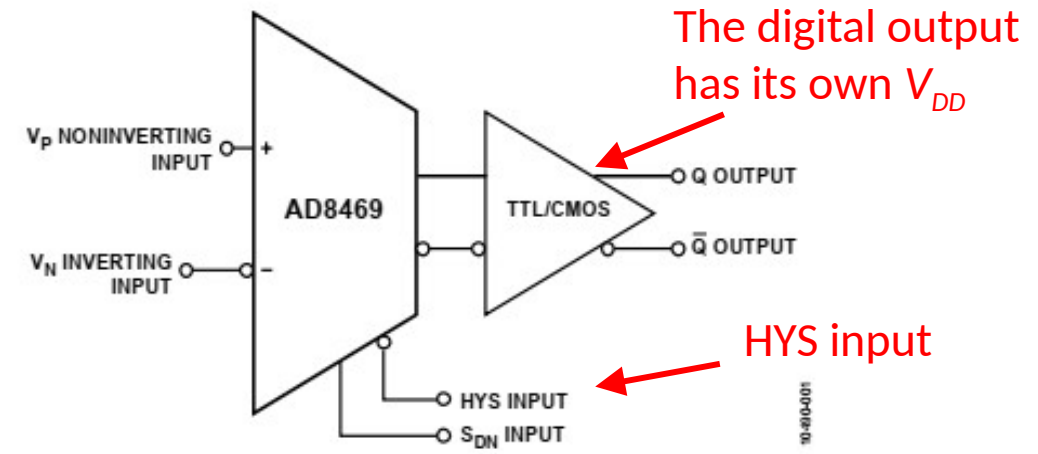



Figure 1.

Programmable hysteresis from 0 to 160 mV ( $\Delta V_H$ ) depending on current on pin

- Input common-mode voltage:  $V_{EE} - 0.2 V$  to  $V_{CC} + 0.2 V$**
- Low glitch TTL-/CMOS-compatible output stage**
- 40 ns propagation delay**


 
# Compact comparator cell for Systems on a Chip



## Four-transistor hysteresis cell

Inputs:  $I_1, I_2$

Outputs:  $V_1, V_2$

Formed by:

Cross-coupled MOSFETs M2-M3

Load MOSFETS M1, M4

Constraint:

$I_1 + I_2 = I_0 = \text{constant}$


Analysis:  $I_2$  in  $[0, I_0]$

Notable points:

$I_2 = 0; I_1 = I_0$


$I_2 = I_1 = I_0/2$

$I_2 = I_0; I_1 = 0$

 



 
## Analysis of the four-transistor cell: starting point



**Design condition:** we size  $\beta_L$  in such a way that:

$$V_1(0) = V_{GS1}(0) < 2V_t \Rightarrow V_{GS1}(0) - V_t < V_t \quad \text{The reason will be clear later}$$
 
# Analysis of the four-transistor cell: increasing $I_2$




As  $I_2$  increases,  $I_1$  decreases by the same amount, then  $V_1$  decreases:

$$V_1 = V_{GS1} = V_t + \sqrt{\frac{2I_1}{\beta_L}}$$

Until  $V_2 < V_t$ : M2, M4 are off


$V_2$  increases:  
as a consequence  
of  $I_2$  increase  
while  $V_{GS3} = V_1$  decrease
 
## Analysis of the four-transistor cell: $V_2$ reaches $V_t$



For  $V_2 = V_t$ , M2 and M4 are still off.  
Then (M1 and M3 have the same VGS):



$$I_1 = I_{D1} \quad I_2 = I_{D3}$$

 

→ **Hypothesis:** If M3 is now in saturation:

$$\frac{I_2}{I_1} = \frac{\beta_C}{\beta_L} > 1 \longrightarrow I_2 > I_1 : \quad I_2 > \frac{I_0}{2}$$
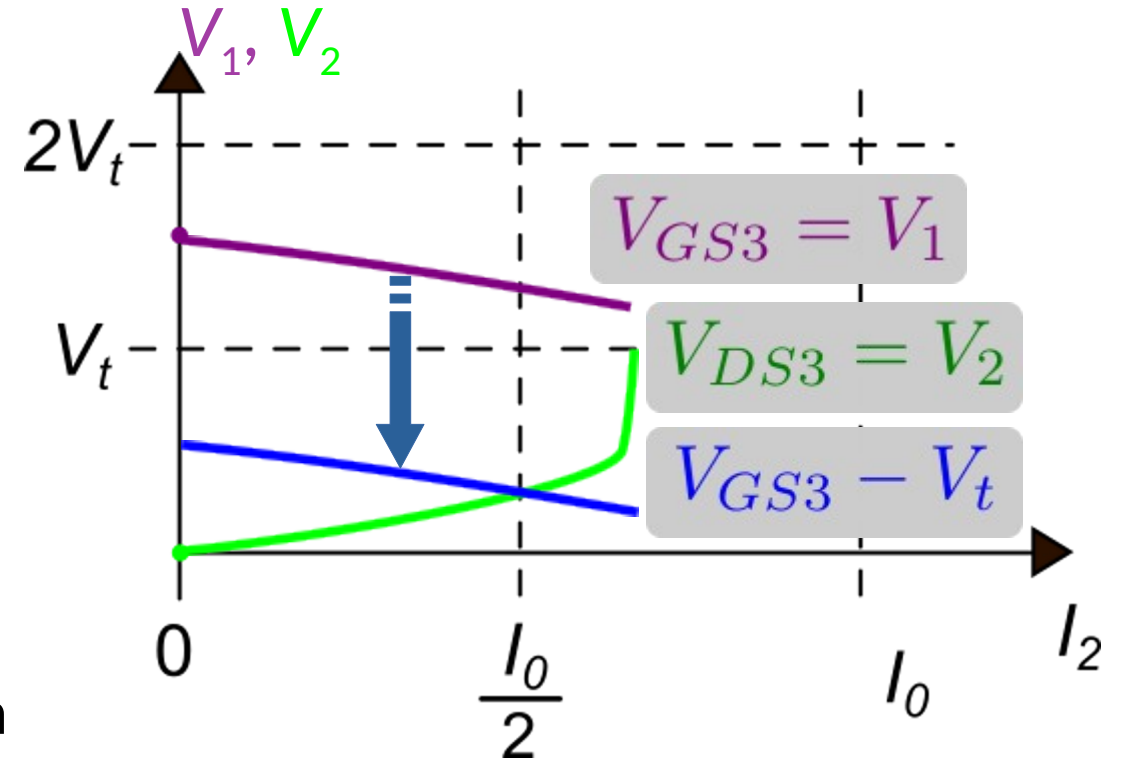 
# Analysis of the four-transistor cell: M3 saturation hypothesis



$$V_2 = V_t$$

Let us check whether M3 is now in saturation (was in triode region at the beginning)



$$V_{DS3} = V_2 = V_t$$

$$V_{GS3} = V_1 < \boxed{V_1(0) < 2V_t} \text{ For the design condition mentioned earlier}$$

$$\rightarrow V_{GS3} - V_t < V_t = V_{DS3}$$

$$\boxed{V_{DS3} > V_{GS3} - V_t \quad \checkmark \text{ OK}}$$
  
# Analysis of the four-transistor cell: $V_2$ reaches $V_t$




$$V_2 = V_t : \quad \frac{I_2}{I_1} = \frac{\beta_C}{\beta_L} \equiv r_H > 1$$

$$I_0 = I_1 + I_2 = (1 + r_H)I_1 = \frac{1 + r_H}{r_H} I_2$$




 
# Analysis of the four-transistor cell: combining the two behaviours





In this **region**, there are two possible stable states, depending on which extreme we started from:

This means that there is **hysteresis**

Now, we investigate what happens when the lower voltage hits the  $V_t$  line


  
# Positive feedback loop: small-signal analysis




$$A = \frac{V_{out}}{V_{in}} = -g_{mC} \left( \frac{1}{g_{mL}} // r_{dL} // r_{dC} \right)$$

$$A \cong -\frac{g_{mC}}{g_{mL}}$$


Due to the presence of the  $r_d$ 's, the magnitude of A is slightly less than

$$\frac{g_{mC}}{g_{mL}}$$

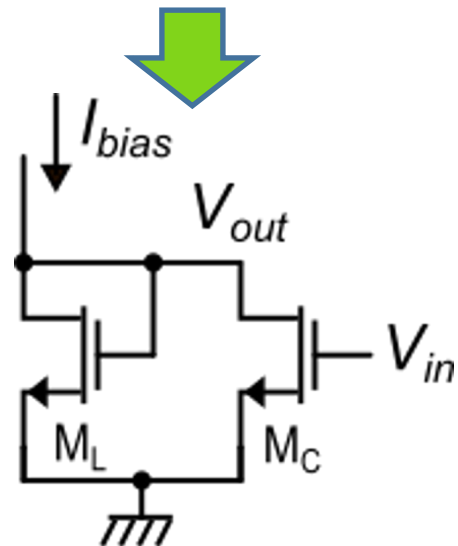Each half circuit is equivalent to an amplifier





Small signal equivalent circuit

 
  
## Positive feedback loop: small-signal analysis

When  $V_2$  overcomes  $V_t$ ,  
all MOSFETs are on:



$$A_1 = -\frac{g_{m2}}{g_{m1}}; \quad A_2 = -\frac{g_{m3}}{g_{m4}}$$

$$\beta A = A_1 A_2 > 0 \quad \text{Positive feedback}$$


$$g_{m1} = \beta_L (V_{GS1} - V_t), \quad g_{m2} = \beta_C (V_{GS2} - V_t)$$

$$g_{m3} = \beta_C (V_{GS3} - V_t), \quad g_{m4} = \beta_L (V_{GS4} - V_t)$$

$$V_{GS1} = V_{GS3} = V_1, \quad V_{GS2} = V_{GS4} = V_2$$

$$\beta A = \frac{\beta_C (V_2 - V_t)}{\beta_L (V_1 - V_t)} \cdot \frac{\beta_C (V_1 - V_t)}{\beta_L (V_2 - V_t)} = \left( \frac{\beta_C}{\beta_L} \right)^2$$

## Positive feedback loop: regeneration

 

$$\frac{\beta_C}{\beta_L} = r_H > 1 \Rightarrow |\beta A| > 1 \text{ (DC instability)}$$

Therefore, a stable condition cannot exist if all MOSFETs are on.

### Important condition

$V_1$  and  $V_2$  cannot be greater than  $V_t$  at same time in a stable condition  
Then, when M1 is on, M4 is off and *vice versa*


## Positive feedback loop: non-regenerative case (no hysteresis)

$$\frac{\beta_C}{\beta_L} = r_H < 1$$




$$|\beta A| = \left( \frac{\beta_C}{\beta_L} \right)^2 < 1$$

 In this case, the positive feedback is unable to cause an abrupt transition:  
Hysteresis is not present



**This configuration is never used  
(should be regarded as a design error)**

## Positive feedback loop: the “click”

 



Proceeding from the left, when  $V_2$  overcomes the  $V_t$  line, the positive feedback makes the voltage evolve autonomously

The new stable solution is the one we already found proceeding back from the right: the regeneration stops when loop gain is no longer  $> 1$
  
# Positive feedback loop: stable characteristics and unstable solution

Only one stable solution exists in these regions

Unstable solutions in this region (all devices are on) + 2 possible stable solutions (either M1, M3 off or M2, M4 off)




● Suppose forced initial condition:  
 ½ probability to evolve to one of the two stable solutions

○ Most probable evolution?

$I_2 > I_1$ :  
 $V_2$  up,  $V_1$  down


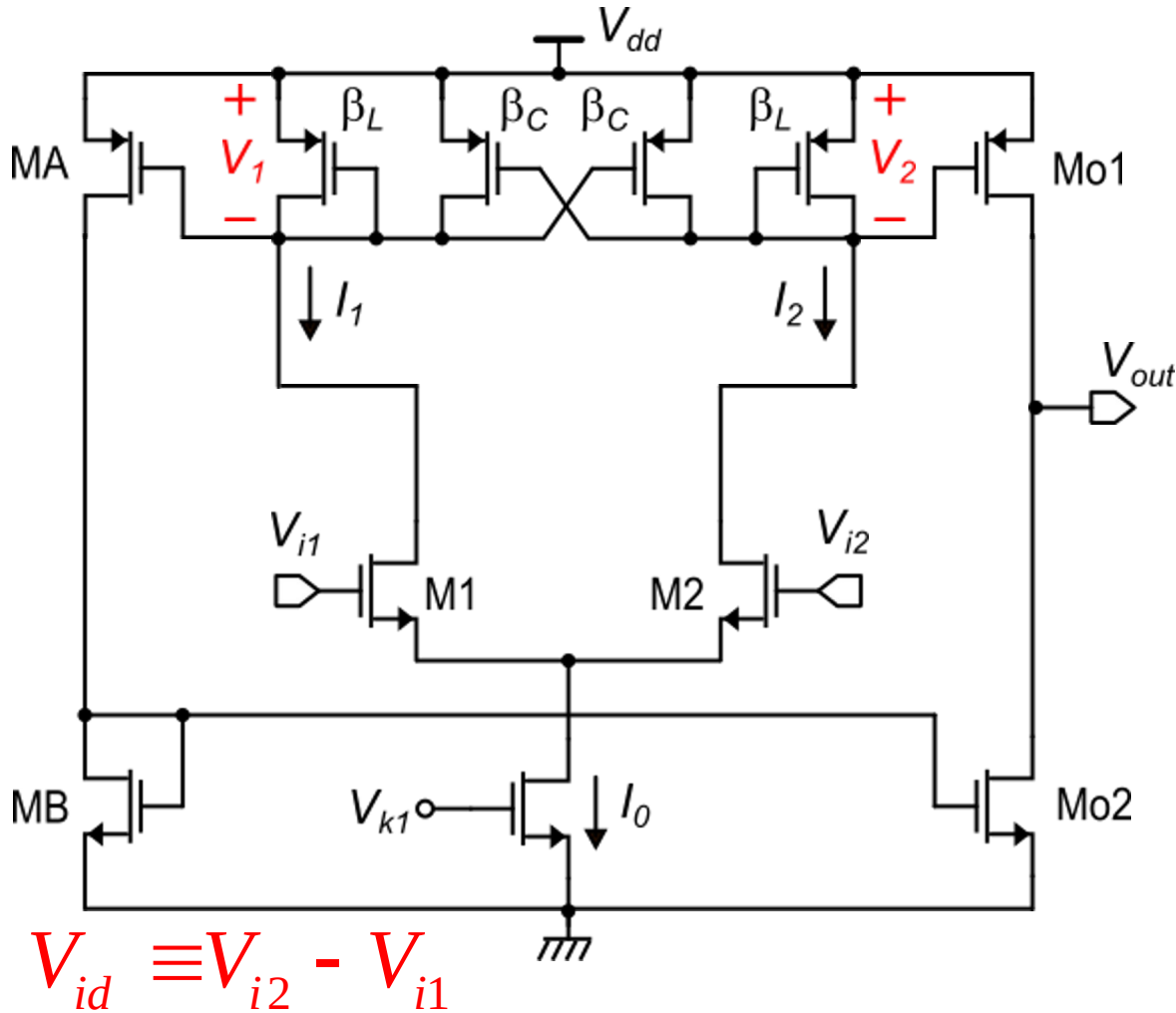
# A simple comparator based on the 4-transistor hysteresis cell



We start with a p-version of the hysteresis cell  
 Currents  $I_1$  and  $I_2$  are derived from the input voltage  $V_{id} = V_{i2} - V_{i1}$  by means of a differential pair



Only one at a time between  $V_1$  and  $V_2$  is greater than the p-mos threshold voltage.

If  $V_1 > |V_{tp}|$ ,  $V_2 < |V_{tp}|$  MA, MB and Mo2 are on, while Mo1 is off:  $V_{out} = 0$

If  $V_2 > |V_{tp}|$ ,  $V_1 < |V_{tp}|$ , only Mo1 is on:

$$\text{color: red; } V_{out} = V_{dd}$$
  
## A simple comparator: upper threshold ( $V_H$ )



Using a linear approximation of the differential pair:

$$\begin{cases} I_2 - I_1 = g_{m1} V_{id} \\ I_2 + I_1 = I_0 \end{cases}$$

## A simple comparator: upper threshold ( $V_H$ )



$$\left\{ \begin{array}{l} I_2 - I_1 = g_{m1} V_H \\ I_2 + I_1 = I_0 \\ \frac{I_2}{I_1} = r_H \end{array} \right. \begin{array}{l} \rightarrow I_2 - I_1 = I_1 (r_H - 1) = g_{m1} V_H \\ \rightarrow I_2 + I_1 = I_1 (r_H + 1) = I_0 \end{array} \quad \begin{array}{l} \text{Dividing the upper equation} \\ \text{by the lower one:} \\ \frac{r_H - 1}{r_H + 1} = \frac{g_{m1}}{I_0} V_H \end{array}$$

In quiescent conditions:  $I_0 = 2I_{D1-Q} = 2V_{TE1} g_{m1}$

$$\frac{r_H - 1}{r_H + 1} = \frac{1}{2V_{TE1}} V_H$$

$$V_H = 2V_{TE1} \frac{r_H - 1}{r_H + 1}$$
  
# A simple comparator: complete characteristics



$$\Delta V_H = V_H - V_L = 4V_{TE} \frac{r_H - 1}{r_H + 1}$$

In strong inversion:  $\Delta V_H = 2(V_{GS} - V_t) \frac{r_H - 1}{r_H + 1}$

## A simple comparator: minimum achievable hysteresis


$$\Delta V_H = V_H - V_L = 4V_{TE} \frac{r_H - 1}{r_H + 1}$$

### To obtain a small hysteresis

- Make  $V_{TE1}$  as small as possible
- Make  $r_H$  just slightly larger than 1

However, other requirements impose to make  $r_H$  significantly larger than 1, because:

- 1) The calculated  $|\beta A| = (r_H)^2$  is overestimated, since we have neglected the  $r_d$ 's
- 2) Process error can make  $r_H < 1$  if the margin to 1 is too small
- 3) The transition is faster with larger  $|\beta A|$

 



### A typical robust choice:

$$r_H = 2 \Rightarrow \Delta V_H = \frac{4}{3} V_{TE}$$

$\Delta V_H$  as small as **50 mV**
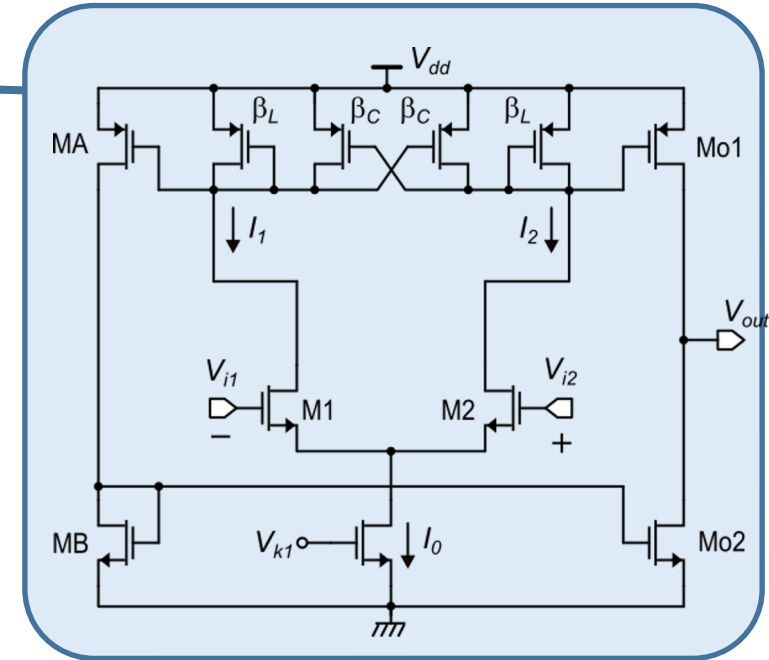 
# A simple comparator: low hysteresis using a preamplifier

The simplest solution is using a pre-amplifier:




$$V_{id}^* = \frac{V_{id}}{G} + v_{io} \quad V_H^* = \frac{V_H}{G} + v_{io}, \quad V_L^* = \frac{V_L}{G} + v_{io} \quad \Delta V_H^* = \frac{\Delta V_H}{G}$$

In discrete time systems the amplifier offset can be canceled with CDS


The hysteresis is divided by the preamplifier gain ( $G$ )
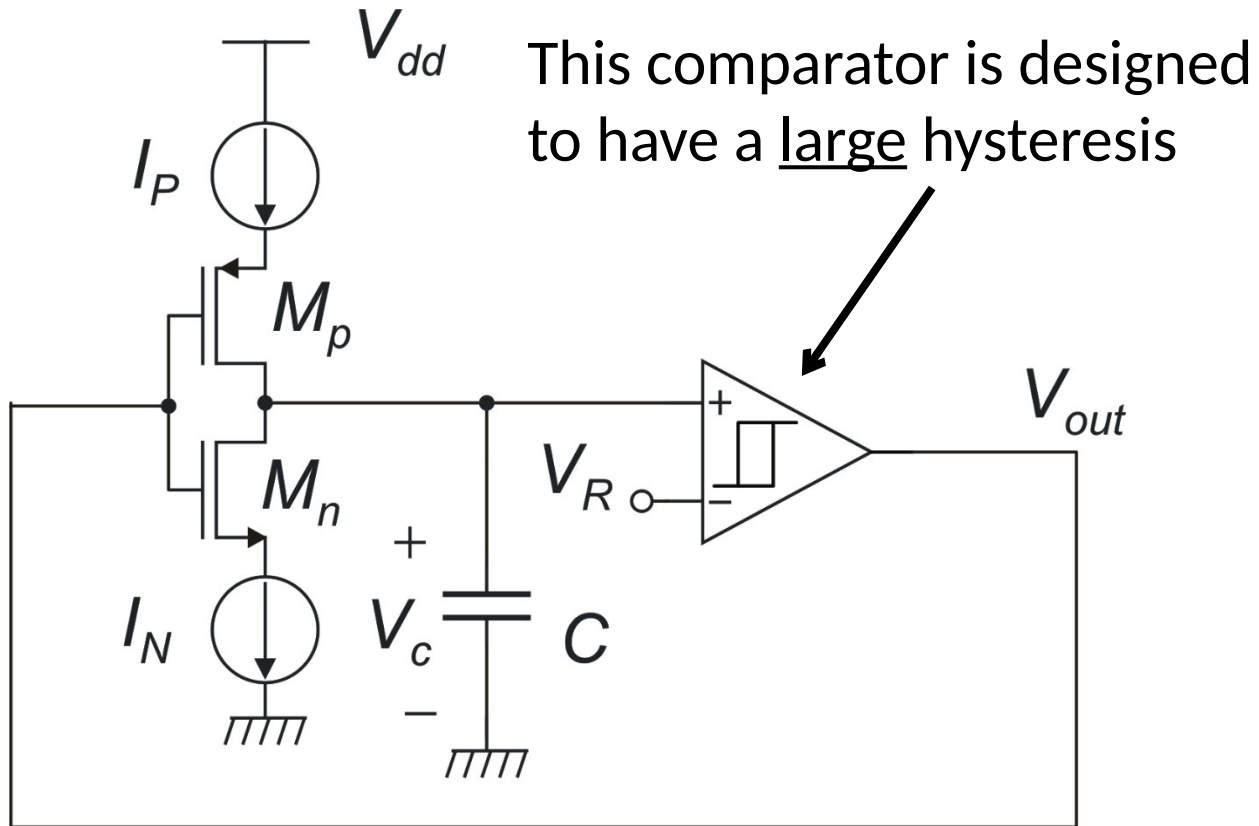
# A simple VCO for low-frequency applications



First step: place the comparator in a feedback loop with a current-controlled charging-discharging mechanism



 - When  $V_{out}=0$ , the capacitor is charged by  $I_P$
- When  $V_{out}=1$ , the capacitor is discharged by  $I_N$


  
# A simple low-frequency VCO: oscillator frequency



$$\text{rise time} = T_R = \frac{\Delta V_H}{I_P / C} = C \frac{\Delta V_H}{I_P}$$


$$\text{fall time} = T_F = \frac{\Delta V_H}{I_N / C} = C \frac{\Delta V_H}{I_N}$$

$$\text{period} = T = T_R + T_F = C \Delta V_H \left( \frac{1}{I_P} + \frac{1}{I_N} \right)$$





## A simple voltage-to-current converter

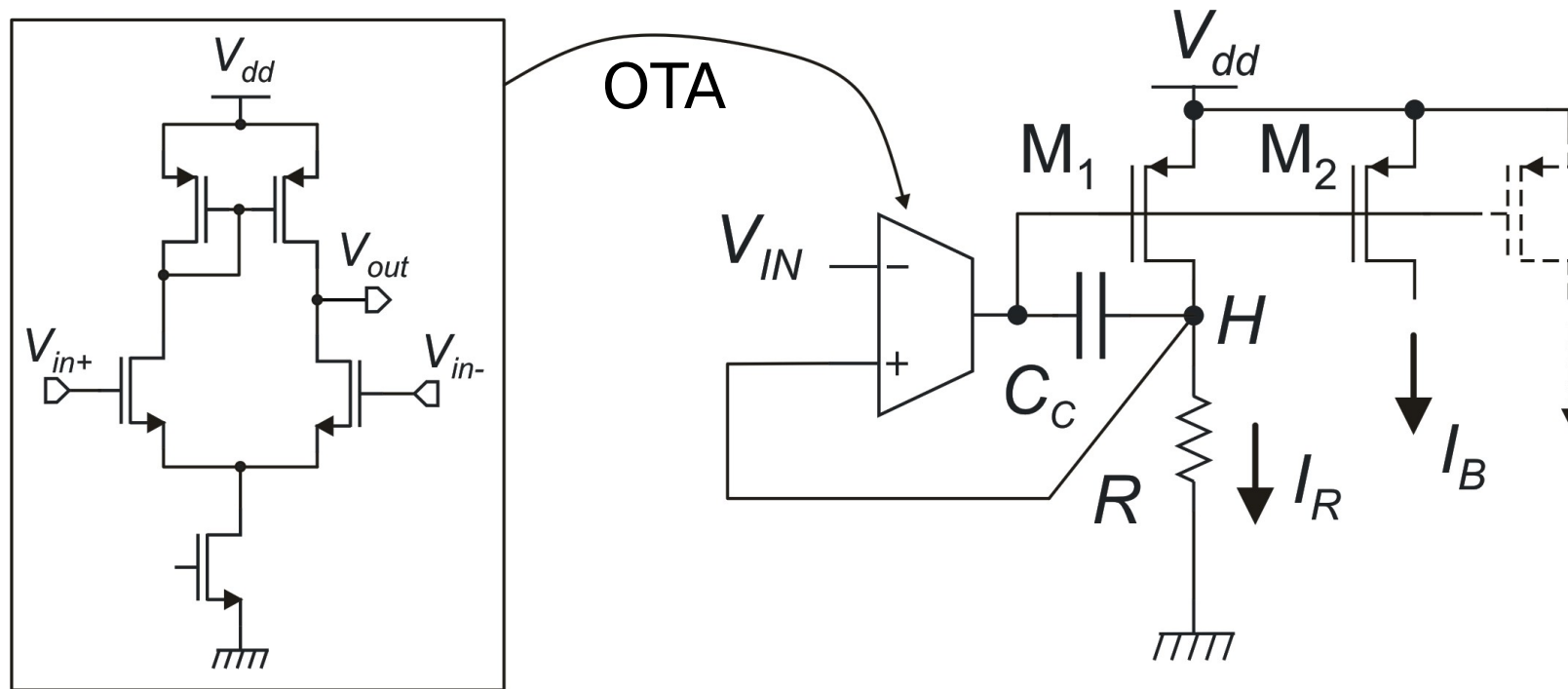


This circuit can be used also to produce constant currents from a single reference voltage

The OTA, and M1 form a two-stage op-amp with output on node H, stabilized by  $C_C$  (Miller compensation).



The op-amp is closed as a buffer:  $V_H = V_{IN} \Rightarrow I_R = I_{D1} = \frac{V_{in}}{R} \Rightarrow I_B = \frac{\beta_2}{\beta_1} I_{D1} = \frac{\beta_2}{\beta_1} \frac{V_{IN}}{R}$
 
## Speed and metastability issues

**Metastability:** the comparator does not provide a clear logical output level in a given amount of time




  Small signal equivalent circuit of half cell: + **inertial component (C)**



$R_V$ : negative signed for regenerative positive feedback

## Speed and metastability issues

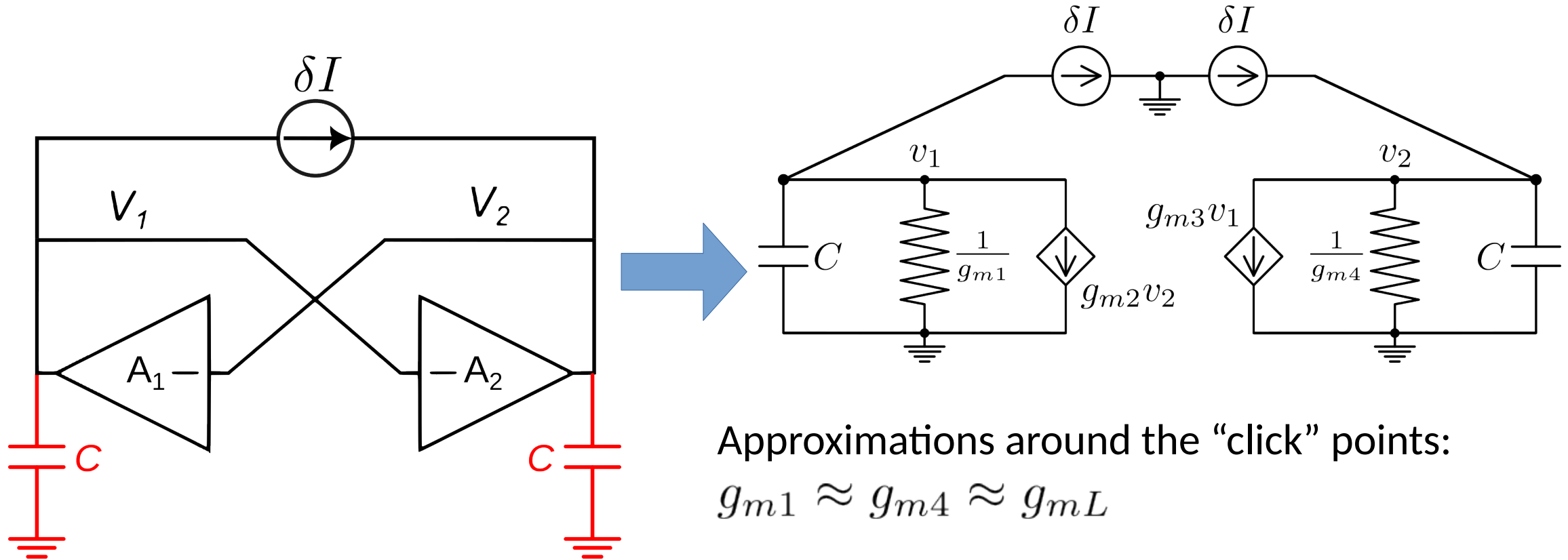

Approximations around the “click” points:



$$g_{m1} \approx g_{m4} \approx g_{mL}$$

$$g_{m2} \approx g_{m3} \approx g_{mC}$$

Not rigorous but useful for understanding purposes:  
the circuit is non-linear anyway.

Accurate results only through electrical simulations


# Speed and metastability issues

 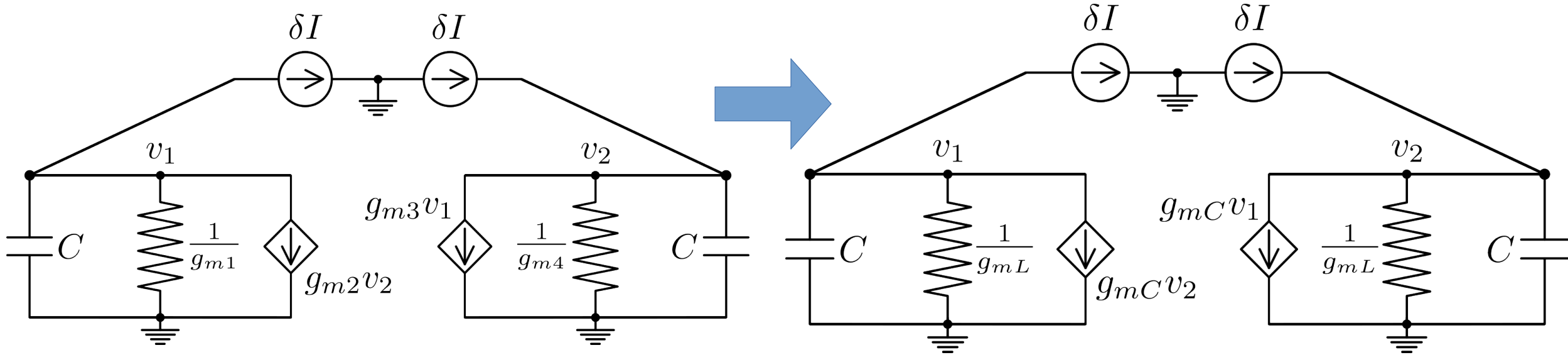

Under this approximation, the circuit is completely symmetric:  
 $v_1 \approx -v_2$

We can study only half circuit, for simplicity

## Speed and metastability issues

 

Transient response characterized by growing exponential response:  $e^{at}$

$$a = \frac{1}{|R_V|C} = \frac{g_{mL}}{C} \left| 1 - \frac{g_{mC}}{g_{mL}} \right| \approx \frac{g_{mL}}{C} |1 - \sqrt{\beta A}|$$

Hence, the higher  $\beta A$ , the faster is the response (as mentioned previously).

Designing low-hysteresis comparator by pushing  $\beta A$  close to 1 is a **BAD IDEA**: not only process sensitivity may lead to lack of hysteresis, but also the comparator would result very slow:

The pre-amp solution with is always used in such cases

# Syllabus

## Design of integrated comparators

### **Done (today's class):**

- 1) Ideal behaviour
- 2) Applications
- 3) Taxonomy
- 4) The 4T-hysteretic cell for SoC
- 5) Simple comparator based on the 4T-hysteretic cell
- 6) Low-frequency relaxation oscillator based on simple VCO
- 7) Notes on speed and metastability (*optional material*)

### **To do (next class):**

- 8) Dynamic comparator example: the StrongARM case
- 9) Other comparator structures from literature (*optional material*)