

# StrongARM: insights from literature

Analysis inspired by “The StrongARM Latch” paper from Prof. B. Razavi

DOI: 10.1109/MSSC.2015.2418155

---



*Behzad Razavi*


***A CIRCUIT FOR ALL SEASONS***

SPRING 2015

***IEEE SOLID-STATE CIRCUITS MAGAZINE***


## The StrongARM Latch
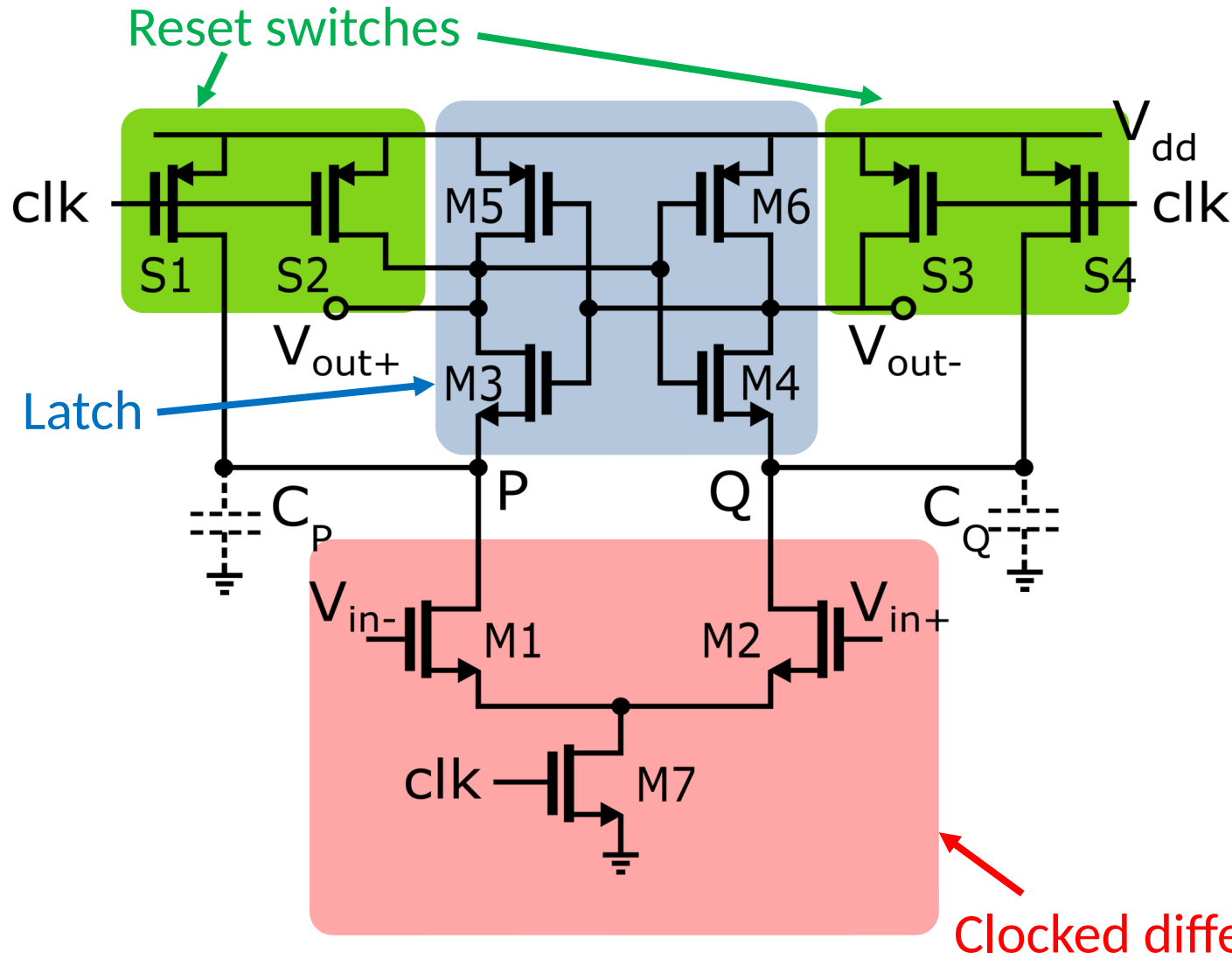
## Dynamic comparator: StrongARM structure



- First proposed as Sense Amplifier for SRAM (used in StrongARM microprocessor, in the '90s)
- No static-power consumption
- Rail-to-rail outputs
- Compares  $V_{id} = V_{in}^+ - V_{in}^-$  on the **rising edge** of the clock signal
- Output valid when  $clk=1$ . During  $clk=0$ , both  $V_{out+}$ ,  $V_{out-}$  are at  $V_{dd}$

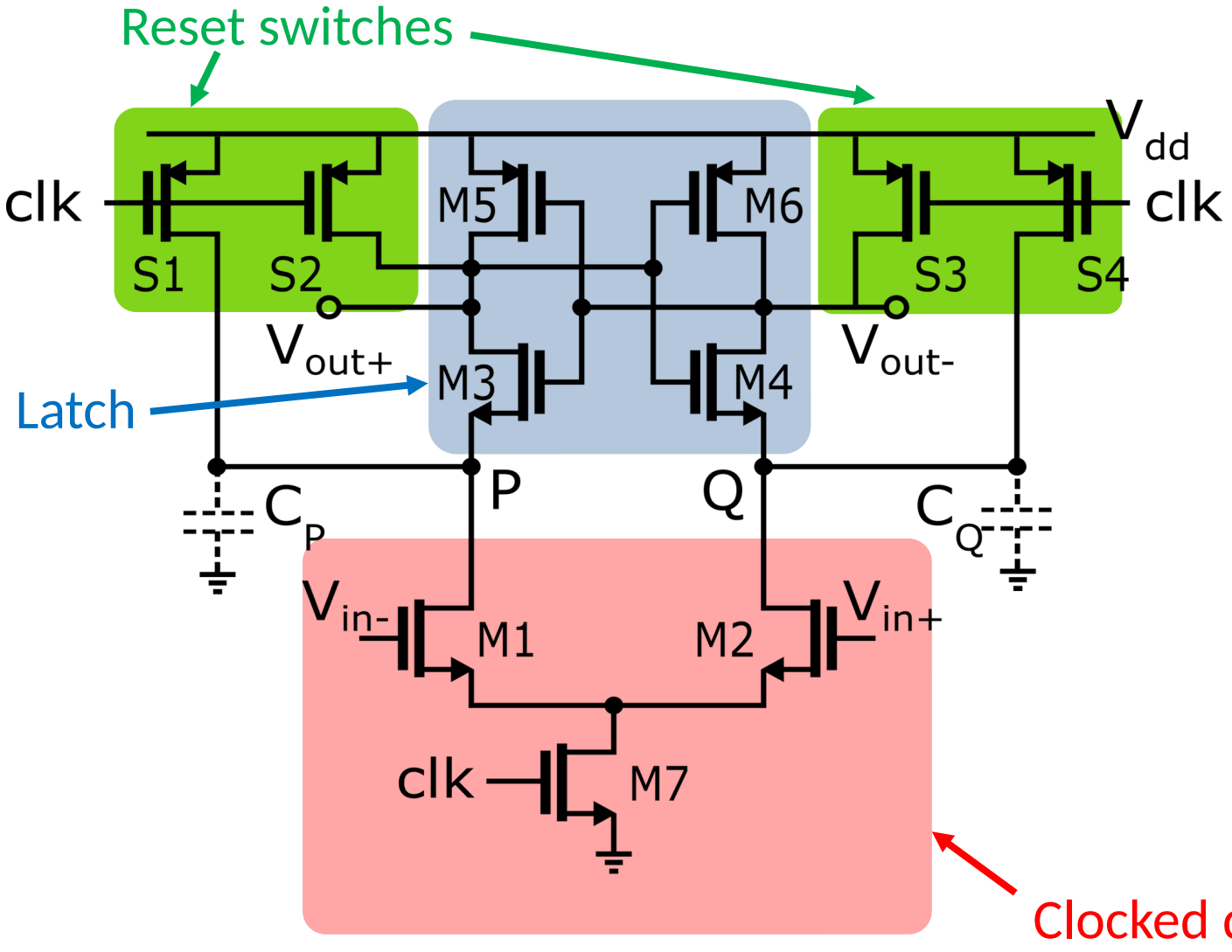
# Dynamic comparator: StrongARM structure



- **Zero input-referred hysteresis:** at each reset phase, the comparator loses 'memory' of the previous cycle state.
- Nevertheless: the comparator will evolve to a full logical state. (Latch: level regeneration)
- Operation in 3 phases: (i) **Reset**, (ii) **Amplification**, (iii) **Regeneration**


Clocked differential pair

## StrongARM: Reset Phase

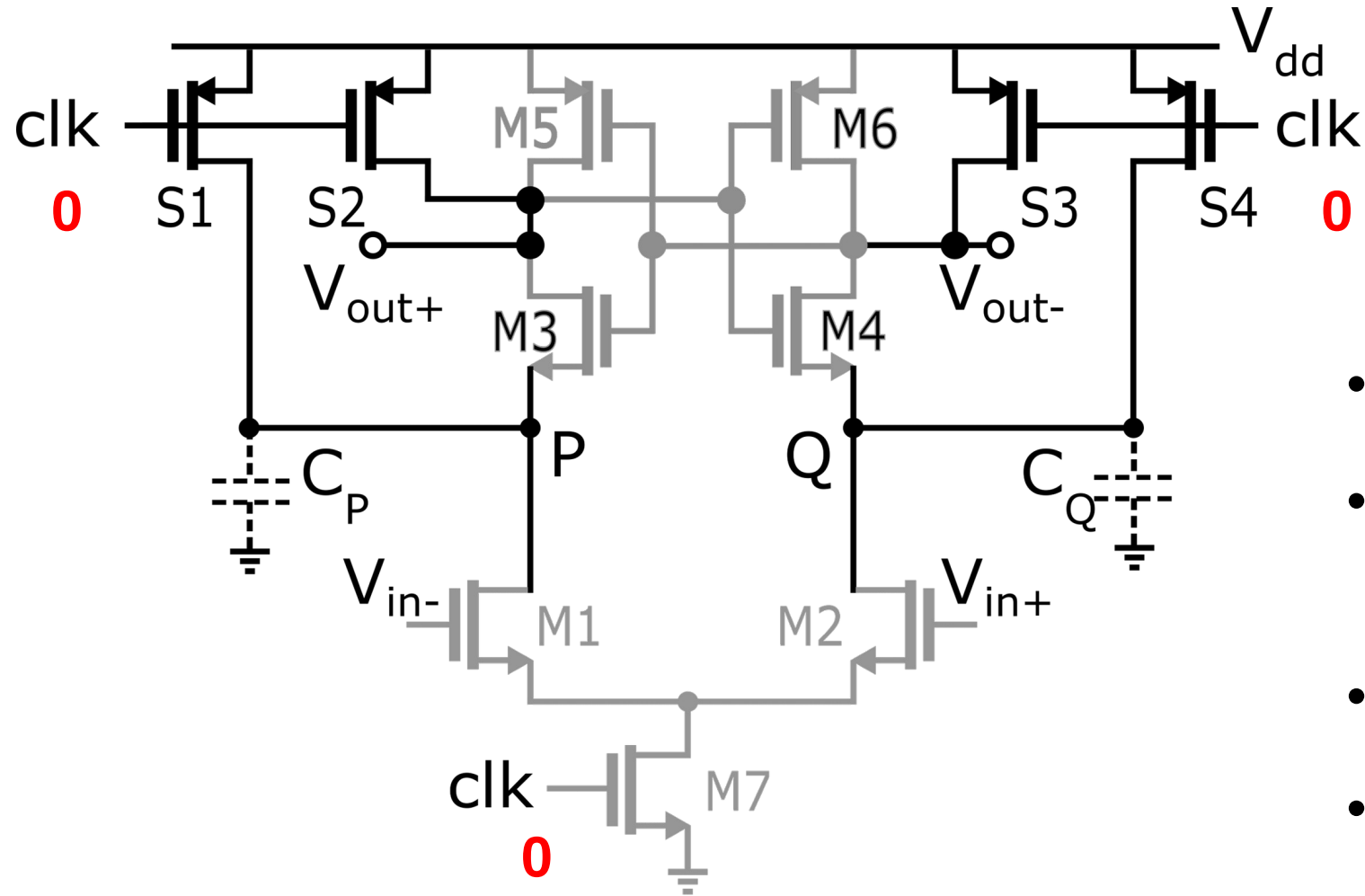


- The input pair devices are off
- Nodes P, Q,  $V_{out+}$ ,  $V_{out-}$  are connected to  $V_{dd}$  through S1-S4
- Latch is inactive
- Parassitic  $C_P$  and  $C_Q$  are precharged to  $V_{dd}$

## StrongARM: Amplification Phase

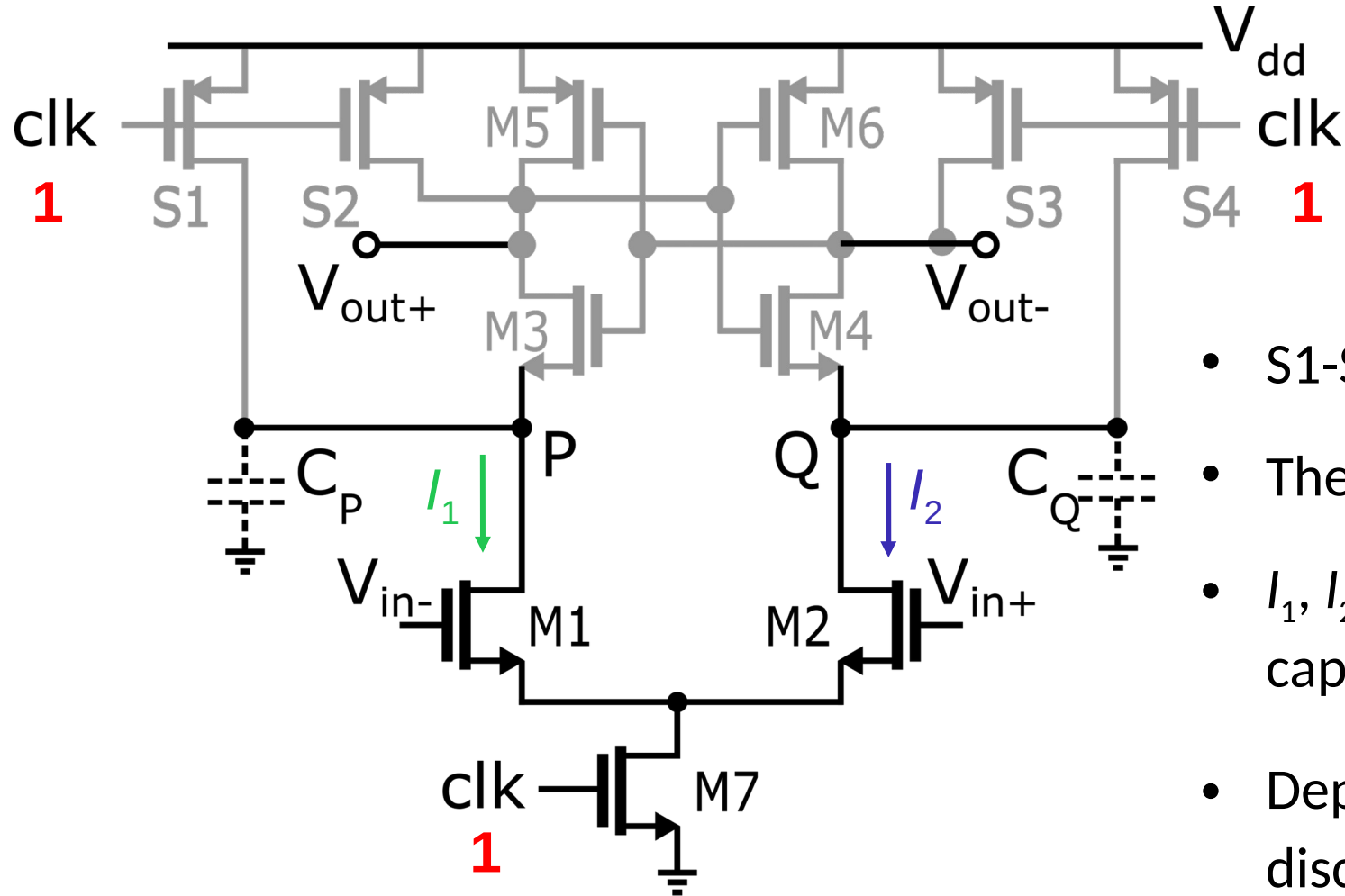

- S1-S4 go off, M7 goes on
- The input pair is on
- $I_1, I_2$  start discharging the parasitic capacitances  $C_p, C_q$  at nodes P, Q
- Depending on  $V_{id} = V_{in+} - V_{in-}$  node P is discharged faster/slower than node Q

# StrongARM: Amplification Phase


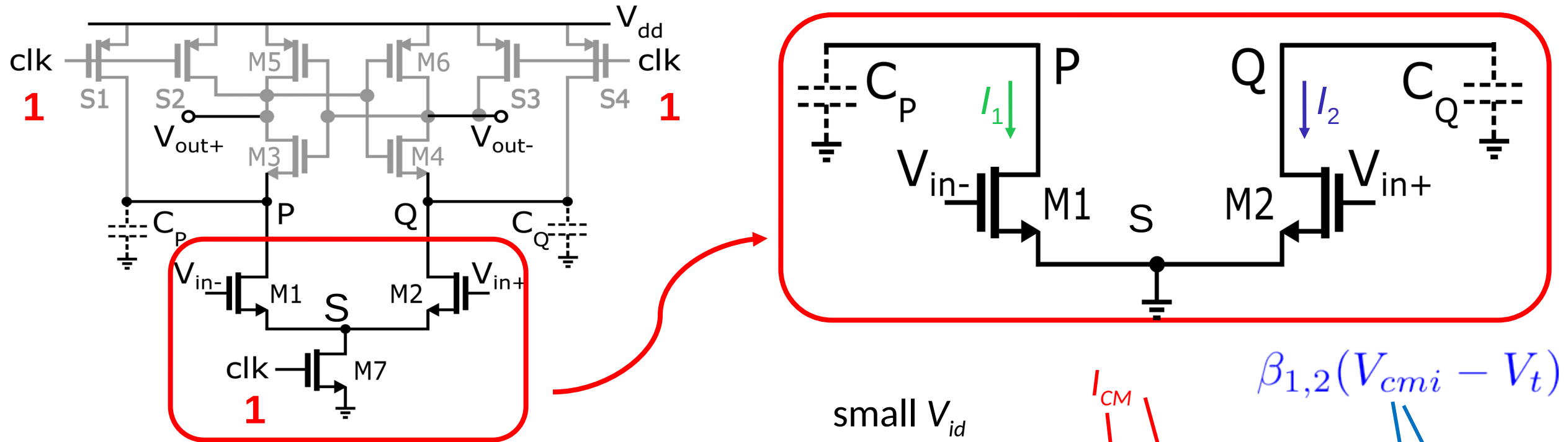


Pseudo-differential pair  
(when  $clk=1$ , M7  
connects node S to gnd)

$$\begin{cases}
 I_1 = \frac{\beta_{1,2}}{2} (V_{in}^+ - V_t)^2 \approx \frac{\beta_{1,2}}{2} (V_{cmi} - V_t)^2 - g_{m1} \frac{V_{id}}{2} \\
 I_2 = \frac{\beta_{1,2}}{2} (V_{in}^- - V_t)^2 \approx \frac{\beta_{1,2}}{2} (V_{cmi} - V_t)^2 + g_{m1} \frac{V_{id}}{2}
 \end{cases}$$


$V_{id}$   
 $I_{CM}$   
 $\beta_{1,2}(V_{cmi} - V_t)$

# StrongARM: Amplification Phase

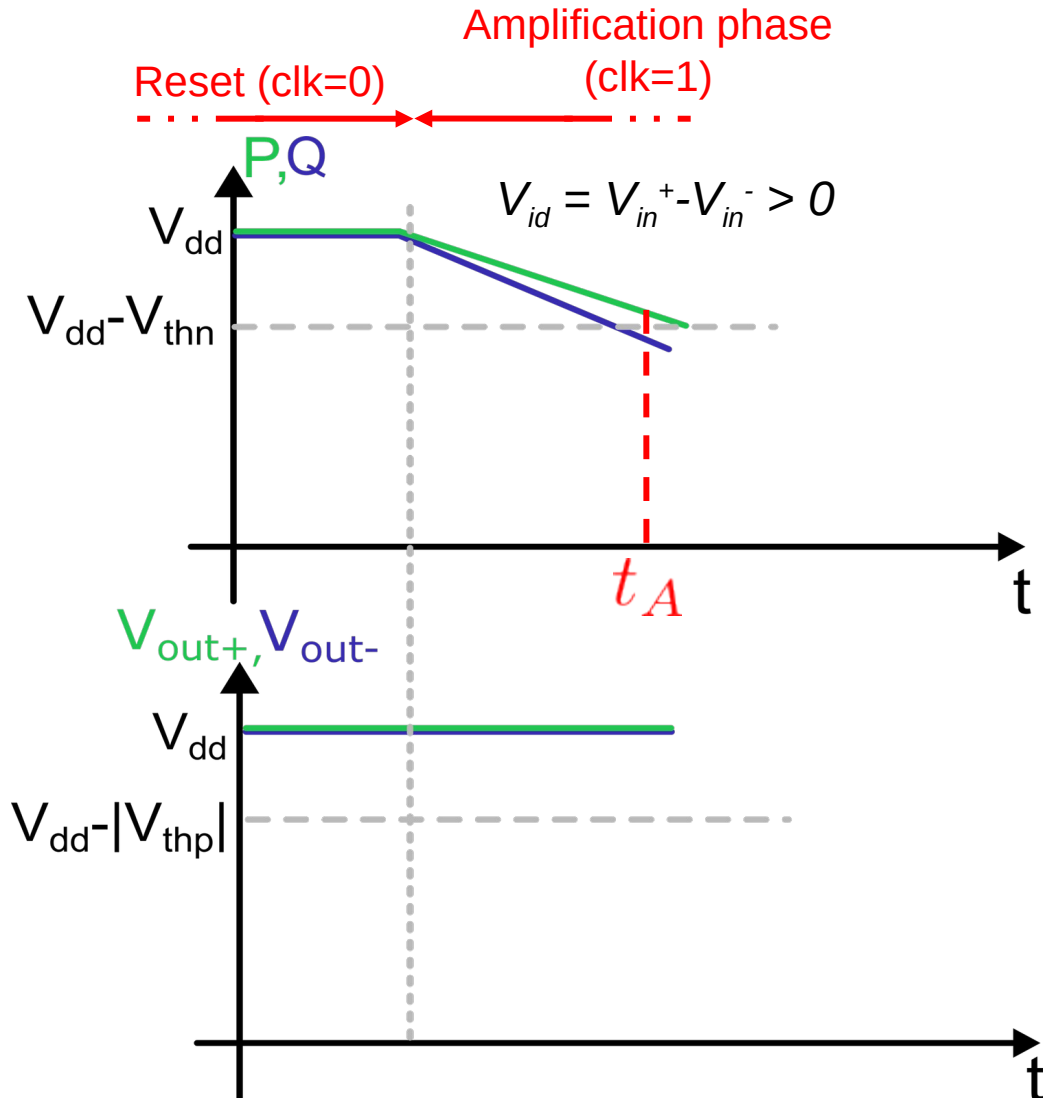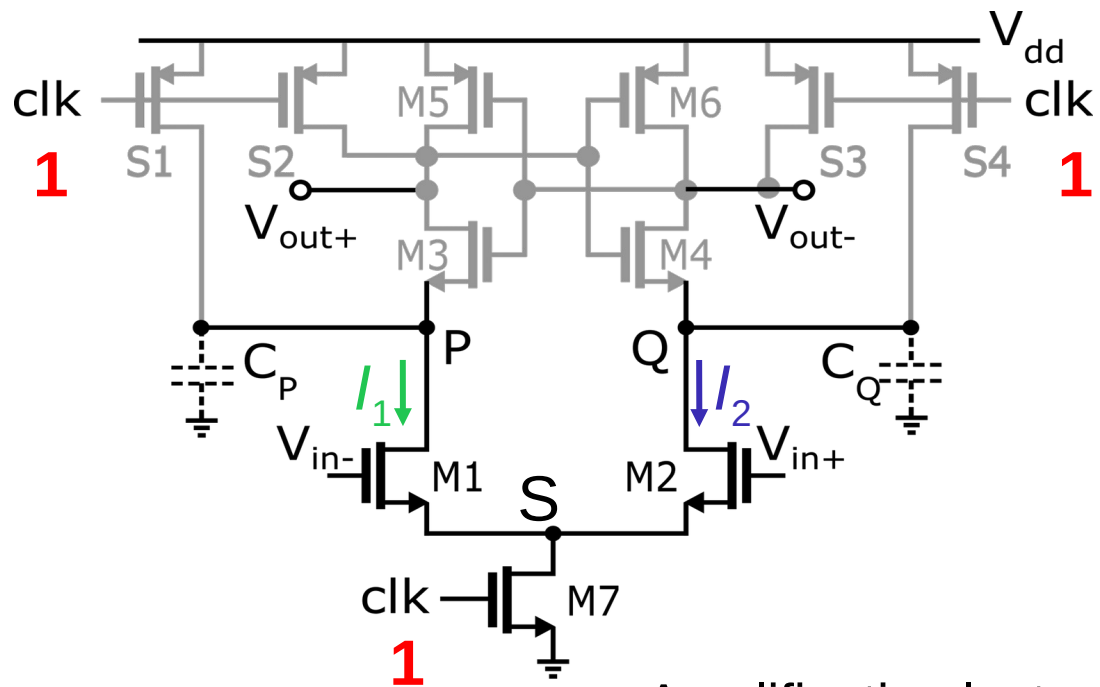

Amplification lasts approximately until  $(V_P + V_Q)/2$  reaches  $V_{dd} - V_{thn}$
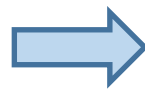
$$\begin{cases} \frac{dV_P}{dt} = -\frac{I_1}{C_P} \\ \frac{dV_Q}{dt} = -\frac{I_2}{C_P} \end{cases}$$



$$t_A \approx \frac{C_{P,Q} V_{thn}}{I_{CM}}$$

# StrongARM: Amplification Phase

$$t_A \approx \frac{C_{P,Q} V_{thn}}{I_{CM}}$$

$t_A$  is also dependent on input common mode, slower for lower  $V_{cmi}$

gain A

$$V_P - V_Q = \frac{g_{m1}}{C_{P,Q}} t_A V_{id}$$

Gain A is not precise, and it is dependent on input common mode:


$$A = g_{m1} \cdot \frac{t_A}{C_{P,Q}} = \frac{2I_{CM}}{V_{cmi} - V_t} \cdot \frac{V_{thn}}{I_{CM}} = \frac{2V_{thn}}{V_{cmi} - V_t}$$

**Is the condition  $A > 1$  always guaranteed?**

Numerical example:  $V_{cmi} = 1.7$  V,  $V_t = 0.5$  V (input pair)


$V_{thn} = 0.6$  V (cross coupled NMOS, beneficial body effect)

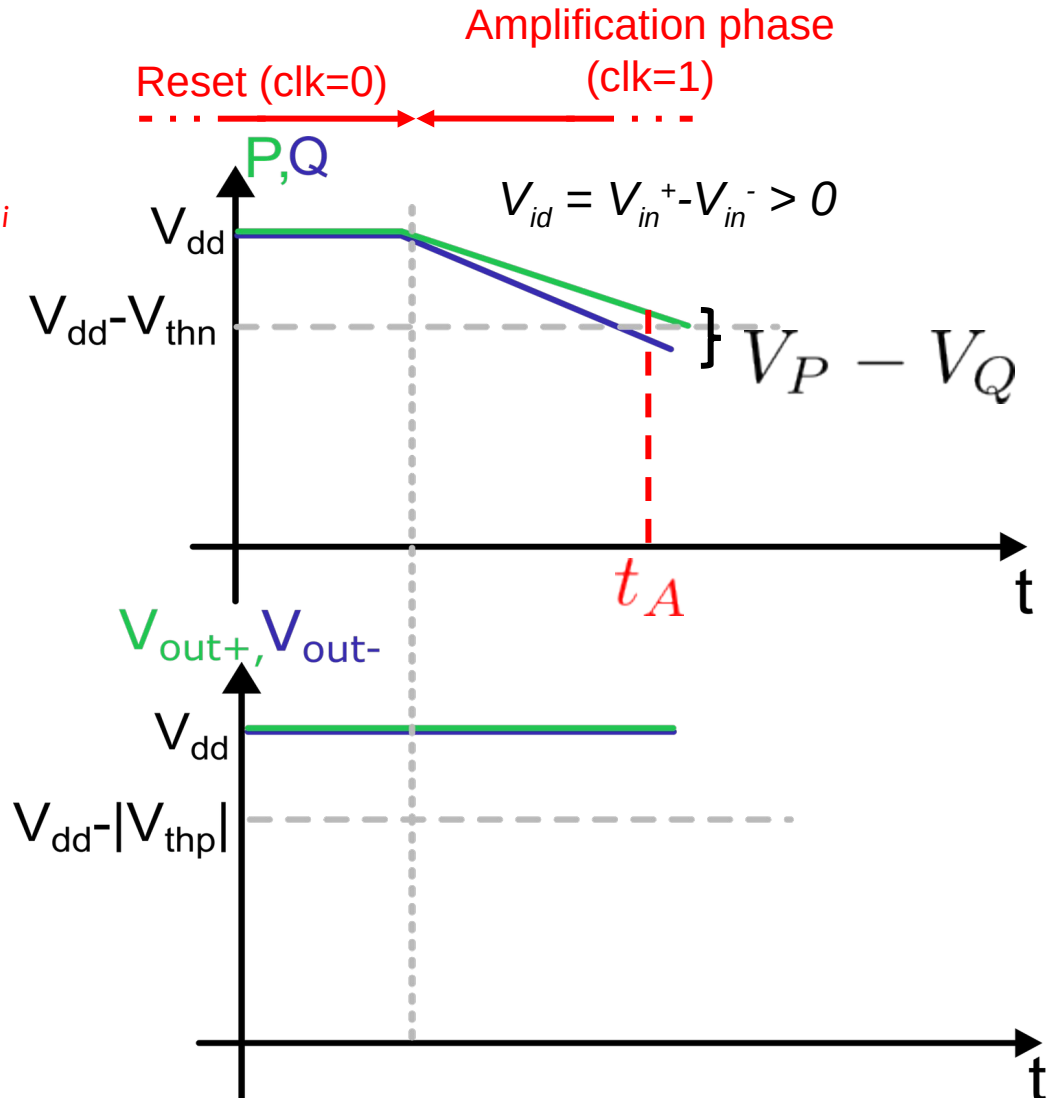→  $A = 1$ . For  $V_{cmi} > 1.7$  V, there is no amplification!




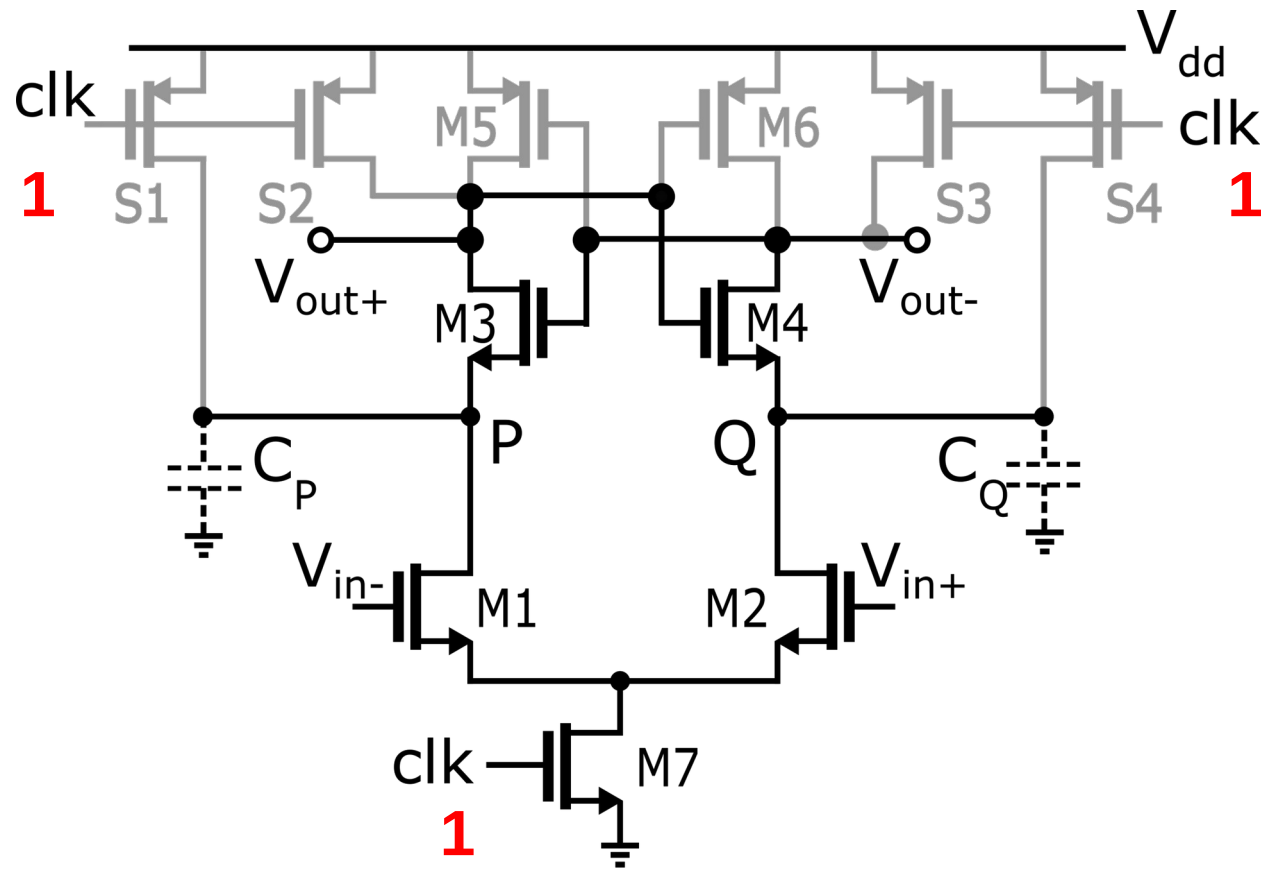
## StrongARM: Amplification Phase, continued




- When voltages at nodes P,Q go lower than  $V_{dd} - V_{thn}$ , M3-M4 turn on
- Once on, M3-M4 can be regarded as batteries ( $\sim V_{thn}$ ):

$$\begin{cases} V_{out}^+ \approx V_Q + V_{thn} \\ V_{out}^- \approx V_P + V_{thn} \end{cases}$$

- Nodes P,Q keep discharging and  $V_{out+}$ ,  $V_{out-}$  start discharging differently according to the unbalance of P and Q

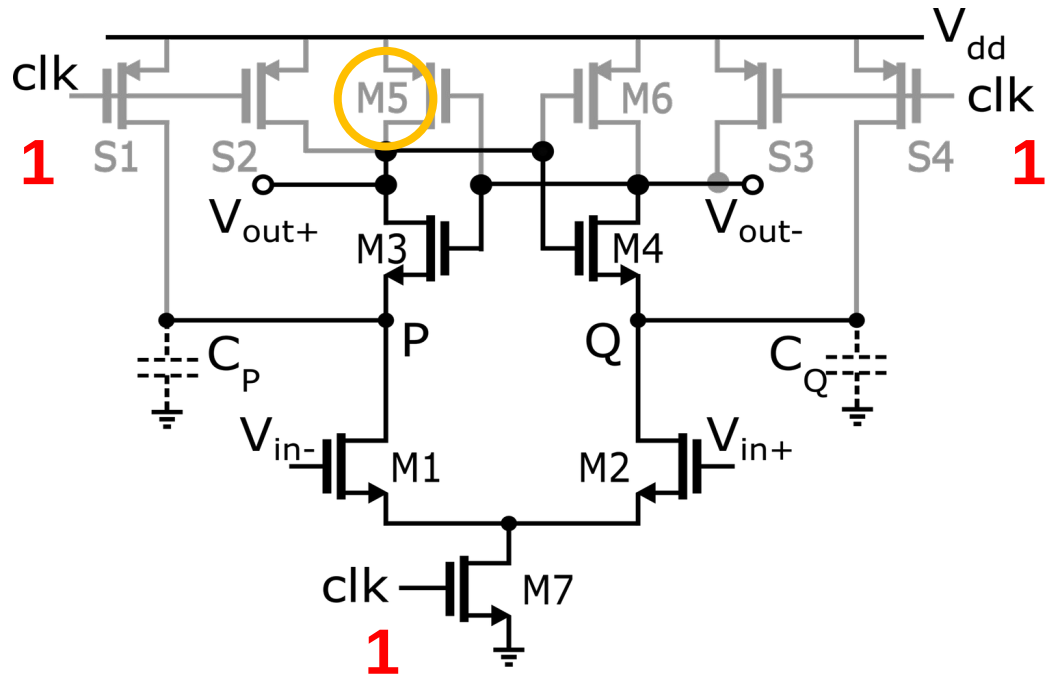
# StrongARM: Amplification Phase, continued




$$V_{id} = V_{in}^+ - V_{in}^- > 0$$

$$V_P - V_Q = AV_{id} > 0$$
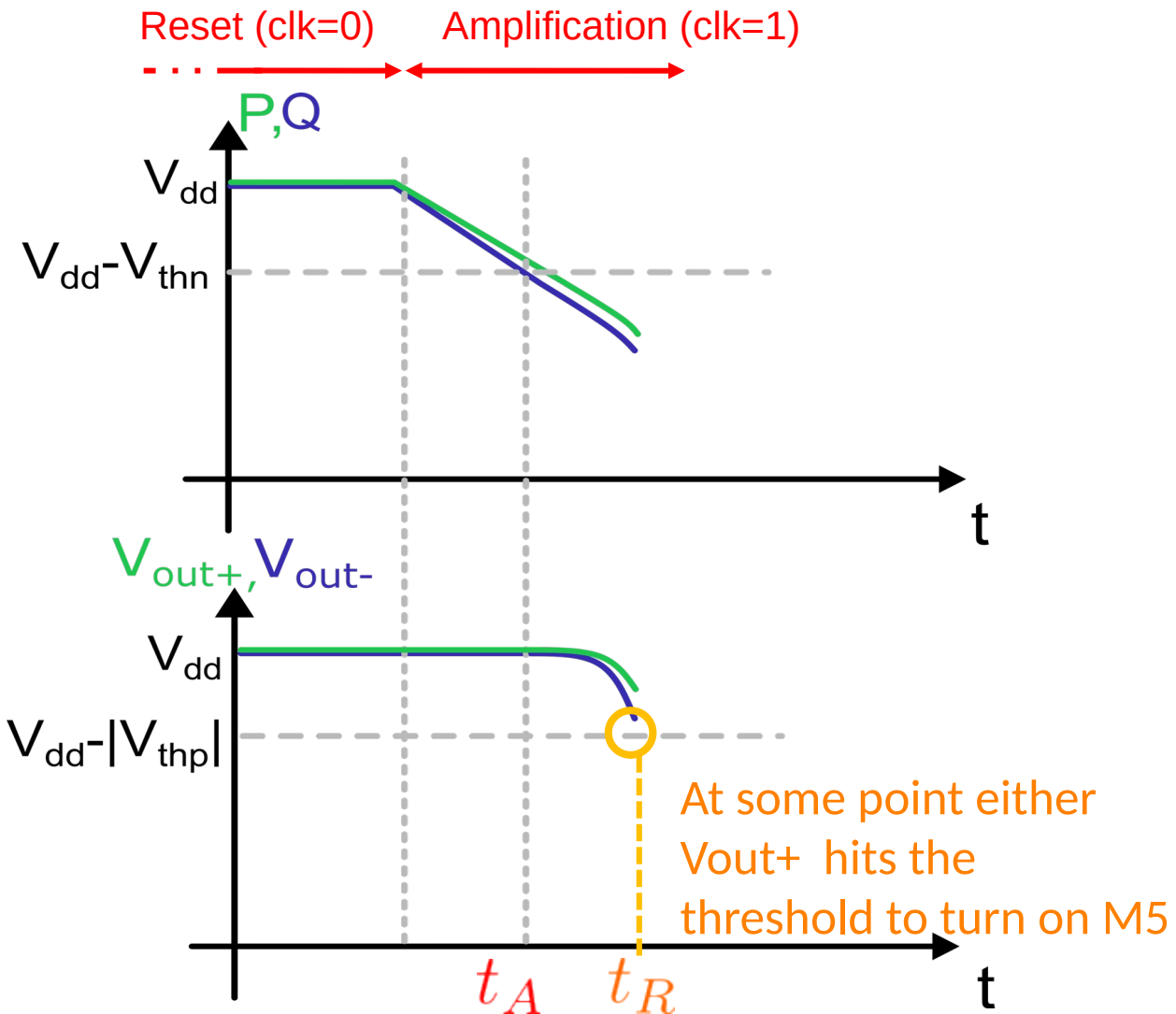
$$V_{out}^+ - V_{out}^- \approx AV_{id} > 0$$



# StrongARM: Regeneration Phase

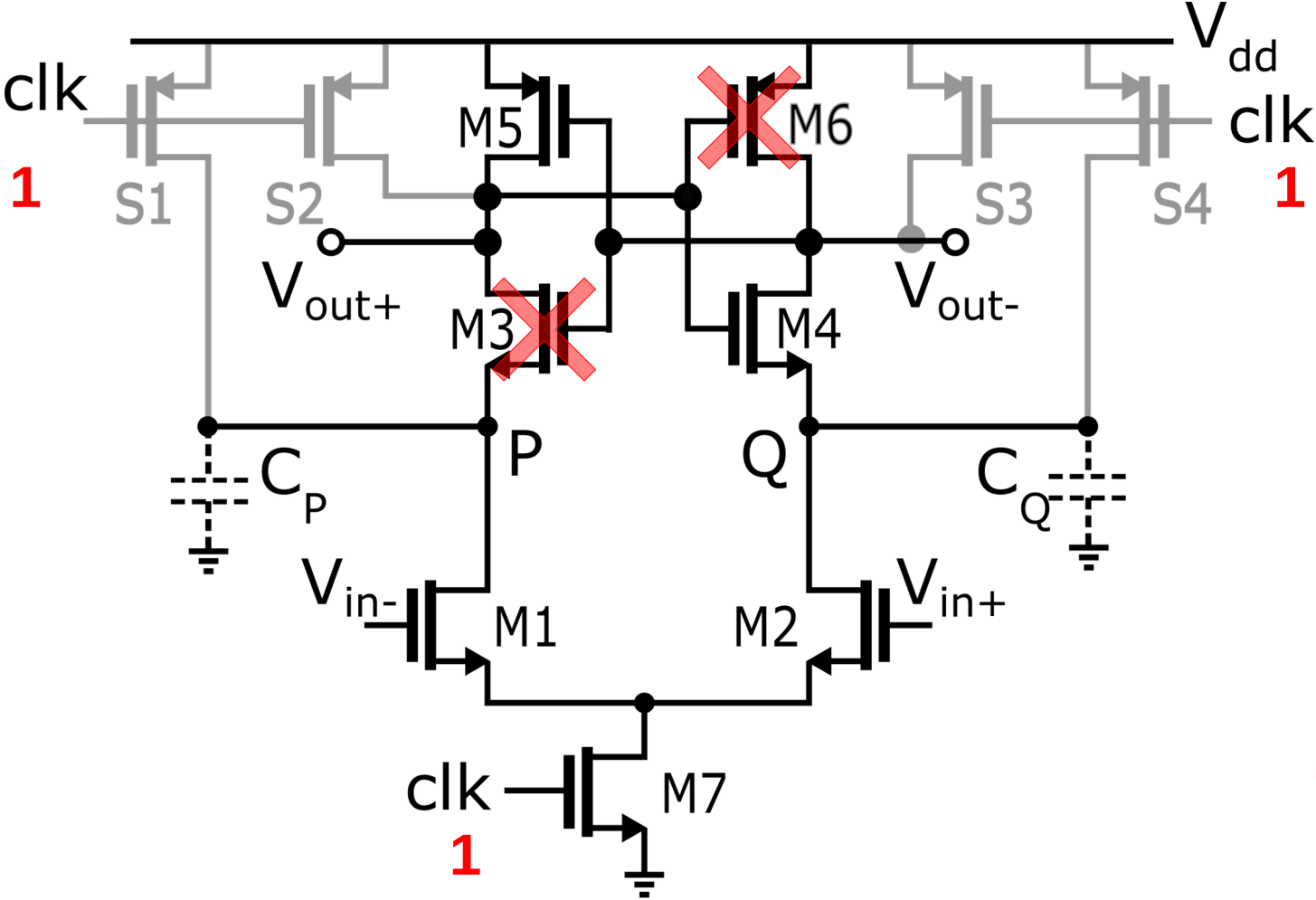


- When  $V_{out}^+$  or  $V_{out}^-$  goes lower than  $V_{dd} - |V_{thp}|$ , one between M5 and M6 turns on:

- 1) If  $V_{out-}$  hits first, M5 turns on, and  $V_{out+}$  is pulled towards  $V_{dd}$  (M6 is off)
- 2) M4 is more "conductive" allowing  $V_{out-}$  to lower. M2 eventually enters linear region.
- 3) M3 progressively turns off due to lowering  $V_{out-}$ . Hence it cuts the M5-M3 DC path


**Positive feedback loop (regenerative)**

# StrongARM: Regeneration Phase


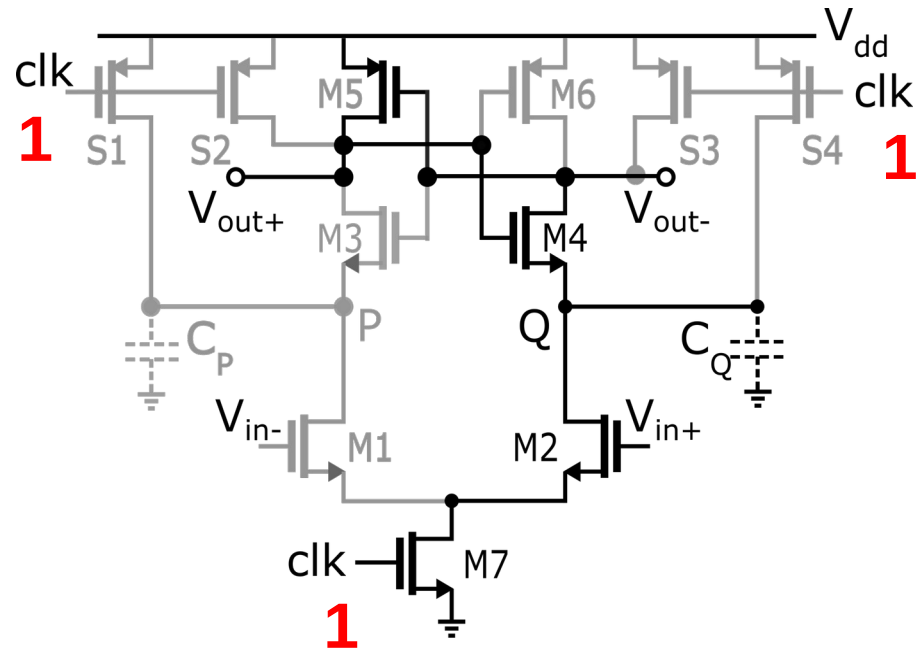


Regeneration Phase:  $V_{out-}$  is allowed to reach gnd

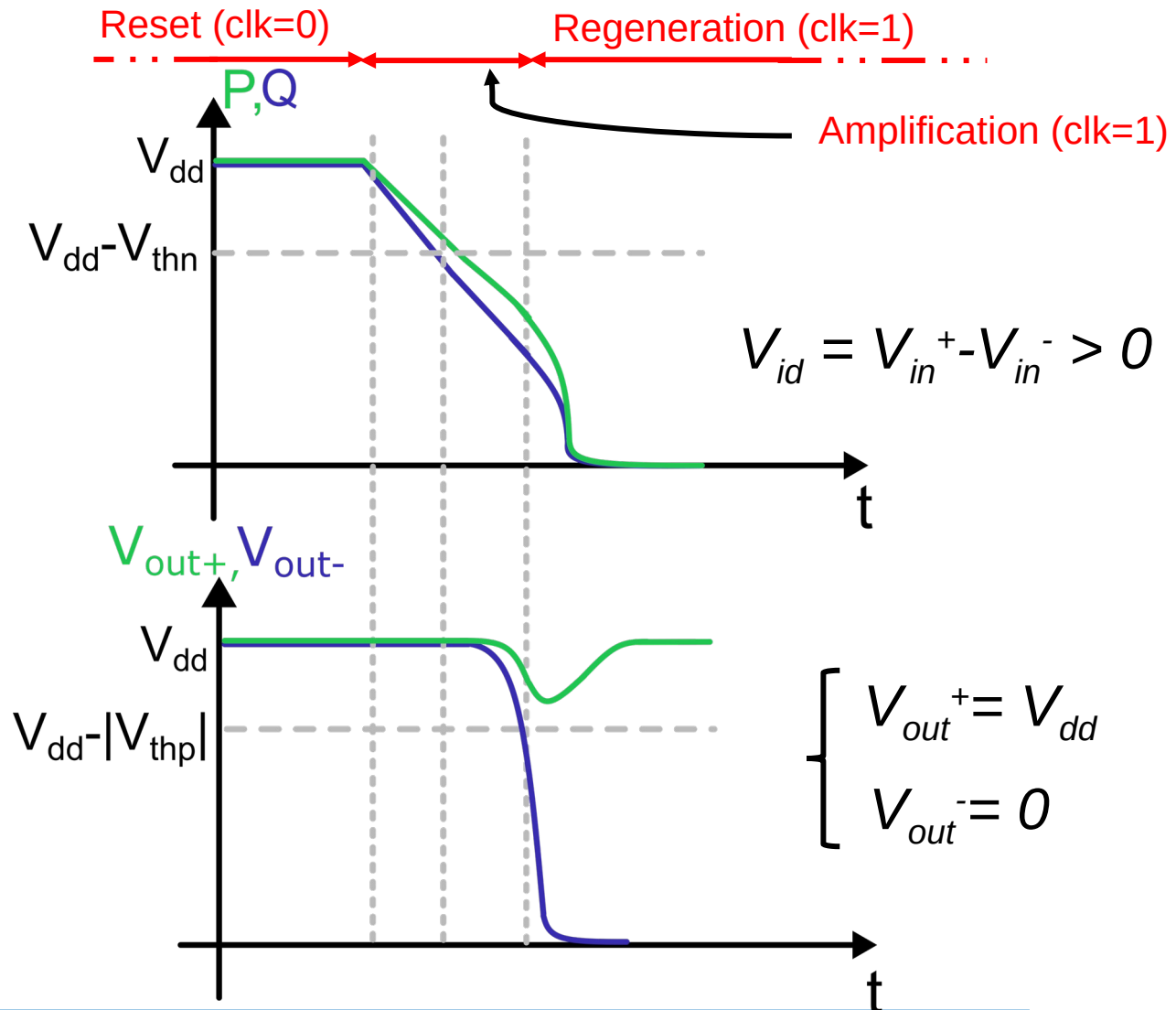Once the regeneration is finished, **no static power consumption** is present  
(M3 cuts off the current path from  $V_{dd}$  to ground)




## StrongARM: (Next) Reset Phase

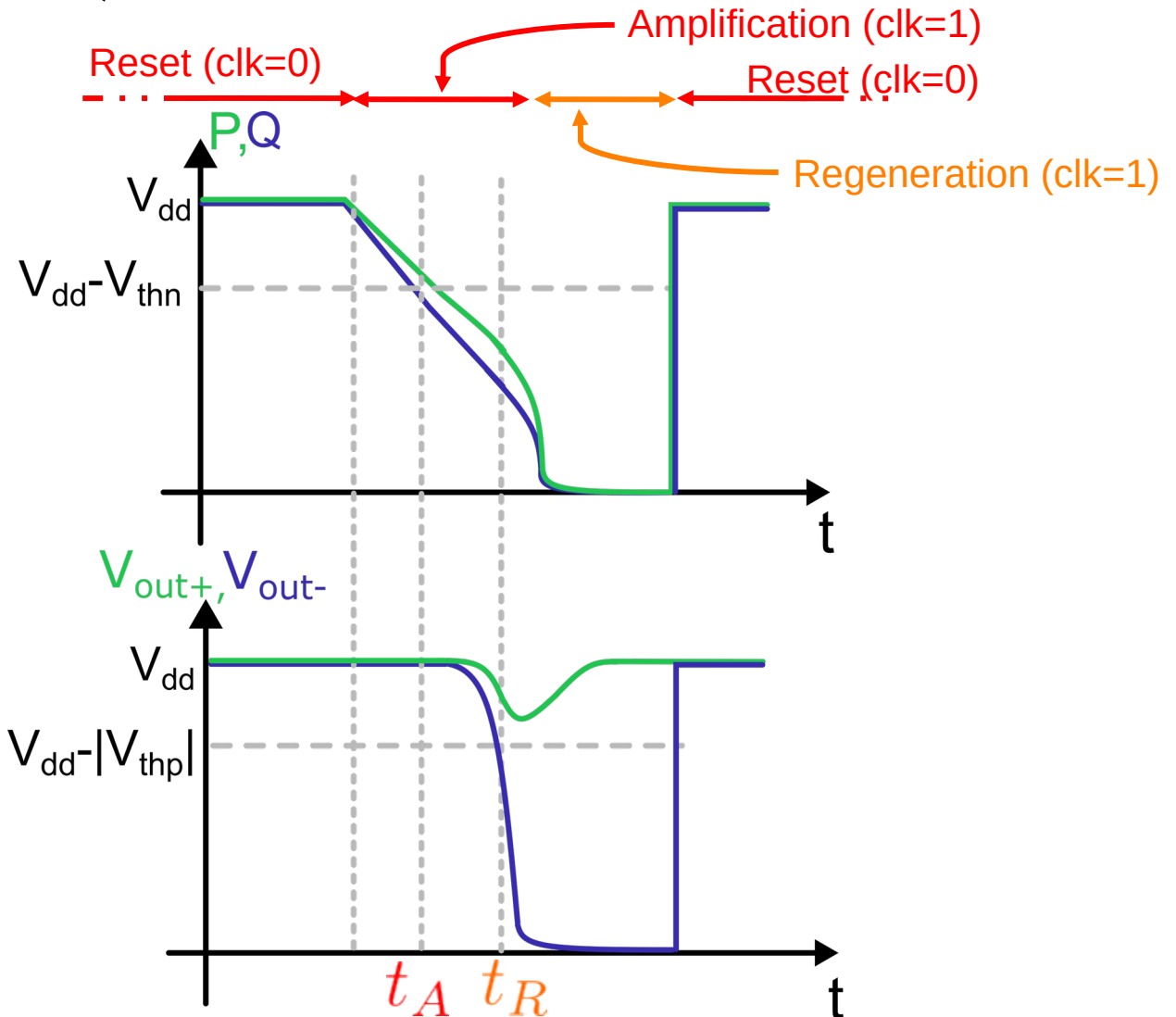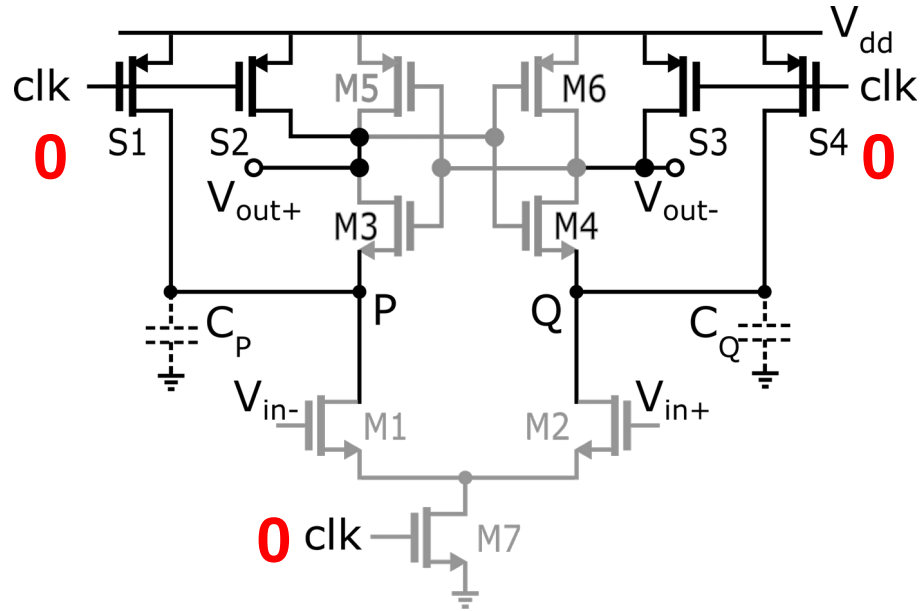

- S1-S4 recharge node P, Q,  $V_{out+}$ ,  $V_{out-}$  to  $V_{dd}$
- Need of a second latch to store the result of the comparison during the reset phase
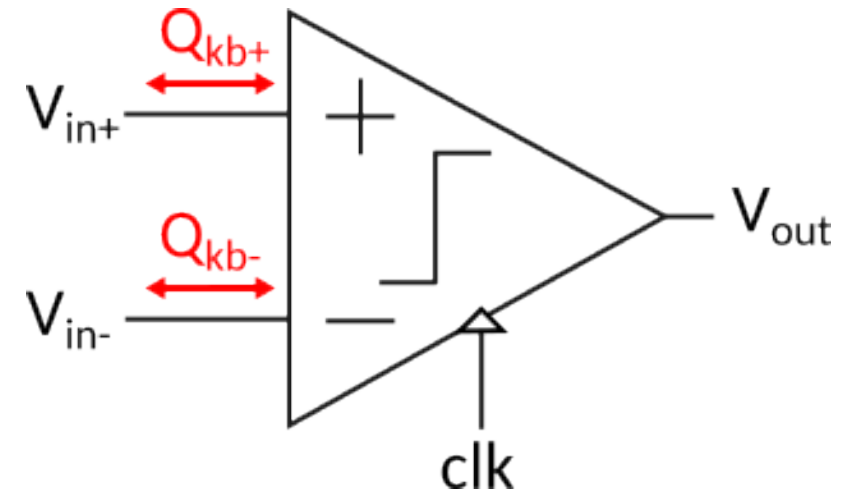
# StrongARM: Kick back effect


- The kick back effect is evident at the comparator inputs  $V_{in-}$  and  $V_{in+}$
- It implies a sudden demand of charge seen at those input terminals due to the **sharp transition of the internal voltages**, similar to the charge injection effects of a switch turn-on and turn-off
- For each comparison cycle, input pair devices (M1, M2) are first turned on, and the regenerative action of the latch bring them again to the off state
- Charge demand is different from port  $V_{in-}$  and port  $V_{in+}$ : it has a differential-mode component ( $Q_{kbd}$ ) and a common-mode component ( $Q_{kbc}$ )
- $Q_{kbd}$  depends on  $V_{id}$  (input differential voltage)



$$Q_{kbd} = Q_{kb+} - Q_{kb-}$$

$$Q_{kbc} = \frac{Q_{kb+} + Q_{kb-}}{2}$$

# StrongARM: Kick back effect

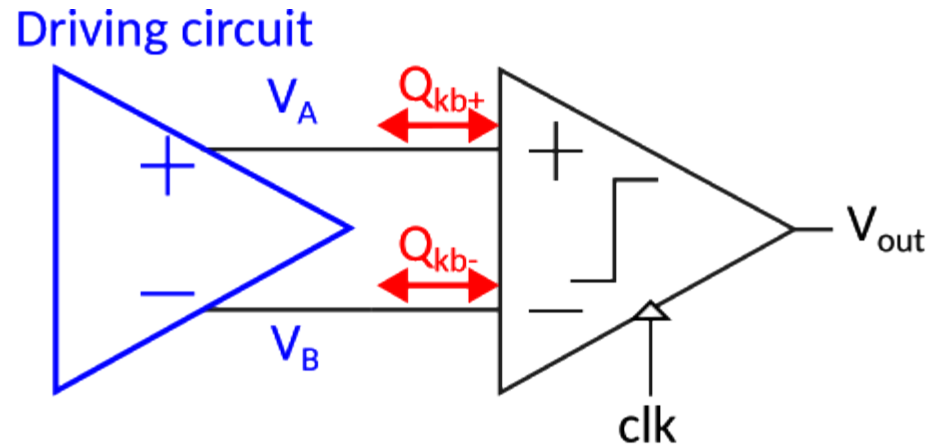


1. Suppose a “weak” driving circuit: (Typically an OTA with high impedance output nodes, cap-loaded, or a compensated 2-stage OTA)
2. Suppose the case of a constant  $V_A > V_B$

The first decision is correct ( $V_{out} = "1"$ ), if  $V_A$  and  $V_B$  would be kept constant all the following decisions should be “1”


However:  $V_A$  and  $V_B$  are upset by a different amount due to  $Q_{kbd}$

The system is slow to recover, hence when the second  $clk$  rising edge occurs  $V_A < V_B$ : the comparator now provides a wrong decision

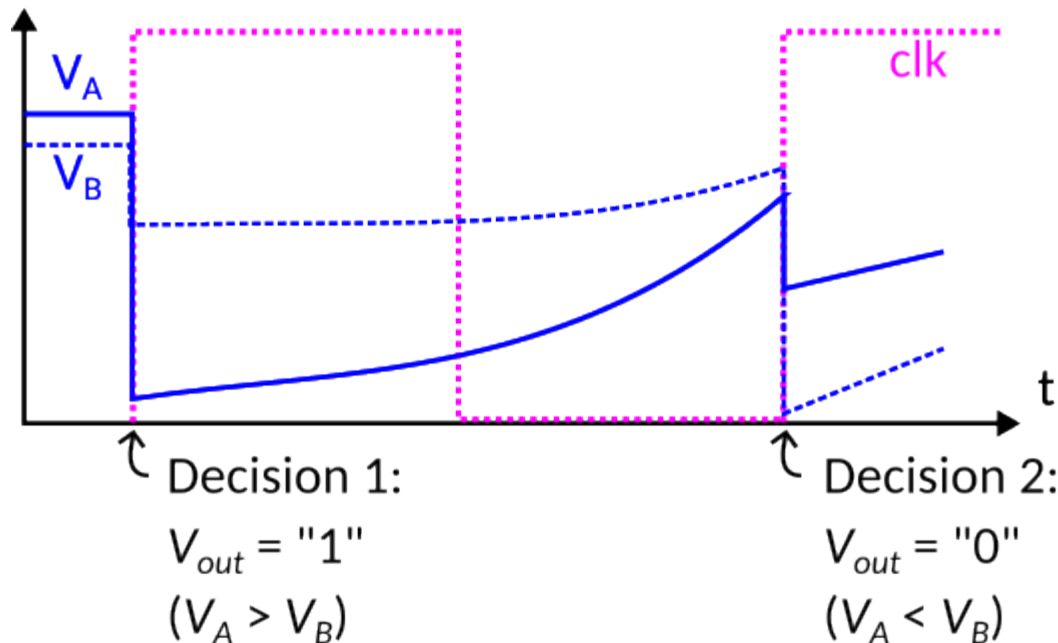**The result of the second decision has been influenced by the result of the previous decision:** this is similar to an hysteretic effect (undesired in this case)




# StrongARM: Kick back effect

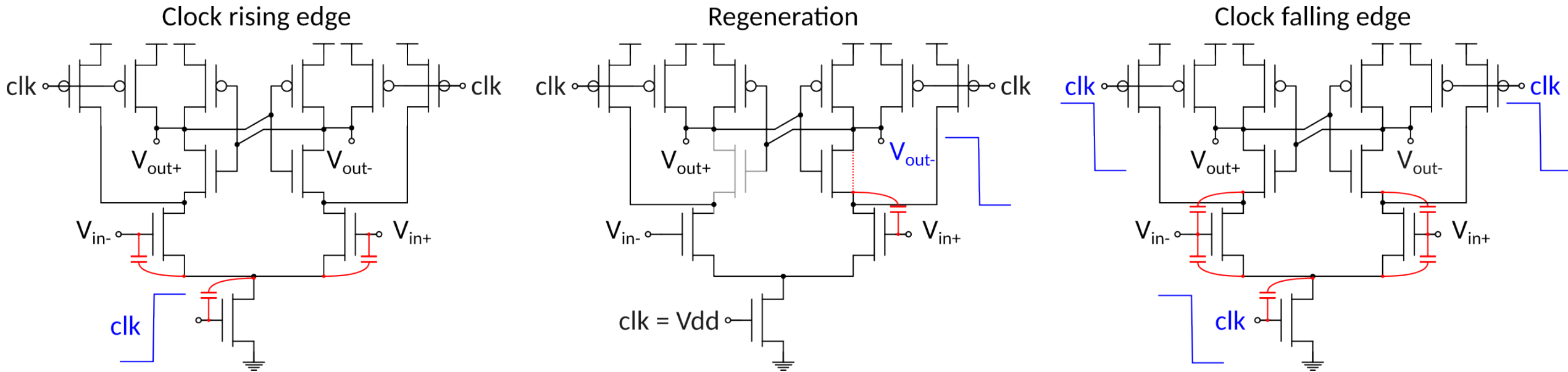



## StrongARM: Kick back effect, possible solution

CT preamplifier

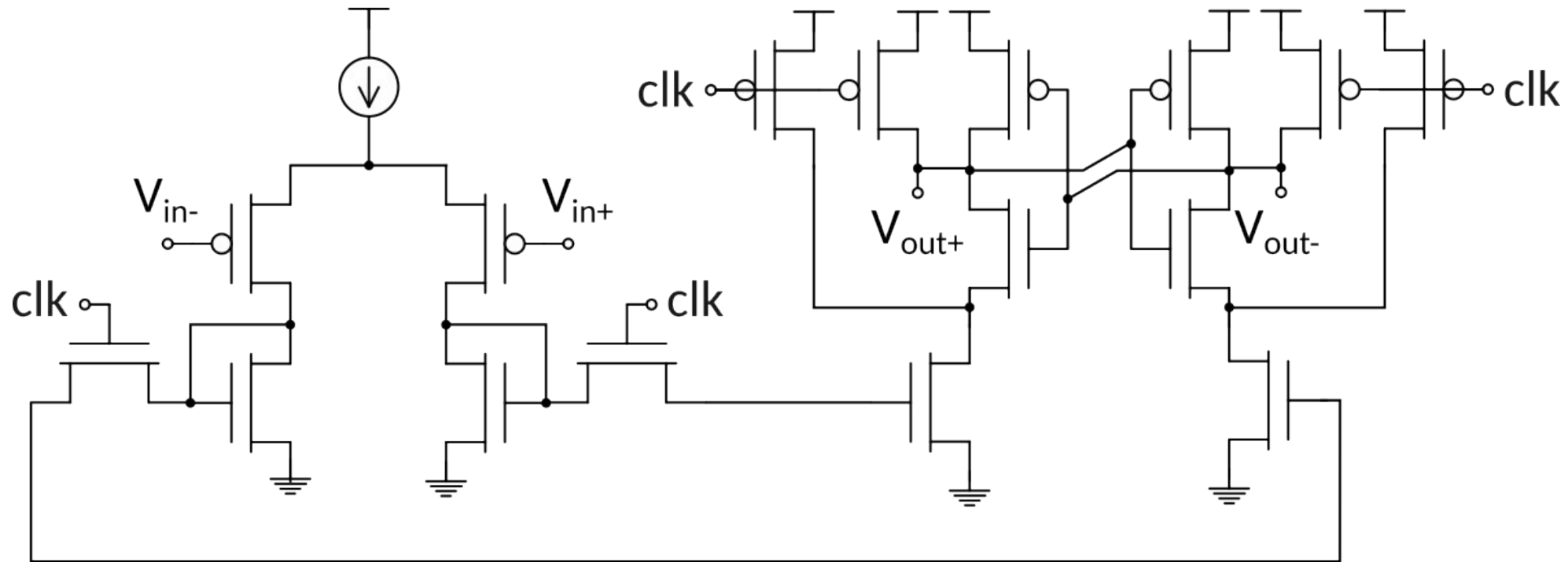


Use of a preamp-like structure:



- ✓ Greatly reduces signal swing coupled to the input pair.
- ✗ Implies static power consumption
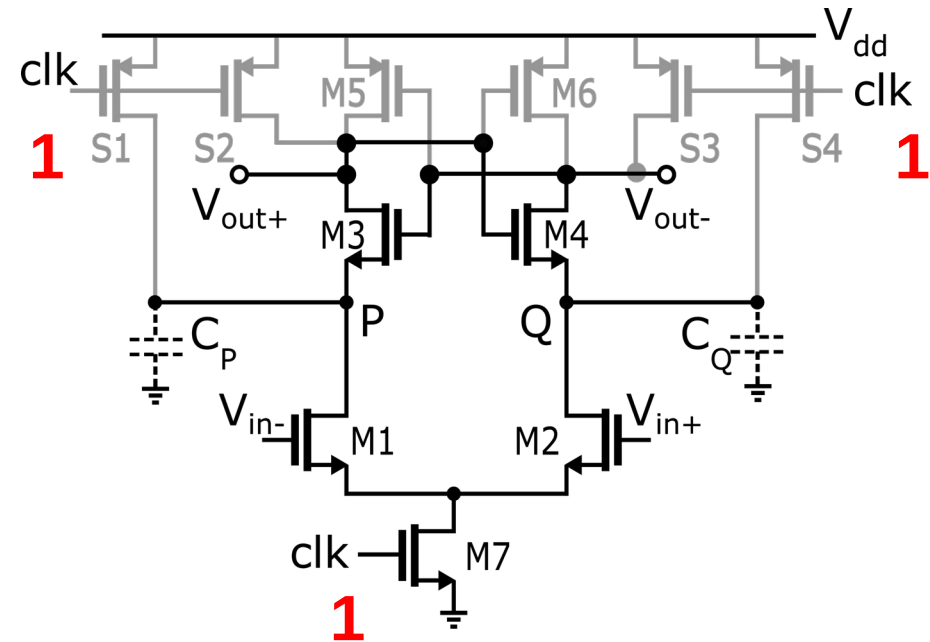
# StrongARM: input referred noise characterization

- For such **strongly non-linear circuit** transfer function is undefined, hence there exist no straight-forward “referring to input” procedure
- Most of the noise that may affect the decision is produced **before the regeneration phase** (i.e. during the amplification phase)
- The amplification phase is governed by the input pair (**M1**, **M2**). Once the cross coupled M3 and M4 turn on (during the last part of the amplification phase) they also provide a small contribution to total accumulated noise charge on CP, CQ.
- The gain during the amplification phase is “dynamic”: it depends on a time interval ( $t_A$ ,  $t_R$ ). Analytical expressions can be found but are complex


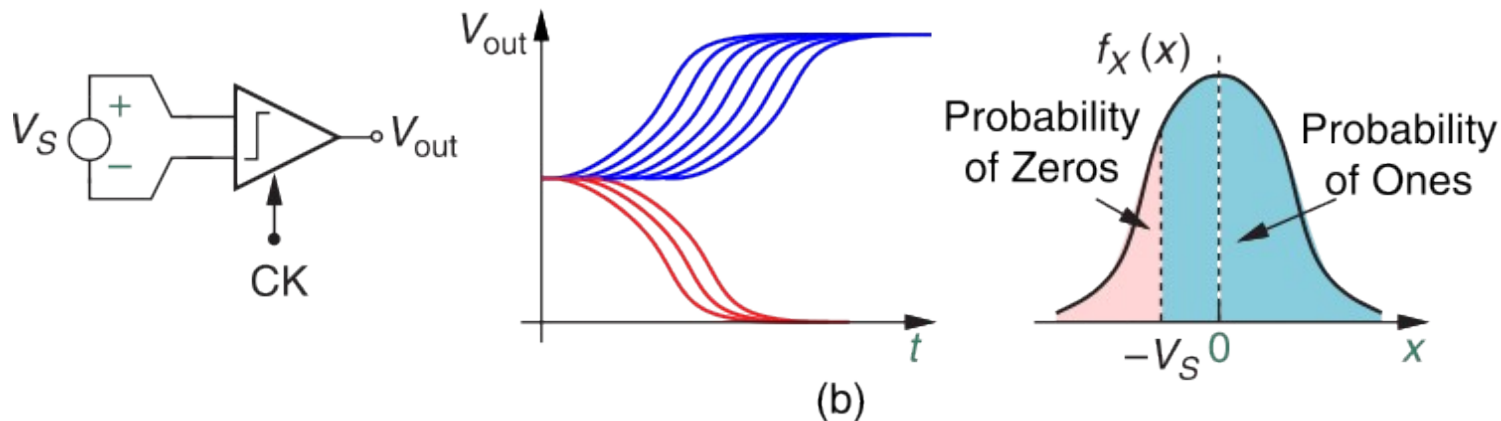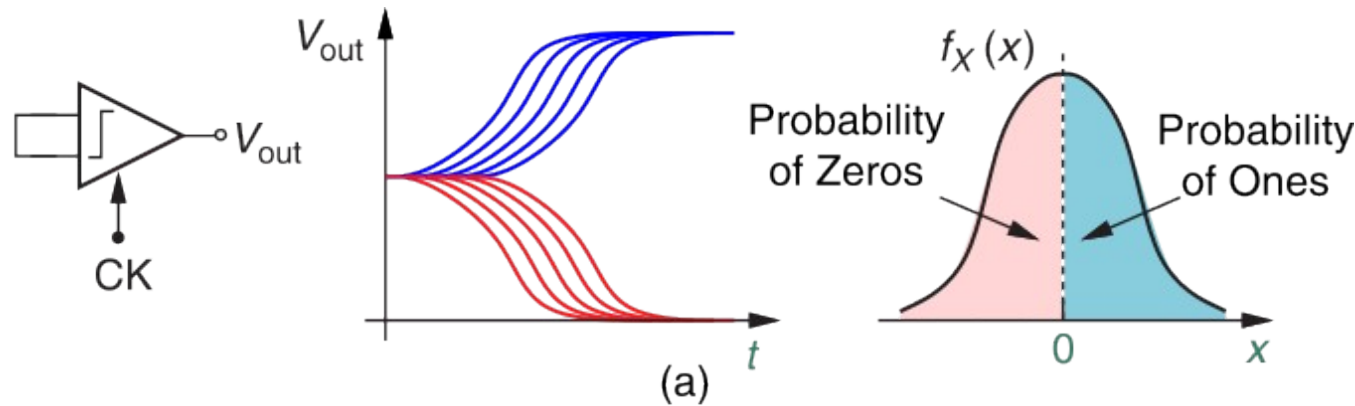
# StrongARM: input referred noise characterization




The goal is to find the sigma of a supposed normal distribution (Transient Noise simulations)

If inputs are at the same potential there is equal probability of having “0s” ( $n_0$ ) and “1s” ( $n_1$ )

Differential input slightly skewed to have different  $n_0$  and  $n_1$  counts. In the example  $n_1 > n_0$

$$\frac{n_0}{n_1} = \frac{\int_{-\infty}^{V_S} f_x(x) dx}{1 - \int_{-\infty}^{V_S} f_x(x) dx}$$
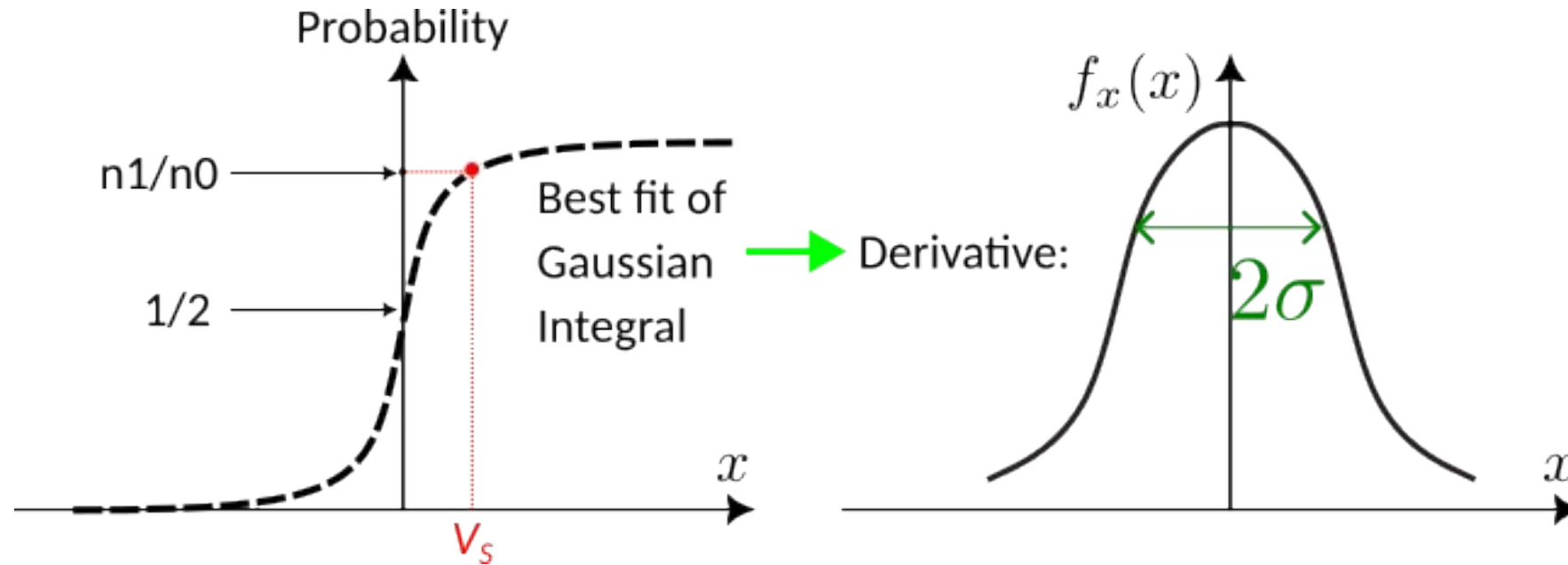
# StrongARM: input referred noise characterization



Eventually try a couple of  $V_S$  values to provide more points for best fit algorithm

Note:  $V_S$  should be chosen to be reasonably distant from probability = 1, 0 and  $\frac{1}{2}$