

DAC Converters Design: Syllabus

General definitions

- Applications
- Basic principles and operating electrical domains
- Performance parameters

Resistor-based DACs

- R-string, **R-string interpolated**, and limits (DNL, INL analysis)
- R-2R ladder: binary weighting, **DNL approximate analysis**, configuration with a TIA.

Current-source (CS) based DACs

- Unary and binary weighted CSs. DNL/INL analysis for binary scales CSs. **Segmentation.**
- **Design for high precision: gradients due to physical processing and due to routing, solutions based on ordered element switching and calibration techniques based on current copier**

Charge-scaling DACs

- Charge redistribution based on parallel capacitor banks

INSIGHT

S

DAC Converters Design: Syllabus

General definitions

- Applications
- Basic principles and operating electrical domains
- Performance parameters

Resistor-based DACs

- R-string, R-string interpolated, and limits (DNL, INL analysis)
- R-2R ladder: binary weighting, DNL approximate analysis, configuration with a TIA.

Current-source (CS) based DACs

- Unary and binary weighted CSs. DNL/INL analysis for binary scales CSs. Segmentation.
- Design for high precision: gradients due to physical processing and due to routing, solutions based on ordered element switching and calibration techniques based on current copier


Charge-scaling DACs

- Charge redistribution based on parallel capacitor banks

INSIGHT

S

General definitions

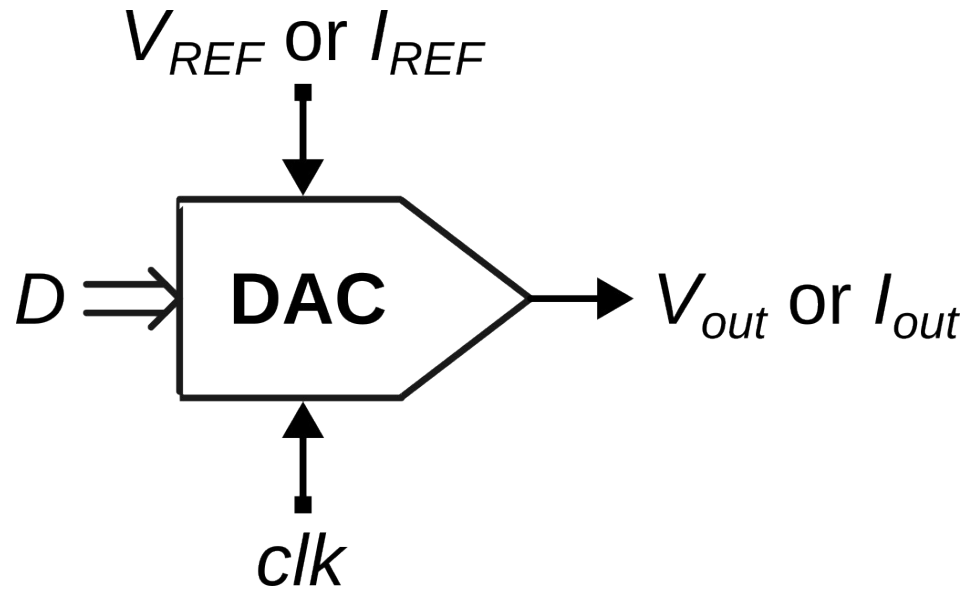

Input: D , digital code of N bits. If unsigned: $[0, 2^N - 1]$, if two's complement: $[-2^{N-1}, 2^{N-1} - 1]$

Output: analog signal (voltage or current) representing an analog equivalent of the input code, can be either single-ended or fully-differential

An analog **reference** is needed, to define the full-scale and minimum value

A **clock** almost always present for synchronization

Ideal voltage-output DAC:


$$V_{out}(D) = V_{min} + \frac{V_{FS}}{2^N} \cdot D$$

Ideal current-output DAC:

$$I_{out}(D) = I_{min} + \frac{I_{FS}}{2^N} \cdot D$$

General definitions: full-scale and LSB
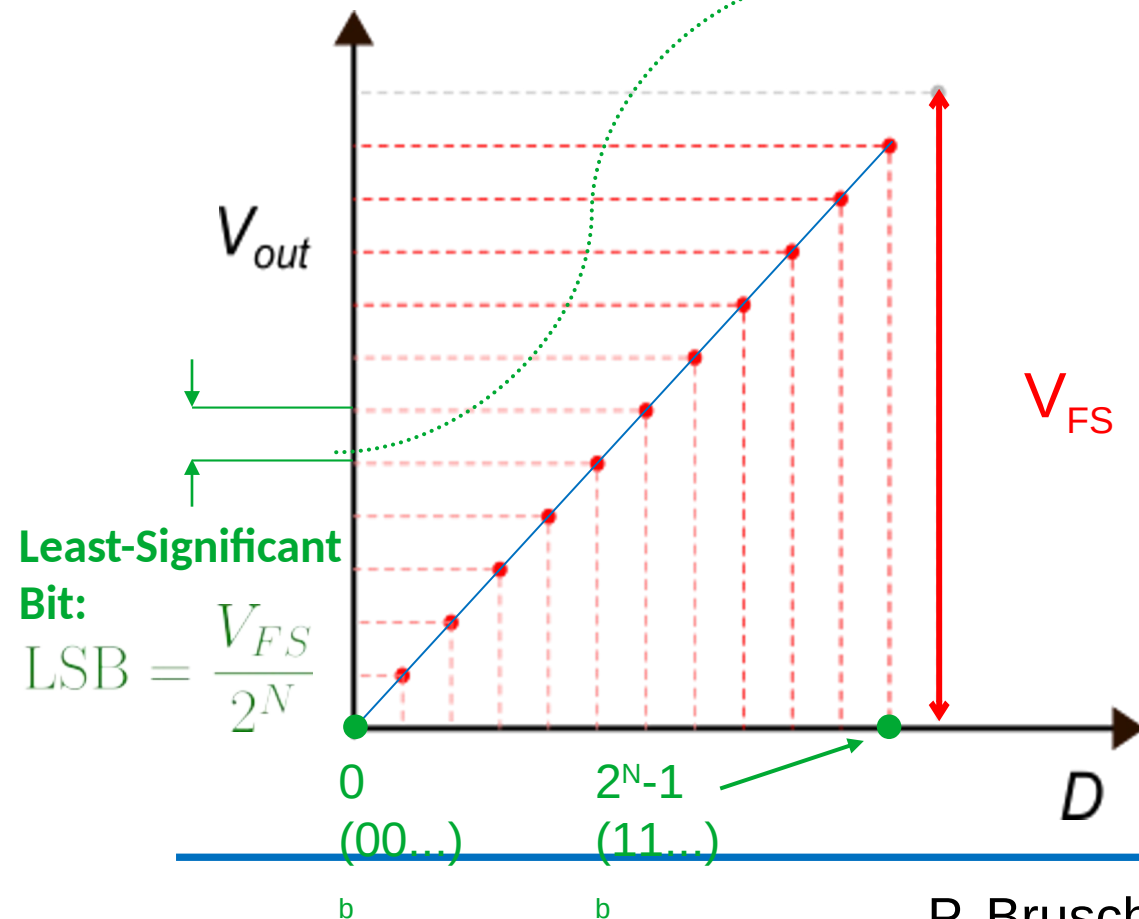
$$V_{out}(D) = V_{min} + \frac{V_{FS}}{2^N} \cdot D$$



Typically in Single-Ended DACs:

- Unsigned input,
- unipolar output
- $V_{min} = 0$ V (ground)
- $V_{FS} = \text{gain} * V_{REF}$
- The gain is determined by circuit implementation

Note:

V_{FS} is not available digitally, it represents the reference quantity to which V_{out} is normalized.


“Full-scale” is a naming convention!

The actual DAC output range is:

$$V_{min} \leq V_{out} \leq (1 - 2^{-N})V_{FS} + V_{min}$$

General definitions: full-scale and LSB
 
$$V_{out}(D) = V_{min} + \frac{V_{FS}}{2^N} \cdot D$$



Typically in **Fully-Differential DACs**:


- Two's complement input
- Differential output
- $V_{min} = -V_{FS}/2$, also differential valued
- Output common mode \geq to V_{min}

$$\begin{cases} V_{out,p} = V_{cmo} + \frac{V_{out}}{2} \\ V_{out,n} = V_{cmo} - \frac{V_{out}}{2} \end{cases}$$

DAC Applications



PRECISION DAC SELECTOR GUIDE

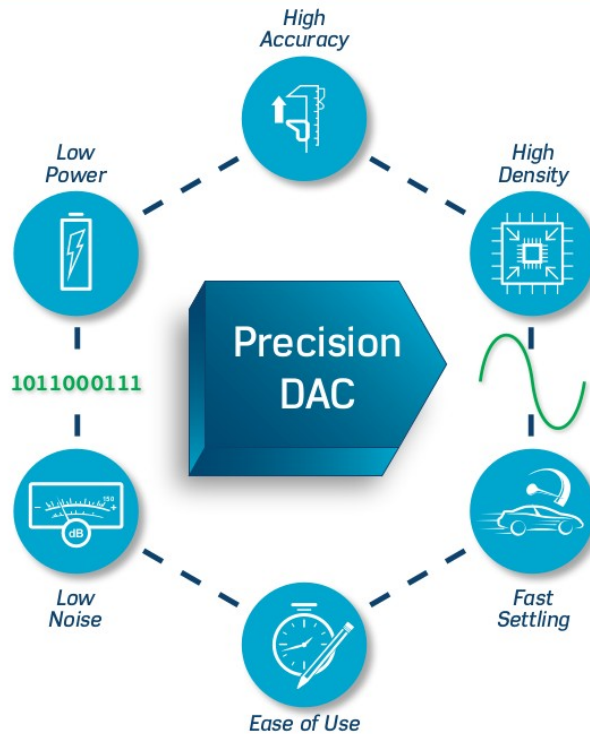

Digital signal reconstruction in DSP-based systems:

LED displays, Direct Digital Synthesis, Medical equipment. Often high-accuracy and high-resolution (16-20 bits) is needed

Actuation of sensory systems

Electrochemical sensors, MEMS, antenna arrays, ultrasound actuators. Often multichannel DACs and/or High-voltage requirements (20-40 V). Compactness for low-cost devices.

Wireless/wired communications

High-speed requirements, up to 10 GS/s. The faster, the better


Embedded block for calibration or as component of an ADC

Offset nulling, trimming, Delta-Sigma Modulator, SAR ADC. Usually ultra-low power requirements


Operating electrical domains

Fundamental functions needed in a DAC: add (perform a linear combination of homogeneous quantities) and select

 
In voltage domain: Voltage piles up in a series of resistive elements biased at V_{REF} , switches are controlled to tap into the desired voltage (digital potentiometer).



 In current domain: currents adds up to a common mode (Kirchhoff law of currents). Selected currents are routed to the summing node.



 In charge domain: pre-charged capacitors are connected together to set a final voltage resulting as (linear) combination of the individual charges



Typical performances vs. operating mode

Operating domain	Architectures	Accuracy	Current consumption range	Max Speed
Voltage	Resistor string, R-2R	8-16 bit HIGH RESOLUTION IF TRIMMED	1 μ A – 1 mA	1 MS/s
Current	Current sources (CS)	10-16 bit HIGH RESOLUTION IF CALIBRATED	1 μ A – 100 mA	10 GS/s HIGH SPEED
Charge	Capacitor bank	10-12 bit	1 nA – 10 μA LOW POWER	100 MS/s

Typical choices for different requirements: resolution, speed, power

Higher resolution? Delta-Sigma approaches, will be discussed later on

Main performance parameters

Precision/accuracy limited by:

quantization error (not DAC's fault)

offset

gain

static non linearity (DNL, INL)

dynamic non linearity (glitches)

Speed is limited by:

settling transients,

load,


operating output voltage

Power consumption is determined by:

electrical operating domain,

bandwidth requirements

Ideal waveform generator:

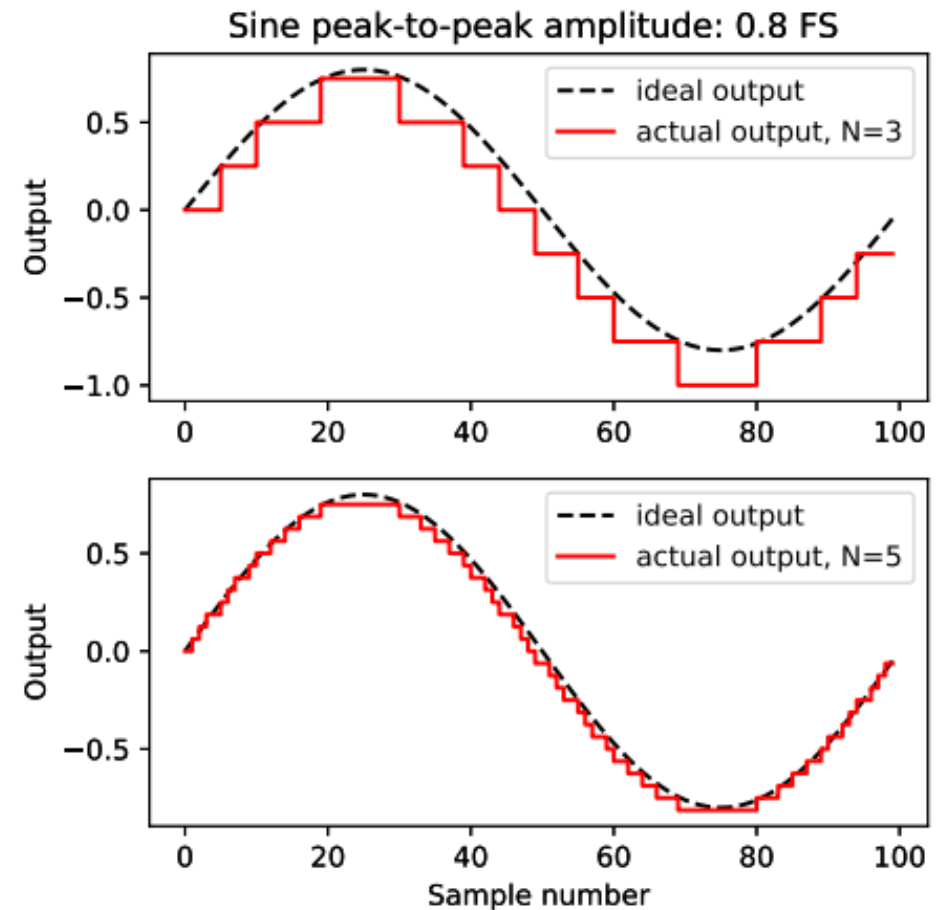

Main performance parameters

Precision/accuracy limited by:

quantization error (not DAC's fault)

offset

gain

static non linearity (DNL, INL)

dynamic non linearity (glitches)

Speed is limited by:

settling transients,

load,

operating output voltage

Power consumption is determined by:


electrical operating domain,

bandwidth requirements

Offset Error

Figure 10.2 illustrates the result of offset error only. The actual transfer function is offset from the ideal by two LSBs. Any such error—either positive or negative—that affects all codes by the same amount is an *offset error*.

 In most DAC testing, the offset error is measured by applying the zero-scale code (e.g. all “0”s) and measuring the output deviation from 0 volts.



THE DC SPECTRAL COMPONENT IS ALTERED

Main performance parameters

Precision/accuracy limited by:

quantization error (not DAC's fault)

offset

gain

END-POINT
ERRORS

static non linearity (DNL, INL)

dynamic non linearity (glitches)

Speed is limited by:

settling transients,

load,

operating output voltage


Power consumption is determined by:

electrical operating domain,

bandwidth requirements

Gain Error

Figure 10.3 shows the effect of a gain error only. The ideal transfer function has a slope defined by drawing a straight line through the two end points. The slope represents the gain of the transfer function. In real DACs, this slope can differ from the ideal, resulting in a *gain error*—which is usually expressed as a percent because it affects each code by the same percentage.

 

NO NEW SPECTRAL COMPONENTS ARE GENERATED

$$\frac{\text{Error}(\%)}{100\%} = \frac{V_{11} - V_{os}}{V_{FSR} (1 - 2^{-n})} - 1$$

Main performance parameters

Precision/accuracy limited by:

quantization error (not DAC's fault)

offset

gain

static non linearity (**DNL**, INL)

dynamic non linearity (glitches)

Speed is limited by:

settling transients,

load,

operating output voltage

Power consumption is determined by:


electrical operating domain,

bandwidth requirements


**REFERS TO THE
STATIC CHARACTERISTICS**

Ideal case

(absence of static non-linearity errors)

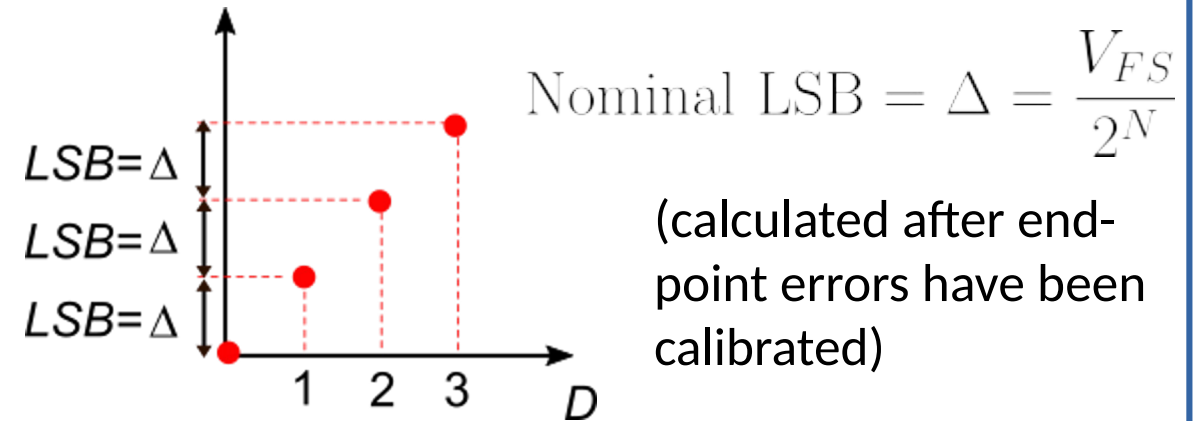

Real case

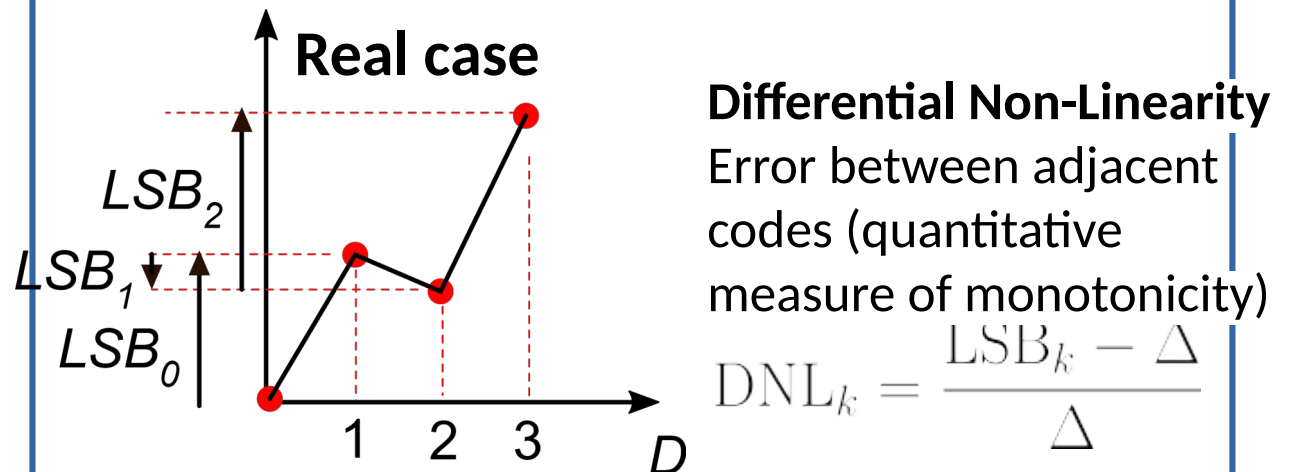

Main performance parameters

$$DNL_k = \frac{LSB_k - \Delta}{\Delta}$$

Precision/accuracy limited by:


- quantization error (not DAC's fault)
- offset
- gain
- static non linearity (**DNL**, INL)
- dynamic non linearity (glitches)

Speed is limited by:

- settling transients,
- load,
- operating output voltage

Power consumption is determined by:

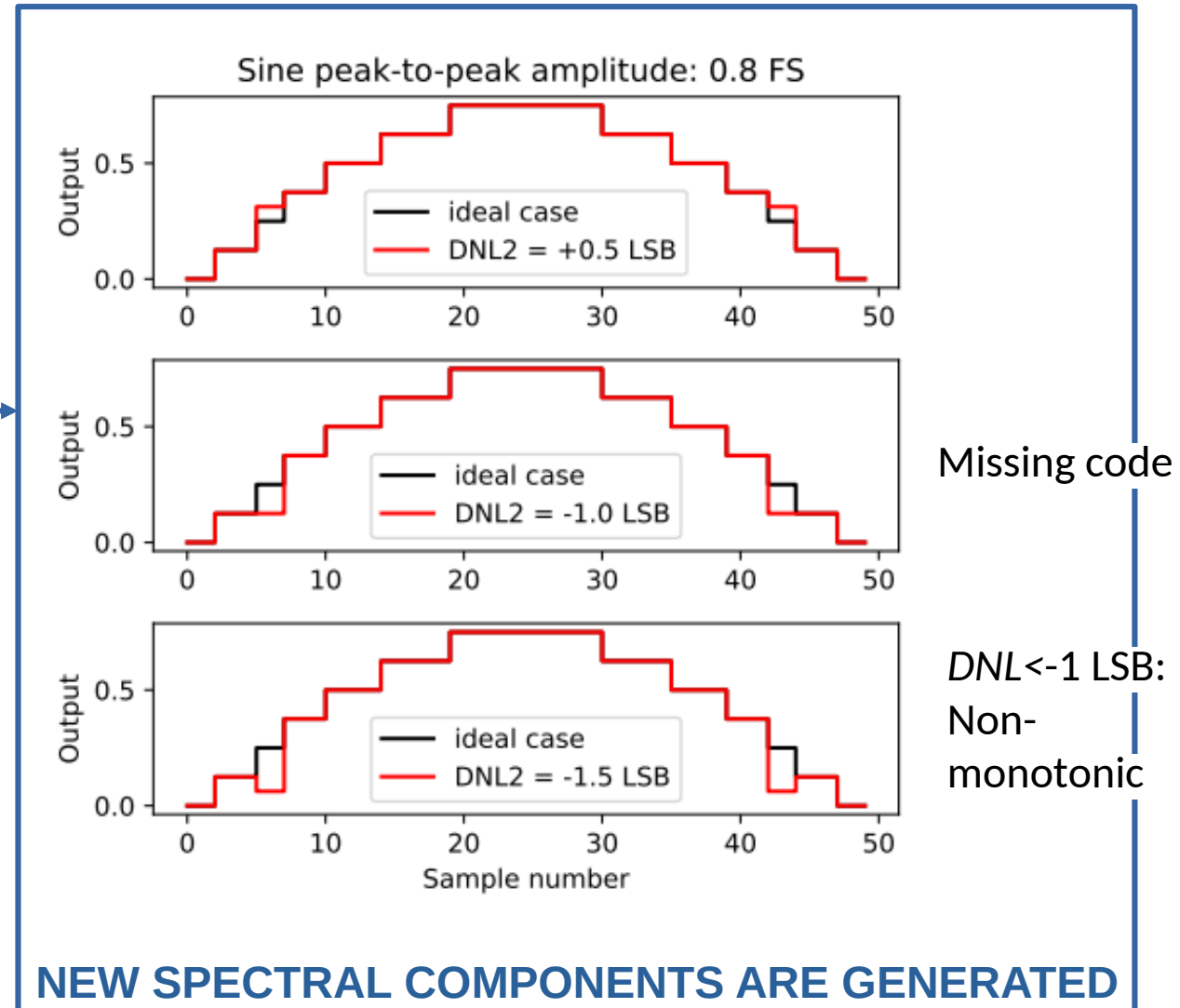- electrical operating domain,
- bandwidth requirements



Main performance parameters

Precision/accuracy limited by:


- quantization error (not DAC's fault)
- offset
- gain
- static non linearity (DNL, **INL**)
- dynamic non linearity (glitches)

Speed is limited by:

- settling transients,
- load,
- operating output voltage

Power consumption is determined by:

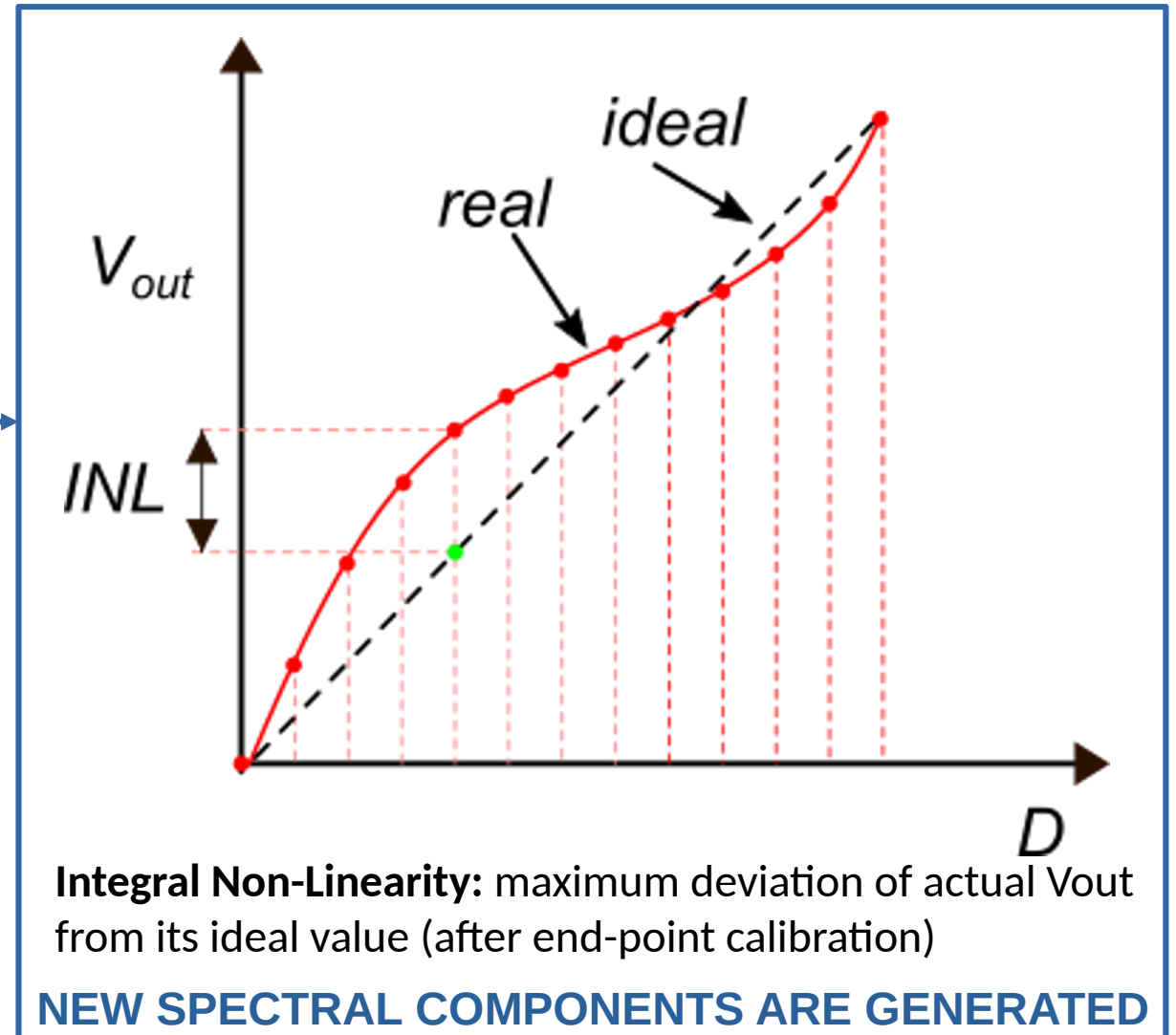- electrical operating domain,
- bandwidth requirements



Main performance parameters

Precision/accuracy limited by:

- quantization error (not DAC's fault)
- offset
- gain
- static non linearity (DNL, INL)
- dynamic non linearity (glitches)


Speed is limited by:

settling transients,

- load,
- operating output voltage

Power consumption is determined by:


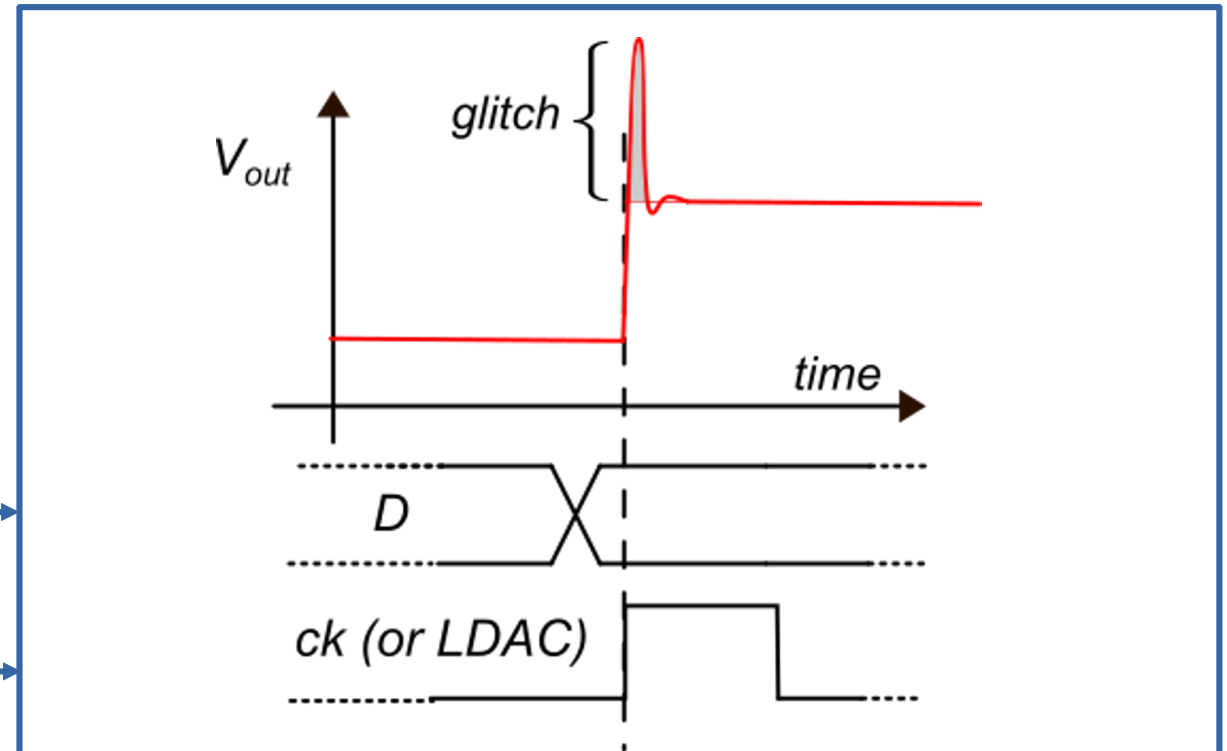
- electrical operating domain,
- bandwidth requirements



ck (or $LDAC$) acts as sync. signal, after D becomes stable.

If T_{ck} is large enough, the energy (area) of the glitch is negligible. As T_{ck} shrinks, the glitch energy is more and more important

Main performance parameters

  

DAC Converters Design: Syllabus

General definitions

- Applications
- Basic principles and operating electrical domains
- Performance parameters

Resistor-based DACs

- R-string, R-string interpolated, and limits (DNL, INL analysis)
- R-2R ladder: binary weighting, DNL approximate analysis, configuration with a TIA.

Current-source (CS) based DACs

- Unary and binary weighted CSs. DNL/INL analysis for binary scales CSs. Segmentation.
- Design for high precision: gradients due to physical processing and due to routing, solutions based on ordered element switching and calibration techniques based on current copier

Charge-scaling DACs

- Charge redistribution based on parallel capacitor banks

INSIGHT

S

R-String DAC

First idea:

Lord Kelvin in the mid-1800s, implemented using resistors and relays

- The string operates as **voltage divider** at each tap:

$$V_{tap} = \frac{R_{down}}{R_{down} + R_{up}} V_{REF}$$

- The accuracy of the partition voltage do depends on how well each resistor is matched to the others, not on the absolute accuracy of each resistor.
- Resistors constructed on the same substrate, deposited and processed together: inherent matching accuracy advantage over discrete solutions.


$$V_{out} = \frac{D}{2^n} V_{REF}$$

2^n resistors
 2^n switches

of device
number

Digital decoder

$$n \Rightarrow 2^n$$

 

R-String DAC


$$V_{out} = \frac{D}{2^n} V_{REF}$$

2^n resistors
 2^n switches

of device
number

Digital decoder


$$n \Rightarrow 2^n$$

 

Operation

- For any value of code D, only one switch at a time is on, selecting one of the 2^N voltage levels produced by the resistive voltage divider
- If code D turns on a certain switch, code D+1 turns on the switch placed in position up, then the output voltage can only grow
- The monotonicity is guaranteed, $|DNL| < 1 \text{ LSB}$
- Usually followed a unity gain buffer to avoid string loading (however, opamp offset and noise are now to be considered)

R-String DAC: DNL

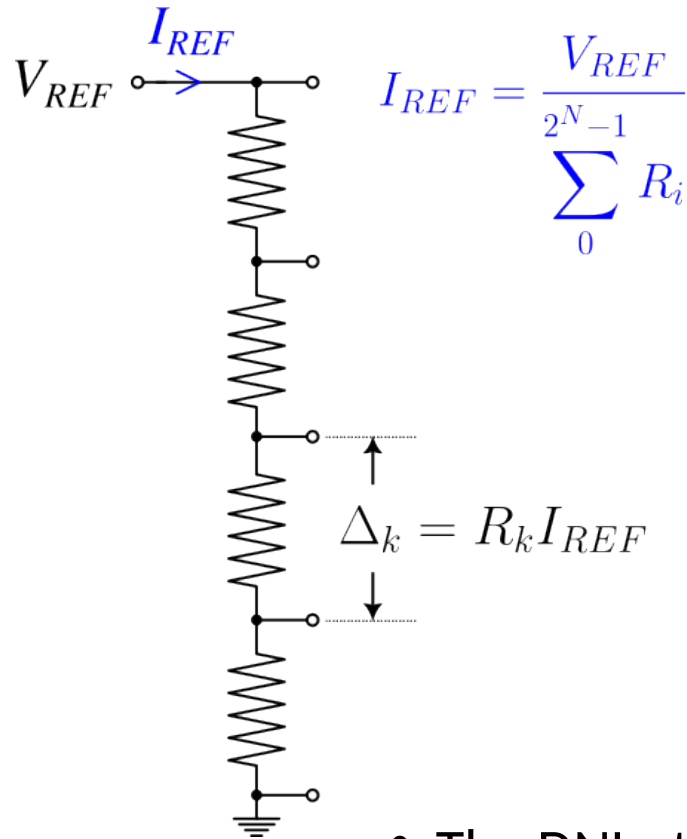

$$\text{LSB} = \Delta = \frac{V_{REF}}{2^N} = \frac{\sum_0^{2^N-1} R_k}{2^N} \cdot I_{REF}$$


\bar{R}

$$\text{DNL}_k = \frac{\Delta_k - \Delta}{\Delta} = \frac{R_k - \bar{R}}{\bar{R}} \approx \frac{\Delta R_k}{R}$$

$$\sigma_{\text{DNL}} = \sigma_{\Delta R/R}$$

- The DNL standard deviation coincides with the standard deviation of $\Delta R/R$ (element matching): **guaranteed monotonicity**
- DNL does not depend of resolution (N)
- DNL does not depend on absolute value of R

R-String DAC: INL

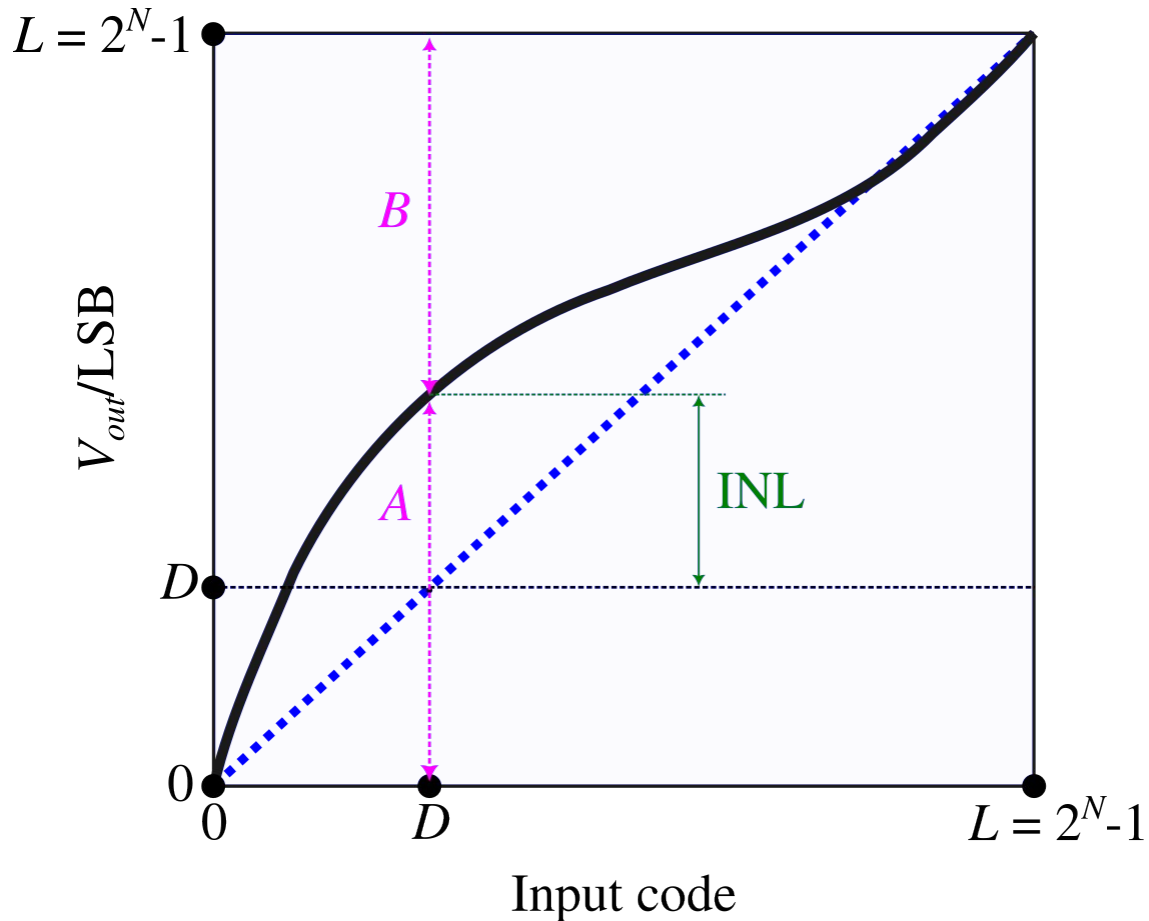

$$\begin{aligned} \text{INL}(D) &= A - D = A - \left(\frac{A+B}{L} \right) \cdot D \\ &= A - \left(\frac{A+B}{L} \right) \cdot D = A \cdot \left(1 - \frac{D}{L} \right) + B \cdot \frac{D}{L} \end{aligned}$$

$$\sigma_{\text{INL}}^2(D) = \boxed{\sigma_A^2} \cdot \left(1 - \frac{D}{L} \right)^2 + \boxed{\sigma_B^2} \cdot \left(\frac{D}{L} \right)^2$$

↑ D series elements ↑ L-D series elements

$$\sigma_{\text{INL}}^2(D) = D \sigma_{\Delta R/R}^2 \left(1 - \frac{D}{L} \right)^2 + (L-D) \sigma_{\Delta R/R}^2 \left(\frac{D}{L} \right)^2$$

$$\sigma_{\text{INL}}(D) = \sqrt{D \left(1 - \frac{D}{L} \right)} \cdot \sigma_{\Delta R/R}$$

R-String DAC: INL

$$\sigma_{\text{INL}}(D) = \sqrt{D \left(1 - \frac{D}{L}\right)} \cdot \sigma_{\Delta R/R}$$

The INL standard deviation is maximum at half code

$$\sigma_{\text{INL,max}} = \frac{\sqrt{L}}{2} \cdot \sigma_{\Delta R/R} \approx 2^{N/2-1} \cdot \sigma_{\Delta R/R}$$


The INL standard deviation depends on the DAC

resolution:


Design case: relative std. deviation of resistors 1%, what is the maximum number of bits for INL standard deviation < 0.1 LSB?

$$N < 2 + 2 \log_2 \frac{\sigma_{\text{INL,max}}}{\sigma_{\Delta R/R}} = 2 + 2 \log_2 \frac{0.1}{0.01} \approx 8.6$$

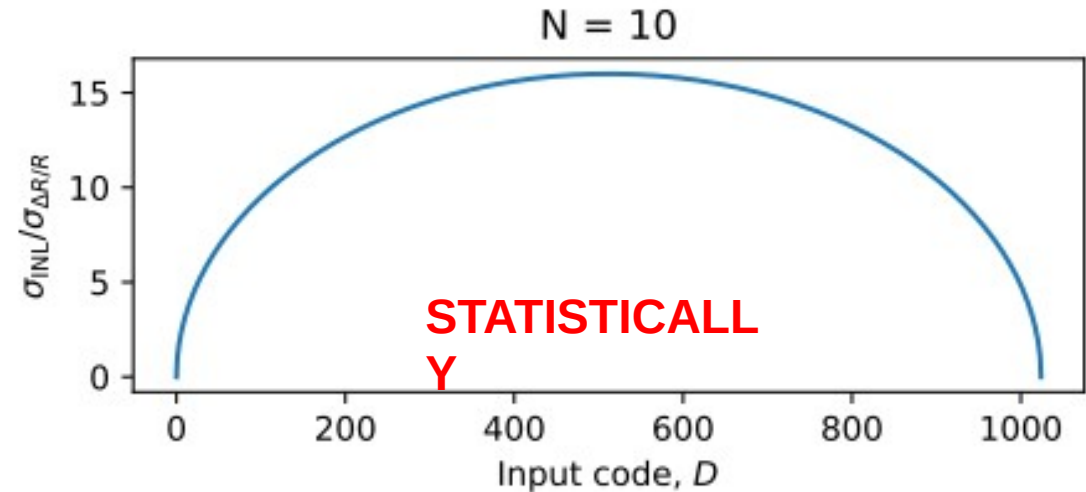Very expensive to reach resolution higher than 10 bit with R-string architecture: routing!




The R-2R ladder

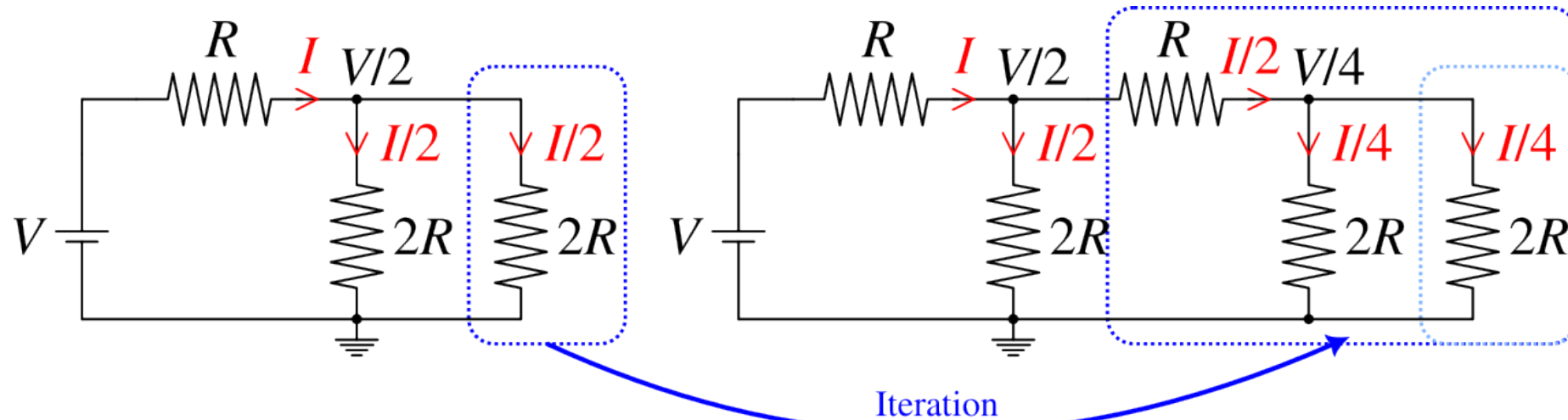

- The simple R-2R ladder provides a **voltage and a current scaling by 2**
- One of the $2R$ can be substituted instantiating another ladder, this way by iteration a **binary scaling** is obtained: [relaxed routing with respect to R-String](#)
- If iterated N times, the total number of unit resistors will be $N \times 3 + 2$ (the last 2 is due to the final termination $2R$ element)

The R-2R DAC

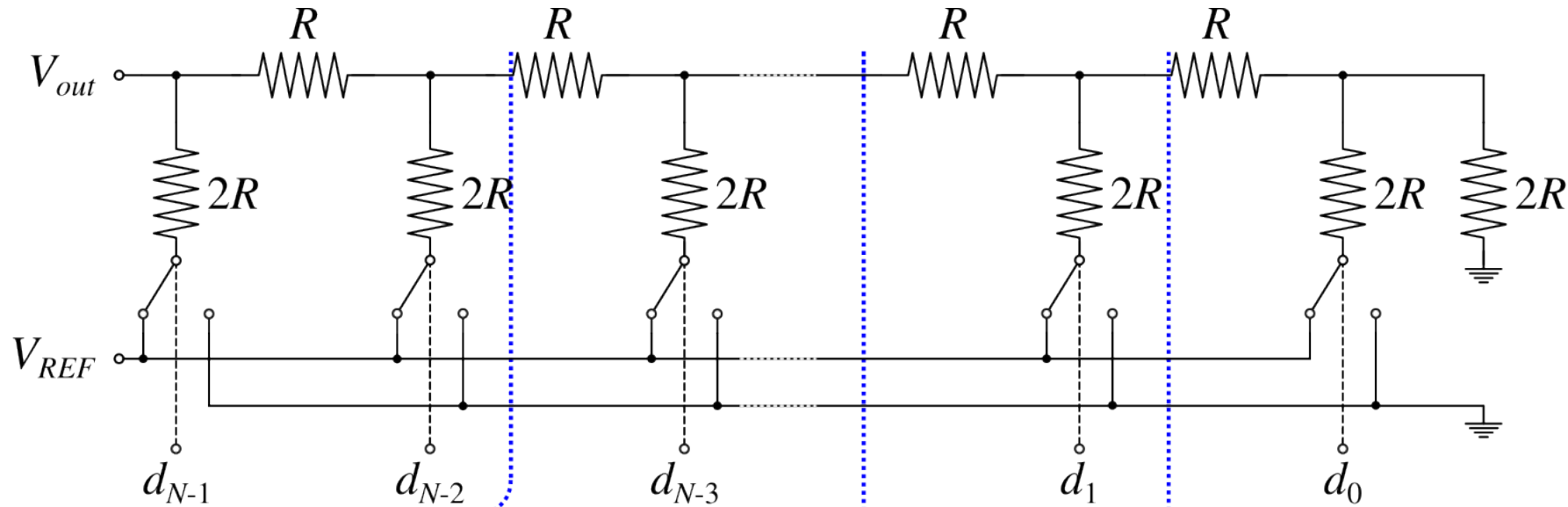

$$\begin{cases} V_{TH} = \frac{1}{2} \left(d_{N-3} + \frac{d_{N-2}}{2} + \dots + \frac{d_0}{2^{N-3}} \right) V_{REF} \\ R_{TH} = 2R \end{cases}$$

$$\begin{cases} V_{TH} = \frac{1}{2} d_0 \cdot V_{REF} \\ R_{TH} = 2R \end{cases}$$

$$\begin{cases} V_{TH} = \frac{1}{2} (d_1 V_{REF} + \frac{1}{2} d_0 \cdot V_{REF}) \\ R_{TH} = 2R \end{cases}$$

$$V_{out} = \left(\frac{d_{N-1}}{2} + \frac{d_{N-2}}{2^2} + \dots + \frac{d_0}{2^N} \right) V_{REF} = \frac{V_{REF}}{2^N} \cdot D$$


LSB = $V_{REF}/2^N$

Operation:

- Thevenin equivalent from LSB section, moving then towards MSB
- At each section a $\frac{1}{2}$ scaling is introduced (nominally)
- As in R-string the scaling depends on resistive voltage dividers
- Output voltage is **binary weighted**
- **Current consumption**



The R-2R DAC, TIA configuration

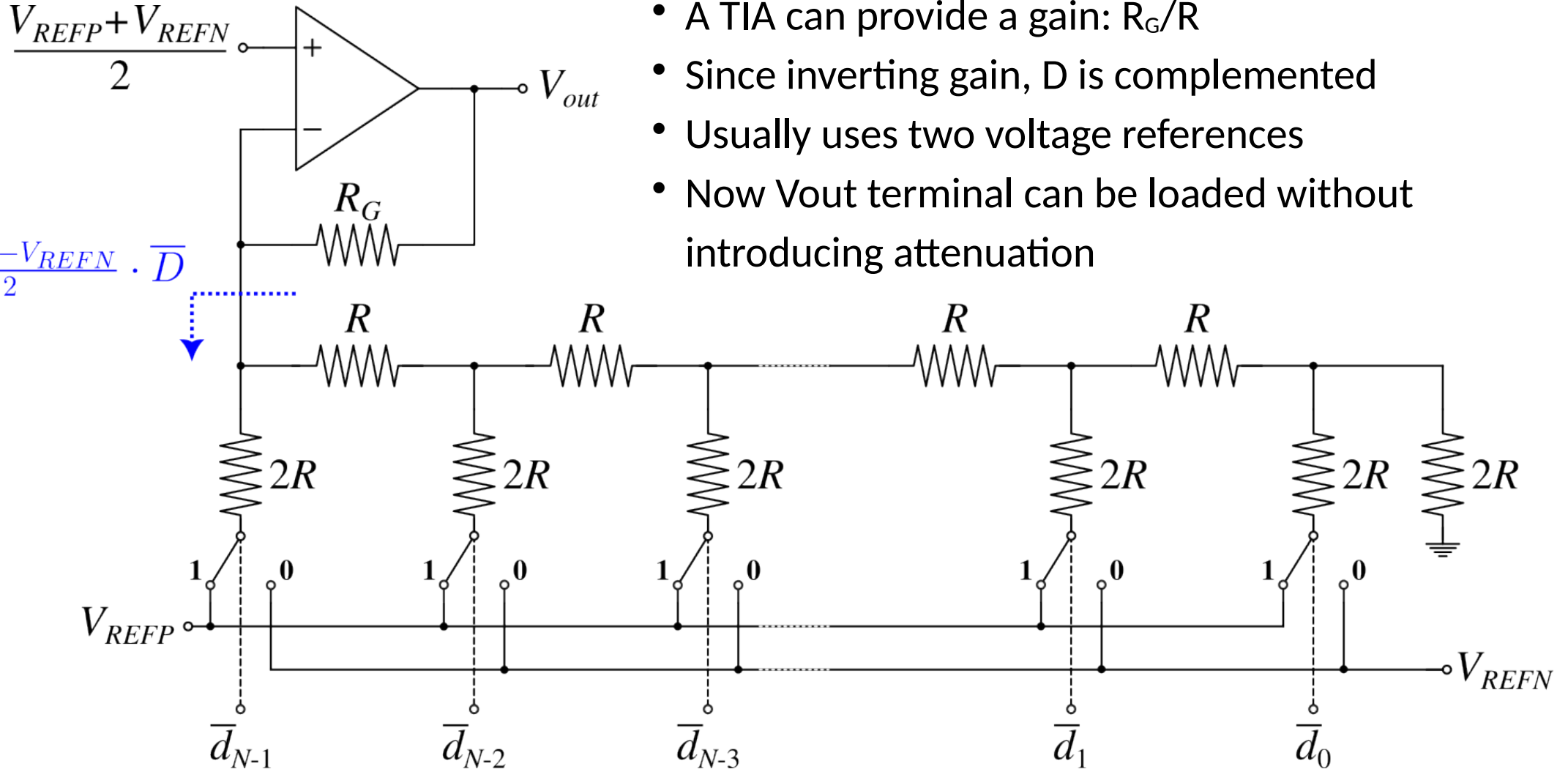- A TIA can provide a gain: R_G/R
- Since inverting gain, D is complemented
- Usually uses two voltage references
- Now V_{out} terminal can be loaded without introducing attenuation



$$\begin{cases} V_{TH} = \frac{V_{REFP} - V_{REFN}}{2} \cdot \bar{D} \\ R_{TH} = R \end{cases}$$

CS DAC: Unary and Binary Weighted

  


The switch steer the current to the output or to V_k (dummy low-impedance node)

In both cases, I_u sources are obtained through current mirrors:

$$I_u = \frac{I_{REF}}{2^N} \quad (\text{LSB})$$
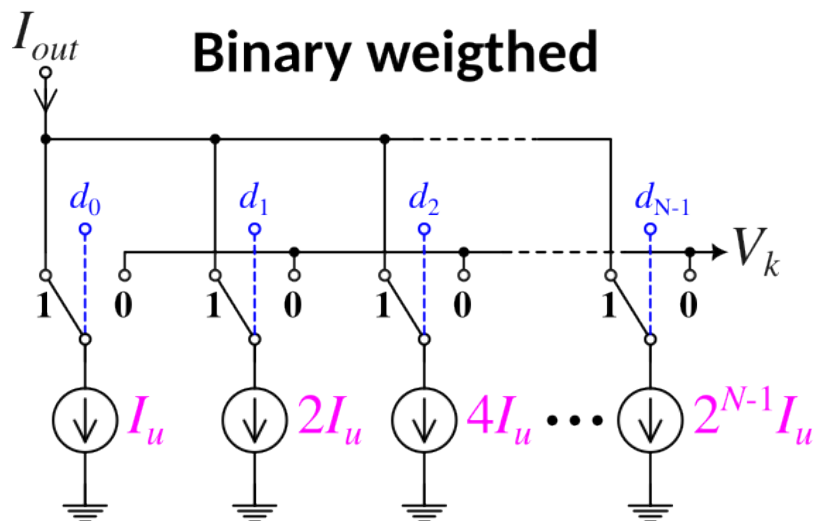
$$I_{out} = \frac{I_{REF}}{2^N} \cdot D$$



$$D = \sum_{k=0}^{N-1} 2^k d_k$$

Accuracy relies on our ability to ensure the correct weight of each current source (CS) element: a **mosfet**

DAC Converters Design: Syllabus

General definitions

- Applications
- Basic principles and operating electrical domains
- Performance parameters

Resistor-based DACs

- R-string, **R-string interpolated**, and limits (DNL, INL analysis)
- R-2R ladder: binary weighting, **DNL approximate analysis**, configuration with a TIA.

Current-source (CS) based DACs

- **Unary and binary weighted CSs. DNL/INL analysis for binary scales CSs. Segmentation.**
- **Design for high precision: gradients due to physical processing and due to routing, solutions based on ordered element switching and calibration techniques based on current copier**


Charge-scaling DACs

- Charge redistribution based on parallel capacitor banks

INSIGHT


S

CS DAC: Unary and Binary Weighted

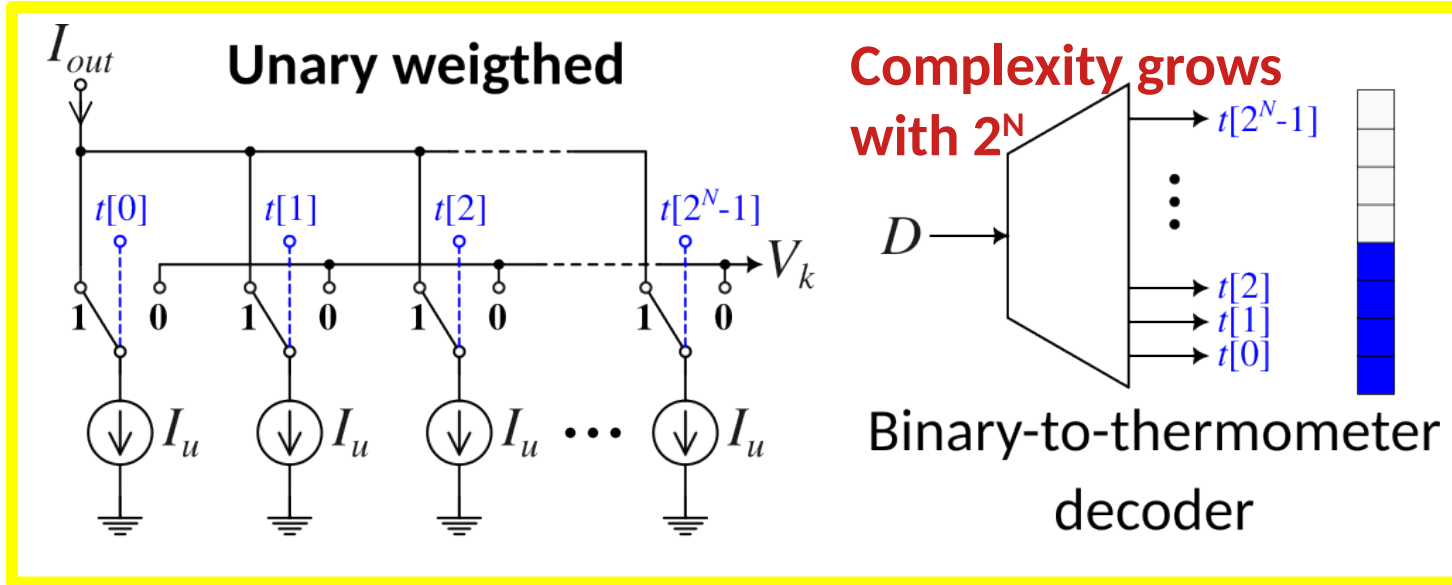

Unary weighted

 - ✓ Can be made monotonic-guaranteed by driving the 2^N mosfets of the array with thermometric coding: D increase +1 : +1 more CS routed to I_{out}
- ✓ Glitches proportional to code transition (small dynamic distortion)
- ✗ It suffers from the same INL problem of the resistor string DAC:



$$D = \sum_{k=0}^{N-1} 2^k d_k$$




$$\sigma_{DNL} = \sigma_{\Delta I/I}$$

$$\sigma_{INL,max} = 2^{N/2-1} \cdot \sigma_{\Delta I/I}$$

$$\frac{\Delta I}{I} = \frac{\Delta \beta}{\beta} + \frac{2\Delta V_T}{V_{GS} - V_T}$$

- Large Area
- Large overdrive

CS DAC: Unary and Binary Weighted

 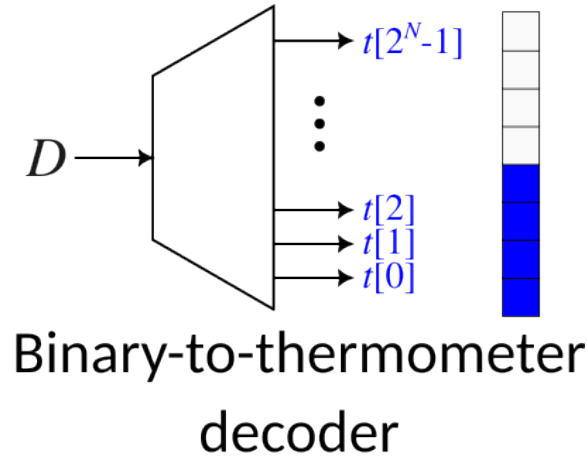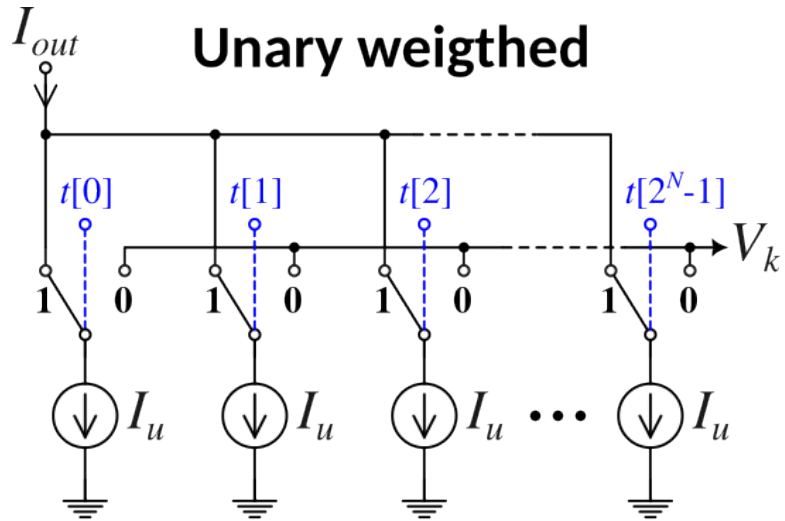

$$D = \sum_{k=0}^{N-1} 2^k d_k$$

Binary weighted

- ✓ Trivial digital decoding (small overhead)
- ✗ Same INL as unary weighted (for the same output level, the same number of nominally identical I_u sources are selected)
- ✗ DNL: as in R-2R, the major code transition is the most critical: 011.. → 100..


$$\sigma_{\text{DNL}} = \underbrace{(2^{N-1} - 1)}_{011\dots} \sigma_{\Delta I/I} + \underbrace{(2^{N-1})}_{100\dots} \sigma_{\Delta I/I}$$

↓

$$\sigma_{\text{DNL}} \approx 2^N \sigma_{\Delta I/I}$$


Critical!

CS DAC: Cell Implementation

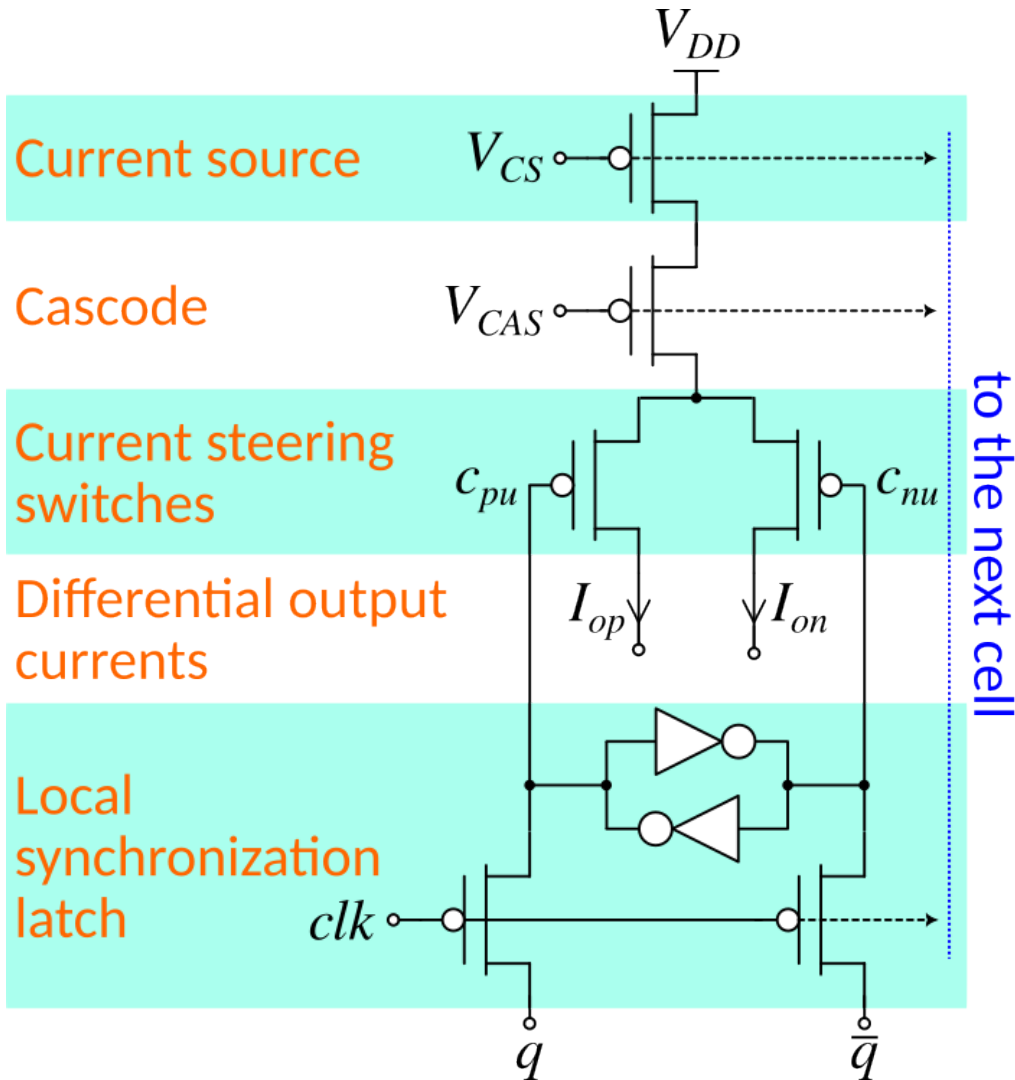


Usually:

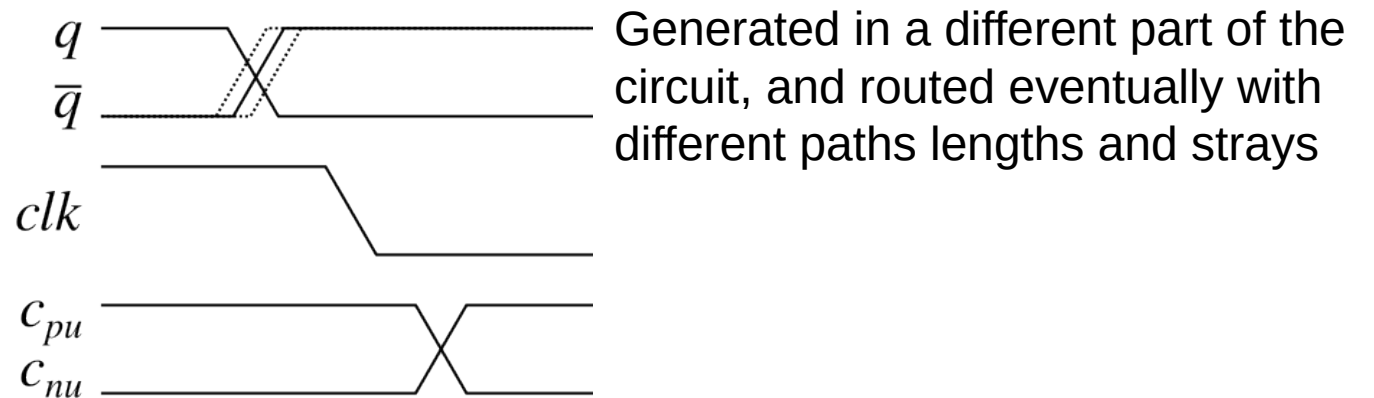- **Fully-differential implementation** (avoids waste of current)
- **PMOS CS** for milder flicker (under area constraint)
- Local synchronization **latch** gated by global clock (very important for high-speed designs): avoids differential glitches at the output currents



CS DAC: Implementations

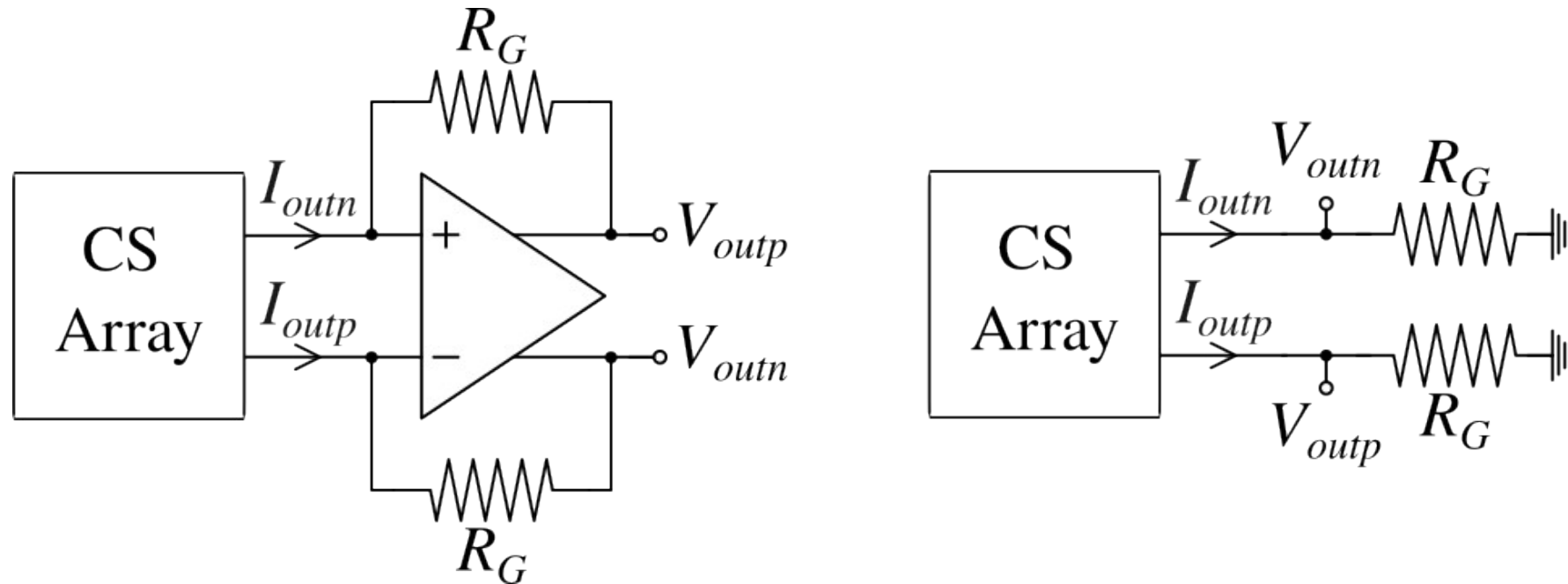

If a voltage output is desired, the CS array output currents can be injected to the virtual ground of a TIA or terminated to a resistive load:

TIA solution: the virtual ground ensures , however distortion, noise of TIA is now of concern. **High-power demanding choice, not compatible with high-speed requirements.**

R-termination solution: output nodes undergo voltage swings, to avoid distortion, cascode (also double) are mandatory. **Not compatible with low-voltage requirements.**

DAC Converters Design: Syllabus

General definitions

- Applications
- Basic principles and operating electrical domains
- Performance parameters

Resistor-based DACs

- R-string, **R-string interpolated**, and limits (DNL, INL analysis)
- R-2R ladder: binary weighting, **DNL approximate analysis**, configuration with a TIA.

Current-source (CS) based DACs

- Unary and binary weighted CSs. DNL/INL analysis for binary scales CSs. **Segmentation**.
- **Design for high precision: gradients due to physical processing and due to routing, solutions based on ordered element switching and calibration techniques based on current copier**



Charge-scaling DACs

- **Charge redistribution based on parallel capacitor banks**

INSIGHT


S

  Charge redistribution: generic capacitors-only network




Equivalent Ohm's law for charge transfer
 
$$\Delta V = \frac{1}{C} \cdot \Delta Q$$



Charge redistribution: binary-scaled capacitor bank

Binary-scaled capacitors bank

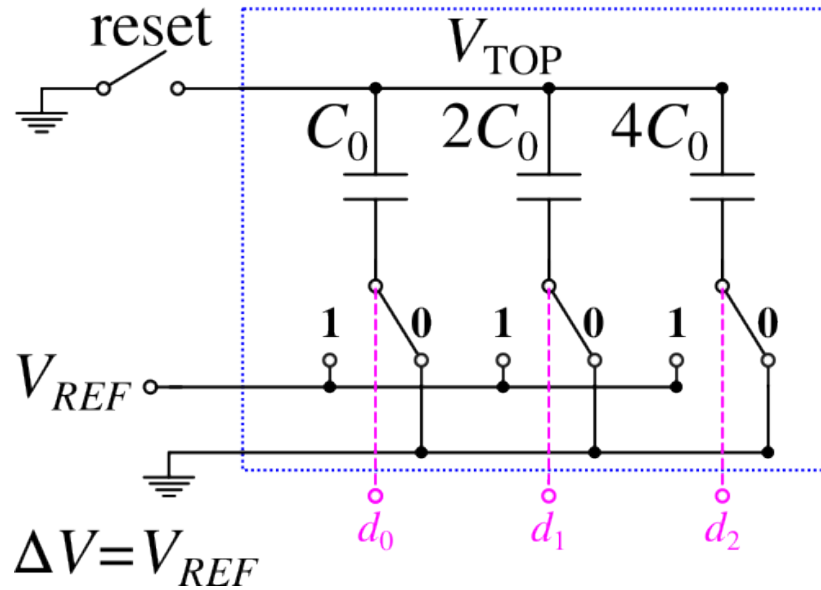


$$d_0(0 \rightarrow 1): \Delta V_{TOP} = \frac{\frac{1}{C_0}}{\frac{1}{C_0} + \frac{1}{2C_0} + \frac{1}{4C_0}} \Delta V = \frac{4}{7} \Delta V$$

$$d_1(0 \rightarrow 1): \Delta V_{TOP} = \frac{\frac{1}{2C_0}}{\frac{1}{C_0} + \frac{1}{2C_0} + \frac{1}{4C_0}} \Delta V = \frac{2}{7} \Delta V$$

$$d_2(0 \rightarrow 1): \Delta V_{TOP} = \frac{\frac{1}{4C_0}}{\frac{1}{C_0} + \frac{1}{2C_0} + \frac{1}{4C_0}} \Delta V = \frac{1}{7} \Delta V$$


Charge redistribution DAC

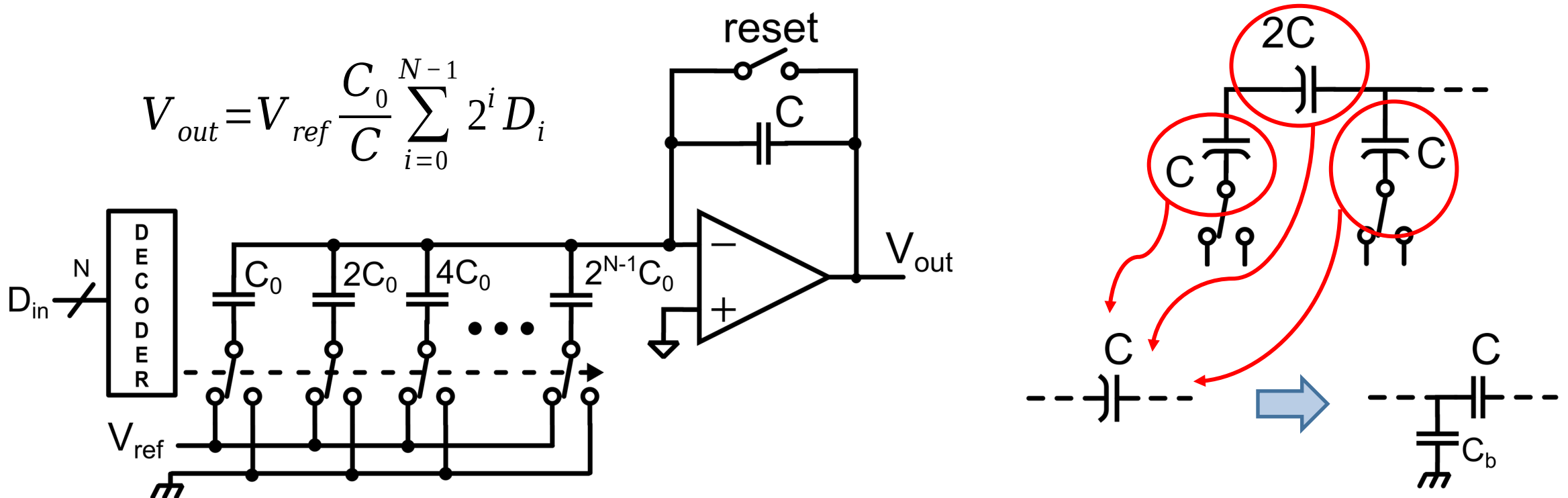- ✓ Capacitor bank has better matching properties than resistor string
- ✓ Low-power solution (no static consumption in the capacitor bank)
- ✗ Output not always valid
- ✗ Troubles with C-2C solutions due to parasitic capacitance of the bottom plate



Charge redistribution DAC with CDS

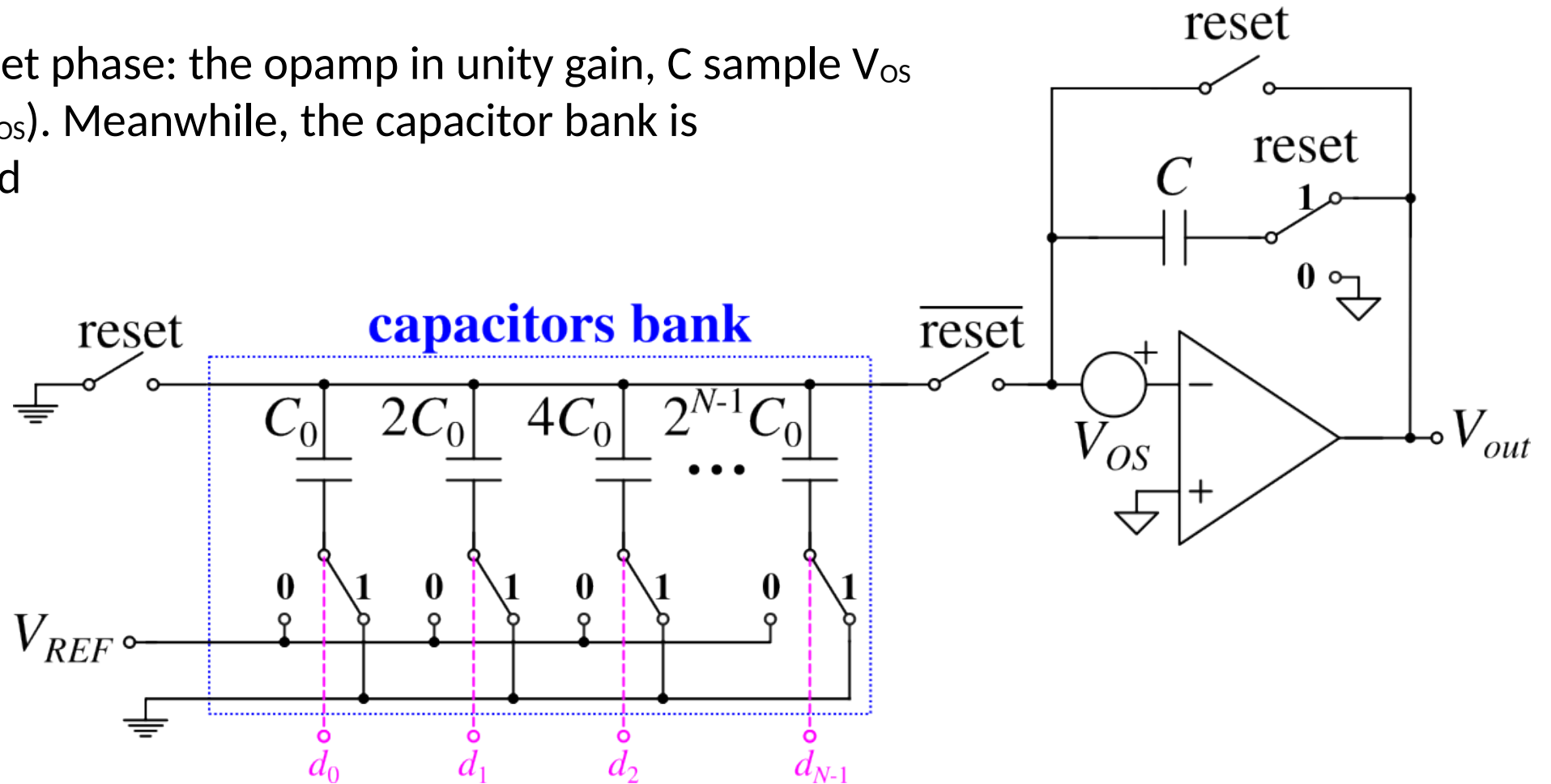During reset phase: the opamp in unity gain, C sample V_{OS} ($V_{out} = -V_{OS}$). Meanwhile, the capacitor bank is precharged



DAC architectures overview

	<i>Pros</i>	<i>Cons</i>
Resistor String	Guaranteed monotonic. Low power consumption	Very large number of resistors
R-2R ladder	Reduced number of resistor of similar value	Not inherently monotonic. Suffers from the on-resistance of the switches. Large glitches
Current Steering	Very fast. No need for resistors. Can be designed to be always monotonic	Current output. Flicker Noise
Switched Capacitors	Optimal power vs speed trade-off	The output may be not available in the whole clock cycle. Large glitches

DAC Converters Design: **Insights**

General definitions

- Applications
- Basic principles and operating electrical domains
- Performance parameters

Resistor-based DACs

- R-string, **R-string interpolated**, and limits (DNL, INL analysis)
- R-2R ladder: binary weighting, **DNL approximate analysis**, configuration with a TIA.


Current-source (CS) based DACs

- Unary and binary weighted CSs. DNL/INL analysis for binary scales CSs. **Segmentation.**
- **Design for high precision: gradients due to physical processing and due to routing, solutions based on ordered element switching and calibration techniques based on current copier**

Charge-scaling DACs

- Charge redistribution based on parallel capacitor banks

R-String DAC (interpolated)

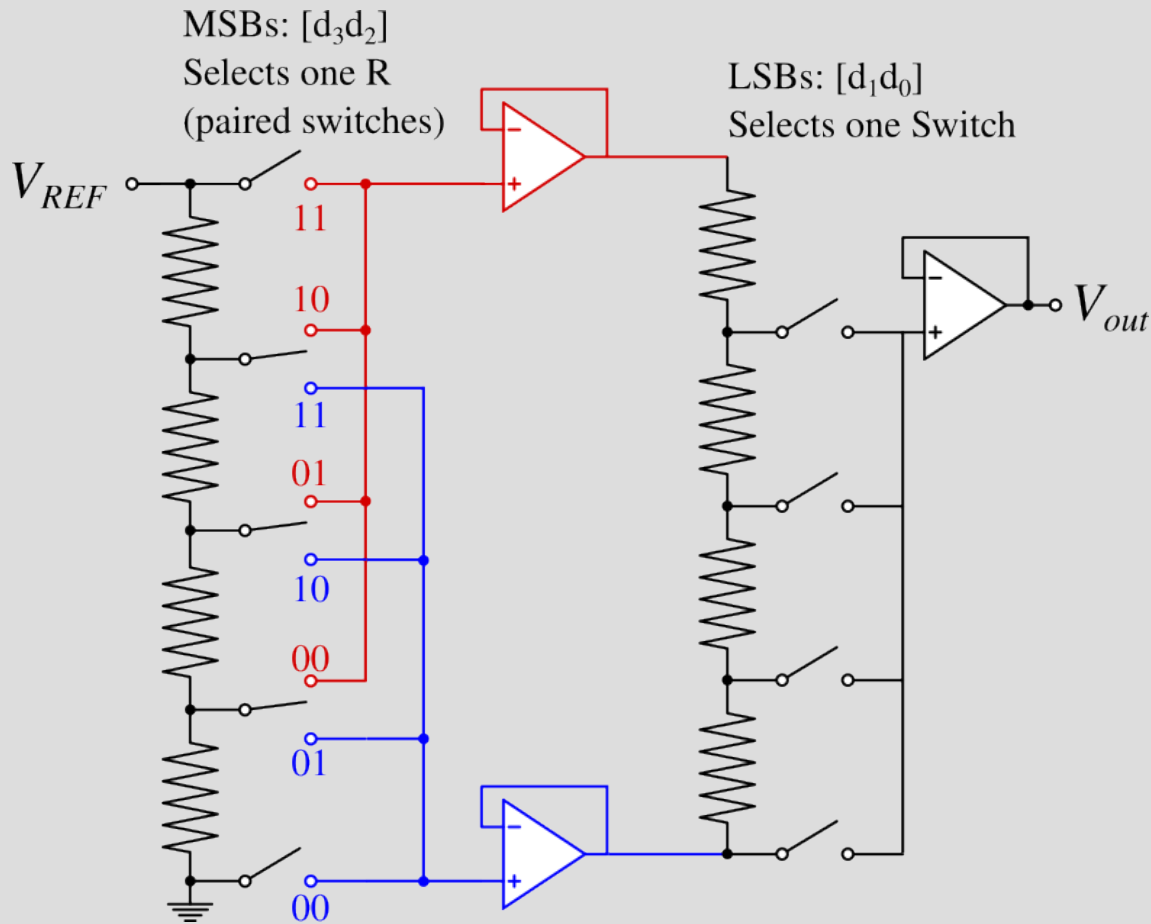


Interpolated R-string DAC: coarse + fine segments

- The input D of N bit is divided in to an MSB segment of length M and an LSB segment of length L :
- $N = M+L$
- Each R in the MSB string is selected at time through the MSB segment of D
- The LSB segment is decoded to select one switch in the LSB segment string as before
- Now the number of levels are still 2^N , but the number of R s is now 2^M+2^L
- Monotonicity not guaranteed (due to opamp offsets). More advanced selection techniques are employed.

The R-2R DAC: DNL and INL

 - DNL and INL analysis is complex: usually the designer relies on Monte Carlo simulations
- The most relevant effect is on DNL, in correspondence with **major code transition**: 011... → 100...
- Empirically $\sigma_{INL} \approx \sigma_{DNL}/2$.



Very approximate analysis:

$$V_{out} \begin{array}{c} \text{---} R_1 \text{---} \\ | \\ R_2 \\ | \\ \text{---} 0 \end{array} \left(\frac{1}{2} + \frac{1}{4} + \dots + \frac{1}{2^{N-1}} \right) V_{REF} \rightarrow 0$$

$$\underbrace{\left(1 - \frac{1}{2^{N-1}} \right) V_{REF}}_{V_{REF} - 2LSB}$$


$$\Delta V_{out} = \frac{R_1}{R_1 + R_2} V_{REF} - \frac{R_2}{R_1 + R_2} (V_{REF} - 2LSB)$$

$$\approx \frac{\Delta R}{2R} V_{REF} + LSB$$

monotonic if: $\frac{\Delta R}{R} < \frac{2LSB}{V_{REF}} = \frac{1}{2^{N-1}}$

In resume: both INL and DNL limited by N and $\sigma_{\Delta R/R}$

CS DAC: Segmentation

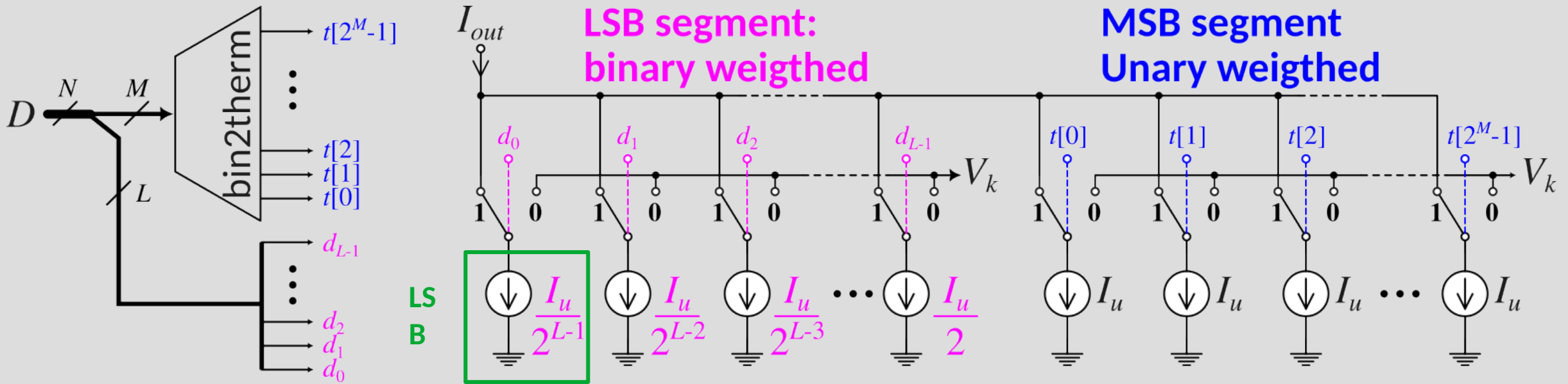

Objective: strike a balance between complexity and accuracy

- N bits are segmented in M bits in the MSB segment and L bits in the LSB segment $N = M + L$

- INL is unaffected $\sigma_{\text{INL,max}} = 2^{N/2-1} \cdot \sigma_{\Delta I/I}$

- DNL is dominated by the LSB segment $\sigma_{\text{DNL}} = 2^L \sigma_{\Delta I/I}$

- The total number of switched elements depends on segmentation ratio $2^M - 1 + L$


CS DAC: Segmentation

$$N = \underbrace{M}_{\text{MSB}} + \underbrace{L}_{\text{LSB}}$$

$$\sigma_{\text{INL,max}} = 2^{N/2-1} \cdot \sigma_{\Delta I/I} \quad \sigma_{\text{DNL}} = 2^L \sigma_{\Delta I/I} \quad 2^M - 1 + L$$



Architecture	$\sigma_{\text{INL,max}} [\sigma_{\Delta I/I}]$	$\sigma_{\text{DNL}} [\sigma_{\Delta I/I}]$	Number of switched elements
Unary, N = 10	16	1	1023
Segmented 6+4	16	16	67
Segmented 5+5	16	32	36
Segmented 4+6	16	64	21
Binary, N = 10	16	1024	10

CS DAC: typical floorplan

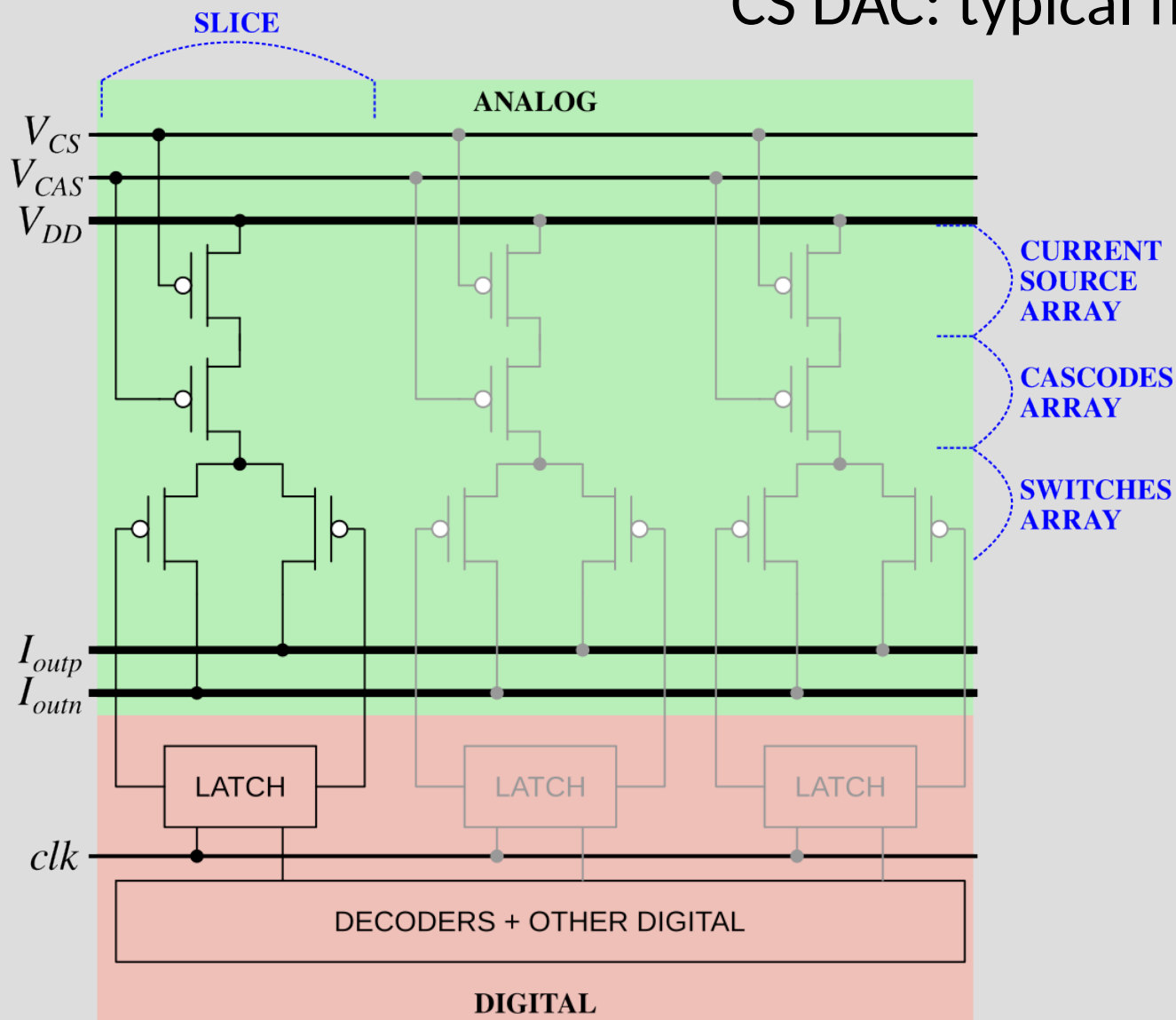

- Usually, **linear floorplan**: homologous devices (having the same functions) are put on the linear arrays for easier connection and compactness: **as the number of elements grow, gradients are important**
- The digital is in the lower part, separated from the quiet analog part
- Controlling signals cross the differential outputs (common-mode couplings)
- The clk line can be distributed in a tree-like structure to compensate for delays

CS DAC: gradients in large arrays

  

Nominally identical devices, under same bias conditions gives different currents due to:


- Manufacturing imperfections (e.g. threshold parameter spreading)
- Interconnection ohmic drops

Both results in current gradients

The switching order is decided by the digital logic

ERRORS DUE TO GRADIENTS ARE CORRELATED WITH THE DEVICE POSITION WITHIN THE ARRAY

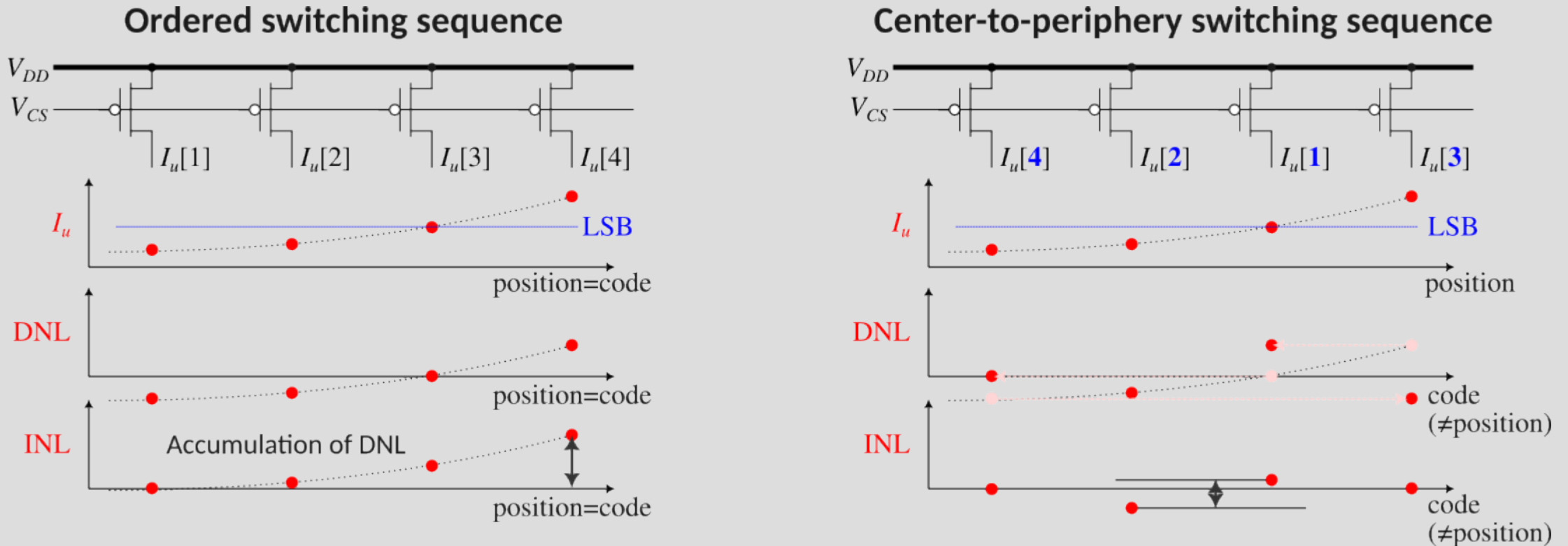CS DAC: switching sequence to brake the gradients



If we activate the CS in an orderly fashion: the gradient errors will accumulate \rightarrow large INL
If the activation sequence starts from the center devices and hops to the outer ones, DNL is almost the same (statistically), but INL error gets tighter
Resembles the **common centroid** layout technique

CS DAC: current copier


Static non linearity (INL/DNL) is main mechanism of distortion especially for medium-to-low bandwidth CS DACs. Intrinsic matching, implies (a) large cell area and (b) large V_{GS} voltages.

(a) In conflict with the need for small strays in high-speed applications;


(b) In conflict with low-voltage operation

Alternatively, mismatch is allowed to happen relaxing the other constraints, and it is corrected after fabrication with **dynamic calibration**

Copy phase

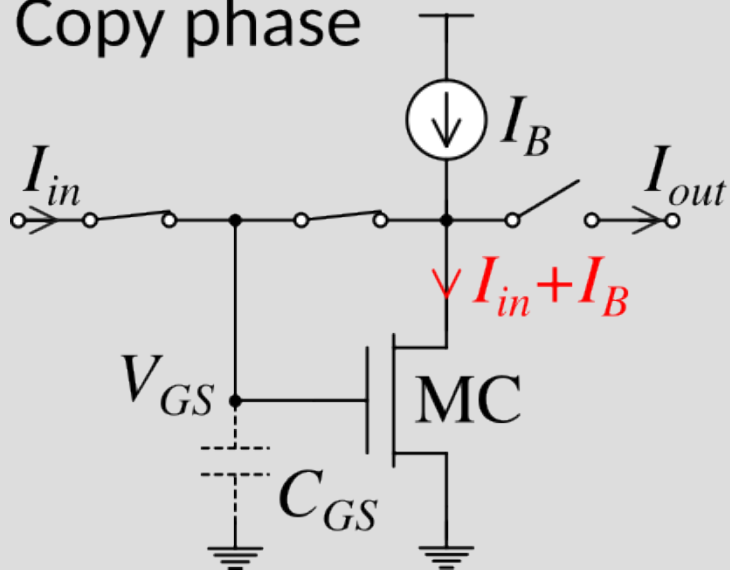

Hold phase

 


Current copier operation:

Copy phase: MC is diode connected, V_{GS} develops into the stray capacitance C_{GS} for a total current in MC of $I_{in} + I_B$

Hold phase: the V_{GS} is hold by the stray C_{GS} : $I_{out} = I_{in}$

A current copier behaves like a virtually **mismatch-free current mirror**: same device for input and output current
Beware charge injections and leakage

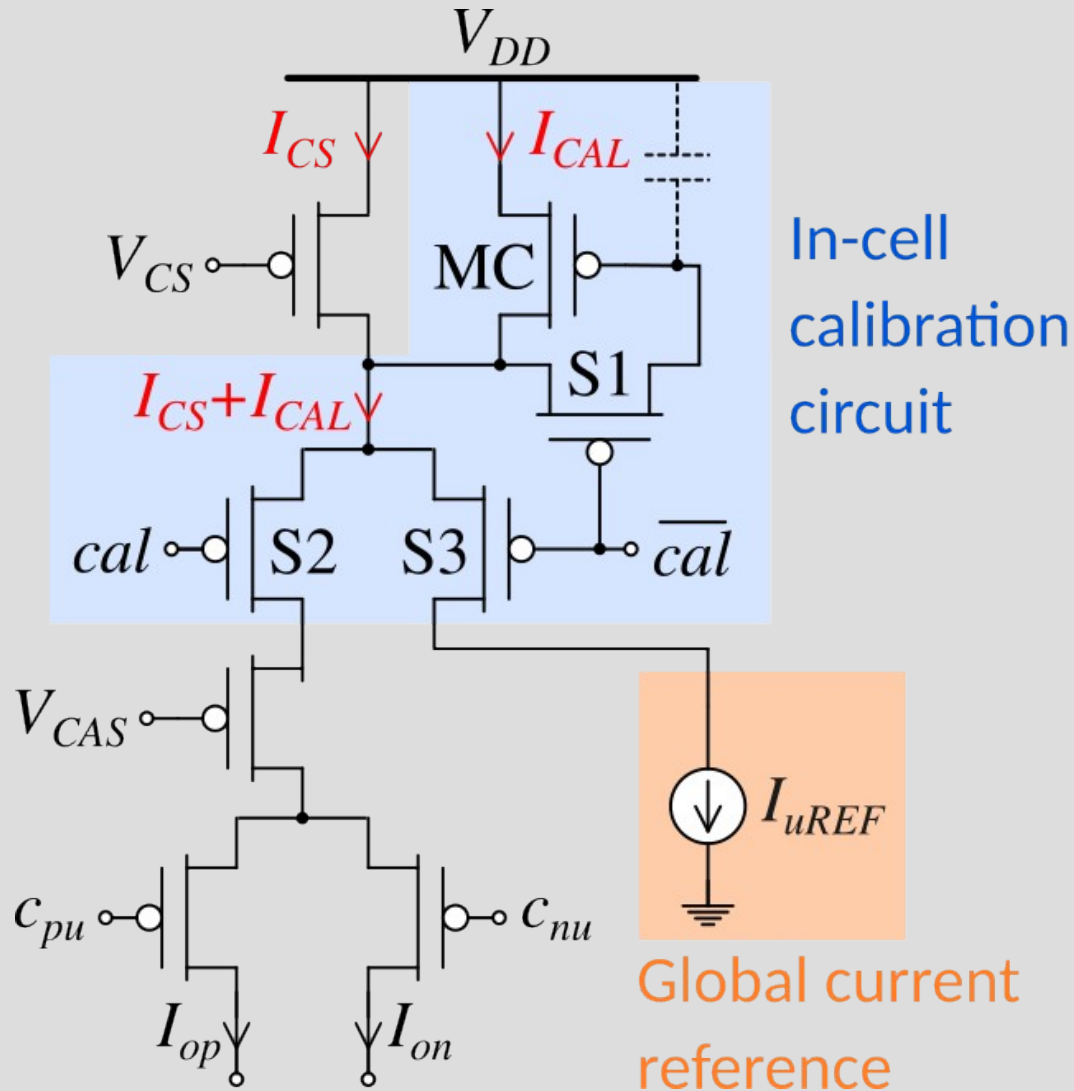CS DAC: calibration technique based on current copier



More switches (S1-S3) are added to the stack + a periodic calibration phase (*cal*) for each cell
 MC adds a bit more current. The total cell current is $I_{CS} + I_{CAL}$, typically MC supplies 10-20% of the nominal current

During calibration: $I_{CS} + I_{CAL} = I_{uREF}$

During normal operation: I_{CAL} is kept thanks to the “analog” memory

All the unary CS are calibrated once at time in a cyclic fashion (refresh and track for changes due to temp)

The calibration runs in the **background** while the rest of the DAC operates as usual. While calibrating the element is not available for normal operation, hence we need at least one redundant element in the array