
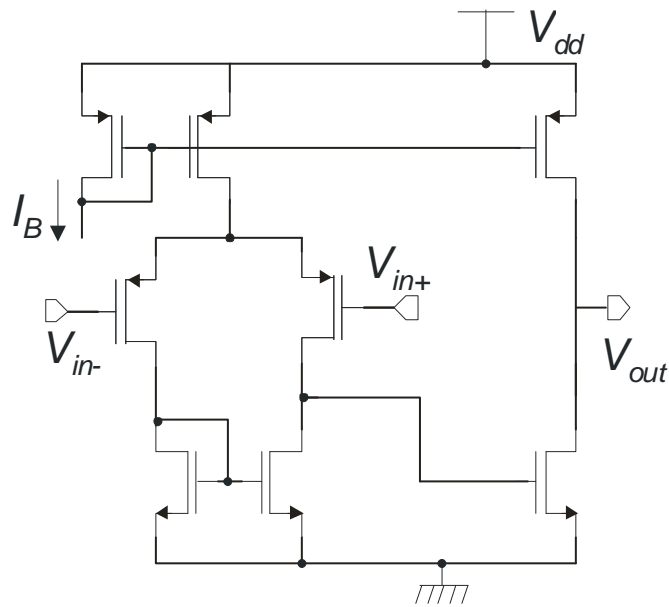


# Two stage – Class AB Op-Amp: principle

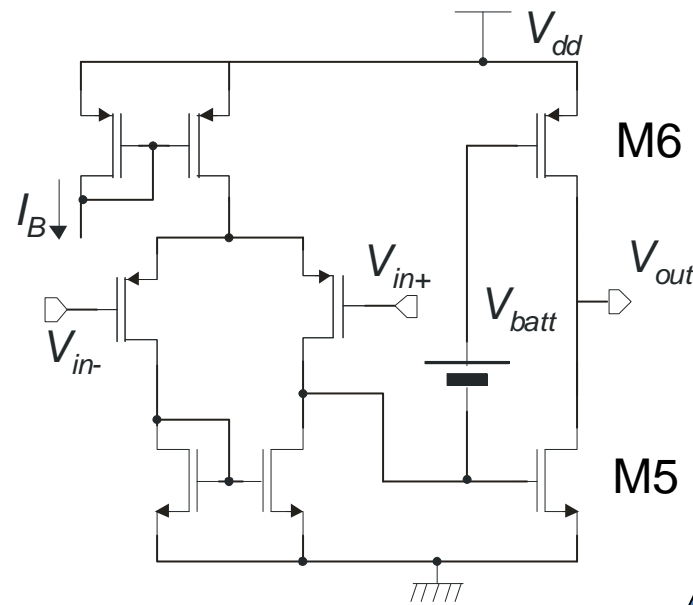

Class - A



Class - B

$$V_{GS6} = V_{DD} - V_{batt} - V_{GS5}$$


$I_{D5}$  depends only on  $I_B$  (bias current), while  $I_{D6}$  depends also on  $V_{DD}$



Very poor PSSR !

# Two stage – Class AB Op-Amp

## Solution 1: Bias Chain

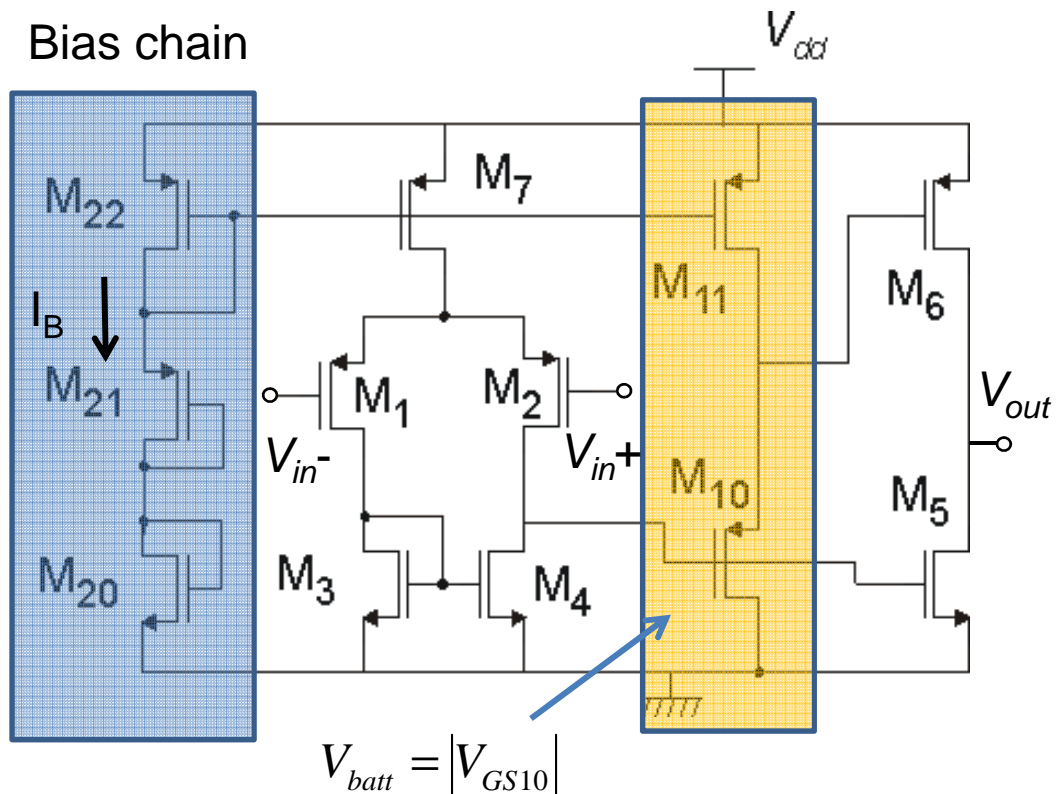

$$I_{D5} = I_{D3} \frac{\beta_5}{\beta_3} = \frac{I_B}{2} \frac{\beta_7}{\beta_{22}} \frac{\beta_5}{\beta_3}$$

By design:

$$\frac{\beta_{10}}{\beta_{21}} = \frac{\beta_{11}}{\beta_{22}} \Rightarrow V_{GS21} = V_{GS10}$$

$$\frac{\beta_3}{\beta_{20}} = \frac{1}{2} \frac{\beta_7}{\beta_{22}} \Rightarrow V_{GS3} = V_{GS20}$$

$$V_{GS6} = V_{GS22} \quad I_{D6} = I_B \frac{\beta_6}{\beta_{22}}$$


Solves:  $I_{D5}$  and  $I_{D6}$  matching is now  $V_{DD}$  independent

But: Limitations remain on the maximum output  $V_{GS}$

$$V_{GS5MAX} = V_{ic} + |V_{tp}| < V_{DD}$$

$$|V_{GS6}|_{MAX} = V_{DD} - V_{batt} < V_{DD}$$

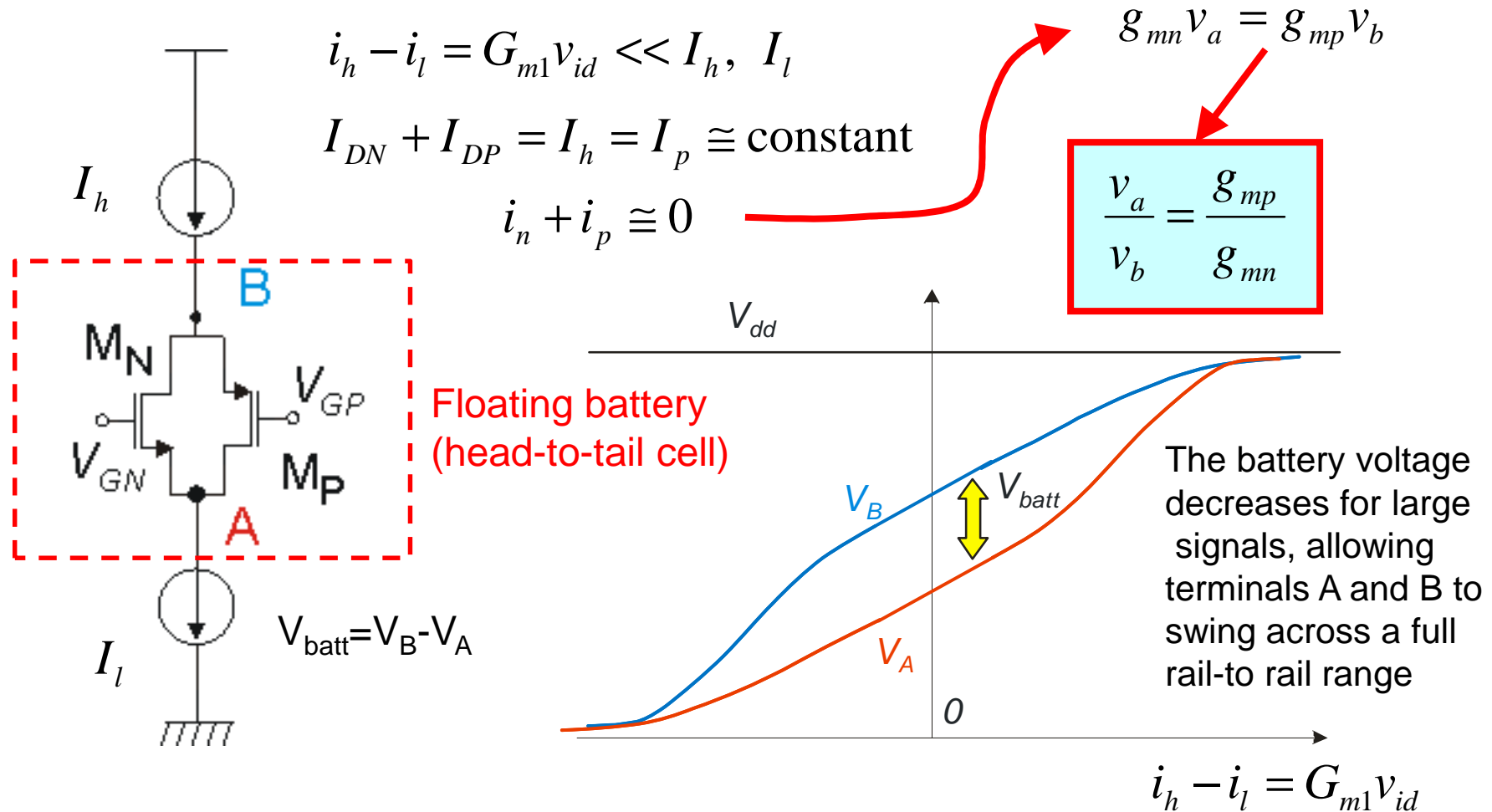
# Solution 2: Floating battery Head-to-Tail Mesh («Monticelli Cell»)




D. M. Monticelli, "A quad CMOS single-supply op amp with rail-to-rail output swing," IEEE J. Solid-State Circuits, vol. SC-21, pp. 1026-1034, Dec. 1986.
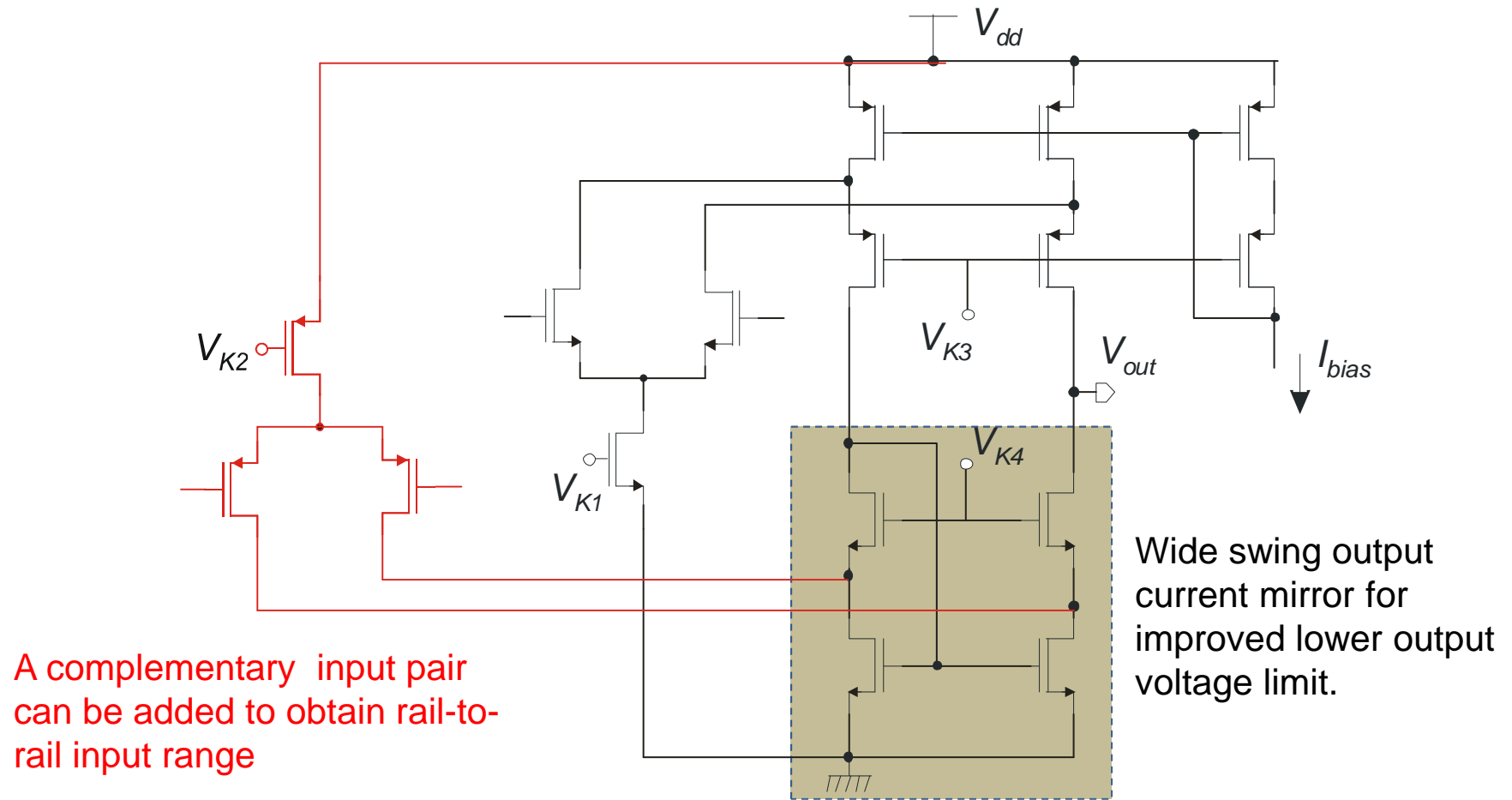
# First stage with folded cascode topology


The floating battery class-AB control is often combined with a first stage with folded cascode structure. This stage provides increased gain and can be easily equipped with complementary input pairs to obtain rail-to-rail input range


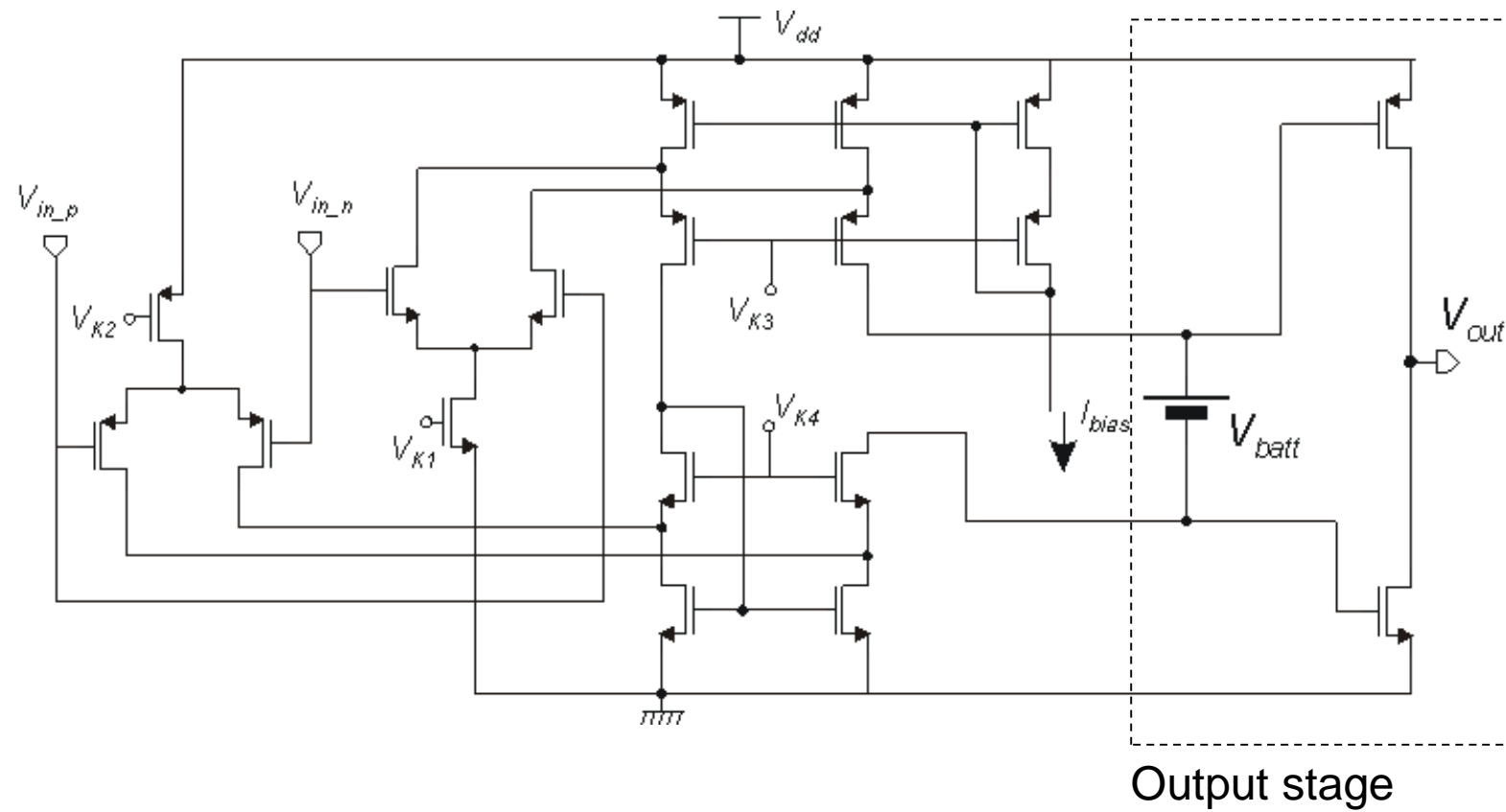
# Two stage opamp with folded cascode input stage


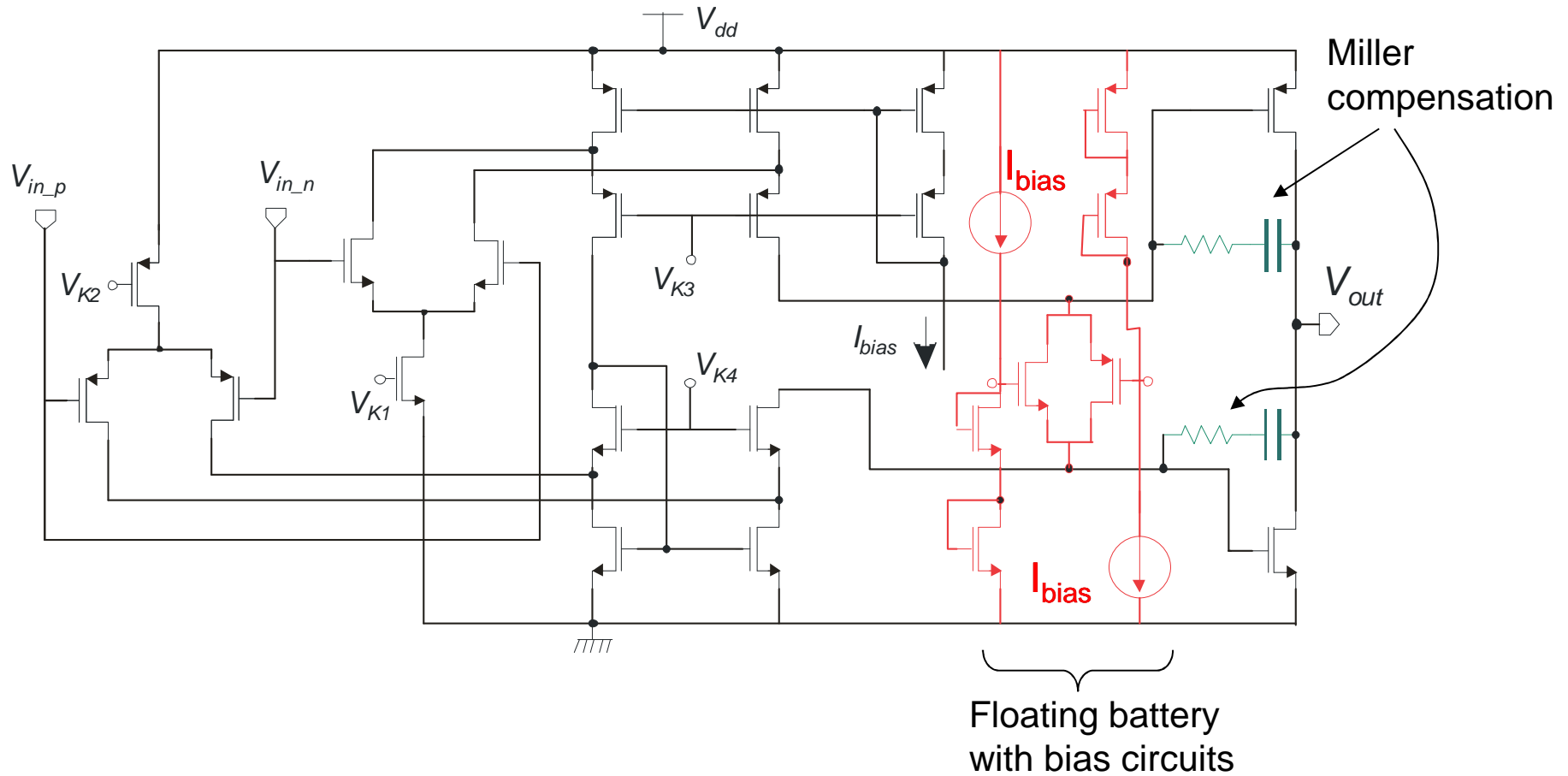
# Two stage opamp with folded cascode input stage and floating battery



R. Hogervorst, J.P. Tero, R. G. H. Eschauzier, and J. H. Huijsing, "A Compact Power-Efficient 3 V CMOS Rail-to-Rail Input/Output Operational Amplifier for VLSI Cell Libraries", IEEE J. SOLID-STATE CIRCUITS, vol. 29, 1994