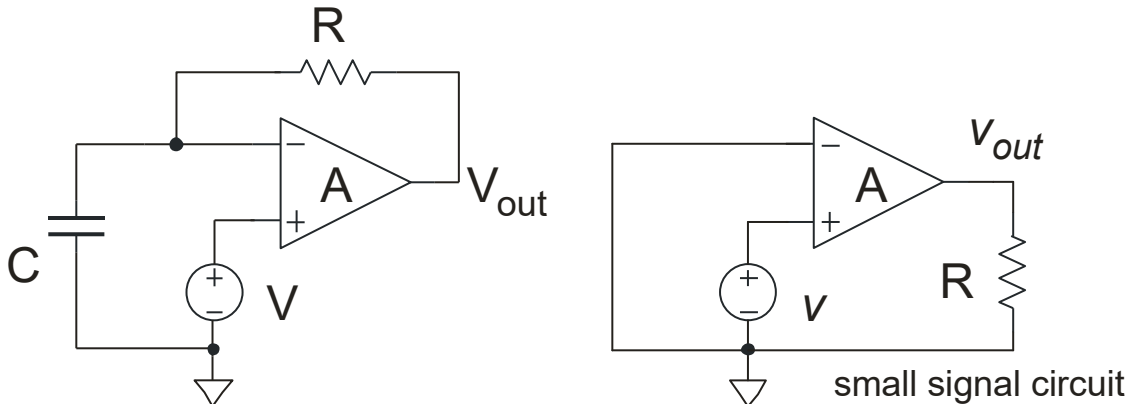


**Simple configuration for simulating the frequency response of Op-amps**



Hypothesis: Input bias currents =0 (Valid approximation in CMOS amplifiers)

Operating point:  $V_{out}=V$ . The d.c. feedback provided by R self-bias the op-amp regardless of possible systematic input offsets. Choose a V value that belongs to both the input (common mode) and output ranges. In this way the amplifier is self-biased in a valid operating point.

The amplifier open loop frequency response is simply given by the  $v_{out}/v$  transfer function.

Demonstration:

$$A_L = \frac{v_{out}}{v} = \frac{A}{1 - \beta A}$$

Where:

$$\beta = -\frac{1}{1 + j \frac{f}{f_{p\beta}}} \quad f_{p\beta} = \frac{1}{2\pi RC}$$

If:  $|\beta A| \ll 1 \Rightarrow A_L \cong A$

Note that:

$$|\beta A| \leq \frac{A_0}{\sqrt{1 + \left(\frac{f}{f_{p\beta}}\right)^2}} < \left(\frac{A_0 f_{p\beta}}{f}\right)$$

$$f_{p\beta} \ll \frac{f_{MIN}}{A_0}$$

**Example:**  $R=1G\Omega$ ,  $C=1F$  (1 Farad !)  $\rightarrow f_{p\beta}=1.6 \times 10^{-10}$  Hz

With  $A_0=10^5$  : our analysis is valid for  $f \gg A_0 f_{p\beta}=1.6 \times 10^{-5}$  Hz.

An additional condition is clearly  $R \gg R_{out}$ , where  $R_{out}$  is the open loop output resistance of the amplifier.