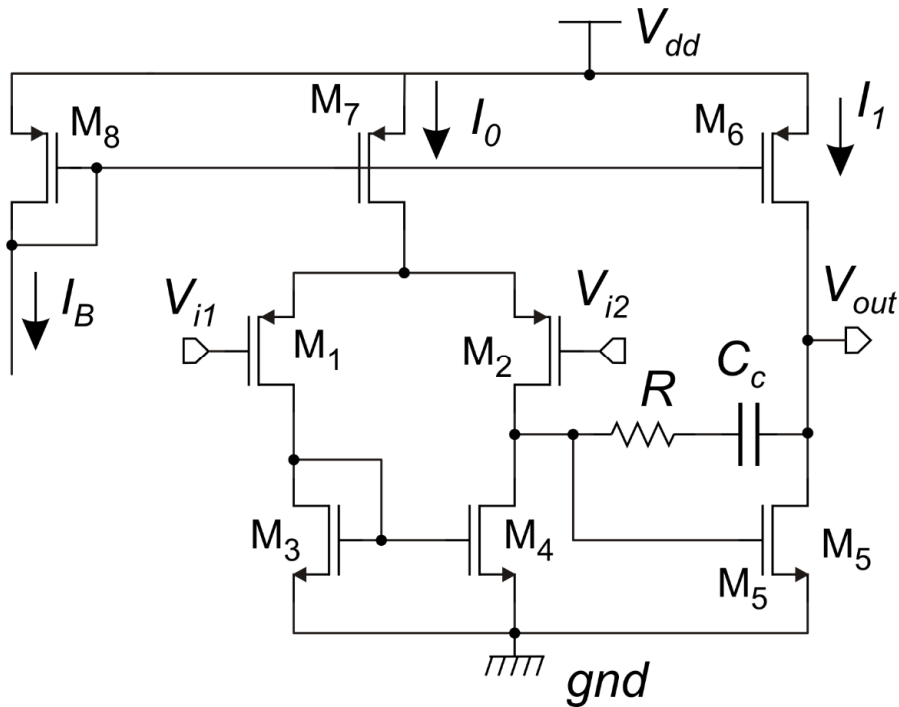


# Exercise: Opamp Design

## Process parameters



Parametro	n-MOS	p-MOS
$\mu_n \text{Cox}, \mu_p \text{Cox}$	$240 \times 10^{-6} \text{ A/V}^2$	$50 \times 10^{-6} \text{ A/V}^2$
$V_{tn}, V_{tp}$	0.43 V	-0.56 V
$\gamma$ (effetto body)	$0.44 \text{ V}^{1/2}$	$0.59 \text{ V}^{1/2}$
$k_\lambda$	$50 \text{ V}/\mu\text{m}$	$50 \text{ V}/\mu\text{m}$
$\alpha$ (coeff. termico della Vt)	-1 mV / °C	1 mV / °C
$N_{fn}, N_{fp}$ (fattore rumore flicker)	$6 \times 10^{-10} \text{ V}^2 \mu\text{m}^2$	$2 \times 10^{-10} \text{ V}^2 \mu\text{m}^2$
$C_{vt}$ (matching Vt)	$8.5 \text{ mV} \cdot \mu\text{m}$	$8.5 \text{ mV} \cdot \mu\text{m}$
$C_\beta$ (matching beta)	$0.03 \mu\text{m}$	$0.03 \mu\text{m}$
$C_{ox}$	$6.2 \text{ fF}/\mu\text{m}^2$	$6.2 \text{ fF}/\mu\text{m}^2$
$L_c$ (lunghezza minima D/S)	1.2 $\mu\text{m}$	1.2 $\mu\text{m}$
$C_j$	$1.8 \text{ fF}/\mu\text{m}^2$	$1.8 \text{ fF}/\mu\text{m}^2$
$C_{gdo}$	$0.6 \text{ fF}/\mu\text{m}$	$0.6 \text{ fF}/\mu\text{m}$
$t_{ox}$	5.6 nm	5.6 nm

## Specifications

- An offset voltage (absolute value) smaller than **3 mV**
- A GBW of **10 MHz** for a load capacitance ( $C_L$ ) up to **10 pF**.
- A phase margin around **70°** in unity gain configuration

## Offset specification

- An offset voltage (absolute value) smaller than 3 mV

$$3\sigma_{vio} = 3 \text{ mV} \Rightarrow \sigma_{vio} = 1 \text{ mV}$$

$$\sigma_{vio}^2 = \frac{A}{W_1 L_1} + \frac{B}{W_3 L_3} \quad A = C_{Vtp}^2 + \left[ \frac{(V_{GS} - V_t)_1}{2} C_{\beta p} \right]^2 \quad B = F^2 C_{Vtn}^2 + \left[ \frac{(V_{GS} - V_t)_1}{2} C_{\beta n} \right]^2$$

$$C_{Vtp} = C_{Vtn} = 8.5 \text{ mV} \cdot \mu\text{m}$$

$$C_{\beta p} = C_{\beta n} = 0.03 \mu\text{m}$$

In order to reduce A and B and then the total area, we choose:


$$|V_{GS} - V_t|_1 = 100 \text{ mV}$$

$$F = \frac{g_{m3}}{g_{m1}} = \frac{|V_{GS} - V_t|_1}{(V_{GS} - V_t)_3} = \frac{1}{3}$$

## Offset specification

$$|V_{GS} - V_t|_1 = 100 \text{ mV}$$

$$F = \frac{g_{m3}}{g_{m1}} = \frac{|V_{GS} - V_t|_1}{(V_{GS} - V_t)_3} = \frac{1}{3}$$

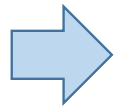

$$(V_{GS} - V_t)_3 = (V_{GS} - V_t)_5 = 300 \text{ mV}$$

$$A = C_{Vtp}^2 + \left[ \frac{(V_{GS} - V_t)_1}{2} C_{\beta p} \right]^2 \quad B = (FC_{Vtm})^2 + \left[ \frac{(V_{GS} - V_t)_1}{2} C_{\beta n} \right]^2$$

$$C_{Vtp} = C_{Vtm} = 8.5 \text{ mV} \cdot \mu\text{m}$$

$$FC_{Vtm} = 2.83 \text{ mV} \cdot \mu\text{m}$$

$$C_{\beta p} = C_{\beta n} = 0.03 \mu\text{m}$$

$$\left[ \frac{|V_{GS} - V_t|_1}{2} C_{\beta p} \right] = \left[ \frac{|V_{GS} - V_t|_1}{2} C_{\beta n} \right] = 1.5 \text{ mV} \cdot \mu\text{m}$$

$$A = 74.5 \times 10^{-6} \text{ V}^2 \mu\text{m}^2$$

$$B = 10.3 \times 10^{-6} \text{ V}^2 \mu\text{m}^2$$

## Offset specification

$$A = 74.5 \times 10^{-6} \text{ V}^2 \mu\text{m}^2$$

$$B = 10.3 \times 10^{-6} \text{ V}^2 \mu\text{m}^2$$

Optimum area distribution between differential pair and current mirror

$$a_{opt} = \left( \frac{W_3 L_3}{W_1 L_1} \right)_{opt} = \sqrt{\frac{B}{A}} = 0.37$$

$$W_1 L_1 = \frac{1}{\sigma_{vio}^2} \left( A + \frac{B}{a_{opt}} \right) \cong 102 \mu\text{m}^2$$

$$W_3 L_3 = a_{opt} W_1 L_1 \cong 38 \mu\text{m}^2$$


With only the offset specification, we cannot determine other amplifier parameters.

Adding the GBW - phase margin specification we can go further into the amplifier design
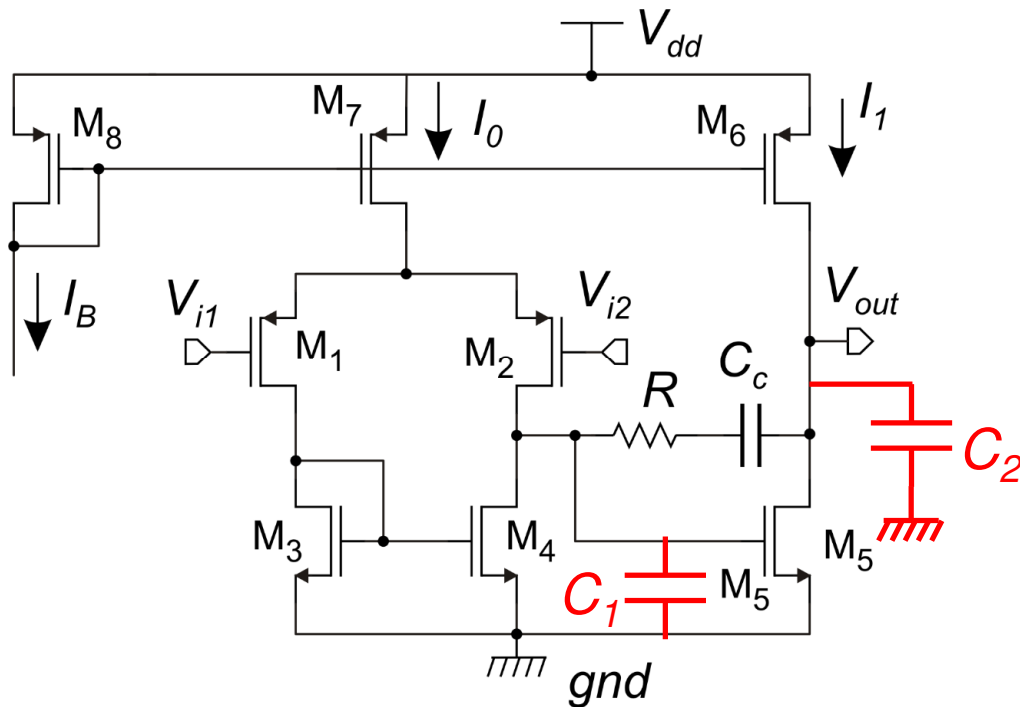
## GBW and phase margin

- A GBW of 10 MHz for a load capacitance ( $C_L$ ) up to 10 pF.
- A phase margin around  $70^\circ$  in unity gain configuration

$$\Rightarrow \sigma = \frac{\omega_2}{\omega_0} = 3$$



$$\text{Hypotheses: } \begin{cases} C_1 \ll C_c, C_2 \\ C_2 = C'_2 + C_L \cong C_L \end{cases}$$

$$g_{m5} = 2\pi\sigma C_L \cdot GBW \cong 1.88 \text{ mS}$$

$$g_{m1} = \frac{1}{\sigma} \frac{C_c}{C_L} g_{m5}$$

Using the rule of thumb  $C_c = C_L$ :

$$g_{m1} = \frac{g_{m5}}{\sigma} \cong 0.63 \text{ mS}$$

## Calculation of device aspect ratios

$$g_{m5} \cong 1.88 \text{ mS} \quad g_{m1} \cong 0.63 \text{ mS}$$

$$g_{m5} = \mu_n C_{OX} \frac{W_5}{L_5} (V_{GS} - V_t)_5 \Rightarrow \frac{W_5}{L_5} = \frac{g_{m5}}{\mu_n C_{OX} (V_{GS} - V_t)_5} = 26.1$$

$$\mu_n C_{ox} = 240 \times 10^{-6} \text{ A/V}^2 \quad 300 \text{ mV}$$

$$\frac{W_1}{L_1} = \frac{g_{m1}}{\mu_p C_{OX} (V_{GS} - V_t)_1} = 126$$

$$\mu_p C_{ox} = 50 \times 10^{-6} \text{ A/V}^2 \quad 100 \text{ mV}$$

$$g_{m3} = F \cdot g_{m1} = 0.21 \text{ } \mu\text{S} \quad \frac{W_3}{L_3} = \frac{g_{m3}}{\mu_n C_{OX} (V_{GS} - V_t)_3} = 2.92 \quad 300 \text{ mV}$$

## Determination of M1, M3 and M5 size

From offset specs

$$\left. \begin{array}{l} W_1 L_1 = 102 \mu\text{m}^2 \\ \frac{W_1}{L_1} = 126 \end{array} \right\} \Rightarrow W_1 = \sqrt{W_1 L_1 \cdot \frac{W_1}{L_1}} \cong 114 \mu\text{m} \quad L_1 = W_1 \cdot \left( \frac{W_1}{L_1} \right)^{-1} \cong 0.9 \mu\text{m}$$

From offset specs

$$\left. \begin{array}{l} W_3 L_3 = 38 \mu\text{m}^2 \\ \frac{W_3}{L_3} = 2.92 \end{array} \right\} \Rightarrow W_3 = \sqrt{W_3 L_3 \cdot \frac{W_3}{L_3}} \cong 10.5 \mu\text{m} \quad L_1 = W_3 \cdot \left( \frac{W_3}{L_3} \right)^{-1} \cong 3.6 \mu\text{m}$$

From  $L_5=L_3$  arbitrary constraint

$$\left. \begin{array}{l} L_5 = 3.6 \mu\text{m} \\ \frac{W_5}{L_5} = 26.1 \end{array} \right\} \Rightarrow W_5 \cong 94 \mu\text{m}$$

## Determination of M6 and M7 size

$$I_{D6} = I_{D5}$$

$$|V_{GS} - V_t|_6 = (V_{GS} - V_t)_5 \quad (\text{Arbitrary constraint})$$

$$I_D = \frac{\beta}{2} (V_{GS} - V_t)^2$$

$$\beta_6 = \beta_5$$

$$\mu_p C_{OX} \frac{W_6}{L_6} = \mu_n C_{OX} \frac{W_5}{L_5} \Rightarrow \frac{W_6}{L_6} = \frac{\mu_n C_{OX}}{\mu_p C_{OX}} \frac{W_5}{L_5} \cong 125$$

In order to introduce no penalization in terms of DC gain we can set:

$$L_6 = L_5 = 3.6 \mu\text{m}$$

$$L_7 = L_6 = 3.6 \mu\text{m} \quad (\text{Arbitrary constraint})$$


$$\frac{\beta_6}{\beta_7} = \frac{1}{2} \frac{\beta_5}{\beta_3} \Rightarrow \frac{\frac{W_6}{L_6}}{\frac{W_7}{L_7}} = \frac{1}{2} \frac{\frac{W_5}{L_5}}{\frac{W_3}{L_3}} \Rightarrow \frac{W_7}{L_7} = 2 \frac{W_6}{L_6} \frac{L_3}{W_5} \cong 28$$

$$W_6 = L_6 \left( \frac{W_6}{L_6} \right) = 450 \mu\text{m}$$

$$W_7 = L_7 \left( \frac{W_7}{L_7} \right) = 101 \mu\text{m}$$



## Bias and supply currents

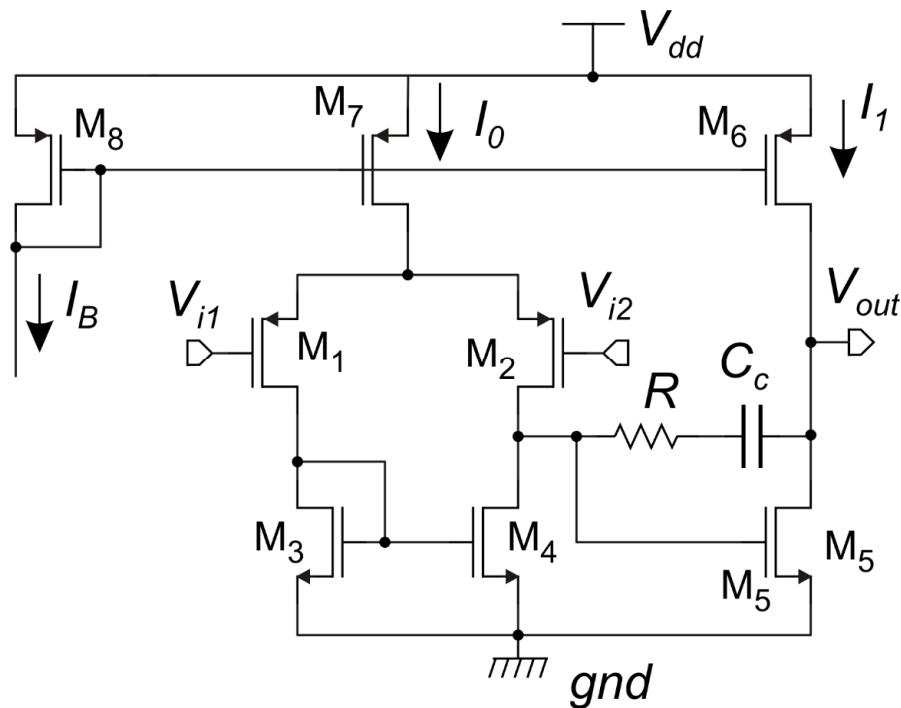


$$I_0 = 2I_{D1} \cong 2g_{m1}V_{TE1} = 2g_{m1} \frac{(V_{GS} - V_t)_1}{2} \cong 63 \mu\text{A}$$

$$I_1 \cong g_{m5}V_{TE5} = g_{m5} \frac{(V_{GS} - V_t)_5}{2} \cong 282 \mu\text{A}$$

In order to simplify the design:

$$I_B = I_0 = 63 \mu\text{A} \Rightarrow M8=M7$$

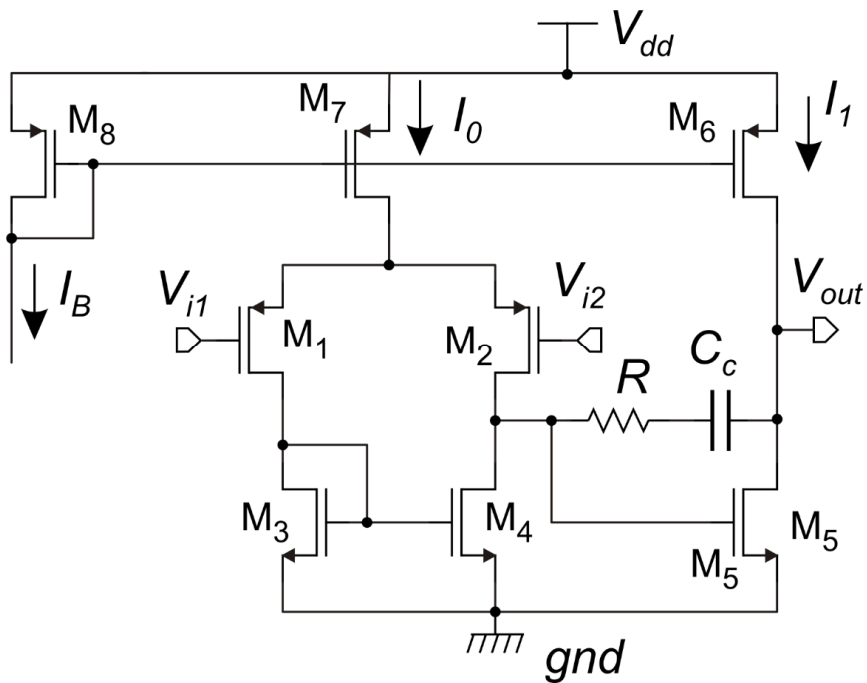Total supply current (including  $I_B$ ):  $I_0 + I_1 + I_B \cong 408 \mu\text{A}$



## Final Design

$$V_{dd} = 2.5 \text{ V}$$

$$C_C = C_L = 10 \text{ pF}$$


$$R_C = \frac{1}{G_{m2}} = \frac{1}{g_{m5}} = 532 \text{ } \Omega$$

Final component table

	W ( $\mu\text{m}$ )	L ( $\mu\text{m}$ )
M <sub>1</sub> , M <sub>2</sub>	114	0.9
M <sub>3</sub> , M <sub>4</sub>	10.5	3.6
M <sub>5</sub>	94	3.6
M <sub>6</sub>	450	3.6

M <sub>7</sub>	101	3.6
M <sub>8</sub>	101	3.6
R	532 $\Omega$	
C <sub>C</sub>	10 pF	
I <sub>B</sub>	63 $\mu\text{A}$	

## Check of initial hypothesis validity

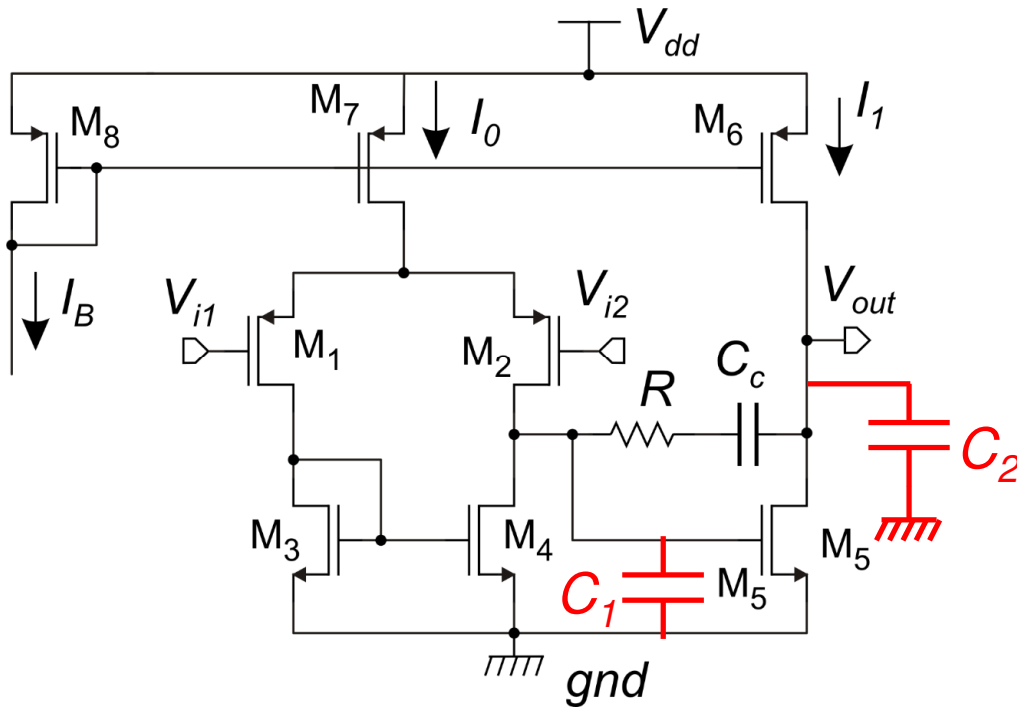

Hypotheses: 
$$\begin{cases} \underline{C_1 \ll C_c, C_2 = 10 \text{ pF}} \\ C_2 = \underline{C'_2} + C_L \cong C_L = 10 \text{ pF} \\ \underline{C'_2 \ll C_L = 10 \text{ pF}} \end{cases}$$

$$C_1 = C_{GS5} + C_{DB2} + C_{DB4}$$

$$C_{GS5} = \frac{2}{3} C_{OX} W_5 L_5 \cong 1.4 \text{ pF}$$

$$C_{DB2} = C_{Jp} L_C W_2 \cong 0.246 \text{ pF}$$

$$C_{DB4} = C_{Jn} L_C W_4 \cong 0.023 \text{ pF}$$

$$\Rightarrow C_1 \cong 1.67 \text{ pF}$$

$$C'_2 = C_{DB5} + C_{DB6} = C_{Jn} L_C W_5 + C_{Jp} L_C W_6 \cong 1.17 \text{ pF}$$

$$C_{OX} = 6.2 \text{ fF}/\mu\text{m}^2$$

$$C_{Jn} = C_{Jp} = 1.8 \text{ fF}/\mu\text{m}^2$$

$$L_C = 1.2 \mu\text{m} \longrightarrow C_{Jn,p} L_C = 2.16 \text{ fF}/\mu\text{m}$$

The hypotheses are acceptable

## Other performance parameters

$$S_{vth} \cong 2 \frac{8}{3} kT \frac{1}{g_{m1}} (1+F) \cong 4.5 \times 10^{-17} \text{ V}^2 / \text{Hz} \quad ( 6.7 \text{ nV} / \sqrt{\text{Hz}} )$$

$$N_{fn} = 6 \times 10^{-10} \text{ V}^2 \mu\text{m}^2 \quad N_{fp} = 2 \times 10^{-10} \text{ V}^2 \mu\text{m}^2$$

$$k_F = 2 \left( \frac{N_{fp}}{W_1 L_1} + F^2 \frac{N_{fn}}{W_3 L_3} \right) \cong 7.42 \times 10^{-12} \text{ V}^2$$

Slew rate:


$$s_R = \frac{I_0}{C_c} = 6.3 \text{ V}/\mu\text{s}$$

Flicker corner frequency

$$\text{at } f_k \Rightarrow S_{vF} = \frac{k_F}{f} = S_{vTh}$$

$$f_k = \frac{k_F}{S_{vTh}} \cong 165 \text{ kHz}$$

## Test-Bench for frequency response

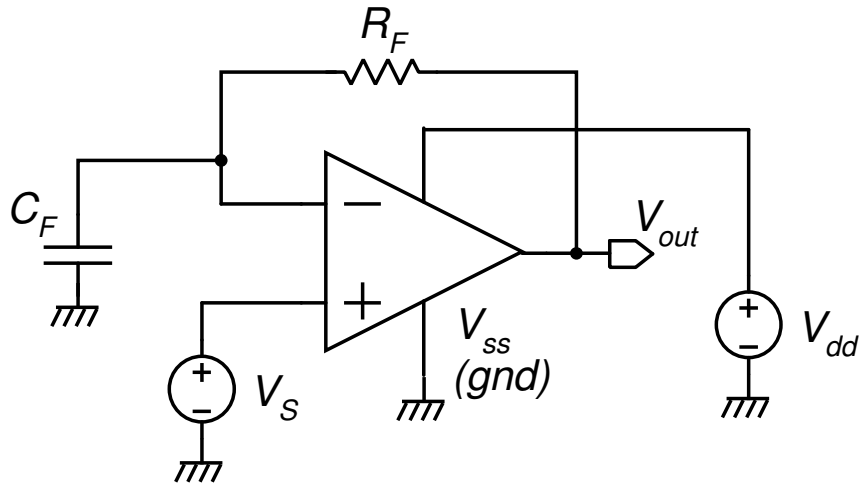


In DC:  $V_{out} = V_S$ . Setting a proper DC value for  $V_S$  we can set a correct operating point (e.g.  $V_S = V_{DD}/2$ )

$$R_F = 1 \text{ G}\Omega$$

Example:  $C_F = 1 \text{ F}$

$$\Rightarrow f_{p\beta} = 1.59 \times 10^{-10} \text{ Hz}$$


if, for all frequencies of interest,  $|\beta A| \ll 1$ , then:  
we can consider that the feedback is not present, thus in terms of small signal:

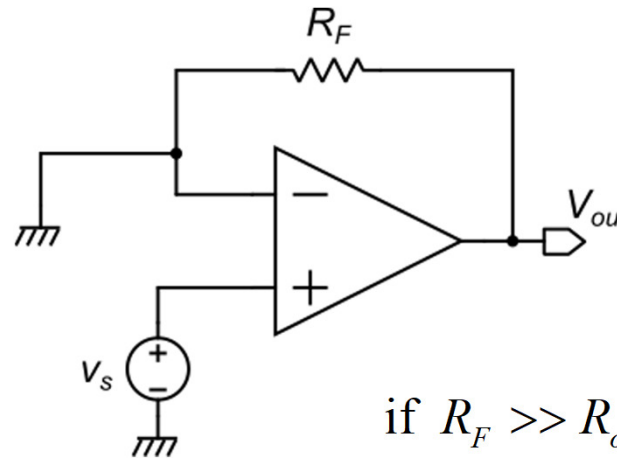


$$\begin{aligned} &\text{if } R_F \gg R_{out} \\ &\text{and } A_C \text{ is } \ll A_D \end{aligned} \Rightarrow \frac{v_{out}}{v_s} \cong A_d \quad (A)$$
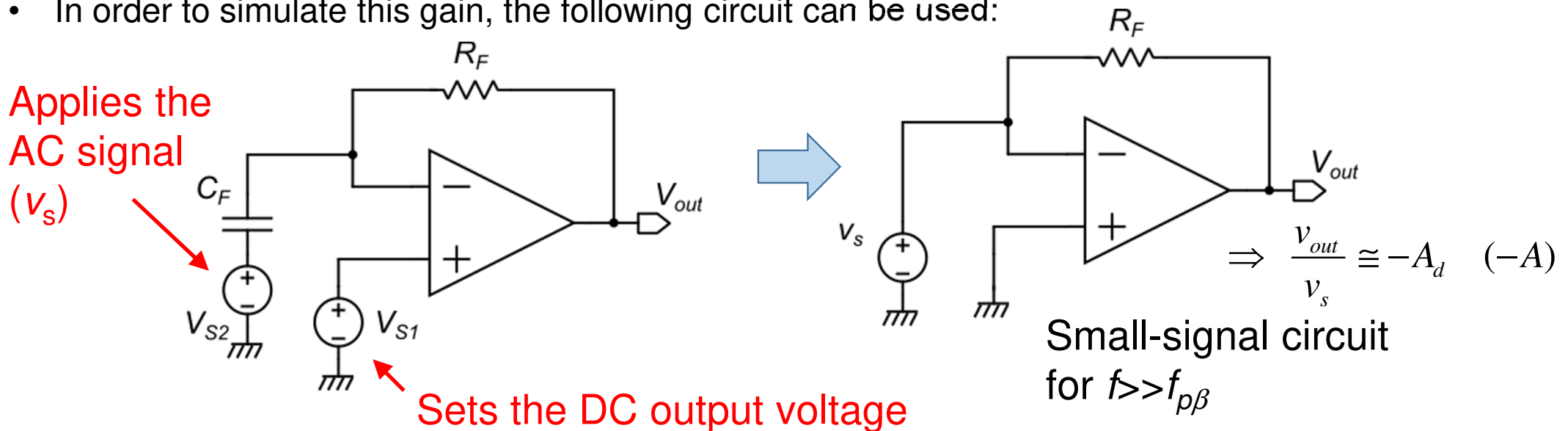
## Amplification from the inverting terminal to the output

- The open-loop gain that we have found with the testbench of previous slide was not strictly the differential mode gain.
- That was the gain from the non-inverting input to the output, which is actually a combination of the differential mode and common mode gains.
- Often, the gain that matters for the stability, is the gain from the **inverting input** and the output, since in most closed-loop circuits the feedback signal stimulates only the inverting input.
- In order to simulate this gain, the following circuit can be used:


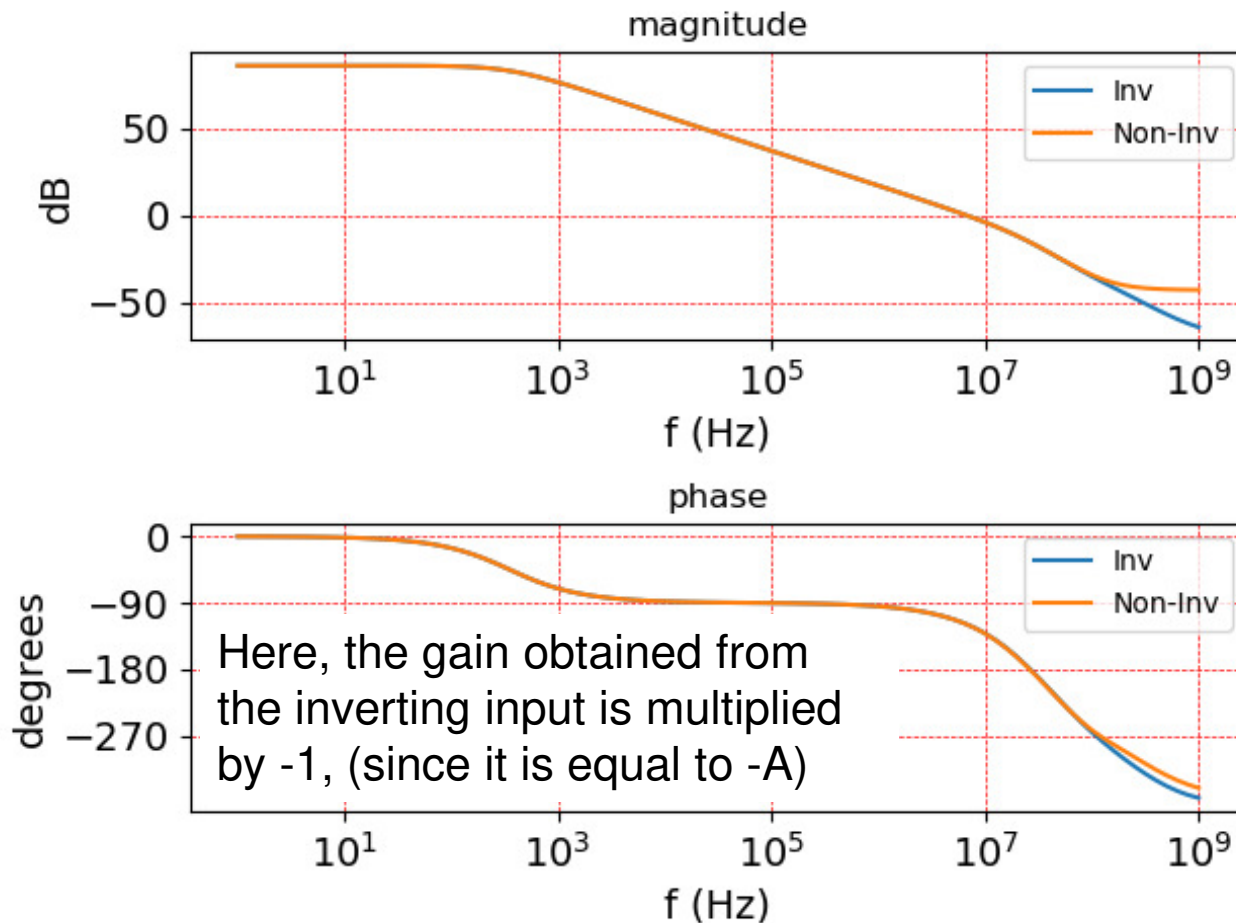
## Difference between the gains measured from the inverting and non-inverting terminals for the op-amp that we have designed (from simulations)



The difference occurs only at frequencies  $\gg f_0$ . Then, to study the stability, we can use one or the other gain, indifferently

The difference is due to the different impact of the first-stage singularities (mirror pole, tail pole)

For different designs (different topologies, different specifications, etc.), the differences may be more important.