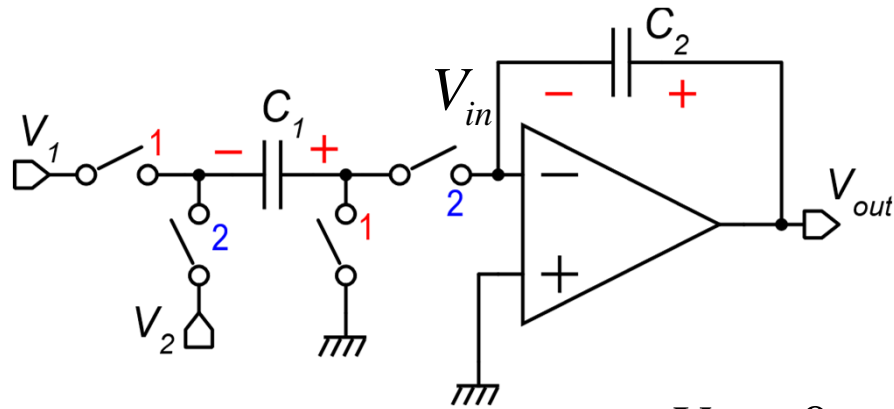


Parasitic insensitive SC integrator




$$V_{in} = 0$$

Simplifying hypotheses: $V_{out} = V_{C2}$


- No offset / noise
- Perfect virtual short circuit
- No charge injection

Phase 1

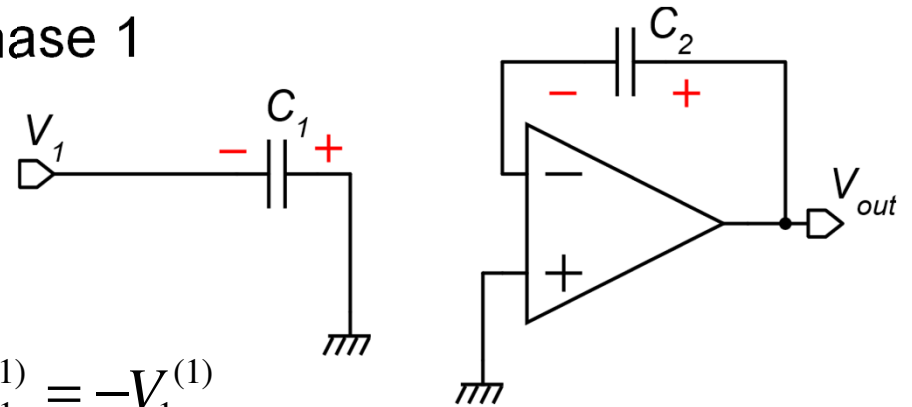

$$V_{C1}^{(1)} = -V_1^{(1)}$$

$$V_{C2}^{(1)} = V_{C2}^{(2-prev)}$$

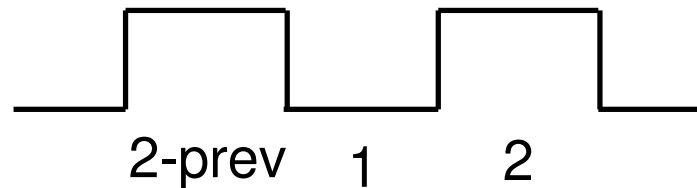

Parasitic insensitive SC integrator


Phase 2 $V_{C1}^{(2)} = -V_2^{(2)}$

$$V_{out}^{(2)} = V_{C2}^{(2)} = V_{C2}^{(1)} + \frac{\Delta Q_{C2}}{C_2} = V_{out}^{(2-prev)} + \frac{\Delta Q_{C2}}{C_2}$$


$$\Delta Q_{C2} = \Delta Q_{C1} = C_1 (V_{C1}^{(2)} - V_{C1}^{(1)})$$

$$\Delta Q_{C2} = C_1 [-V_2^{(2)} - (-V_1^{(1)})] = C_1 (V_1^{(1)} - V_2^{(2)})$$
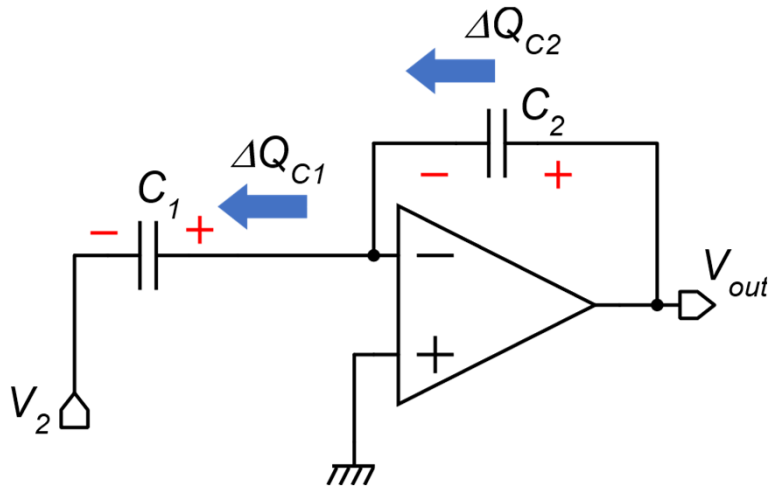
$$V_{out}^{(2)} = V_{out}^{(2-prev)} + \frac{C_1}{C_2} (V_1^{(1)} - V_2^{(2)})$$




Parasitic insensitive SC integrator

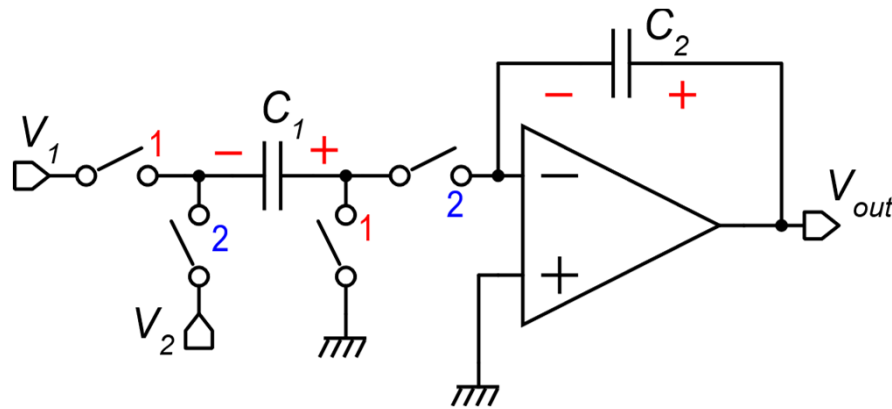

$$V_{out}^{(2)} = V_{out}^{(2-prev)} + \frac{C_1}{C_2} (V_1^{(1)} - V_2^{(2)})$$

If we consider that V_1 is sampled at the end of phase 2 and maintained across phase 1:
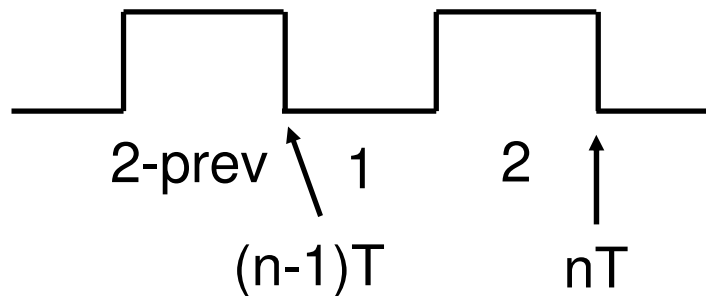
$$V_{out}^{(2)} = V_{out}^{(2-prev)} + \frac{C_1}{C_2} (V_1^{(2-prev)} - V_2^{(2)})$$



$$V_{out}(n) = V_{out}(n-1) + \frac{C_1}{C_2} [V_1(n-1) - V_2(n)]$$


Block diagram and Z-transform

$$V_{out}(n) = V_{out}(n-1) + \frac{C_1}{C_2} [V_1(n-1) - V_2(n)]$$

Z-transform

$$V_{out}(z) = V_{out}(z) z^{-1} + \frac{C_1}{C_2} [V_1(z) z^{-1} - V_2(z)]$$

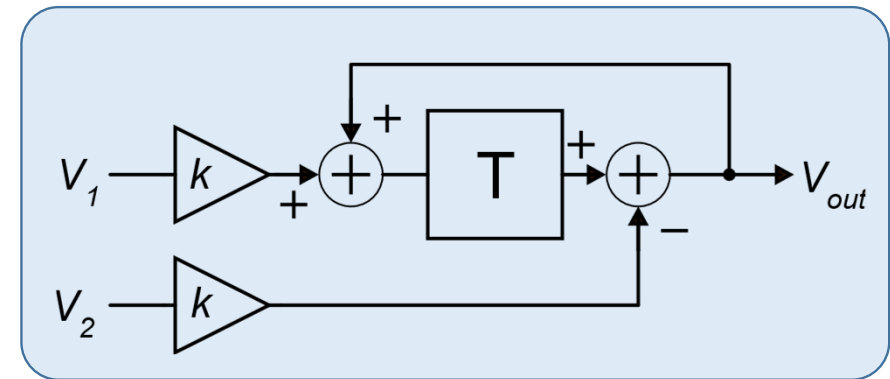
$$V_{out}(z) = + \frac{C_1}{C_2} \frac{z^{-1}}{1 - z^{-1}} V_1(z) - \frac{C_1}{C_2} \frac{1}{1 - z^{-1}} V_2(z)$$



Equivalent block diagram

Frequency response

Integrators compared

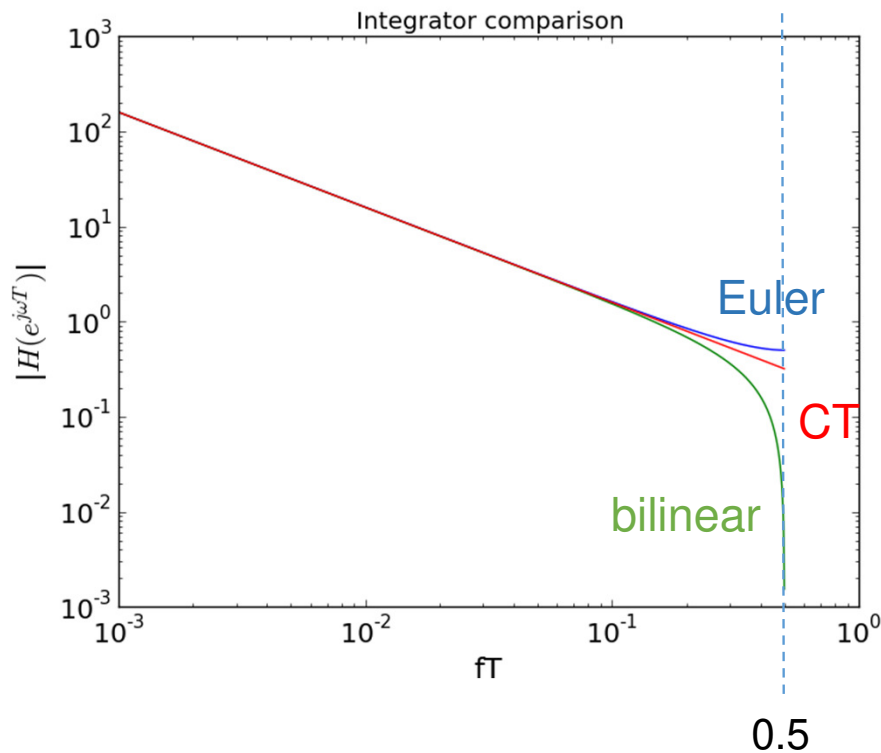

CT: continuous time integrator

$$V_{out}(z) = +\frac{C_1}{C_2} \frac{z^{-1}}{1-z^{-1}} V_1(z) - \frac{C_1}{C_2} \frac{1}{1-z^{-1}} V_2(z)$$

$$H_1(z) = \left. \frac{V_{out}(z)}{V_1(z)} \right|_{V_2=0} = \frac{C_1}{C_2} \frac{z^{-1}}{1-z^{-1}} \quad \begin{array}{l} \text{Forward} \\ \text{Euler} \\ \text{Integrator} \end{array}$$

$$H_2(z) = \left. \frac{V_{out}(z)}{V_2(z)} \right|_{V_1=0} = -\frac{C_1}{C_2} \frac{1}{1-z^{-1}} \quad \begin{array}{l} \text{Backward} \\ \text{Euler} \\ \text{Integrator} \end{array}$$

$$\left| H_1(e^{j\omega T}) \right| = \left| H_2(e^{j\omega T}) \right|$$