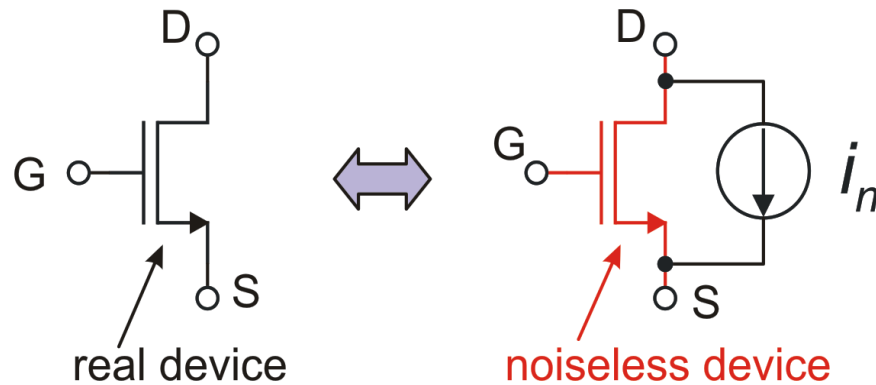



Noise in active devices

MOSFETs



This noise schematization is valid up to a frequency that depends on the process and device length. Generally, for integrated MOSFETs, it is possible to use this single-source model up to frequencies of several hundred MHz

Mosfet Thermal noise

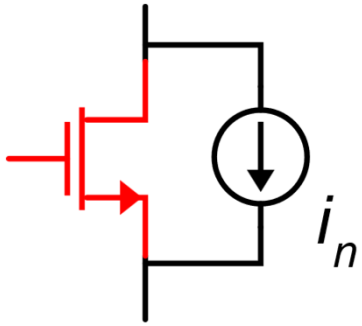

Being frequency independent, thermal noise is the origin of the **broad-band** noise in MOSFETs

$$S_{In-T}(f) = \frac{8}{3} kT g_m \cdot m$$

$$m = 1 + \frac{g_{mB}}{g_m}$$


Typically:

$$1 < m < 1.5$$

A more general expression:


$$S_{In-T}(f) = \gamma_n \underline{4kTg_m}$$

$$\gamma_n = \frac{2}{3} m \approx 1$$

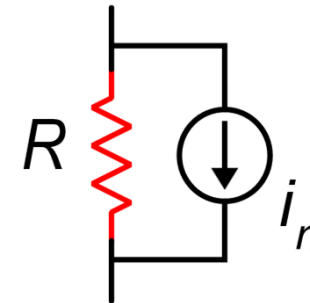

$$S_{In-R} = 4kT \frac{1}{R} = \underline{4kTG}$$

Mosfet flicker noise

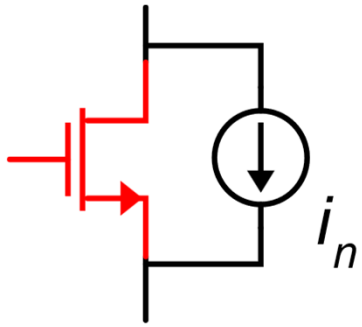

"design friendly expression"

$$S_{In-F}(f) = \frac{N_f}{WL} \frac{1}{f} g_m^2$$

Frequently used by designers of analog integrated circuits

N_f is a parameter that depends on the process

N-MOS: N_{fn}

P-MOS: N_{fp}

Dimensions of N_f are: $V^2 \cdot (\mu\text{m})^2$

$$S_{In-F}(f) = \frac{k_{fi} I^\alpha}{C_{OX} L_{eff}^2} \frac{1}{f^\gamma}$$

A more general expression of the flicker PSD (can be used in SPICE)

Relationship between the two noise expressions

$$S_{In-F}(f) = \frac{N_f}{WL} \frac{1}{f} g_m^2 \quad g_m = \sqrt{2\beta I_D} \quad \beta = \mu C_{OX} \frac{W}{L}$$



$$S_{In-F}(f) = \frac{N_f}{WL} \frac{1}{f} 2\mu C_{OX} \frac{W}{L} I_D = \frac{N_f 2\mu C_{OX} I}{L^2} \cdot \frac{1}{f}$$

$$S_{In-F}(f) = \frac{k_{fi} I^\alpha}{C_{OX} L_{eff}^2} \frac{1}{f^\gamma}$$

$$\begin{cases} \gamma = 1 \\ \alpha = 1 \end{cases} \quad N_f = \frac{k_{fi}}{2\mu C_{OX}^2}$$

with this choice, the general expression is equivalent to the design-friendly one


Equivalent gate noise

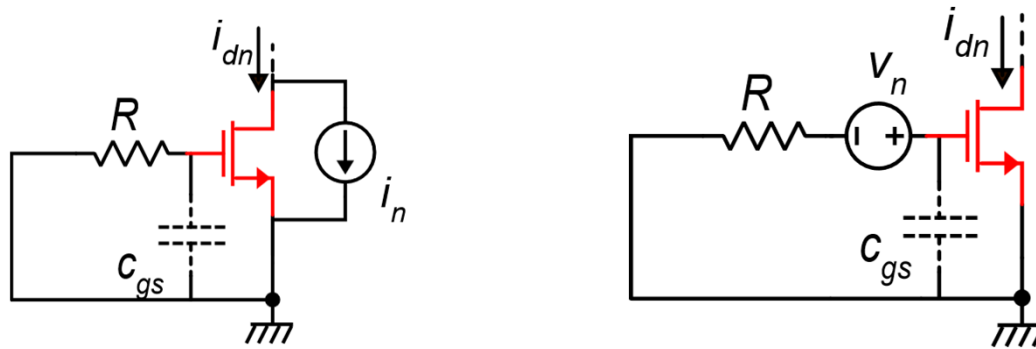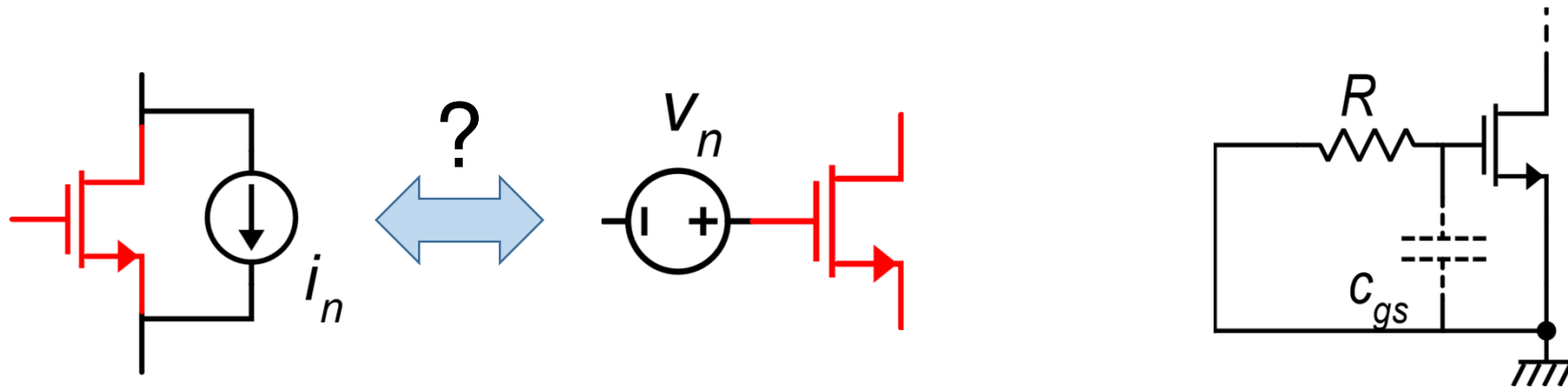

Substituting i_n with a single voltage source in series with the gate gives a contribution that depends on the resistance (R) seen by the gate.

$$i_{dn} = i_n \quad i_{dn} = g_m v_{gs} = g_m v_n \frac{1}{1 + j\omega R C_{gs}}$$

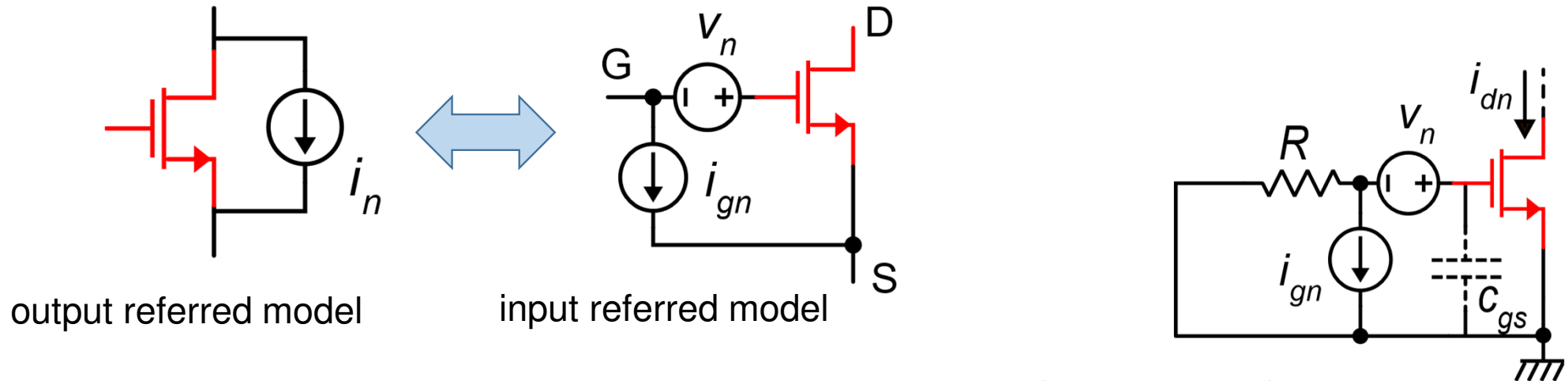Equivalence between the output referred and input referred noise models



$$i_{dn} = g_m \left(v_n \frac{1}{1 + j\omega R c_{gs}} - i_{gn} \frac{1}{1/R + j\omega c_{gs}} \right) = g_m \left(\frac{v_n - i_{gn} R}{1 + j\omega R c_{gs}} \right)$$

By setting:


$$i_{gn} = -j\omega c_{gs} v_n$$

$$i_{dn} = v_n g_m$$

Independent of R, as required for the equivalence with the output referred model, which results in:

$$i_{dn} = i_n$$

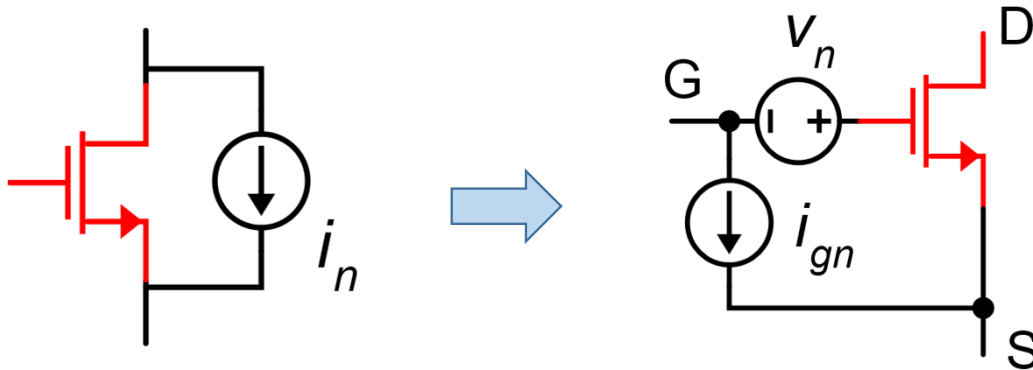Equivalence between the output referred and input referred noise models



$$i_n \longrightarrow \begin{cases} v_n = \frac{i_n}{g_m} \\ i_{gn} = -j\omega c_{gs} v_n \end{cases}$$

$(i_n = v_n g_m)$

Note that i_{gn} is dependent on v_n
(they are correlated stochastic processes)

Transformations between drain noise current and gate noise voltage



$$v_n = \frac{i_n}{g_m} \quad i_n = v_n g_m$$

$$S_{Vn}(f) = \frac{S_{In}(f)}{g_m^2} \quad S_{In}(f) = g_m^2 S_{Vn}(f)$$

Thermal noise: $S_{In-T}(f) = \frac{8}{3} kT g_m \cdot m \Rightarrow S_{Vn-T}(f) = \frac{8}{3} kT m \frac{1}{g_m}$

Flicker noise: $S_{In-F}(f) = \frac{N_f}{WL} \frac{1}{f} g_m^2 \Rightarrow S_{Vn-F}(f) = \frac{N_f}{WL} \frac{1}{f}$

Noise in BJTs

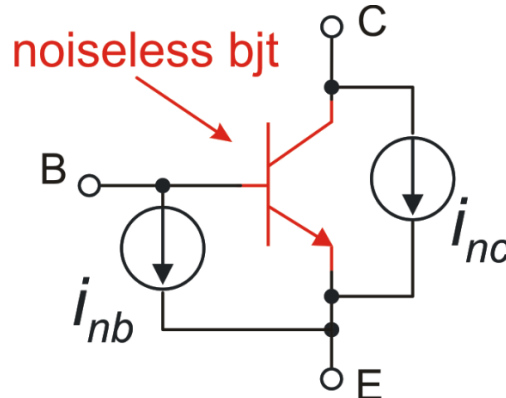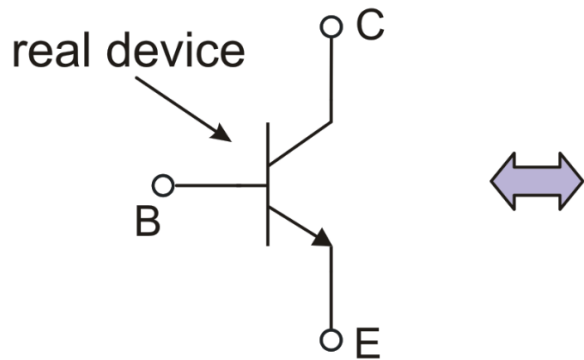

Simplified BJT
noise model

Since the BJT has a non negligible base current, it is necessary to use two distinct current noise sources for the base and the collector

Collector noise current

$$S_{InC} = 2qI_C$$


Only shot noise (broad-band)

Base flicker noise

$$S_{InB} = 2qI_B + k_{fB} \frac{I_B^\alpha}{f}$$

Base shot noise (broad-band)


MOSFET vs BJT

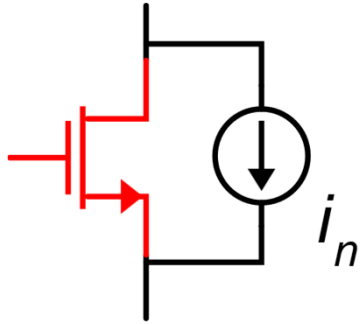

Let us consider only the drain (i_n) and collector (i_{nc}) noise sources.

$$S_{In-T}(f) = \gamma_{n-MOS} 4kTg_m$$
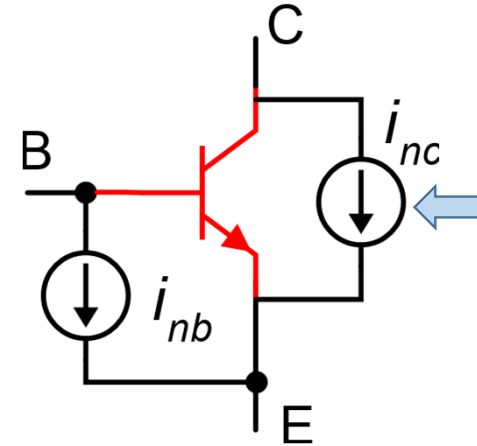
$$\gamma_{n-MOS} = \frac{2}{3}m \approx 1$$




$$S_{InC} = 2qI_C$$

$$g_m = \frac{I_C}{V_T} \rightarrow I_C = g_m V_T = g_m \frac{kT}{q}$$

$$S_{InC} = 2qg_m \frac{kT}{q} = 2kTg_m$$

$$S_{InC}(f) = \gamma_{n-BJT} 4kTg_m \quad \gamma_{n-BJT} = \frac{1}{2}$$

BJT input referred noise voltage

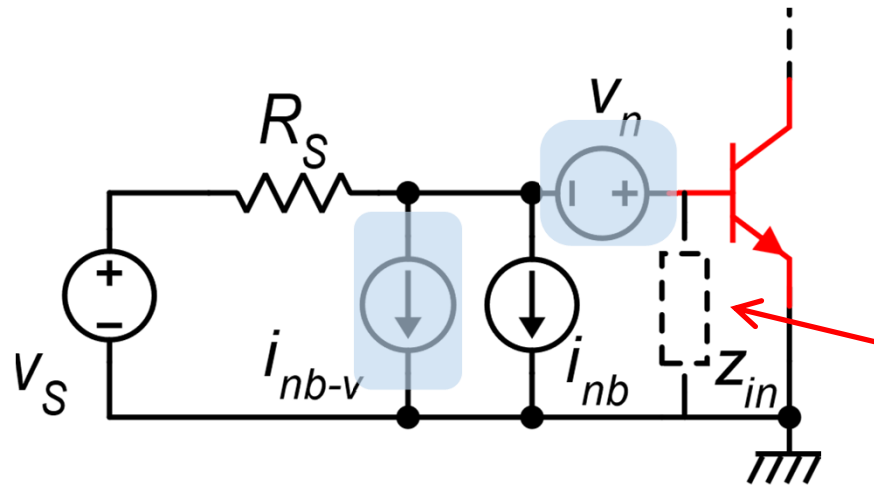

$$v_n = \frac{i_{nC}}{g_m}$$

$$i_{bn-v} = -\frac{v_n}{z_{in}}$$

$$\frac{1}{z_{in}} \cong \frac{1}{r_{be}} + j\omega C_{be}$$

$$\text{if } |z_{in}| \gg R_S \quad v_{be} \cong v_S + v_n$$

$$\text{BJT: } S_{v_n} = 2kT \frac{1}{g_m} = 2kT \left(\frac{V_T}{I_C} \right)$$

$$\text{MOSFET } S_{v_n} \cong 4kT \frac{1}{g_m} = 4kT \frac{V_{TE}}{I_D}$$

In this case, the noise voltage source v_n is the only significant contribution to the input referred noise

Much more noise for the same static current consumption!

The Noise Efficiency Factor (NEF)

Since the single-BJT amplifier offers an excellent trade-off between noise and power consumption, in 1987 M. Steyaert (KU Leuven University) proposed a FOM (figure of merit) called NEF to characterize all voltage amplifiers in terms of noise efficiency

$$NEF = \frac{V_{rms-rti}}{\sqrt{4kT \left(\frac{V_T}{I_{supply}} \right) B \frac{\pi}{2}}}$$

Total *rms* noise of the amplifier under consideration

Effective noise bandwidth and total current consumption of the amplifier under consideration

$$\text{Denominator} = \sqrt{2} \cdot V_{rms-bjt}$$

Input *rms* voltage of a BJT with same current and BW of the amplifier