 


# Popular op-amp topologies


Two stage op-amp with simple differential amplifier in the input stage and class-A common-source output stage



p-input version

Input range may include *gnd*

May **sink** large currents

 


n-input version

Input range may include  $V_{dd}$

May **source** large currents
 
## Improved topologies (better performances, but greater complexity)




Cascode stages

Larger gain, simpler Rail-to-Rail input stages

Class AB stages


Large output current with small quiescent power consumption

# Class-AB output stages

 

$$I_{D5} = \frac{1}{2} \frac{\beta_5}{\beta_3} \frac{\beta_7}{\beta_8} I_{bias}$$
 
$$I_{D6} = \frac{\beta_6}{2} \left( V_{GS6} - V_{tp} \right)^2$$




$I_{D5}$  does not depend on  $V_{dd}$ , while  $I_{D6}$  does.  
The output short circuit current depends on  $V_{dd}$

$$V_{GS6} = V_{DD} - V_{batt} - V_{GS5}$$

# Poor PSSR

# Op-amps with class-AB output stages

 


If we want to save this solution, we need to adapt both  $V_{GS5}$  and  $V_{GS6}$  when  $V_{dd}$  changes, and guarantee that:

$$I_{D5} = I_{D6}$$

is always valid

# Op-amps with class-AB output stages

Bias chain

 

$$I_{D6} = \frac{\beta_6}{\beta_{22}} I_B$$

$$|V_{GS6}| = |V_{GS22}|$$

$$I_{D5} = \frac{1}{2} \frac{\beta_5}{\beta_3} \frac{\beta_7}{\beta_{22}} I_B$$

$$I_{D6} = \frac{\beta_6}{2} (V_{GS6} - V_{tp})^2$$

$$|V_{GS6}| = V_{DD} - |V_{GS10}| - V_{GS3}$$




$$|V_{GS22}| = V_{DD} - |V_{GS21}| - V_{GS20}$$

$$\frac{\beta_{21}}{\beta_{10}} = \frac{I_B}{I_{D10}}$$

$$\frac{\beta_{20}}{\beta_3} = \frac{I_B}{I_{D3}}$$

# Op-amps with class-AB output stages


Second stage

   

$$G_{m2} = g_{m5} + g_{m6}$$


Voltage shifter:  
additional singularities  
 $Y_{m2}(s) \rightarrow G_{m2}(s)$

## Limitations: minimum $V_{dd}$

 


Minimum  $V_{dd}$ :  $3V_{GS} \approx 2.1$  V

 For the class-A amplifier,  
the minimum  $V_{dd}$  was  
only  $V_{GS} + 2V_{DSAT} \approx 0.9$  V


 
## Reduced $V_{GS}$ excursion for the output devices



$$V_{GS5-MAX} = V_{iC} + V_{GS} - V_{DSAT}$$


$$V_{GS6-MAX} = V_{dd} - V_{GS10}$$

$$I_{OP-MAX} = \frac{\beta_6}{2} (V_{GS6-MAX} - V_{tp})^2$$

$$I_{ON-MAX} = \frac{\beta_5}{2} (V_{GS5-MAX} - V_{tn})^2$$

- Both  $V_{GS5}$  and  $V_{GS6}$  cannot reach  $V_{dd}$ . If large output currents are required, this means that M5 and M6 should be designed with very large W
- $I_{ON-MAX}$  strongly depends on the input common mode voltage

## The Monticelli's class-AB stage

 

$I_h$  and  $I_k$  includes also the variations due to the input signal and have a high output differential resistance (not shown for simplicity)

$$I_h \approx I_k = const$$

$$I_p + I_n \approx const \quad i_n + i_p \approx 0$$


$$i_n = -g_{mMN} v_{gn} \quad i_p = g_{mMP} v_{gp}$$

$$g_{mMN} v_{gn} = g_{mMP} v_{gp}$$

$$\frac{v_{gn}}{v_{gp}} = \frac{g_{mMP}}{g_{mMN}}$$


D. M. Monticelli, "A quad CMOS single-supply op amp with rail-to-rail output swing," IEEE J. Solid-State Circuits, vol. SC-21, pp. 1026-1034, Dec. 1986.

## The Monticelli's class-AB stage

 

$$\frac{v_{gn}}{v_{gp}} = \frac{g_{mMP}}{g_{mMN}}$$


$$g_m = \sqrt{2I_D\beta}$$

 


$M_{NM}$  and  $M_{MP}$ , are designed to have same  $g_m$  in the operating point:  $v_{gn}=v_{gp}$  (variations)

First stage: folded cascode for improved gain and larger swing

n-input folded cascode

 

 Folded cascode with rail-to-rail input range



# High performance - two-stage CMOS op-amp

- High gain:  $\approx (g_m r_d)^3$
- Class-AB output stage
- Rail-to-Rail input range

M24 and M35 form the Monticelli's cell


M22-M23 and M33-M34 produce the gate bias for M24 and M35, respectively

In quiescent conditions, we design  $I_{bias}$ , M23 and M34 to make:  $V_{GS24}=V_{GS23}$  and  $V_{GS35}=V_{GS34}$

$$V_{GS1} = V_{GS22}$$

$$V_{GS2} = V_{GS33}$$

 This simplify setting of M1,M2 quiescent current



R. Hogervorst et al., "A Compact Power-Efficient 3 V CMOS Rail-to-Rail Input/Output Operational Amplifier for VLSI Cell Libraries", IEEE JSSC, 1994

# Commercial products

 


Figure 1. OPA30x Classic Two-Stage Topology