
 


# Comparators

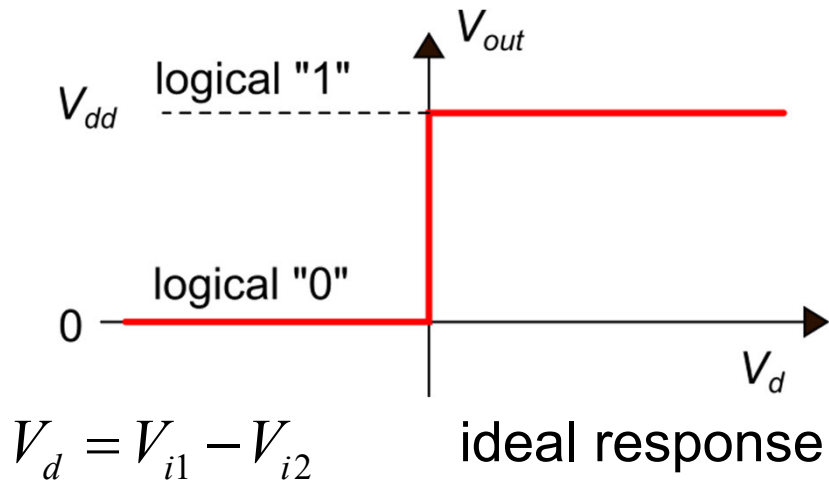



Symbol

$$V_{out} = \begin{cases} \text{"0"} & \text{if } V_d \leq 0 \\ \text{"1"} & \text{if } V_d > 0 \end{cases}$$

## Continuous-time vs dynamic comparator

 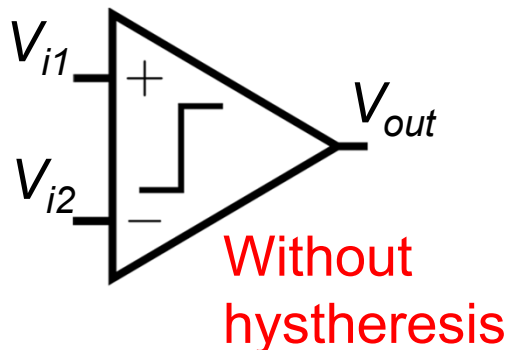
### Continuous-time comparator:

- Higher power consumption
- Hysteresis
- Output always valid



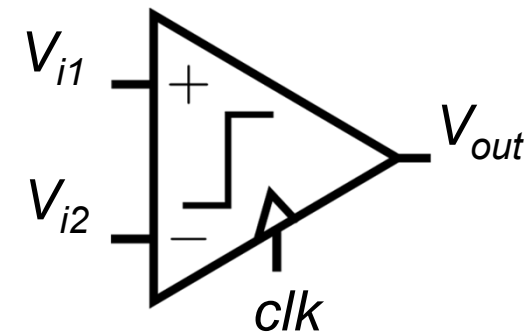
### Dynamic comparator (or latched comparator):

- Lower power consumption
- No hysteresis
- Need a clock signal



 
## Comparators: amplifier-based implementations

An amplifier with very high gain can be used as a comparator. Op-amp topologies can be used with no need of frequency compensation



 since the comparator is used in open loop configuration or positive feedback.




### Note:

a region exists where the logical level is undefined

In several application this may lead to unwanted stable or metastable states. For slow-varying signals, threshold crossing may be too noisy


# Regenerative comparators: hysteresis

 

Thanks to the hysteresis, the comparator produces a valid output level across the whole input range

The hysteresis introduces an uncertainty band that reduces the accuracy but helps rejecting noise when the input voltage is close to zero.

Possible regenerative comparator

 

Op-amp based Smith trigger.

## Drawbacks

- Oversized solution for integrated cells
- Low impedance on the non-inverting input

# Commercial products




Fast, Rail-to-Rail, Low Power, 2.5 V to 5.5 V,  
Single-Supply TTL/CMOS Comparator

Data Sheet

AD8469

## FUNCTIONAL BLOCK DIAGRAM

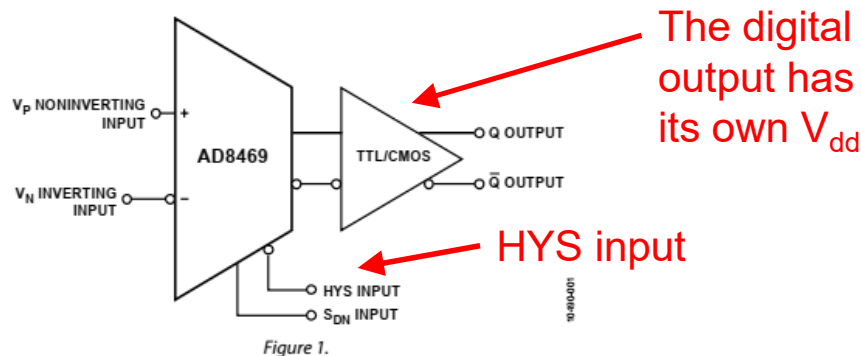

Programmable hysteresis from 0 to 160 mV  
 $\Delta V_h$  depending on current on pin HYS

**Input common-mode voltage:  $V_{EE} - 0.2\text{ V}$  to  $V_{CC} + 0.2\text{ V}$**

**Low glitch TTL-/CMOS-compatible output stage**

**40 ns propagation delay**






TLV9022, TLV9032, TLV9024, TLV9034  
SNOSDA3B – JUNE 2020 – REVISED NOVEMBER 2020
   
## TLV902x and TLV903x High-Precision Dual and Quad Comparators

- Rail-to-Rail input with fault-tolerance
- 100ns Typ propagation delay


No built-in hysteresis. The datasheet suggests Schmitt trigger configuration


 
# Compact comparator cell for Systems on a Chip

Four-transistor hysteresis cell

Currents  $I_1$  and  $I_2$  varies with the input signal in such a way that:  $I_1 + I_2 = I_0 = \text{constant}$



Load  
MOSFET


Cross-coupled  
MOSFETs

Load  
MOSFET


$$\beta = \beta_L$$

$$\beta = \beta_C$$

$$\beta = \beta_L$$

 
 
# Analysis of the four-transistor hysteresis cell: starting point



Let us start from:  $I_2=0$  ( $I_1=I_0$ )

$$I_2 = I_{D3} + I_{D4} = 0$$

since:  $I_{D3}, I_{D4} \geq 0 \quad I_{D3} = I_{D4} = 0$


Considering M4:  $V_{GS4} \leq V_t$

$$V_{GS2} = V_{GS4} \quad I_{D2} = 0$$

Then it is M1 that carries all current  $I_1$ :  $V_1 = V_{GS1} = V_t + \sqrt{\frac{2I_1}{\beta_L}} = V_t + \sqrt{\frac{2I_0}{\beta_L}}$


$$\left. \begin{array}{l} V_{GS3} = V_{GS1} \geq V_t \quad (\text{M3 is on}) \\ I_{D3} = 0 \end{array} \right\} V_{DS3} = V_2 = 0$$

## Analysis of the 4-transistor cell

 

$$V_1(0) = V_t + \sqrt{\frac{2I_0}{\beta_L}}$$

$$V_2(0) = 0$$

 


Design condition:  
we size  $\beta_L$  in such a way that:

$$V_1(0) = V_{GS1}(0) < 2V_t \Rightarrow V_{GS1}(0) - V_t < V_t$$

The reason will be clear later





Increasing  $I_2$

 


As  $I_2$  increases,  $I_1$  decreases of the same amount, then  $V_1$  decreases:


$$V_1 = V_{GS1} = V_t + \sqrt{\frac{2I_1}{\beta_L}}$$

$V_2$  increases:

  

 


Increasing  $I_2$

 

As  $I_2$  progressively increases,  $V_2$  increases. Until  $V_2$  remains below the threshold voltage  $V_t$ , M2 and M4 are off

$V_2$  reaches the threshold

 

For  $V_2 = V_t$ , M2 and M4 are still off. Then:

$$I_1 = I_{D1} \quad I_2 = I_{D3}$$

Since M3 is in saturation:

$$\frac{I_2}{I_1} = \frac{\beta_C}{\beta_L}$$

$$V_2 = V_t$$

Let us check whether M3 is now in saturation (was in triode region at the beginning)

$$V_{DS3} = V_2 = V_t$$

$$V_{GS3} = V_1 < V_1(0) < 2V_t$$

For the design condition mentioned earlier

$$V_{GS3} - V_t < V_t = V_{DS3}$$


$$V_{DS3} > V_{GS3} - V_t \Rightarrow \text{M3 is in saturation}$$

$V_2$  reaches the threshold

Case of interest:  $\frac{\beta_C}{\beta_L} > 1$

$$V_2 = V_t \text{ for } \frac{I_2}{I_1} = \frac{\beta_C}{\beta_L} \equiv r_H > 1$$

 For  $\beta_C > \beta_L$ ,  $V_2$  reaches the threshold when  $I_2$  has overcome the middle of the allowed range  $[0, I_0]$






## Putting the two behaviors together:


In this region, there are two possible states, depending on which extreme we started from

This means that there is hysteresis

 

Now we have to investigate what happens when the lower voltage hits the  $V_t$  line
 
## Phenomena that happen when $V_2$ overcome $V_t$



M2 and M4 turn on (while M1 and M3 are still on)

Let us focus on M2

Positive feedback loop


1. As M2 turns on, it start stealing current from M1

2.  $V_1$  decreases:  $V_1 = V_{GS1} = V_t + \sqrt{\frac{2I_{D1}}{\beta_L}}$


3.  $V_{GS3} = V_1$ , then  $I_{D3}$  reduces, increasing the current that flows into M4

4.  $V_2$  increases:  $V_2 = V_{GS4} = V_t + \sqrt{\frac{2I_{D4}}{\beta_L}}$

 
5.  $V_{GS2} = V_2$ , then  $I_{D2}$  increases further




 
## Positive feedback loop: small signal analysis



 Each half circuit is equivalent to an amplifier



Small signal equivalent circuit

  

$$A = \frac{v_{out}}{v_{in}} = -g_{mC} \left( \frac{1}{g_{mL}} // r_{dL} // r_{dC} \right)$$

$$A \approx -\frac{g_{mC}}{g_{mL}}$$


Due to the presence of the  $r_d$ 's, the magnitude of  $A$  is slightly less than

$$\frac{g_{mC}}{g_{mL}}$$


 
## Positive feedback loop: dc instability

When  $V_2$  overcomes  $V_t$ , all MOSFETs are on:



$$A_1 = -\frac{g_{m2}}{g_{m1}}; \quad A_2 = -\frac{g_{m3}}{g_{m4}}$$

$$\beta A = A_1 A_2 > 0 \quad \text{Positive feedback}$$


$$g_{m1} = \beta_L (V_{GS1} - V_t), \quad g_{m2} = \beta_C (V_{GS2} - V_t)$$

$$g_{m3} = \beta_C (V_{GS3} - V_t), \quad g_{m4} = \beta_L (V_{GS4} - V_t)$$

$$V_{GS1} = V_{GS3} = V_1, \quad V_{GS2} = V_{GS4} = V_2$$

$$\beta A = \frac{\beta_C (V_2 - V_t)}{\beta_L (V_1 - V_t)} \cdot \frac{\beta_C (V_1 - V_t)}{\beta_L (V_2 - V_t)} = \left( \frac{\beta_C}{\beta_L} \right)^2$$

## The effect of positive feedback

 


$$\frac{\beta_C}{\beta_L} = r_H > 1 \Rightarrow |\beta A| > 1 \text{ (dc instability)}$$

Therefore, a stable condition cannot exist if all MOSFETs are on.

**Important condition**

$V_1$  and  $V_2$  cannot be greater than  $V_t$  at same time in a stable condition  
Then, when M1 is on, M4 is off and vice versa

## The "click"

 

Proceeding from the left, when  $V_2$  overcomes the  $V_t$  line, the positive feedback makes the voltage evolve autonomously.


The new stable solution is the one we already found proceeding back from the right

M1,M3: on M2,M4 off





M2,M4: on M1,M3 off

## The two stable characteristics

 


Only one solution exists (stable)

  Three solutions exist:  
2 stable  
1 unstable (all devices are on)




## Non regenerative case (no hysteresis)

$$\frac{\beta_C}{\beta_L} = r_H < 1 \quad \Rightarrow \quad |\beta A| = \left( \frac{\beta_C}{\beta_L} \right)^2 < 1$$

 

In this case, the positive feedback is unable to cause a real abrupt transition  
A hysteresis is not present
 
# A simple comparator based on the 4-transistor hysteresis cell



$$V_{id} \equiv V_{i2} - V_{i1}$$

We start with a p-version of the hysteresis cell

Currents  $I_1$  and  $I_2$  are derived from the input voltage  $v_{id} = v_{i2} - v_{i1}$  by means of a differential pair

Only one at a time between  $V_1$  and  $V_2$  is greater than the p-mos threshold voltage.



If  $V_1 > |V_{tp}|$ ,  $V_2 < |V_{tp}|$  MA, MB and Mo2 are on, while Mo1 is off:

$$V_{out} = 0$$

If  $V_2 > |V_{tp}|$ ,  $V_1 < |V_{tp}|$ , only Mo1 is on:

$$V_{out} = V_{dd}$$
  
## Calculation of the comparator upper thresholds



Using a linear approximation of the differential pair:

$$\begin{cases} I_2 - I_1 = g_{m1} V_{id} \\ I_2 + I_1 = I_0 \end{cases}$$

## Calculation of the comparator upper thresholds

$$\left\{ \begin{array}{l} I_2 - I_1 = g_{m1} V_H \\ I_2 + I_1 = I_0 \\ \frac{I_2}{I_1} = r_H \end{array} \right. \begin{array}{l} \rightarrow I_2 - I_1 = I_1 (r_H - 1) = g_{m1} V_H \\ \rightarrow I_2 + I_1 = I_1 (r_H + 1) = I_0 \end{array} \quad \frac{r_H - 1}{r_H + 1} = \frac{g_{m1}}{I_0} V_H$$



Dividing the upper equation by the lower one

In quiescent conditions:  $I_0 = 2I_{D1-Q} = 2V_{TE1}g_{m1}$

$$\frac{r_H - 1}{r_H + 1} = \frac{1}{2V_{TE1}} V_H \quad V_H = 2V_{TE1} \frac{r_H - 1}{r_H + 1}$$


  
# Complete characteristics of the comparator



$$V_L = -V_H$$

$$V_H = 2V_{TE} \frac{r_H - 1}{r_H + 1}$$

$$\Delta V_H = V_H - V_L = 4V_{TE} \frac{r_H - 1}{r_H + 1}$$

In strong inversion:  $\Delta V_H = 2(V_{GS} - V_t)_1 \frac{r_H - 1}{r_H + 1}$

## Minimum achievable hysteresis


$$\Delta V_H = V_H - V_L = 4V_{TE} \frac{r_H - 1}{r_H + 1}$$

To obtain a small hysteresis

- Make  $V_{TE1}$  as small as possible
- Make  $r_H$  just slightly larger than 1

However, other requirements impose to make  $r_H$  significantly larger than 1, because:

- 1) The calculated  $|\beta A| = (r_H)^2$  is overestimated, since we have neglected the  $r_d$ 's
- 2) Process error can make  $r_H < 1$  if the margin to 1 is too small
- 3) The transition is faster with larger  $|\beta A|$

 



A typical robust choice:

$$r_H = 2 \Rightarrow \Delta V_H = \frac{4}{3} V_{TE}$$

$\Delta V_H$  as small as **50 mV**
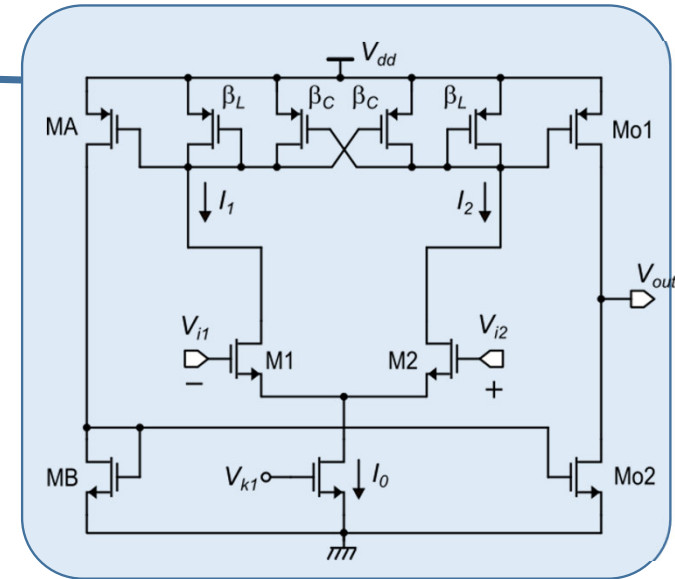 
# How to obtain a comparator with very low hysteresis

The simplest solution is using a pre-amplifier:




$$V_{id}^* = \frac{V_{id}}{G} + v_{io} \quad V_H^* = \frac{V_H}{G} + v_{io}, \quad V_L^* = \frac{V_L}{G} + v_{io} \quad \Delta V_H^* = \frac{\Delta V_H}{G}$$

The hysteresis is divided by the preamplifier gain ( $G$ )


In discrete time systems the amplifier offset can be cancelled with CDS
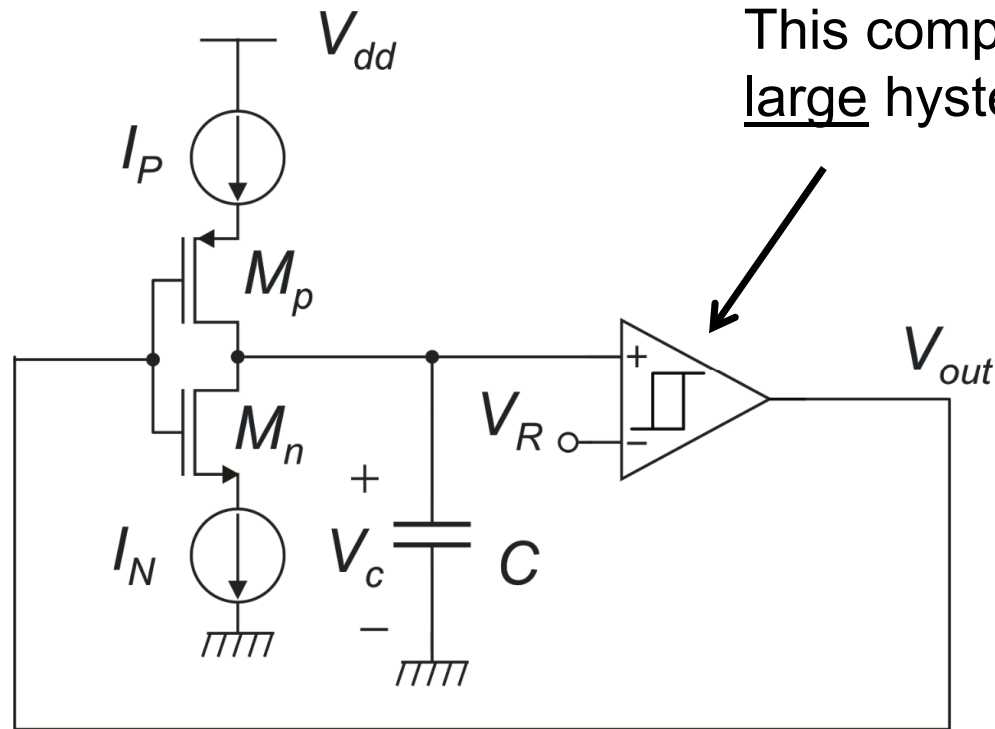
# A simple low-frequency VCO based on comparator hysteresis





This comparator is designed to have a large hysteresis

 - When  $V_{out}=0$ , the capacitor is charged by  $I_P$
- When  $V_{out}=1$ , the capacitor is discharged by  $I_N$


  
## Calculation of the oscillator frequency




$$\text{rise time} = T_R = \frac{\Delta V_H}{I_P / C} = C \frac{\Delta V_H}{I_P}$$

$$\text{fall time} = T_F = \frac{\Delta V_H}{I_N / C} = C \frac{\Delta V_H}{I_N}$$

$$\text{period} = T = T_R + T_F = C \Delta V_H \left( \frac{1}{I_P} + \frac{1}{I_N} \right)$$
 
## Implementation with "current starved" inverter




If  $I_P = I_N = I_{tune}$ :

$$T = 2 \frac{C \Delta V_H}{I_{tune}} \quad f = \frac{I_{tune}}{2C \Delta V_H}$$


The frequency is proportional to the tuning current (CCO)

Using a linear voltage to current converter it is possible to make  $I_{tune}$  to be proportional to a voltage, transforming the CCO into a VCO

# A simple voltage-to-current converter

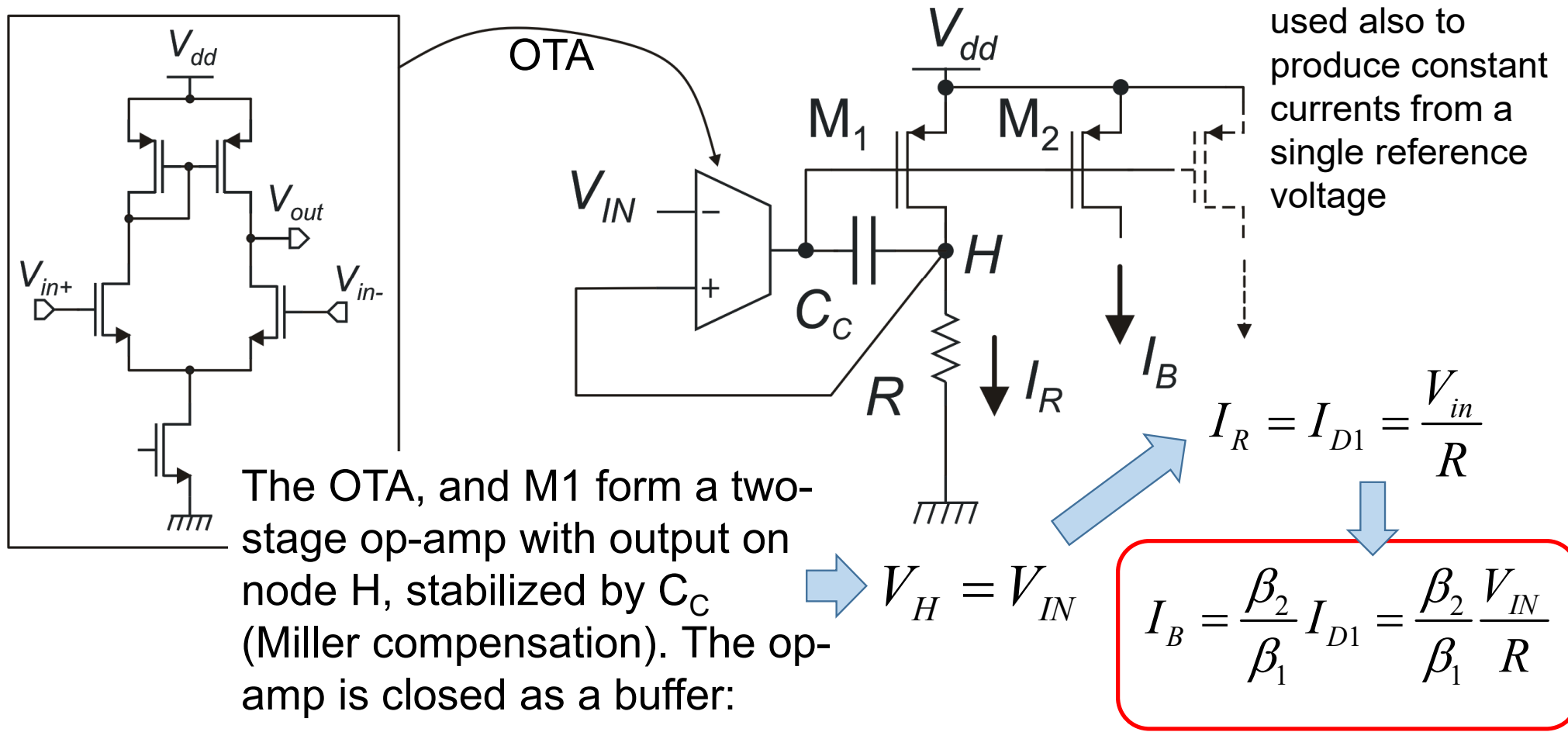

# StrongARM Comparator

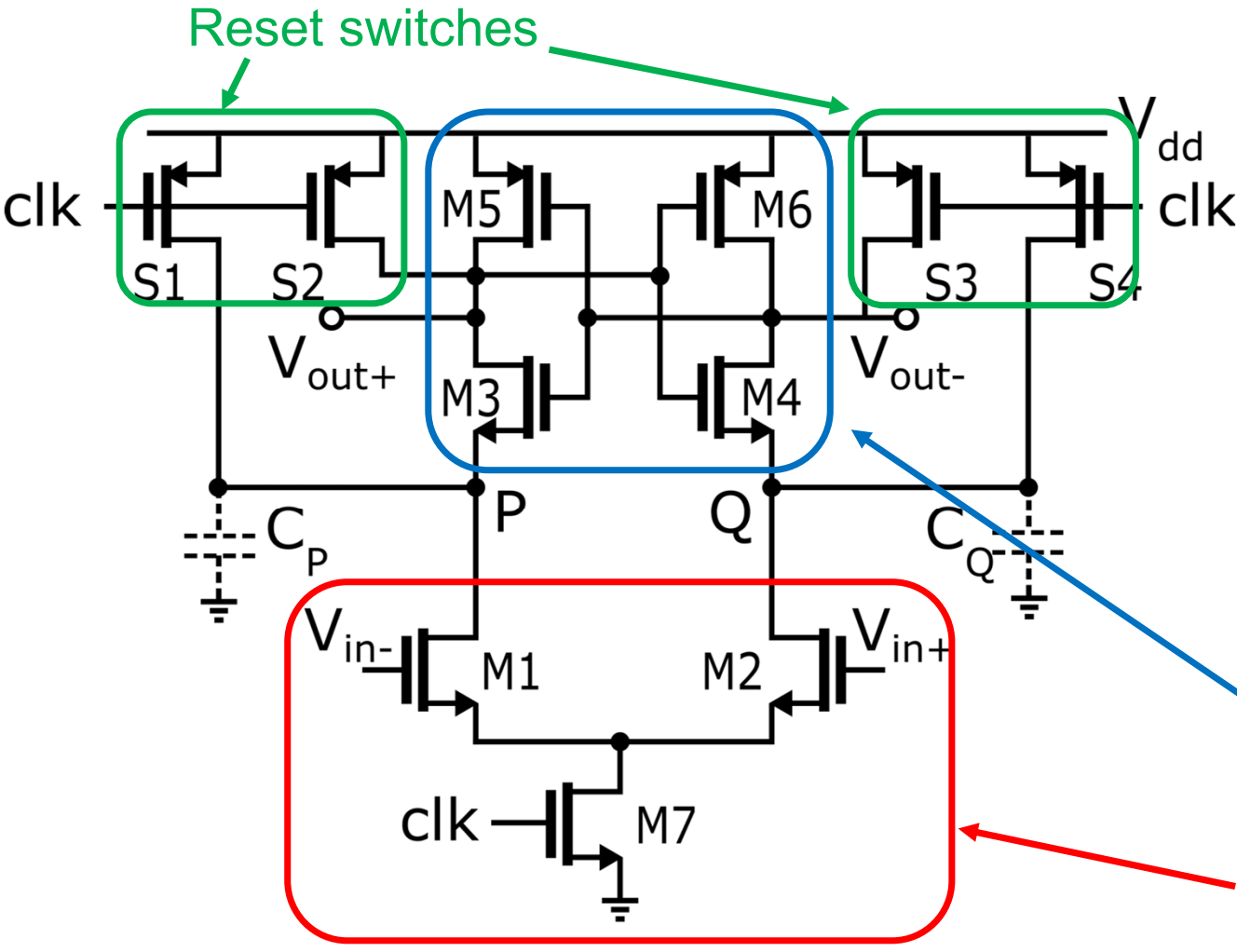


- First proposed as Sense Amplifier for SRAM (used in StrongARM microprocessor)
- No static power consumption
- Rail-to-rail outputs
- Compare  $V_{id} = V_{in+} - V_{in-}$  on the rising edge of the clock signal

Latch

Clocked differential pair




## Reset Phase

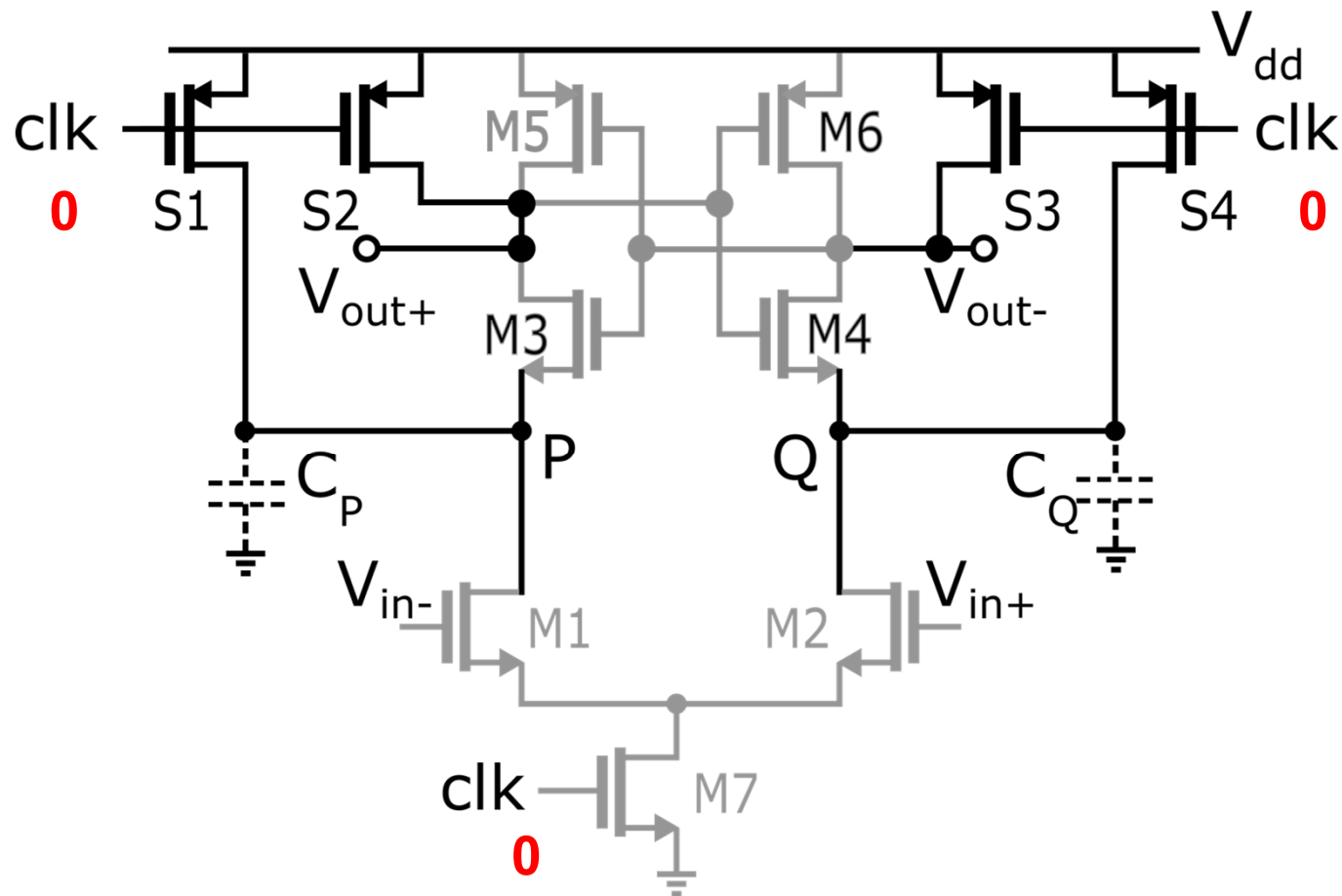



- Nodes P, Q,  $V_{out}^+$ ,  $V_{out}^-$  are connected to  $V_{dd}$  through S1-S4
- The input pair is off
- Each reset phase, the comparator loses 'memory' of the previous cycle → No hysteresis

## Amplification Phase

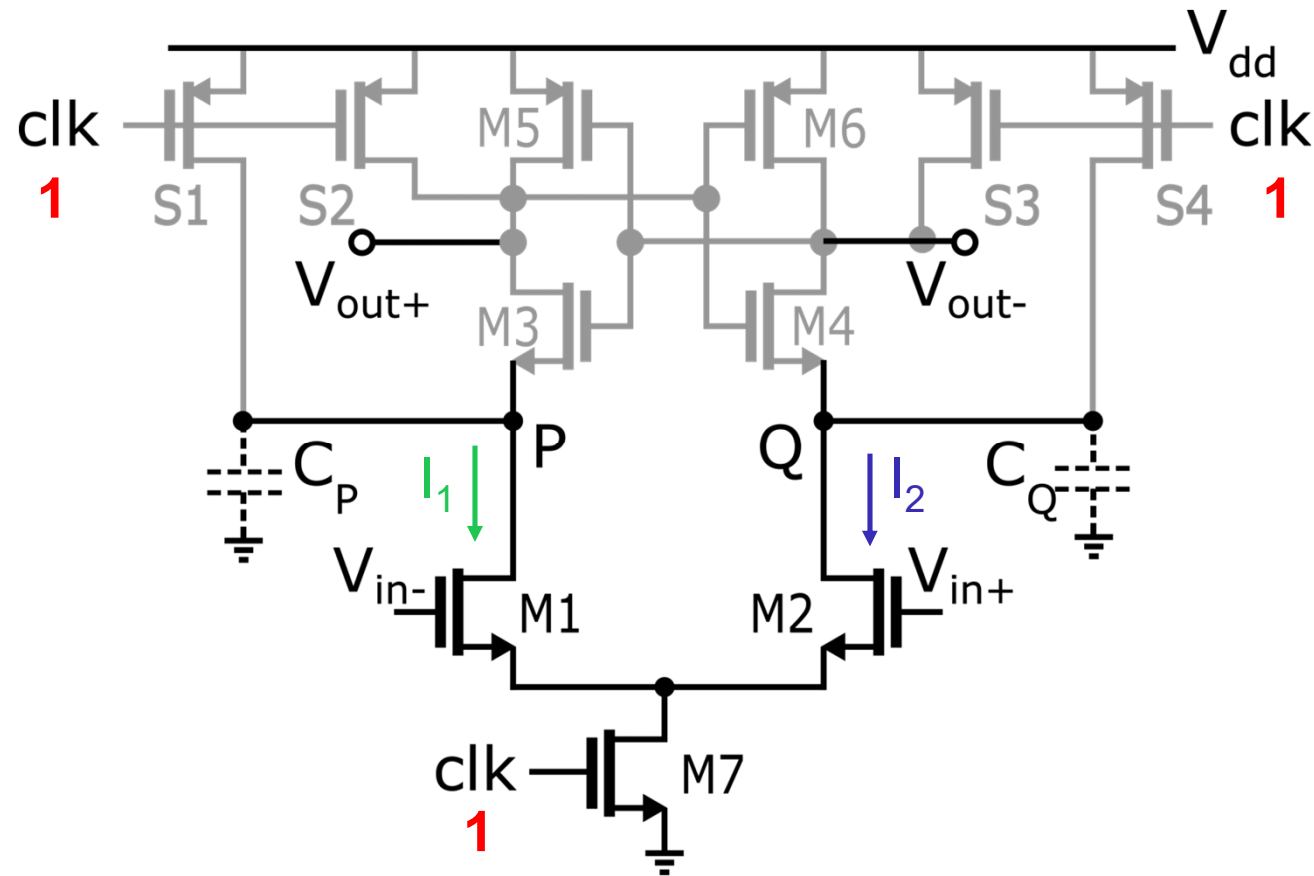

- S1-S4 go off, M7 goes on
- The input pair is on
- $I_1$ ,  $I_2$  start discharging the parasitic capacitances  $C_P$ ,  $C_Q$  at nodes P,Q
- Depending on  $V_{id}=V_{in^+}-V_{in^-}$  node P is discharged faster/slower than node Q

# Amplification Phase

 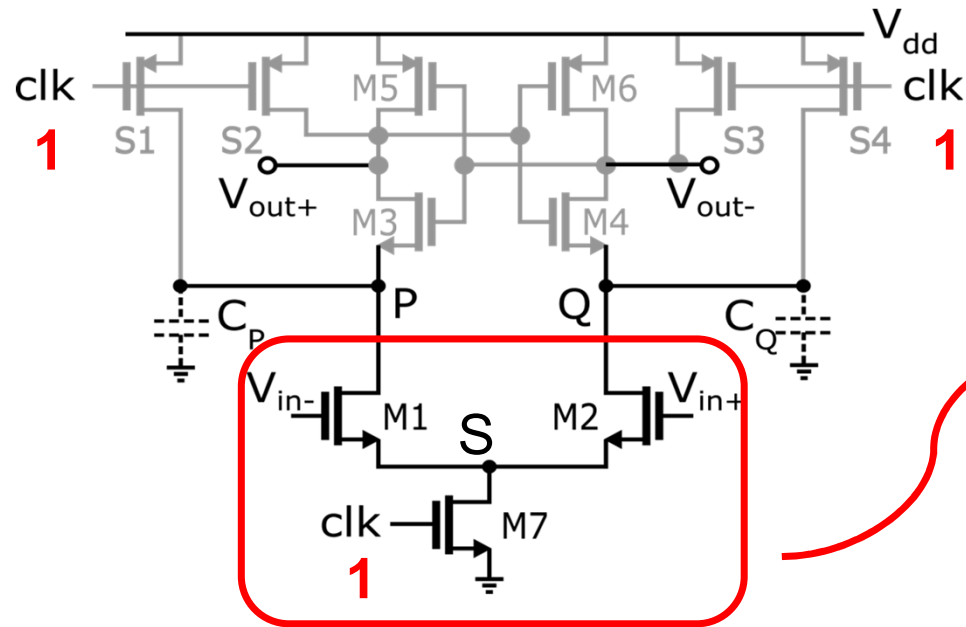


Pseudo-differential pair  
(when clk=1, M7  
connects node S to gnd)

$$\begin{cases}
 I_1 = \frac{\beta_{1,2}}{2} (V_{in}^- - V_{thn})^2 \cong \frac{\beta_{1,2}}{2} (V_{CMI} - V_{thn})^2 - \frac{g_{m1} V_{id}}{2} \\
 I_2 = \frac{\beta_{1,2}}{2} (V_{in}^+ - V_{thn})^2 \cong \frac{\beta_{1,2}}{2} (V_{CMI} - V_{thn})^2 + \frac{g_{m1} V_{id}}{2}
 \end{cases}$$

small  $V_{id}$    
 $I_{CM}$    
 $\beta_{1,2}(V_{CMI} - V_{th})$

# Amplification Phase

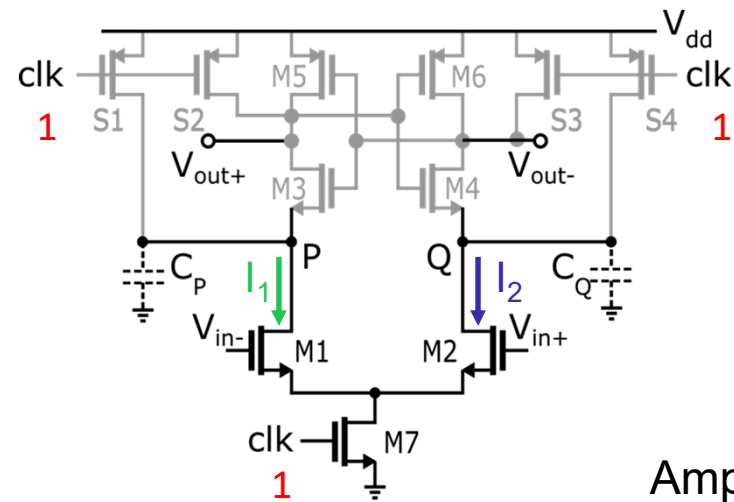


Amplification lasts until  
P,Q reaches  $V_{dd}-V_{thn}$

$$\begin{cases} \frac{dP}{dt} = -\frac{I_1}{C_P} \\ \frac{dQ}{dt} = -\frac{I_2}{C_P} \end{cases}$$



 
$$t_A \cong \frac{V_{thn}}{I_{CM}} C_{P,Q}$$





$$(P - Q) \Big|_{t_A} \cong \frac{g_{m1}}{C_{P,Q}} t_A V_{id}$$

gain A

 




# Regeneration phase (1/2)

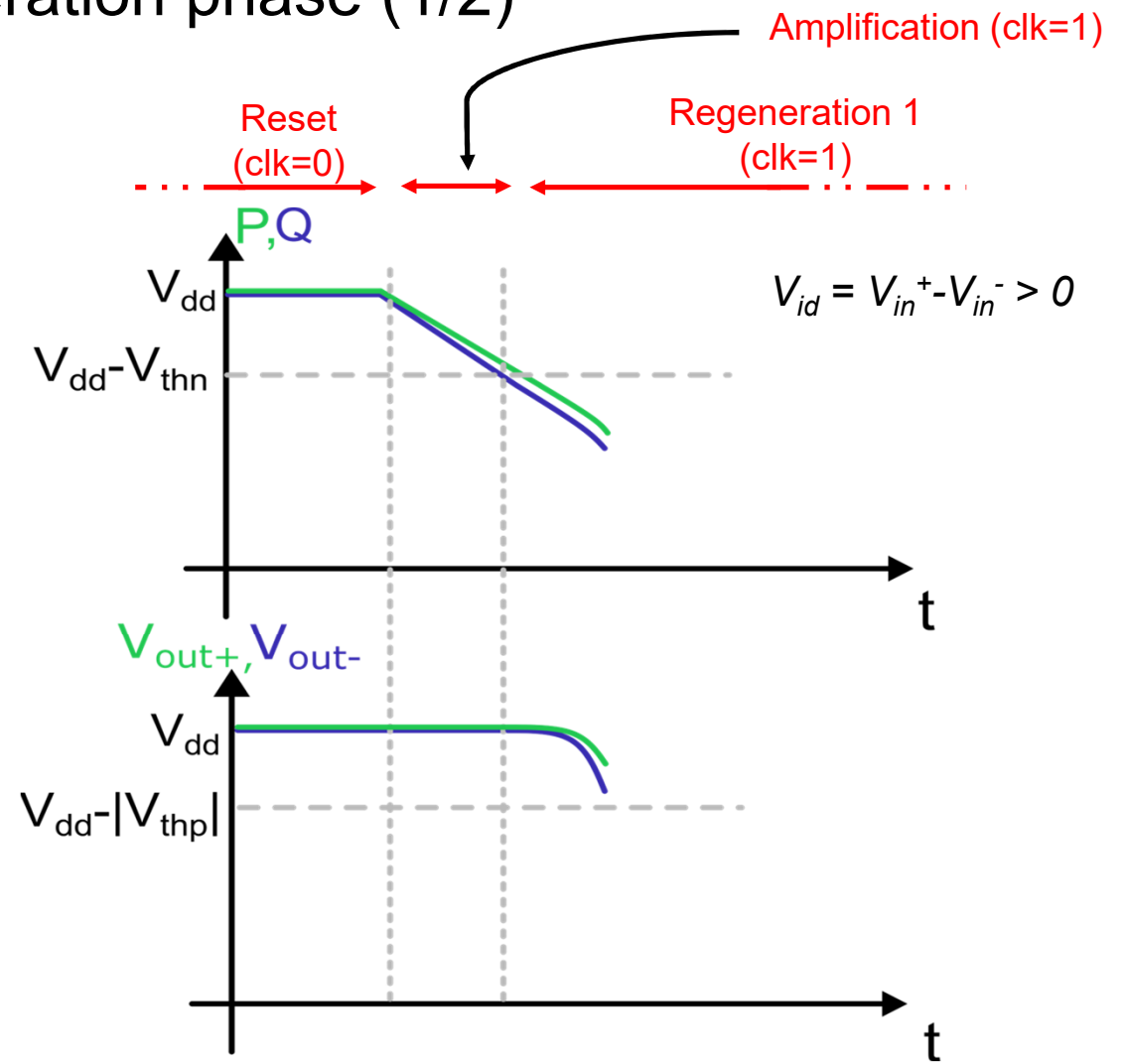 


## Regeneration phase (2/2)

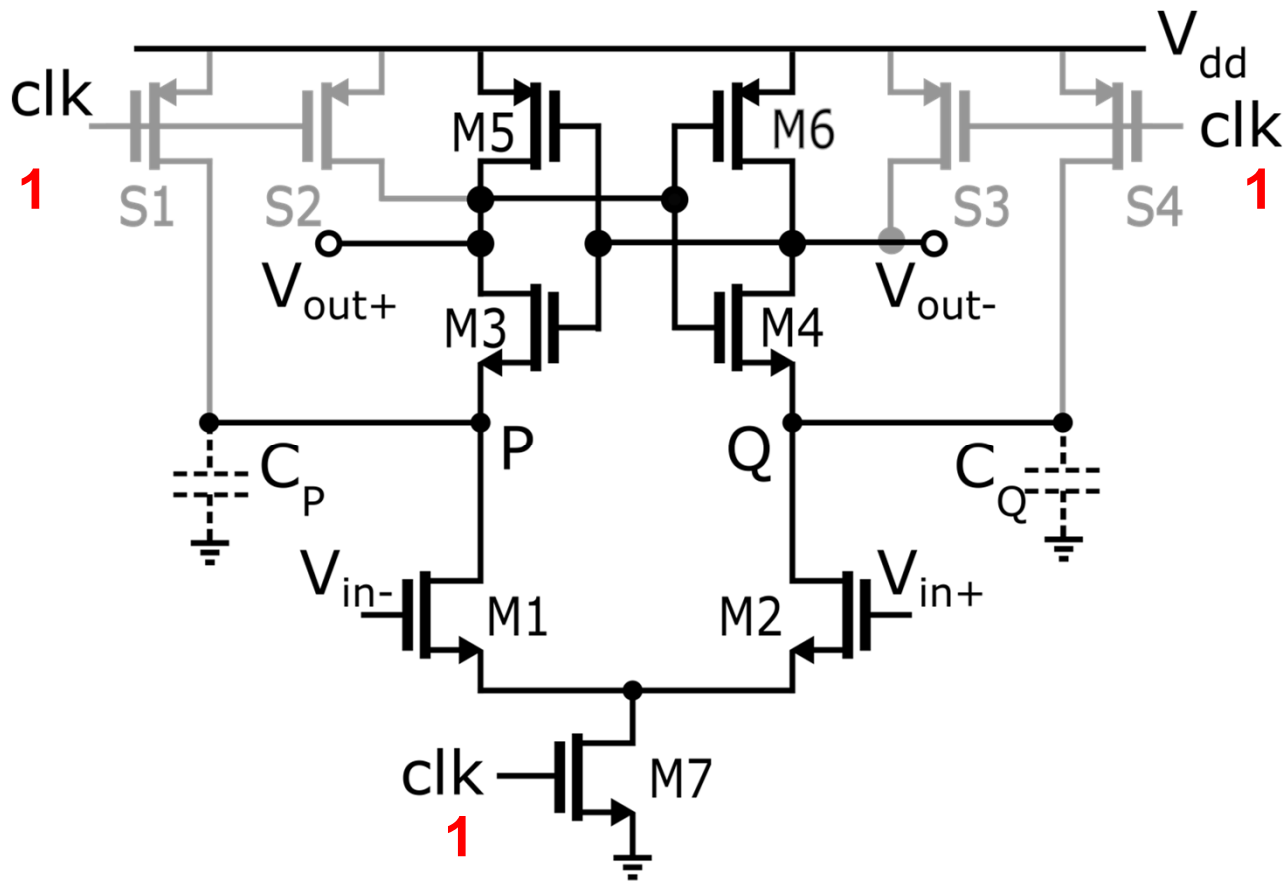


- When  $V_{out}^+$  or  $V_{out}^-$  goes lower than  $V_{dd} - |V_{thp}|$ , one between M5 and M6 turns on
- Positive feedback of latch M3-M6 brings quickly one output to  $V_{dd}$  and the other to ground (rail-to-rail outputs)

# Regeneration phase (2/2)

 


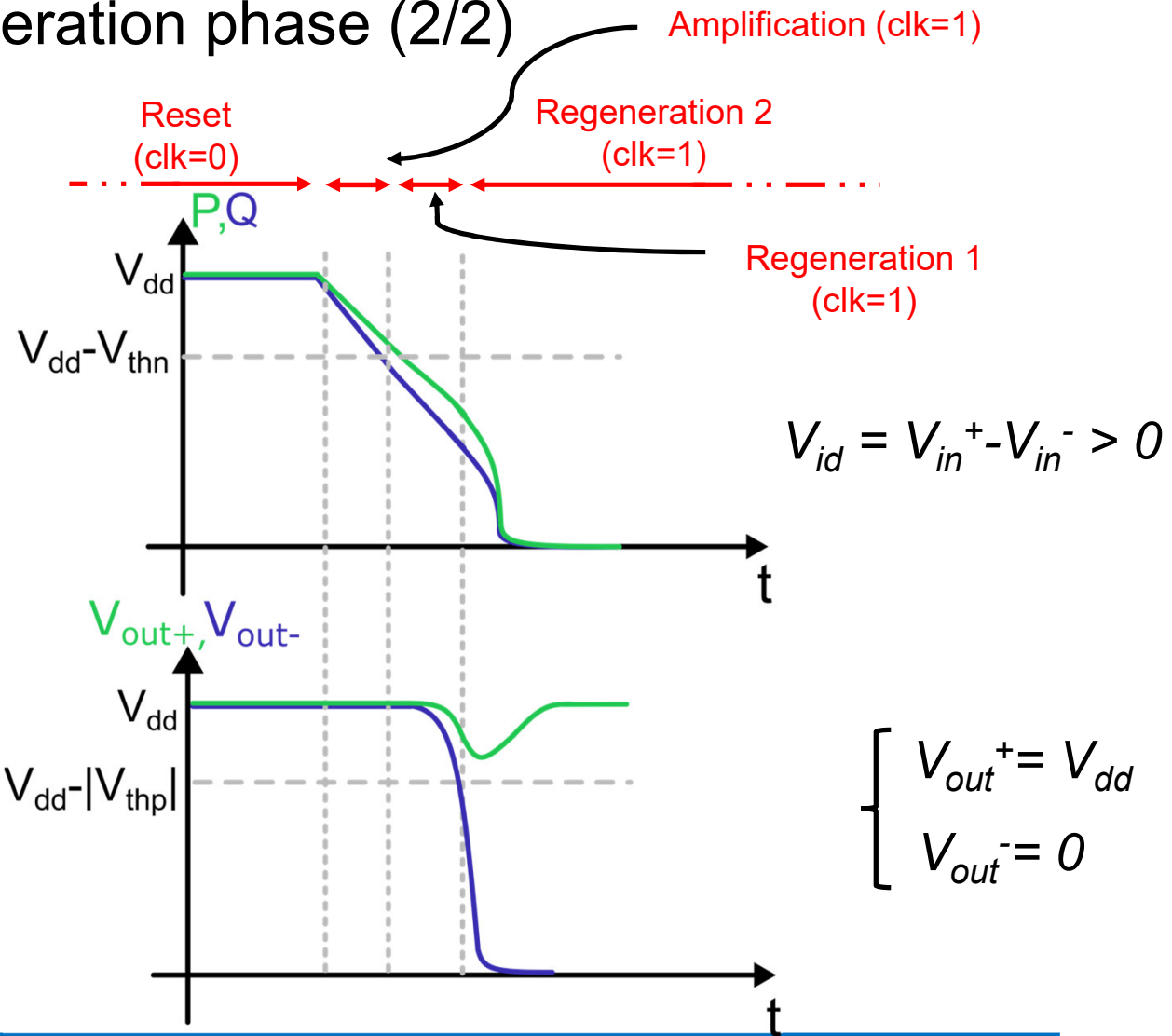No static power consumption (M3 cuts off the current path from  $V_{dd}$  to ground)





## (Next) Reset Phase

 

- S1-S4 recharge node P,Q,  $V_{out+}$ ,  $V_{out-}$  to  $V_{dd}$
- Need of a latch to store the result of the comparison during the reset phase

