 


Digital to Analog Converters



Input: digital code


Output: analog signal

A **clock** can be present for synchronization reasons or to avoid glitches during data update


Ideal function:
$$V_{out} = V_{MIN} + \frac{V_{FS}}{2^n} D$$

n= nominal resolution (in number of bits)

unipolar output range

 

bipolar output range

 

D can be signed
e.g, two's complement

DAC applications

- Digital to analog signal reconstruction: e.g. audio and video signals, actuator control (e.g. control of motors, solenoids, piezoactuators)
- Sensor excitation: generation of bias voltages, sinusoidal waveforms, etc)
- Direct Digital Synthesis (DDS) of waveforms for telecommunications
- Trimming of analog blocks (e.g. offset nulling)
- Feedback components in ADCs

DAC performance parameters

DAC errors

Quantization error

Offset

Gain

Non-linearity $\left\{ \begin{array}{l} \text{INL} \\ \text{DNL} \end{array} \right.$


Noise

Energy of the glitches ($\text{nV} \cdot \text{s}$)

DAC speed: settling time, sample per seconds (sps),


Maximum output current

Power consumption

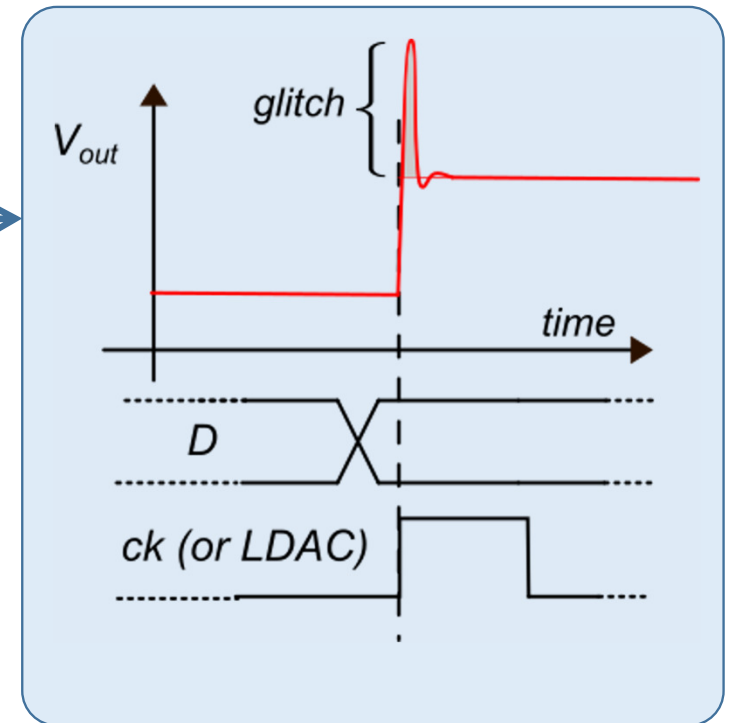


INL, DNL

 
Ideal case
(absence of non-linearity errors)


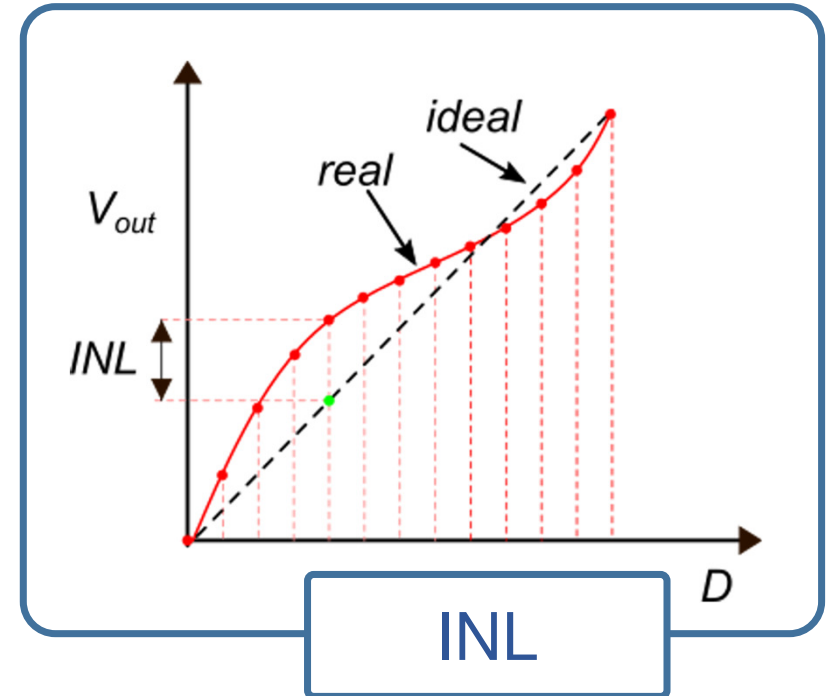
$$LSB \equiv \Delta = \frac{V_{FS}}{2^n}$$



real case

 


$$DNL_k = \frac{LSB_k - LSB}{LSB} \quad (Unit = LSB)$$

$|DNL| > 1$ LSB: non-monotonicity

DAC Architectures

	Pros	Cons
R-2-R ladder	Reduced number of resistor of similar value	Potentially non-monotonic Suffer from the on-resistance of the switches
Resistor String	Guaranteed monotonic Low power consumption	Very large number of resistors
Current Steering	Very fast. No need for resistors. Can be designed to be always monotonic	Current output. Flicker Noise
Switched Capacitors	Optimal power vs speed trade-off	The output may be not available in the whole clock cycle. Large glitches

DAC resistor string

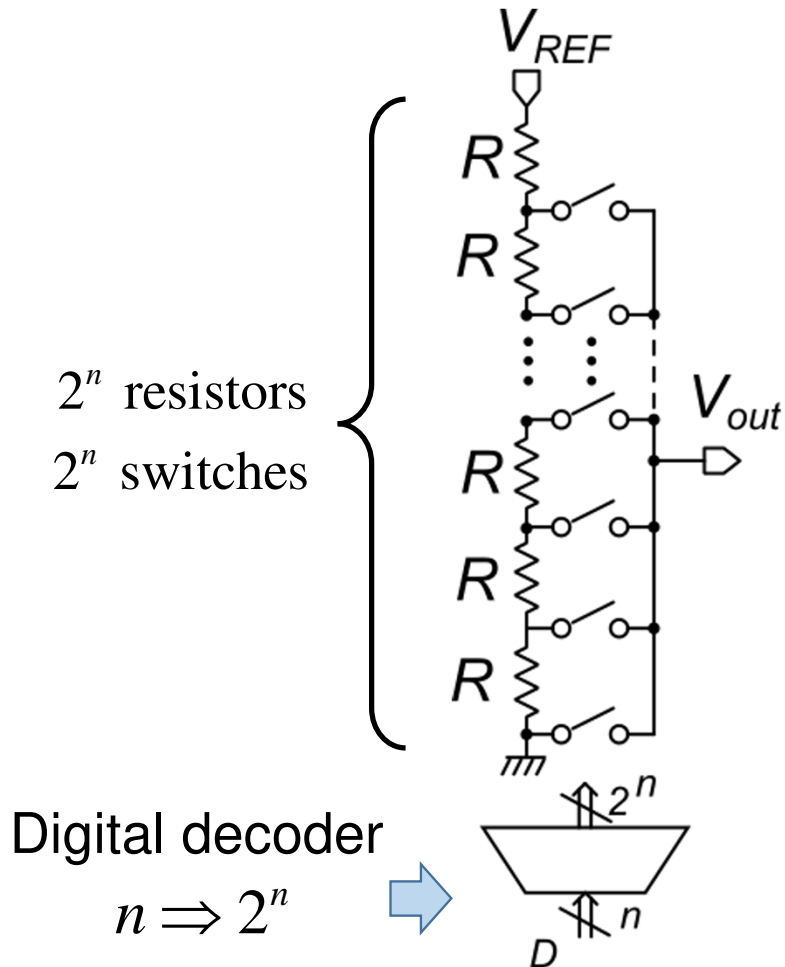

For any value of code D , only one switch at a time is on, selecting one of the 2^n voltage levels produced by the resistive divider

If code D turns on a certain switch, code $D+1$ turns on the switch placed in position up, then the output voltage can only grow

The monotonicity is guaranteed

INL in a resistor string: a simple estimate

We consider a code that, in the ideal case, select the mid voltage:


$$\Rightarrow V_{out-id} = \frac{V_{REF}}{2}$$

Ideally $R_1 = R_2$

In a real case: $R_1 = \bar{R} + \frac{\Delta R}{2}$, $R_2 = \bar{R} - \frac{\Delta R}{2}$

$$V_{out} = V_{ref} \frac{R_1}{R_1 + R_2} = \frac{\bar{R} + \frac{\Delta R}{2}}{2\bar{R}} = \frac{V_{ref}}{2} \left(1 + \frac{\Delta R}{2\bar{R}} \right)$$
 
$$\left\{ \begin{array}{l} V_{INL} = \frac{V_{ref}}{2} \frac{\Delta R}{2\bar{R}} \\ LSB = \frac{V_{REF}}{2^n} \end{array} \right. \quad \frac{V_{INL}}{LSB} = \frac{2^n}{V_{ref}} \frac{V_{ref}}{2} \frac{\Delta R}{2\bar{R}} = 2^{n-2} \frac{\Delta R}{\bar{R}}$$



INL and resistor matching

$$\frac{V_{INL}}{LSB} = 2^{n-2} \frac{\Delta R}{\bar{R}}$$

In an n-bit DAC, to have an $|INL| < 1$ LSB, the relative matching errors should be:

$$2^{n-2} \frac{\Delta R}{\bar{R}} < 1 \quad \Rightarrow \quad \frac{\Delta R}{\bar{R}} < \frac{1}{2^{n-2}}$$

Example: 12 bit DAC:

$$\frac{\Delta R}{\bar{R}} < \frac{1}{2^{10}} \cong 10^{-3}$$


Feasible, with large area occupation

Example: 16 bit DAC:

$$\frac{\Delta R}{\bar{R}} < \frac{1}{2^{14}} \cong 6 \times 10^{-5}$$

Unfeasible. Requires complicated post-production trimming

Current Steering DAC

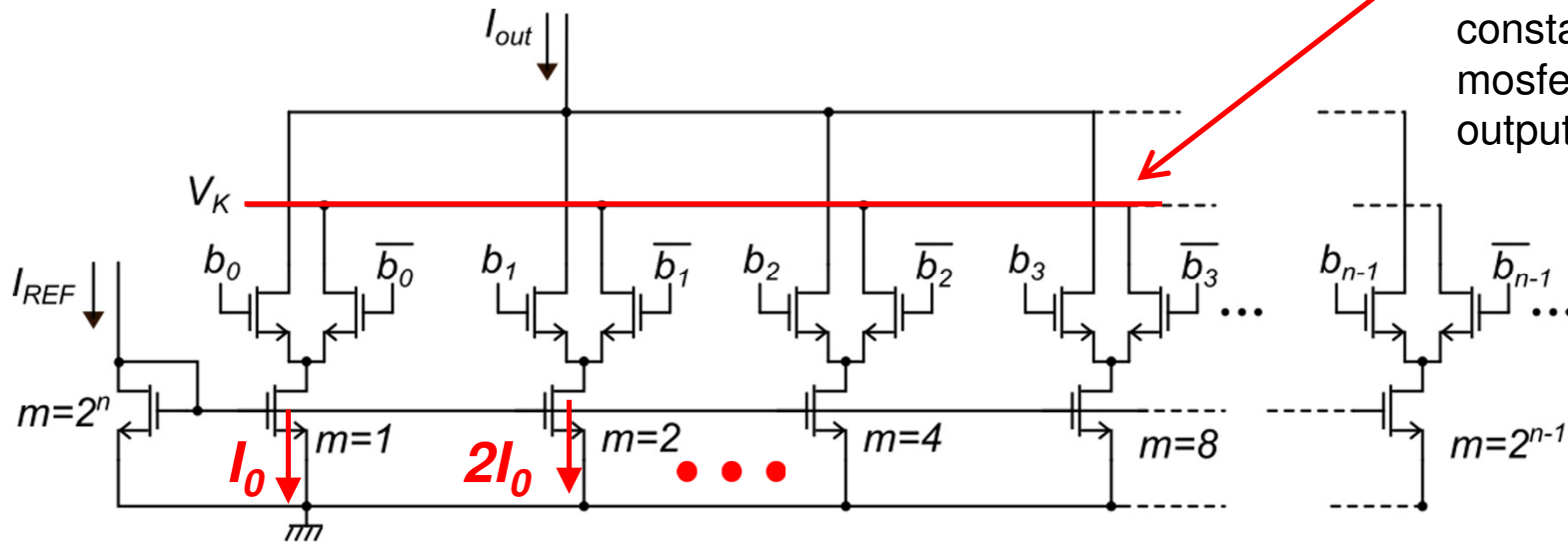

The current of mosfets that are not routed to the output (their bit is 0), is not interrupted but is routed to a constant voltage (V_K) to keep the mosfet ready to be connected to the output in a short time



$$I_0 = \frac{I_{REF}}{2^n}$$

$$I_{out} = I_0 \sum b_k 2^k = \frac{I_{REF}}{2^n} \sum b_k 2^k = \frac{I_{REF}}{2^n} D \rightarrow D = \sum b_k 2^k$$

It can be made monotonic-guaranteed by driving the 2^n mosfets of the array with thermometric coding


It suffers from the same INL problem of the resistor string DAC

Thermometric coding

 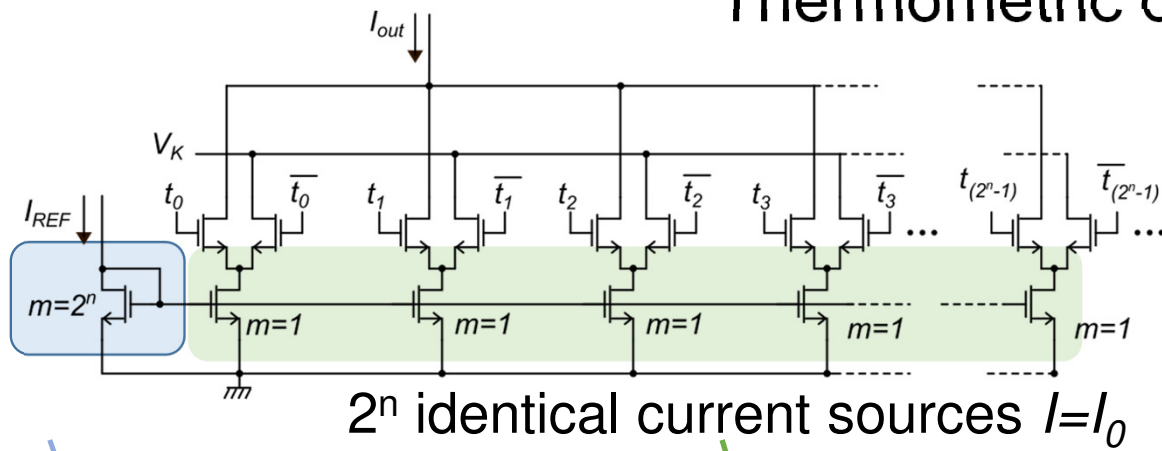


thermometric coding

randomly placed
into the matrix

 


2^n devices
(always in parallel)

 

2^n devices

 D devices
of the matrix
are routed to
the output




The first D lines are
set to 1

*If D is incremented by one,
one more device is routed to
the output: I_{out} increases.
Monotonicity is guaranteed*

Capacitive DAC

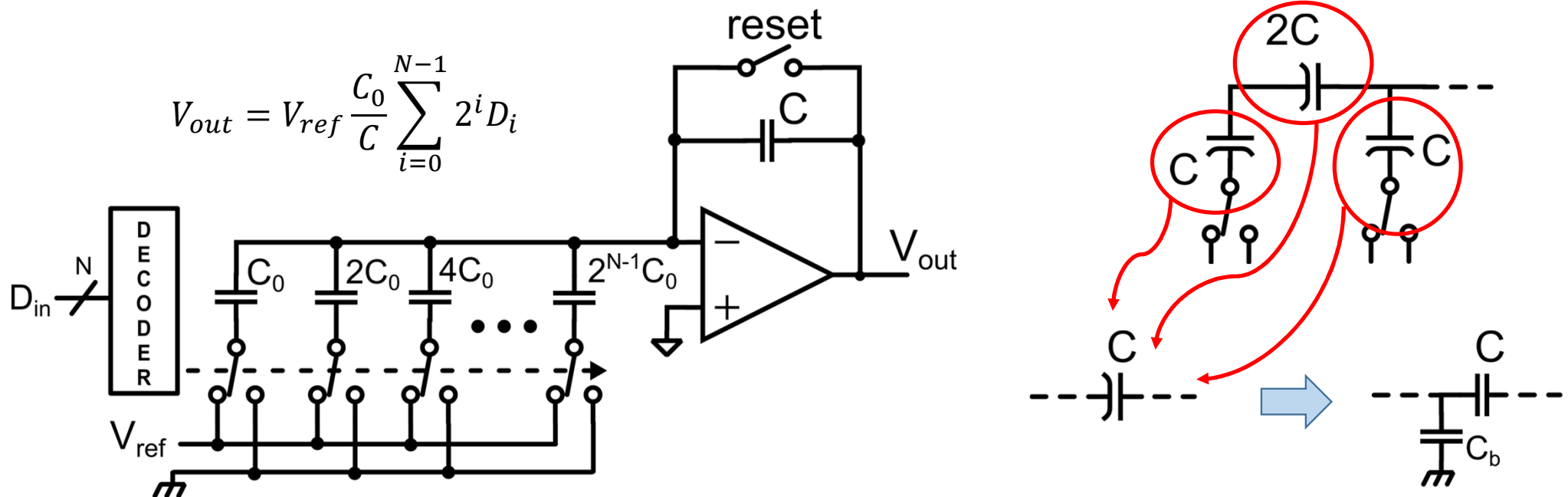
- Capacitor bank has better matching properties than resistor string
- Low-power solution (no static consumption in the capacitor bank)
- Output not always valid
- Troubles with C-2C solutions due to parasitic capacitance of the bottom plate



DAC Comparison

	Type	Accuracy	Current consumption	Speed
Voltage	Resistor string, R-2R	Up to 12 bit	1 μ A – 1 mA	Up to 100 MS/s (limited by buffer)
Current	Current steering, I-2I	Up to 10 bit	10 μ A – 30 mA	Up to 10 GS/s
Charge	Capacitor bank	Up to 14 bit	1 nA – 10 μ A	Up to 100 MS/s (limited by buffer)

Analog to Digital Converters

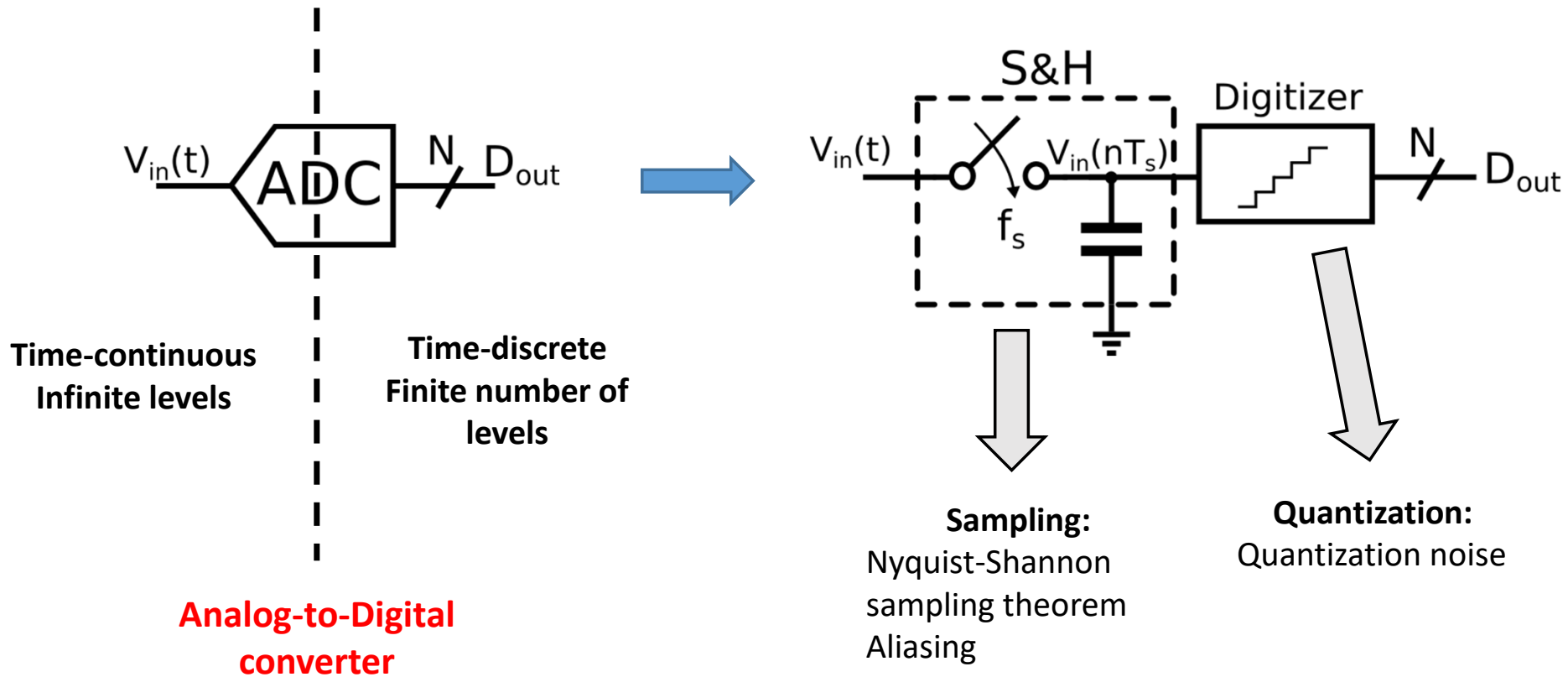


ADC applications

- Measurements and data acquisition
- Industrial (control systems, PLCs, ...)
- Sensor integration (robotics, IoT, ...)
- Commercial electronics (mobile phones, video and audio devices, microcontrollers ...)
- High-speed communications (data link, IF conversion...)

Analog to Digital Converters (ADCs)

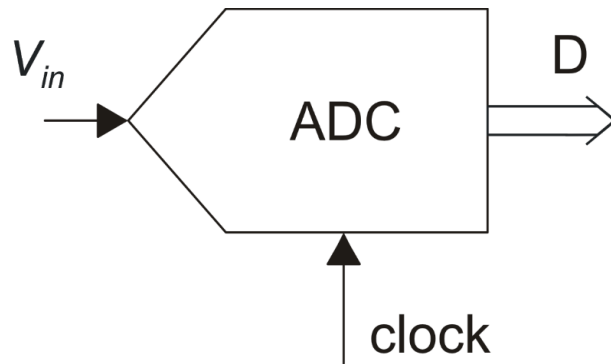
The characteristic of an n-bit ADC with no offset, gain, and non-linearity errors (only quantization errors)



It is useful to refer to the equivalent voltage of D

$$v_{in-dig} = V_{MIN} + \frac{V_{FS}}{2^n} D$$

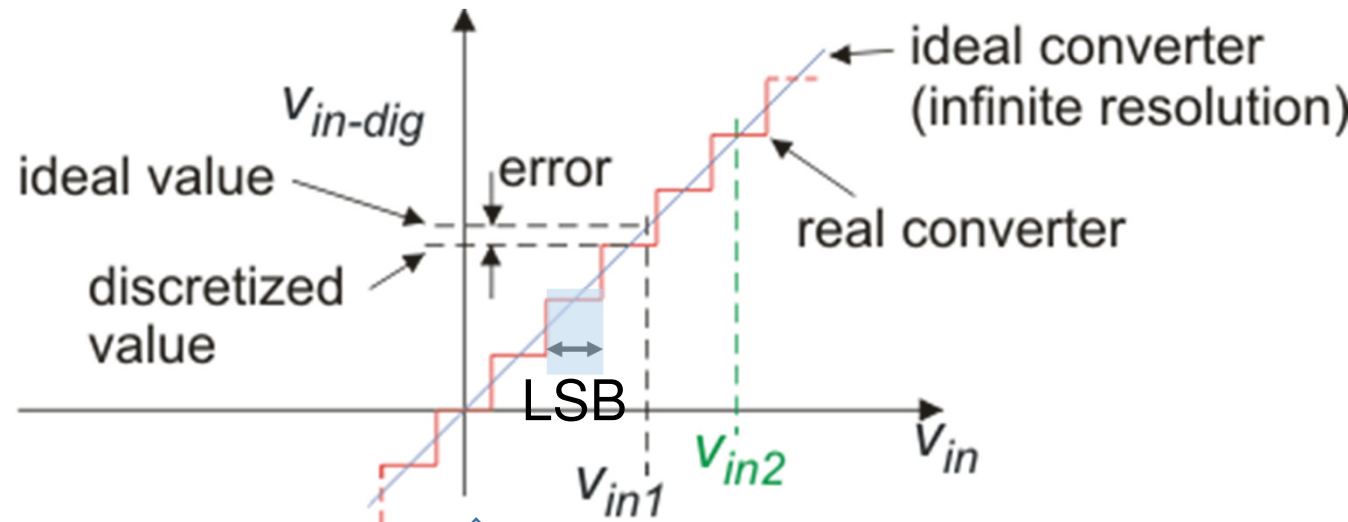
v_{in-dig} must be the best approximation of v_{in} , given the number of bit of D



$$\Delta \equiv LSB = \frac{V_{FS}}{2^n}$$

ADCs - Main Performances

Speed

 

Depending on f_s :

- Nyquist Rate ADCs
- Oversampling ADCs

Resolution

$$ENOB = \frac{SINAD - 1.76}{6.02}$$

Effective Number of Bits

Signal to Noise And Distortion ratio

Affected by:

- quantization noise
- electrical noise
- harmonic distortion

Power consumption

$$P_D \propto f_s$$

Depending on the ADC architecture:

$$P_D \propto \begin{cases} N & \text{Pipeline} \\ N^2 & \text{SAR} \\ 2^N & \text{Flash} \\ 2^{2N} & \text{Thermal noise limited} \end{cases}$$

N : ADC resolution

Nyquist-Rate vs. Oversampling ADCs

Nyquist Rate ADC: $f_s \cong 2B_s$
 $f_s \cong f_{s-Nyq}$


The output code depends only on the last conversion.
Previous conversions do not affect the present code

Oversampling ADC: $f_s \gg 2B_s$
 $f_s \gg f_{s-Nyq}$


The output code depends also on the previous history of sampled data.

ADCs – Static Parameters

 - **Offset error:** difference between the actual ADC characteristic and the perfect ADC characteristic, evaluated at the zero transition



 
- **Gain error:** difference between the last step midpoint of the actual ADC and the last step midpoint of the ideal ADC, after the compensation of the offset error




http://ww1.microchip.com/downloads/en/appnotes/atmel-8456-8-and-32-bit-avr-microcontrollers-avr127-understanding-adc-parameters_application-note.pdf

ADCs – Static Parameters

 - **DNL error:** difference in the step width between the actual characteristic and the ideal one



 - **INL error:** vertical difference between the actual input-output characteristic and the ideal one, after the compensation of the offset and gain error



http://ww1.microchip.com/downloads/en/appnotes/atmel-8456-8-and-32-bit-avr-microcontrollers-avr127-understanding-adc-parameters_application-note.pdf

ADCs – Static Parameters

Complete 12-Bit, 40 MSPS Monolithic A/D Converter

AD9224

Parameter	Min	Typ	Max	Units
ACCURACY				
Integral Nonlinearity (INL)		±1.5	±2.5	LSB
Differential Nonlinearity (DNL)		±0.33	±1.0	LSB
No Missing Codes Guaranteed	12			Bits
Zero Error (@ +25°C)		±0.12	±0.3	% FSR
Gain Error (@ +25°C) ¹		±0.3	±2.2	% FSR
Gain Error (@ +25°C) ²		±0.4	±1.6	% FSR

NOTES
¹Includes internal voltage reference error.
²Excludes internal voltage reference error.

Typical Performance Characteristics (AVDD, DVDD = +5 V, F_s = 40 MHz [50% duty cycle] unless otherwise noted.)

PRODUCT DESCRIPTION

The AD9224 is a monolithic, single supply, 12-bit, 40 MSPS, analog-to-digital converter with an on-chip, high performance sample-and-hold amplifier and voltage reference. The AD9224 uses a multistage differential pipelined architecture with output error correction logic to provide 12-bit accuracy at 40 MSPS data rates, and guarantees no missing codes over the full operating temperature range.

 


Figure 2. Typical DNL

 


Figure 5. Typical INL

ADCs – Dynamic Parameters



$$SNR = \frac{P_S}{P_N}$$

$$THD = \frac{P_D}{P_S}$$


$$SINAD = \frac{P_S}{P_N + P_D} = (SNR^{-1} + THD)^{-1}$$

(or SNDR)

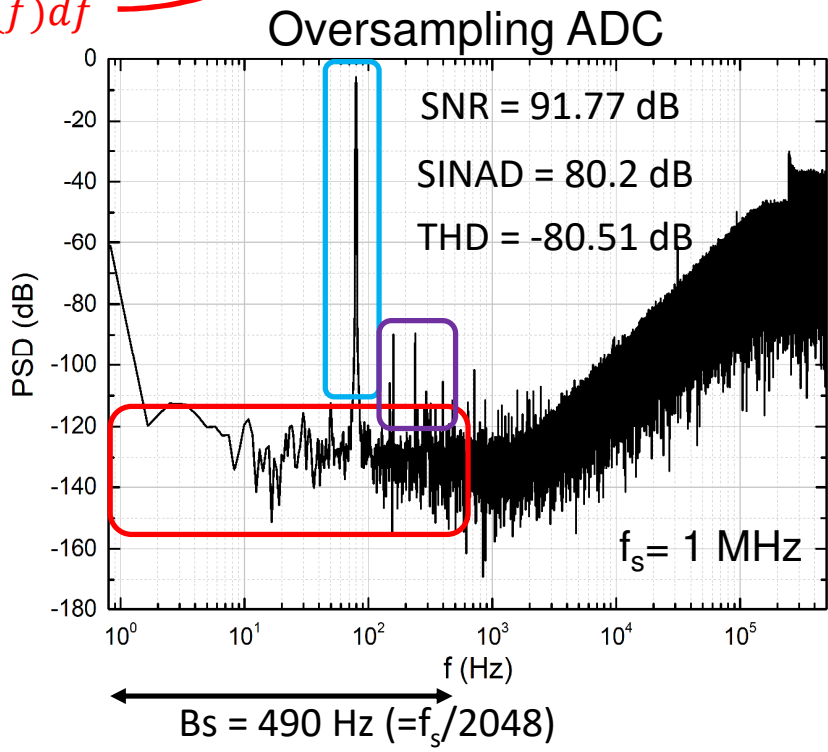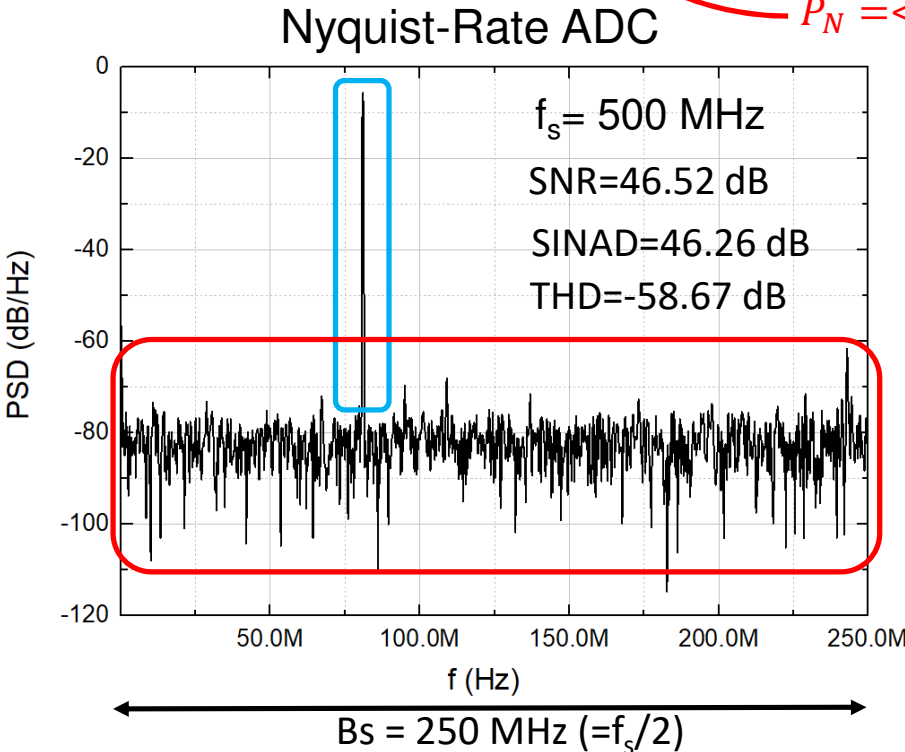
$$P_N = \langle v_n^2 \rangle = \int_0^{B_S} S_{v_n}(f) df$$



 Quantization noise in the frequency domain




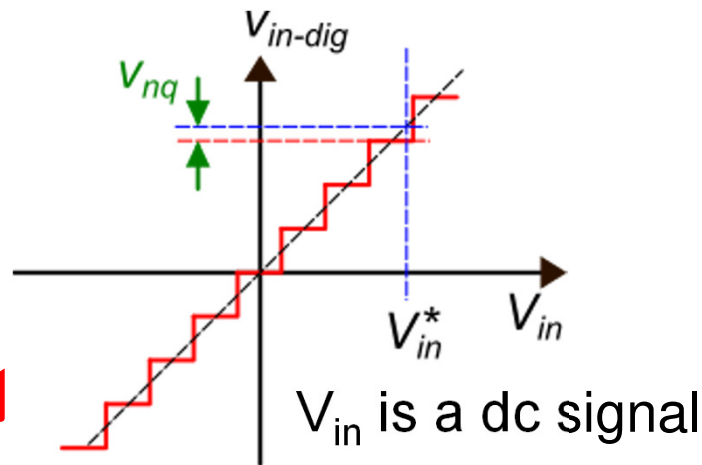Since the ADC samples the input data, the output frequency domain is $[-f_s/2, +f_s/2]$




V_{in} is a dc signal


The v_{nq} spectrum is a Dirac delta

 

Two extreme cases

 


 V_{in} is fast-varying signal of magnitude \gg LSB



uniform distribution

 The uniform power spectral density (PSD) model for the quantization noise



$$\Delta = \frac{V_{FS}}{2^N} = LSB$$

$$\langle v_{nq}^2 \rangle = \frac{\Delta^2}{12}$$

This model is very useful and simple **but should be applied with much care.**

In real cases, the quantization noise depends on the input signal, and so does its spectrum.


The uniform spectral density model is acceptable when the input signal has **magnitude** and/or **frequency** such that the output levels are changed in a **fast** and almost **random** way.

This happens when the average time spent by the signal on a single level is short (of the order of the sampling time).

Signal to Noise Ratio and resolution

$$SNR_{max} = \frac{P_{MAX}}{\langle v_n^2 \rangle}$$

Input range of the ADC

 

$$P_{MAX} = \frac{V_{FS}^2}{8}$$


Considering only quantization noise: $\langle v_{nq}^2 \rangle = \frac{\Delta^2}{12}$ $SNR = SQNR = \frac{V_{FS}^2}{8} \frac{12}{\Delta^2} = \frac{3}{2} \frac{V_{FS}^2}{\Delta^2}$

$$\Delta = \frac{V_{FS}}{2^n} \quad SQNR = \frac{V_{FS}^2}{2} \frac{3 \cdot 2^{2n}}{V_{FS}^2} = \frac{3}{2} \cdot 2^{2n}$$

$$SQNR_{dB} = 10 \log_{10} (SQNR) \cong 6.02n + 1.76$$

Effective Number Of Bits (ENOB)

 Distortion and SFDR (spurious free dynamic range)



P_D = total power of the harmonics

$$SINAD = \frac{P_{MAX}}{\langle v_n^2 \rangle + P_D}$$

Also indicated with *SNDR*

Quantization and electrical noise

$$SQNR_{dB} = 10 \log_{10} (SQNR) \cong 6.02n + 1.76$$


$$SINAD_{dB} \cong 6.02 \cdot ENOB + 1.76$$

$$ENOB = \frac{SINAD_{dB} - 1.76}{6.02}$$

ADCs – Figure of Merits


Walden FoM:
 
$$FoM_W = \frac{P_D}{f_{s-Nyq} 2^{ENOB}} \text{ [J/conv]}$$




Schreier FoM:

$$FoM_S = SNDR \Big|_{dB} + 10 \log \left(\frac{f_{s-Nyq}/2}{P_D} \right) \text{ [dB]}$$

 



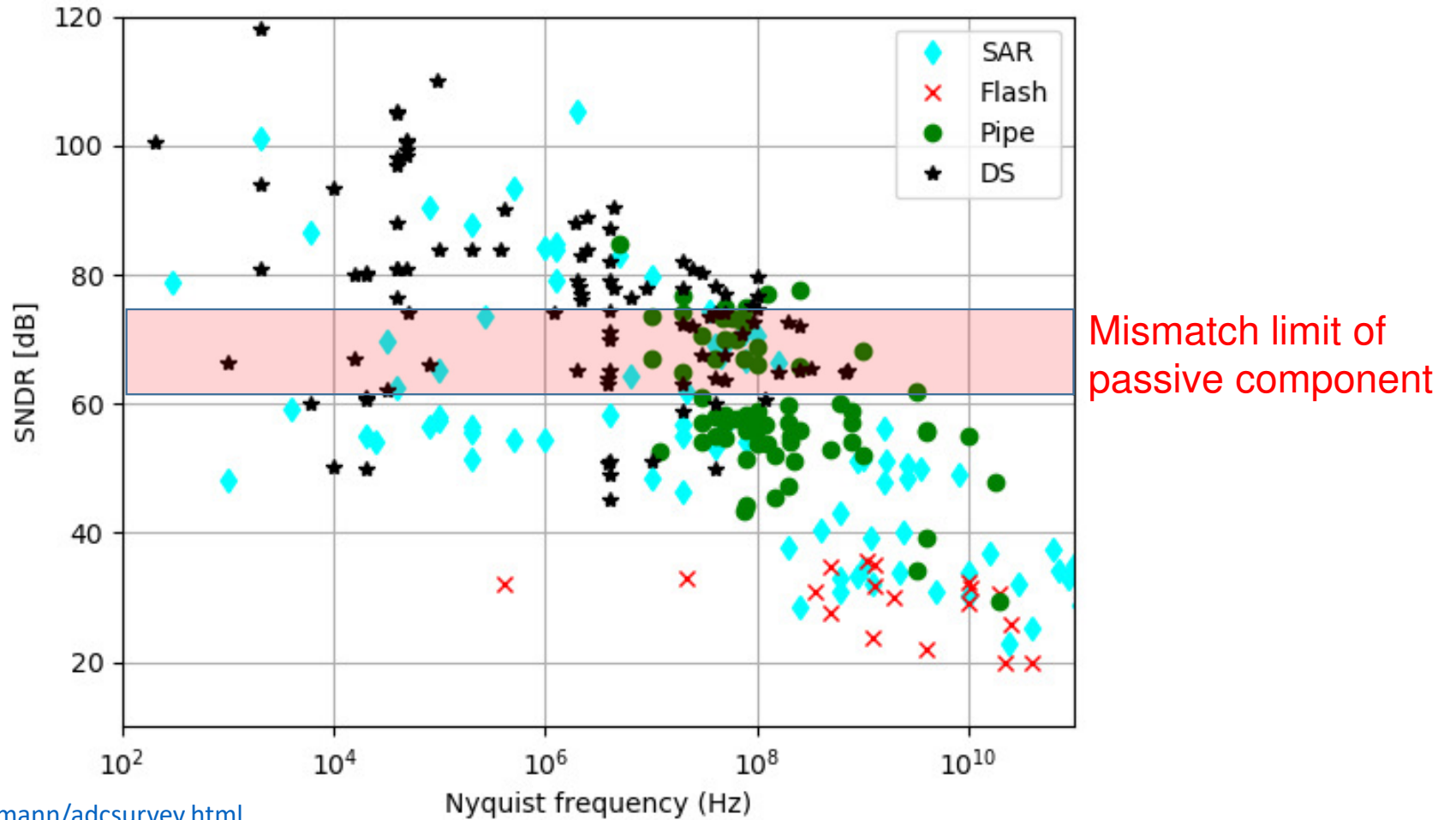


Comparison of different topologies




<https://web.stanford.edu/~murmans/adcsurvey.html>

Nyquist rate ADCs

N-bit ADC

- Direct conversion:
 - Flash converters  1 cycle of comparison
(fast but with low resolution)
- Counting and Integrating ADCs:
 - Counting converters 
 - Dual-slope  2^N cycles of comparison
(simple/accurate but slow)
- Binary-Search Algorithm based:
 - Successive approximation converters (SAR) 
 - Pipelined converters  N cycles of comparison
(good trade-off speed/resolution)

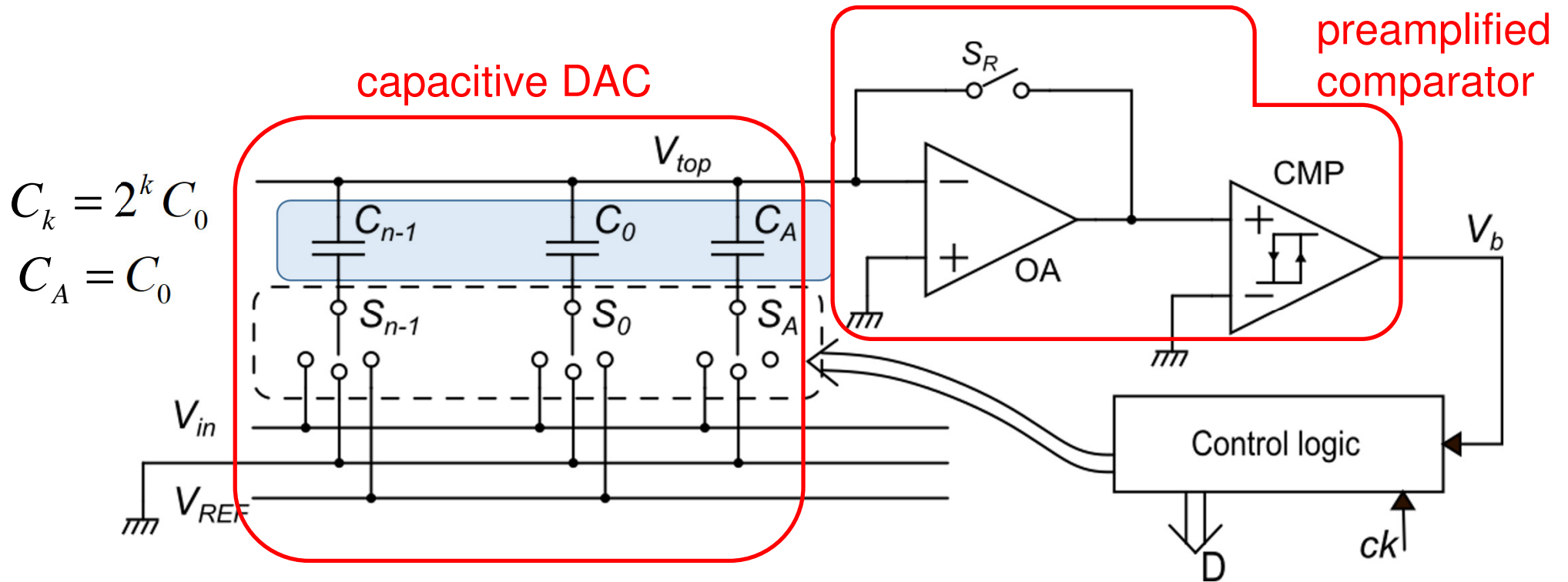A very common SAR ADC: the charge-redistribution ADC




$$C_{tot} = C_A + \sum_{k=0}^{n-1} C_k = C_0 + C_0 \sum_{k=0}^{n-1} 2^k = C_0 + C_0 (2^n - 1) = 2^n C_0$$

Reset phase


analog input
signal $V_{in} \geq 0$

The op-amp is closed
in unity gain

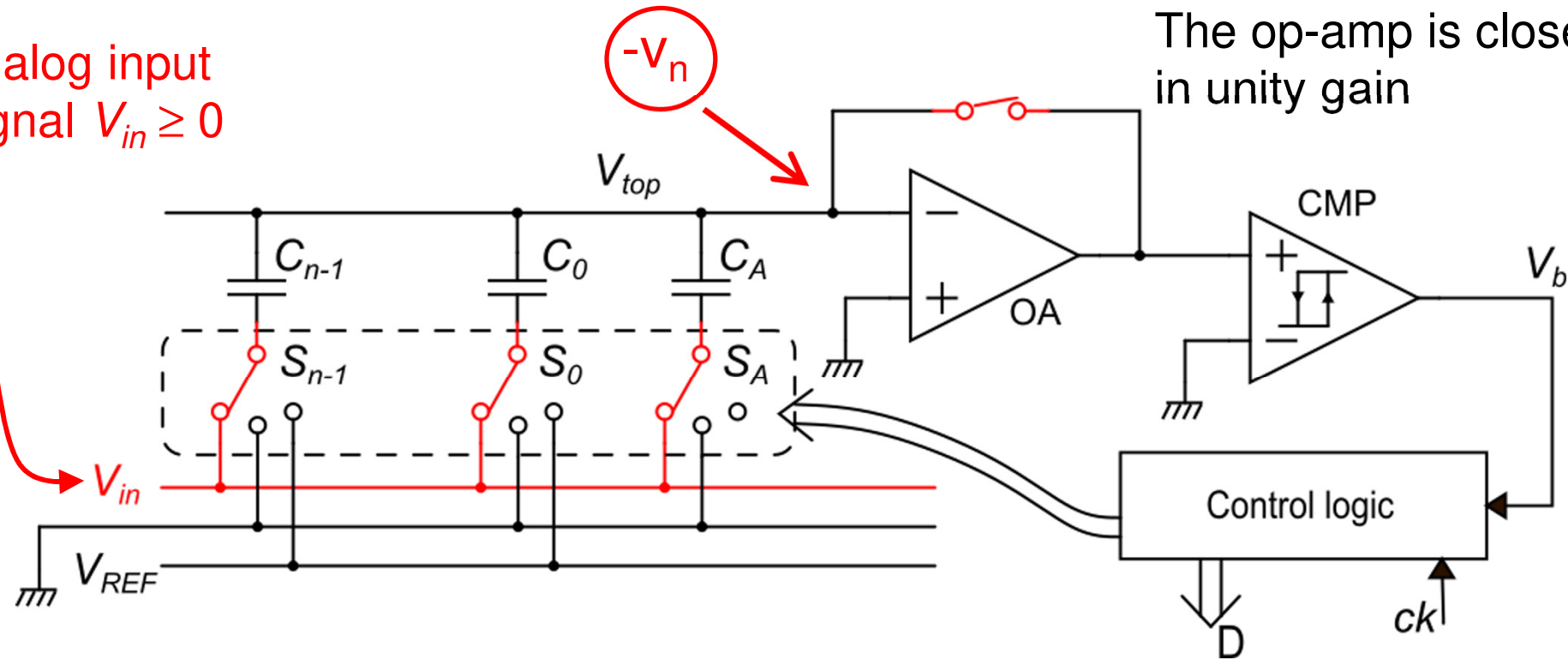


All capacitors are in parallel, with one terminal connected to the input voltage V_{in} .


Sampling phase

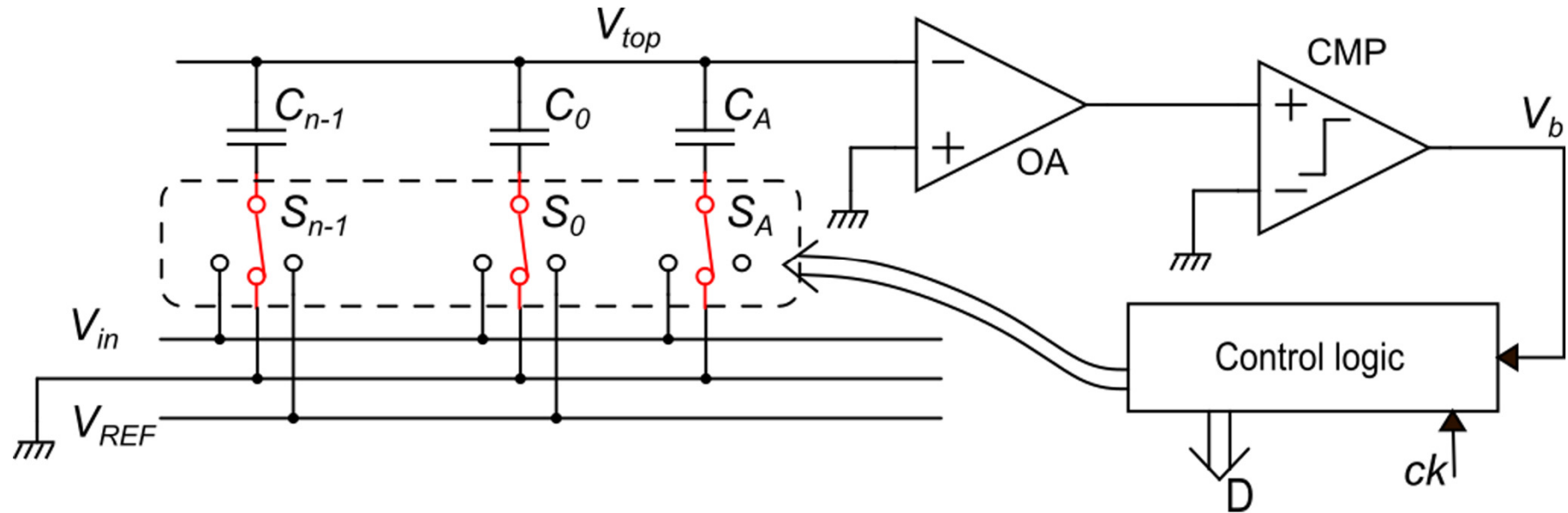

- The op-amp is placed in open loop configuration and the bottom plates of all capacitors are connected to gnd.
- The voltage of the top plates (V_{top}) is free to evolve (it is floating, no current comes from the OP to V_{top})


Top voltage in the sampling phase

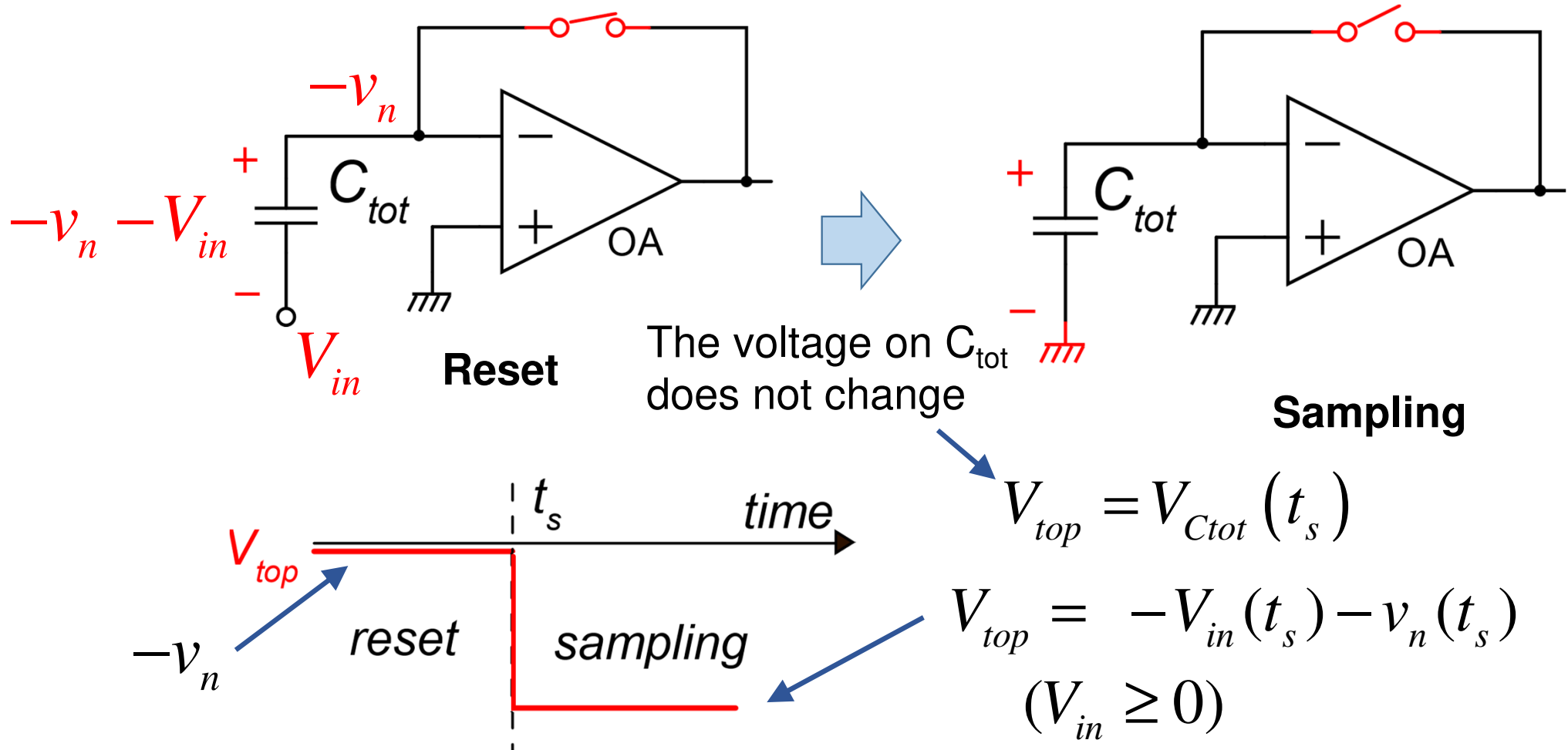

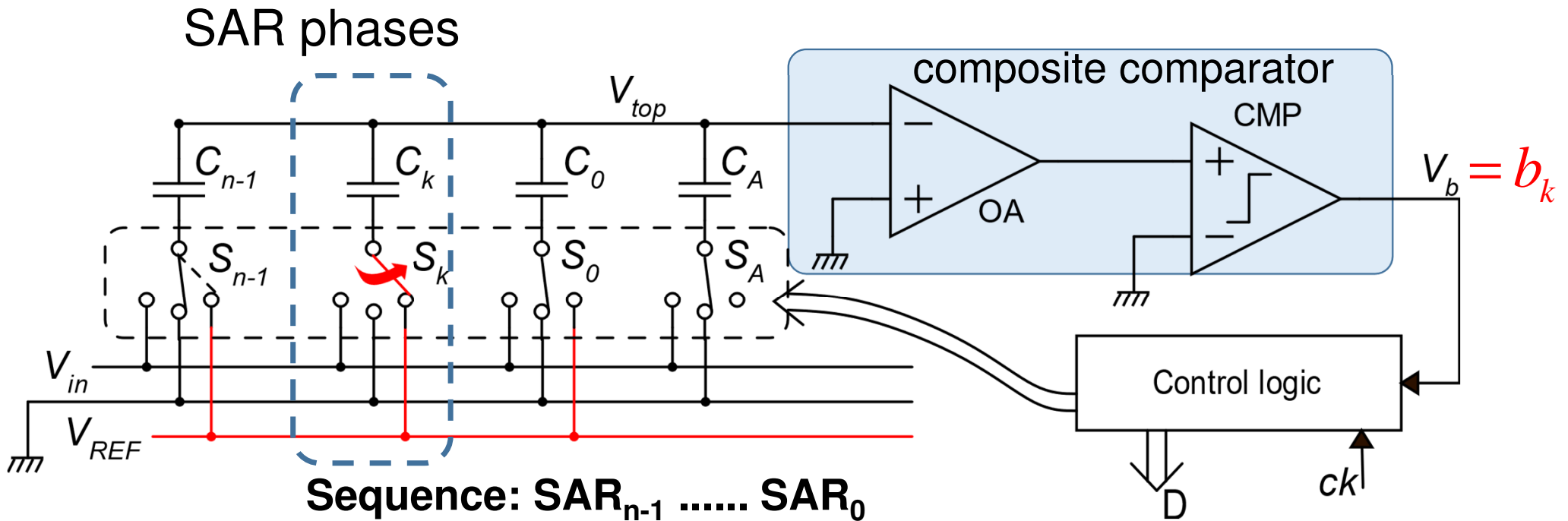

- Phase SAR_k
- Phase SAR_k begins by connecting the bottom plate of C_k to the reference voltage V_{REF} through switch S_k
 - This causes a jump in voltage V_{top} .
 - Bit k-th is the output of the composite comparator (V_b) at the end of phase SAR_k
 - If $b_k = 0$ S_k comes back to gnd , else it remains at V_{REF}

Composite comparator

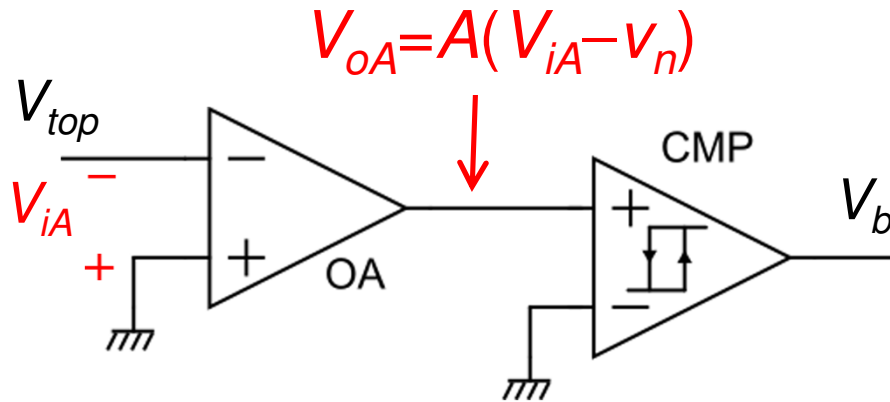




The gain of OA is so large that the offset and hysteresis of CMP has negligible impact on the composite comparator characteristics.

$$V_{iA} = -V_{top}$$

$$V_b = \begin{cases} 1 & \text{if } V_{iA} > v_n \\ 0 & \text{if } V_{iA} \leq v_n \end{cases}$$

$$V_b = \begin{cases} \underline{1} & \text{if } -V_{top} > v_n \Leftrightarrow \underline{V_{top} < v_n} \\ \underline{0} & \text{if } -V_{top} \leq v_n \Leftrightarrow \underline{V_{top} \geq v_n} \end{cases}$$

  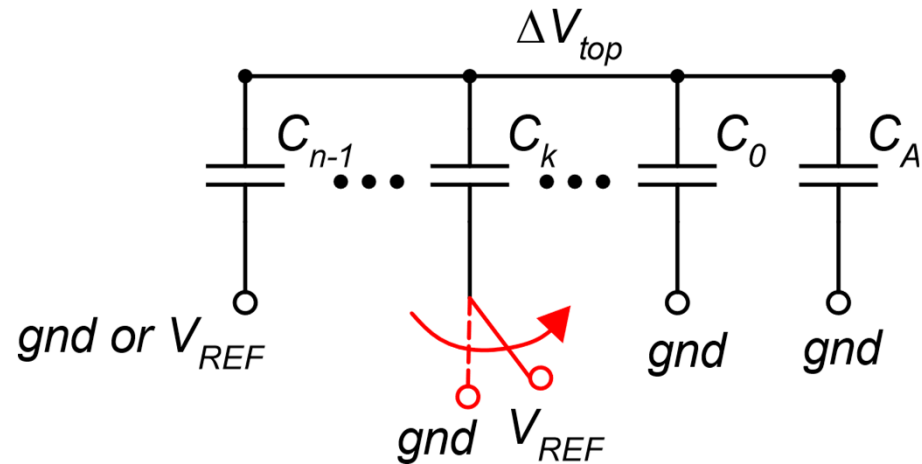Phase \mathbf{SAR}_k : calculation of the V_{top} jump



ΔV_{top} at phase \mathbf{SAR}_k


$$\Delta V_{top} = \Delta V_k = \Delta V \frac{C_k}{C_{tot}} = V_{REF} \frac{2^k C_0}{2^n C_0}$$

$$V_{LSB} = \frac{V_{REF}}{2^n} = \Delta$$

$$\Delta V_k = 2^k V_{LSB}$$

All-capacitor network:
equivalent circuit for
variations. Capacitors
can be replaced by a
resistors of value $1/C$

Phase SAR_{n-1}

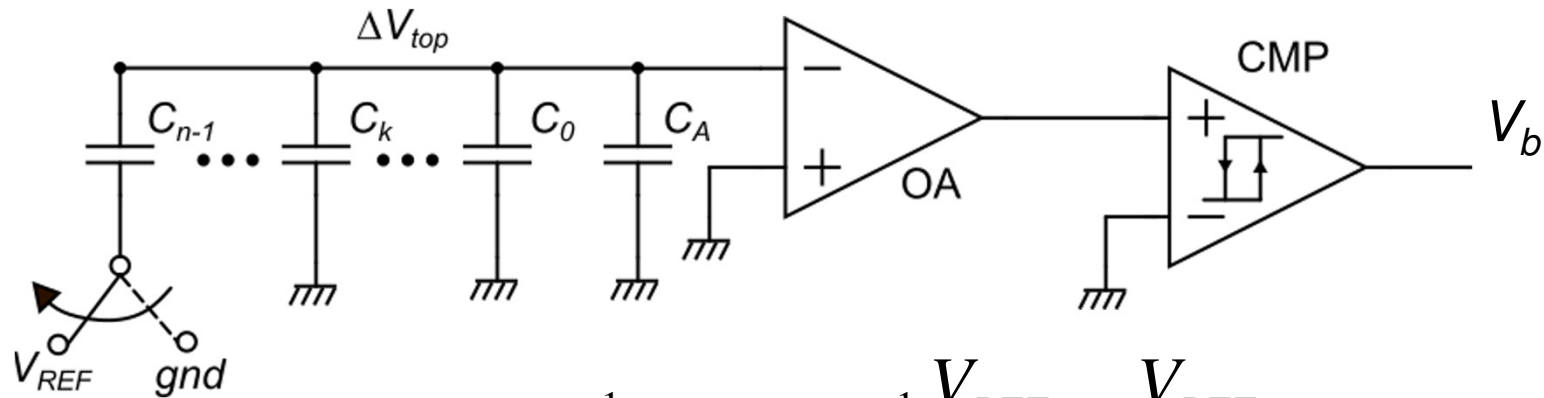

$$\Delta V_{n-1} = 2^{n-1} V_{LSB} = 2^{n-1} \frac{V_{REF}}{2^n} = \frac{V_{REF}}{2}$$

from sampling phase

$$V_{top} = \overbrace{-V_{in}(t_s) - v_n(t_s)} + \Delta V_{n-1} = -V_{in}(t_s) - v_n(t_s) + \frac{V_{REF}}{2}$$

Decision for bit b_{n-1} (taken at time t_{n-1} = end of phase SAR_{n-1})

$$V_b = 1 \text{ if } V_{top}(t_{n-1}) < -v_n(t_{n-1}) \implies -V_{in}(t_s) - v_n(t_s) + \frac{V_{REF}}{2} < -v_n(t_{n-1})$$

Phase SAR_{n-1}

$$b_{n-1} = 1 \text{ if: } -V_{in}(t_s) - v_n(t_s) + \frac{V_{REF}}{2} < -v_n(t_{n-1})$$


$$V_{in}(t_s) > \frac{V_{REF}}{2} - \underbrace{v_n(t_s) + v_n(t_{n-1})}$$

Subtraction of two noise samples taken at different times: constant and correlated components are rejected (CDS).

Neglecting noise / offset components, the condition becomes:


$$V_{in}(t_s) > \frac{V_{REF}}{2}$$

 possible values
of $V_{in}(t_s)$ and resulting
value of b_{n-1}



This is in conformity with the successive approximation algorithm

Phase SAR_{n-2}

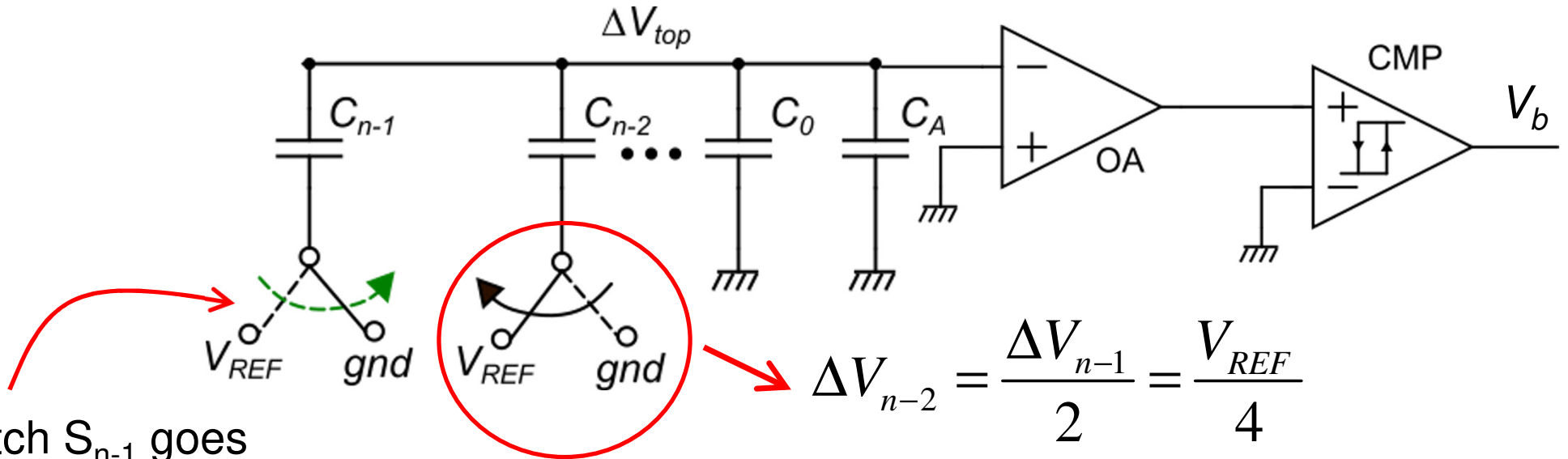

Switch S_{n-1} goes back to gnd if $b_{n-1}=0$. Otherwise, it remains to V_{REF} .

$$\Delta V_{n-2} = \frac{\Delta V_{n-1}}{2} = \frac{V_{REF}}{4}$$


Decision : bit $b_{n-2} = 1$ if:

$$V_{top} = -V_{in}(t_s) - v_n(t_s) + \underline{b_{n-1} \Delta V_{n-1}} + \Delta V_{n-2} < -v_n(t_{n-2})$$

If S_{n-1} comes back to gnd , it subtracts ΔV_{n-1} from V_{top} .

Decision for b_{n-2}
 
$$b_{n-2} = 1 \text{ if: } V_{in}(t_s) > \underbrace{b_{n-1}\Delta V_{n-1} + \Delta V_{n-2}}_{V_{tst}(n-2)}$$



Generalization

At k-th step (phase SAR_k), bit b_k is determined from the comparison of $V_{in}(t_s)$ with:

$$V_{tst}(k) = \underbrace{b_{n-1}\Delta V_{n-1} + b_{n-2}\Delta V_{n-2} + \dots + b_{k+1}\Delta V_{k+1}} + \Delta V_k$$

Increments applied in previous phases and maintained only if the corresponding bits are 1

At any step the increment is halved

$$\Delta V_k = \frac{\Delta V_{k+1}}{2}$$

At the last phase, SAR_0 , the LSB (b_0) is determined and the conversion is complete. The bits determined in the successive phases are stored inside a register of the control logic and can be retrieved at the end of conversion.

Examples of conversion cycle

