
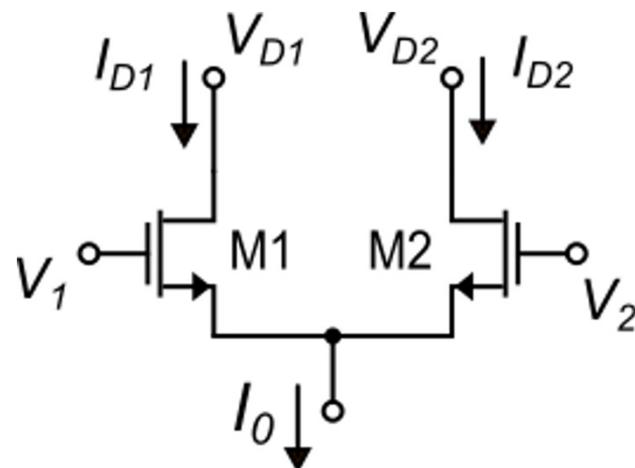

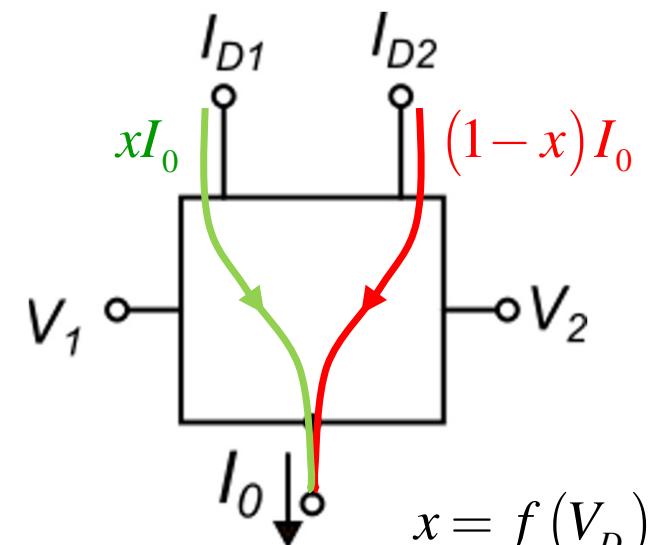
# Source coupled MOSFET pair (differential MOSFET pair)



**Inputs:**  $V_1, V_2$  (effective input signal:  $V_D = V_1 - V_2$ )  
 $I_0$  ("Tail current")


**Outputs:**  $I_{D1}, I_{D2} (I_{D1} - I_{D2})$



## Function

- The input current  $I_0$  is split into  $I_{D1}$  and  $I_{D2}$ , according to fractions  $x$  and  $(1-x)$
- $x$  depends on  $V_D$  ( $x=0.5$  for  $V_D=0$ )
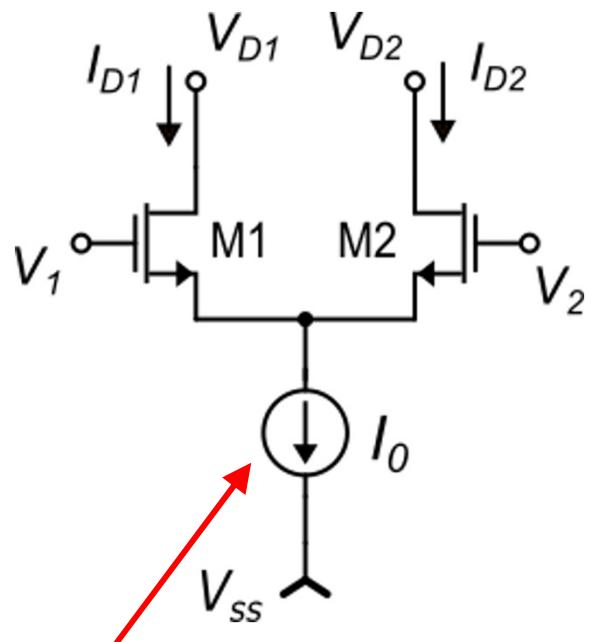
## Analysis of the source coupled MOSFET pair (differential MOSFET pair)



Target: obtain the relationship between the ratio  $x$  and the input differential voltage  $V_D$

$$I_{D1} = xI_0 \quad I_{D2} = (1-x)I_0 \quad \rightarrow \quad x \triangleq \frac{I_{D1}}{I_0}$$


### Hypotheses

- M1 and M2 work in saturation and the effect of  $V_{DS}$  can be neglected
- Strong inversion equation can be applied
- $I_0$  does not depend on  $V_1, V_2$

For this analysis,  $I_0$  is represented as an ideal current source and we will focus on the effect of  $V_D = V_1 - V_2$

$$I_D = \frac{\beta}{2} (V_{GS} - V_t)^2 \Rightarrow V_{GS} = V_t + \sqrt{\frac{2I_D}{\beta}}$$
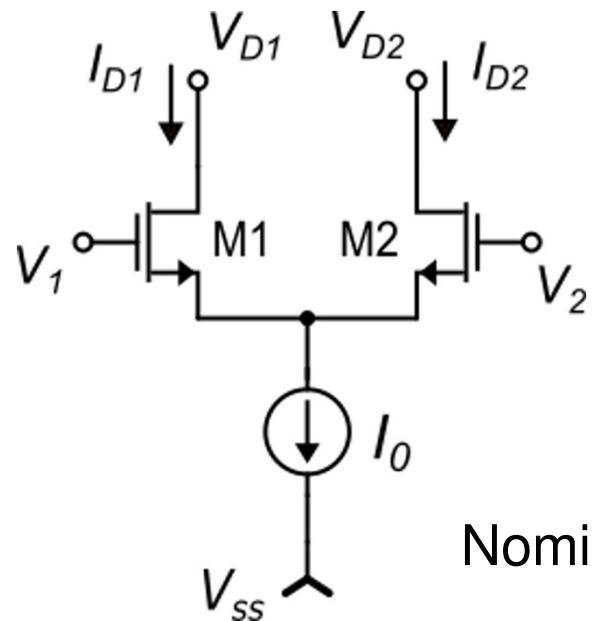
## Analysis of the source coupled MOSFET pair (differential MOSFET pair)



$$\begin{cases} V_1 = V_{S1} + V_{GS1} \\ V_2 = V_{S2} + V_{GS2} \end{cases} \quad V_{S1} = V_{S2} \triangleq V_S$$


$$V_D = V_1 - V_2 = V_{GS1} - V_{GS2}$$

$$V_D = V_{t1} + \sqrt{\frac{2I_{D1}}{\beta_1}} - \left( V_{t2} + \sqrt{\frac{2I_{D2}}{\beta_2}} \right)$$

Nominal conditions:  $M1=M2$ :  $\beta_1=\beta_2=\beta$  and  $V_{t1}=V_{t2}$  ( $V_{BS1}=V_{BS2}$ ).

$$V_D = \sqrt{\frac{2I_{D1}}{\beta}} - \sqrt{\frac{2I_{D2}}{\beta}} = \sqrt{\frac{2}{\beta}} \cdot \left( \sqrt{I_{D1}} - \sqrt{I_{D2}} \right)$$
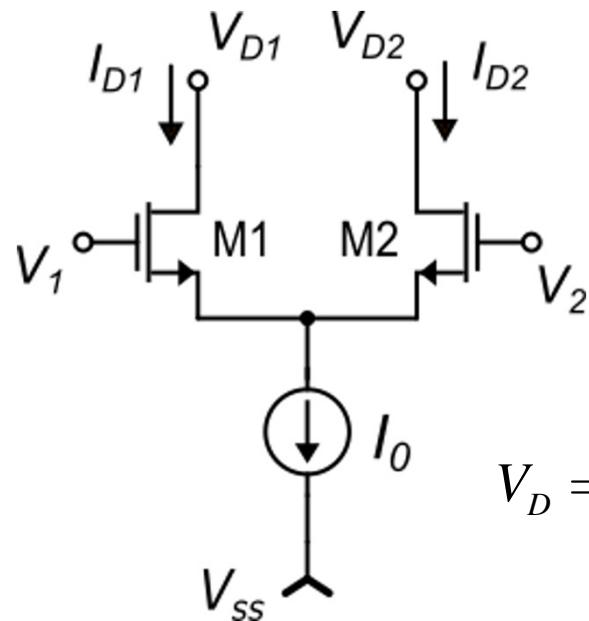
## Analysis of the source coupled MOSFET pair (differential MOSFET pair)



$$V_D = \sqrt{\frac{2I_{D1}}{\beta}} - \sqrt{\frac{2I_{D2}}{\beta}} = \sqrt{\frac{2}{\beta}} \cdot \left( \sqrt{I_{D1}} - \sqrt{I_{D2}} \right)$$

$$I_{D1} = xI_0 \quad I_{D2} = (1-x)I_0$$


$$V_D = \sqrt{\frac{2}{\beta}} \cdot \left[ \sqrt{xI_0} - \sqrt{(1-x)I_0} \right] = \boxed{\sqrt{\frac{2I_0}{\beta}} \cdot \left[ \sqrt{x} - \sqrt{(1-x)} \right]}$$

↓      ↓

$$\sqrt{\frac{2I_0}{\beta}} \triangleq V_{DMAX}$$

$$\frac{V_D}{V_{DMAX}} = \left[ \sqrt{x} - \sqrt{(1-x)} \right]$$
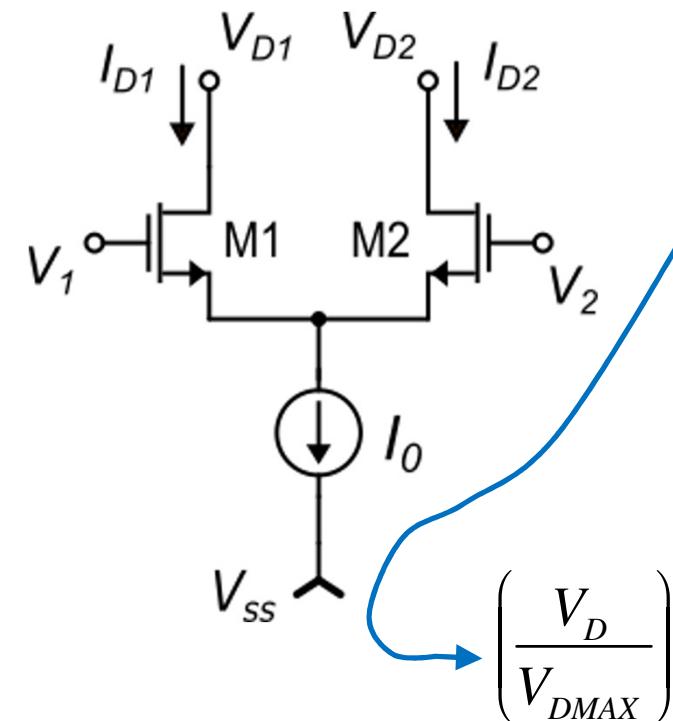
## Analysis of the source coupled MOSFET pair (differential MOSFET pair)



$$\frac{V_D}{V_{D\text{MAX}}} = \left[ \sqrt{x} - \sqrt{(1-x)} \right]$$

Before squaring, we have to note that:

$$V_D > 0 \Rightarrow \sqrt{x} > \sqrt{(1-x)}$$

$$\left( \frac{V_D}{V_{D\text{MAX}}} \right)^2 = x + (1-x) - 2\sqrt{x(1-x)}$$

$$\left( \frac{V_D}{V_{D\text{MAX}}} \right)^2 - 1 = -2\sqrt{x(1-x)}$$


To solve this equation, we have to square both hands. In this way we add new solutions that are not valid.

$$V_D > 0 \Rightarrow x > (1-x)$$

$$V_D > 0 \Rightarrow x > \frac{1}{2}$$

condition 1
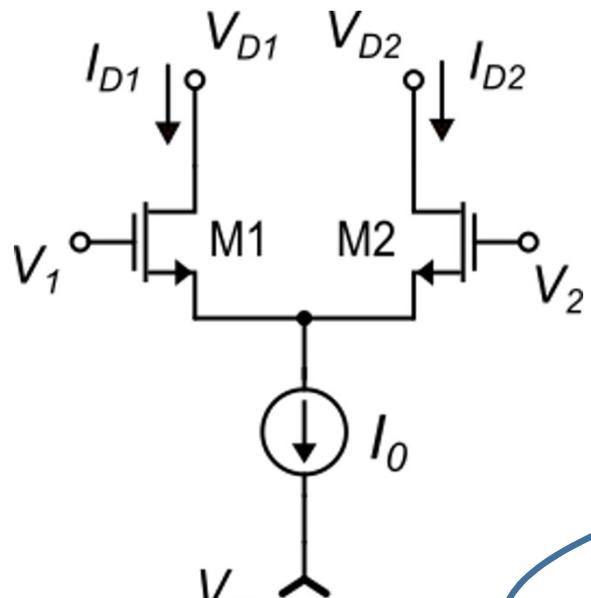
## Analysis of the source coupled MOSFET pair (differential MOSFET pair)



$$\left( \frac{V_D}{V_{D\text{MAX}}} \right)^2 - 1 = -2\sqrt{x(1-x)}$$

We have to square this equation again.  
This time, the condition is:

$$\left[ \left( \frac{V_D}{V_{D\text{MAX}}} \right)^2 - 1 \right]^2 = 4x(1-x)$$

$$\frac{1}{4} \left[ \left( \frac{V_D}{V_{D\text{MAX}}} \right)^2 - 1 \right]^2 = x - x^2$$

$$V_D > 0 \Rightarrow x > \frac{1}{2}$$


condition 1

$$\left( \frac{V_D}{V_{D\text{MAX}}} \right)^2 - 1 \leq 0$$

condition 2

$$x^2 - x + \frac{1}{4} \left[ \left( \frac{V_D}{V_{D\text{MAX}}} \right)^2 - 1 \right]^2 = 0$$
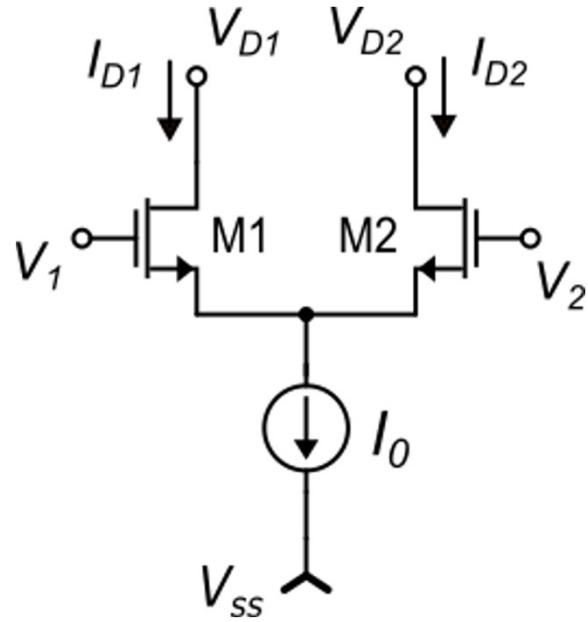
## Analysis of the source coupled MOSFET pair (differential MOSFET pair)



$$V_D > 0 \Rightarrow x > \frac{1}{2}$$

condition 1

$$\left(\frac{V_D}{V_{DMAX}}\right)^2 - 1 \leq 0$$

condition 2

$$x^2 - x + \frac{1}{4} \left[ \left( \frac{V_D}{V_{DMAX}} \right)^2 - 1 \right]^2 = 0$$

$$x = -\frac{b}{2a} \pm \frac{1}{2a} \sqrt{b^2 - 4ac}$$


$$ax^2 + bx + c$$

$$a = 1, b = -1, c = \frac{1}{4} \left[ \left( \frac{V_D}{V_{DMAX}} \right)^2 - 1 \right]^2$$

$$x = \frac{1}{2} \pm \frac{1}{2} \sqrt{1 - \left[ \left( \frac{V_D}{V_{DMAX}} \right)^2 - 1 \right]^2}$$

$$x = \frac{1}{2} \pm \frac{1}{2} \sqrt{1 - \left[ \left( \frac{V_D}{V_{DMAX}} \right)^4 - 2 \left( \frac{V_D}{V_{DMAX}} \right)^2 + 1 \right]}$$
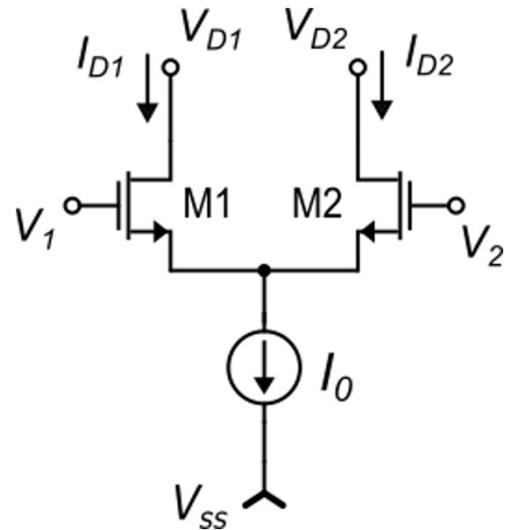
## Analysis of the source coupled MOSFET pair (differential MOSFET pair)



$$x = \frac{1}{2} \pm \frac{1}{2} \sqrt{2 \left( \frac{V_D}{V_{DMAX}} \right)^2 - \left( \frac{V_D}{V_{DMAX}} \right)^4} = \frac{1}{2} \pm \frac{1}{2} \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2}$$


condition 1

$$V_D > 0 \Rightarrow x > \frac{1}{2}$$

$$\begin{cases} x = \frac{I_{D1}}{I_0} = \frac{1}{2} + \frac{1}{2} \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2} \\ 1 - x = \frac{I_{D2}}{I_0} = \frac{1}{2} - \frac{1}{2} \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2} \end{cases}$$


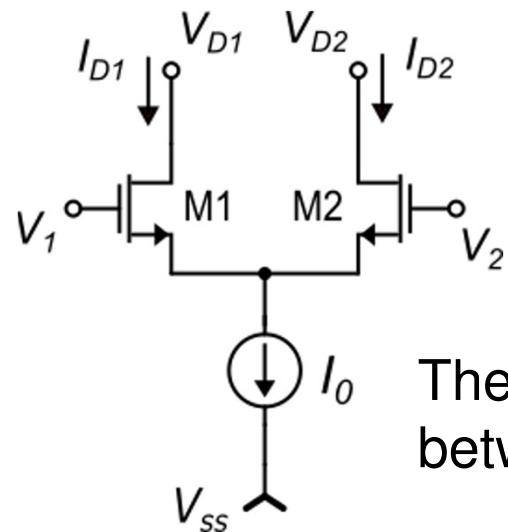
$$\begin{cases} I_{D1} = \frac{I_0}{2} + \frac{I_0}{2} \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2} \\ I_{D2} = \frac{I_0}{2} - \frac{I_0}{2} \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2} \end{cases}$$



$$\left(\frac{V_D}{V_{DMAX}}\right)^2 - 1 \leq 0$$

condition 2


The analysis is applicable only between  $-V_{DMAX}$  and  $+V_{DMAX}$

$$I_{D1} = \frac{I_0}{2} + \frac{I_0}{2} \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2}$$

$$I_{D2} = \frac{I_0}{2} - \frac{I_0}{2} \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2}$$

$$V_D = -V_{DMAX} \Rightarrow I_{D1} = 0$$

$$\left| \frac{V_D}{V_{DMAX}} \right| \leq 1 \Rightarrow -V_{DMAX} \leq V_D \leq V_{DMAX}$$

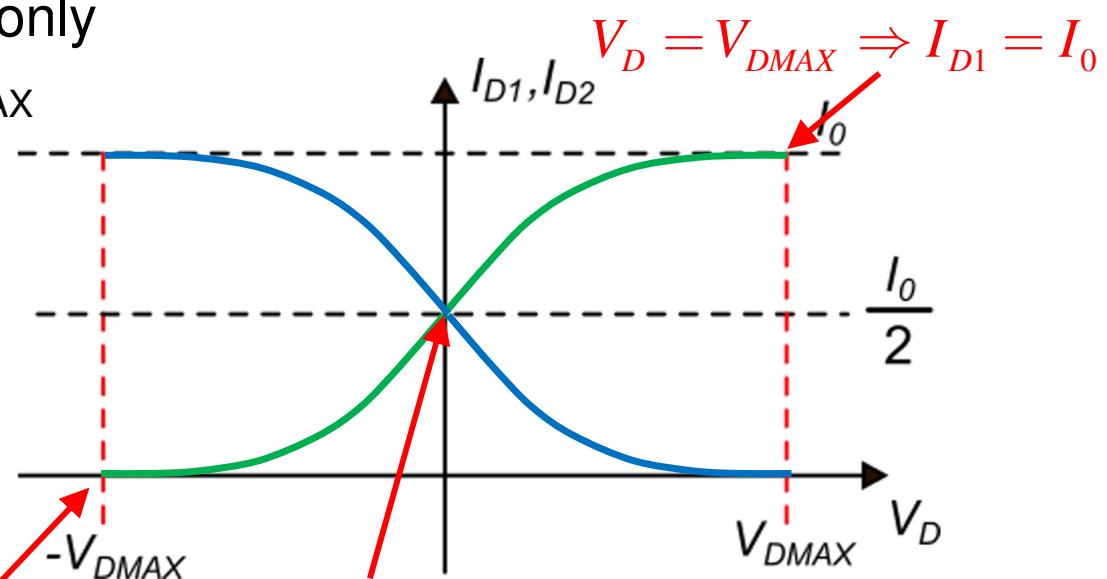


$$V_D = 0 \Rightarrow I_{D1} = \frac{I_0}{2}$$
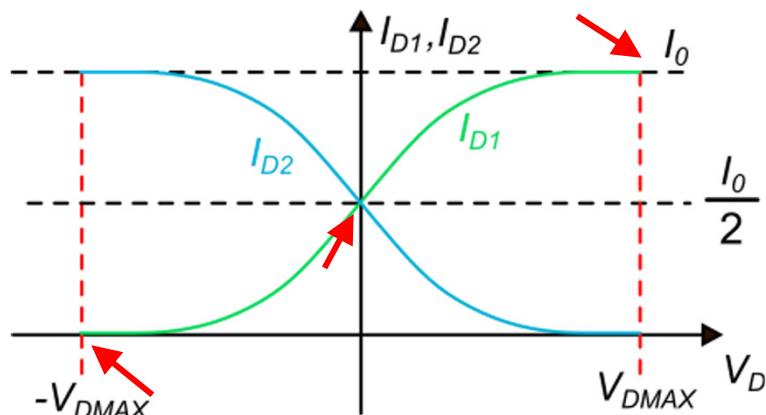
# Derivative of the differential pair input-output curves (optional)


$$I_{D1} = \frac{I_0}{2} + \frac{I_0}{2} \left( \frac{V_D}{V_{D\text{MAX}}} \right) \sqrt{2 - \left( \frac{V_D}{V_{D\text{MAX}}} \right)^2} = \frac{I_0}{2} \left[ 1 + z \sqrt{2 - z^2} \right] \quad \text{with } z = \left( \frac{V_D}{V_{D\text{MAX}}} \right)$$

$$\frac{dI_{D1}}{dV_D} = \frac{I_0}{2V_{D\text{MAX}}} \left[ \sqrt{2 - z^2} - \frac{2z^2}{2\sqrt{2 - z^2}} \right] = \frac{I_0}{2V_{D\text{MAX}}} \frac{2 - z^2 - z^2}{\sqrt{2 - z^2}} = \frac{I_0}{V_{D\text{MAX}}} \frac{1 - z^2}{\sqrt{2 - z^2}}$$



$$\left\{ \begin{array}{l} V_D = \pm V_{D\text{MAX}} \rightarrow \frac{dI_{D1}}{dV_D} = 0 \quad \sqrt{\frac{2I_0}{\beta}} \triangleq V_{D\text{MAX}} \\ V_D = 0 \rightarrow \frac{dI_{D1}}{dV_D} = \frac{I_0}{\sqrt{2}V_{D\text{MAX}}} = \sqrt{\frac{I_0^2 \beta}{4I_0}} = \frac{1}{2} \sqrt{\beta I_0} \end{array} \right.$$
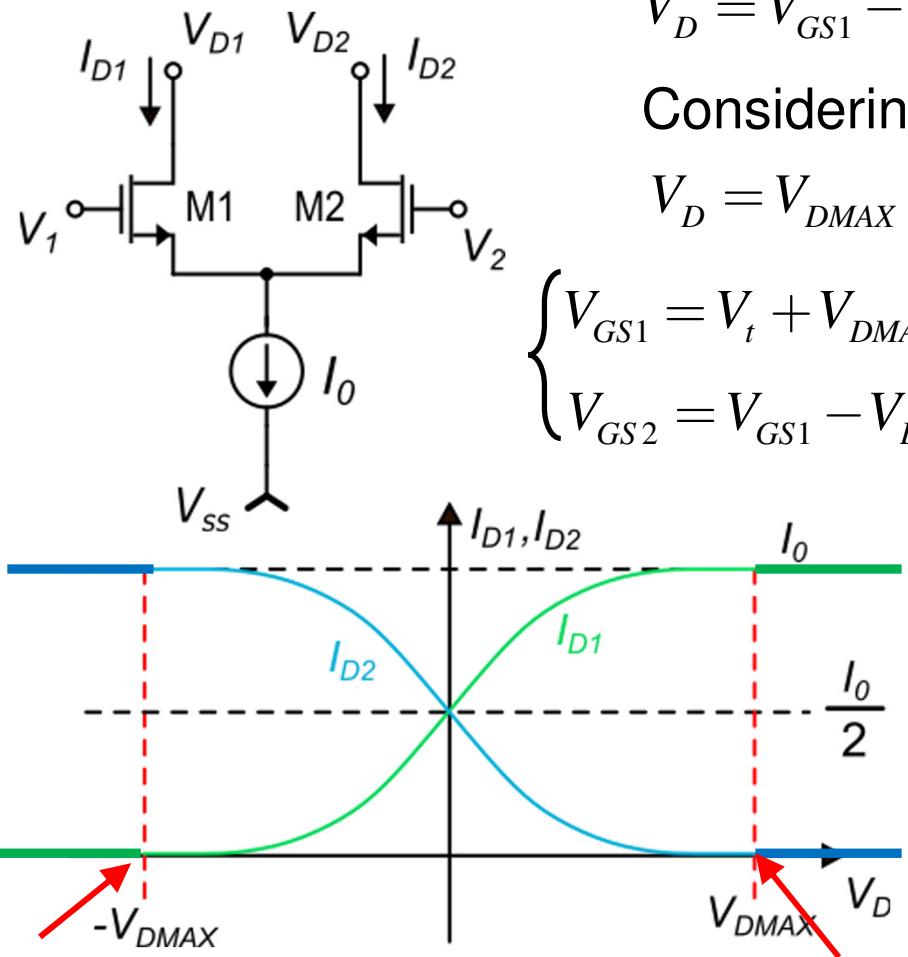
## Extrapolation outside the $-V_{D\text{MAX}} \leq V_D \leq V_{D\text{MAX}}$ region



$$V_D = V_{GS1} - V_{GS2} \Rightarrow V_{GS2} = V_{GS1} - V_D$$

Considering the boundary:



$$V_D = V_{D\text{MAX}}$$

$$I_{D1} = I_0 \Rightarrow V_{GS1} = V_t + \sqrt{\frac{2I_0}{\beta}} V_{D\text{MAX}}$$

If  $V_D$  increases over  $V_{D\text{MAX}}$ :  
 $V_{GS1}$  cannot increase because  
 $I_{D1}$  would become  $> I_0$ , which is  
impossible.

Then  $V_{GS2}$  gets smaller than  $V_t$   
 $I_{D2}$  keeps being  $= 0$   
 $I_{D1}$  keeps being  $= I_0$   
The opposite occurs when  $V_D$   
decreases below  $V_{D\text{MAX}}$ :

## Mosfet differential pair: parameters

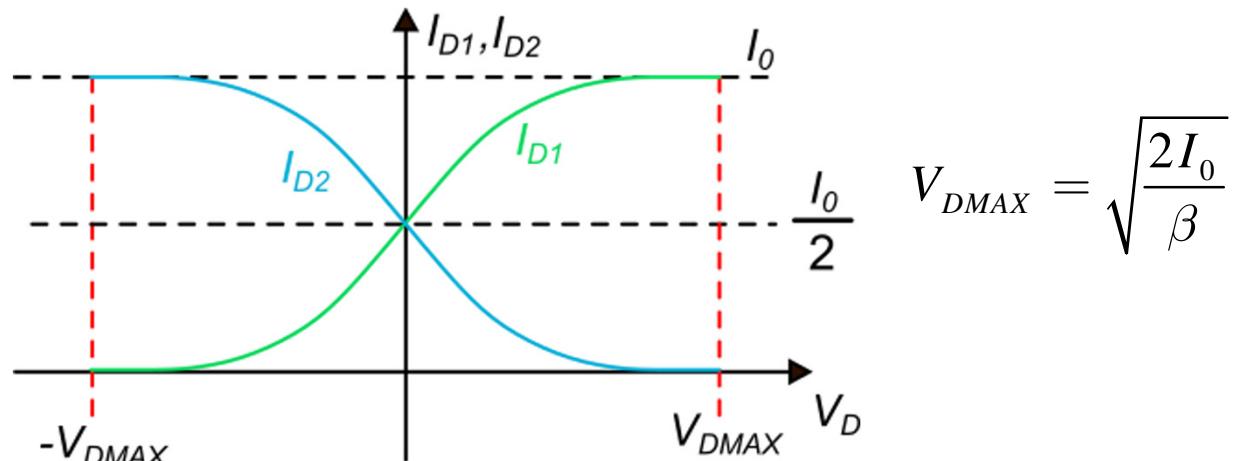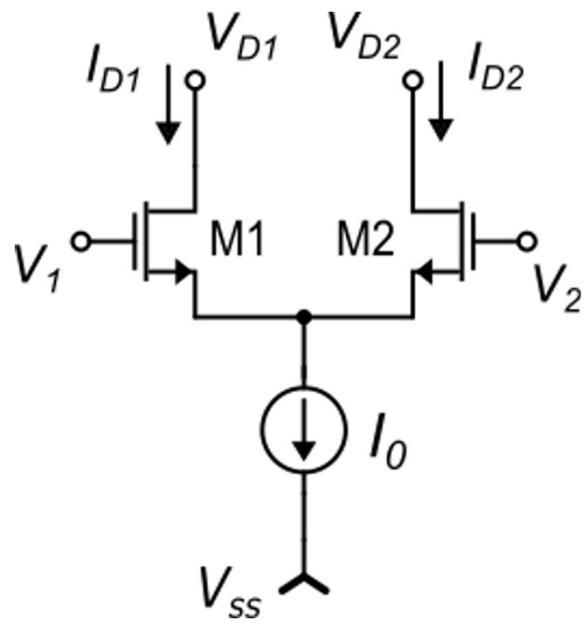


For  $V_D=0$  (typical operating point):  $I_{D1} = I_{D2} \triangleq I_{DQ} = \frac{I_0}{2}$

$$V_{DMAX} = \sqrt{\frac{2 \cdot 2I_{DQ}}{\beta}} = \sqrt{2} \sqrt{\frac{2I_{DQ}}{\beta}} = \underline{\underline{\sqrt{2}(V_{GS} - V_t)_Q}}$$

$$\left. \frac{dI_{D1}}{dV_D} \right|_{V_D=0} = \frac{1}{2} \sqrt{2\beta I_{DQ}} = \frac{g_m}{2}$$
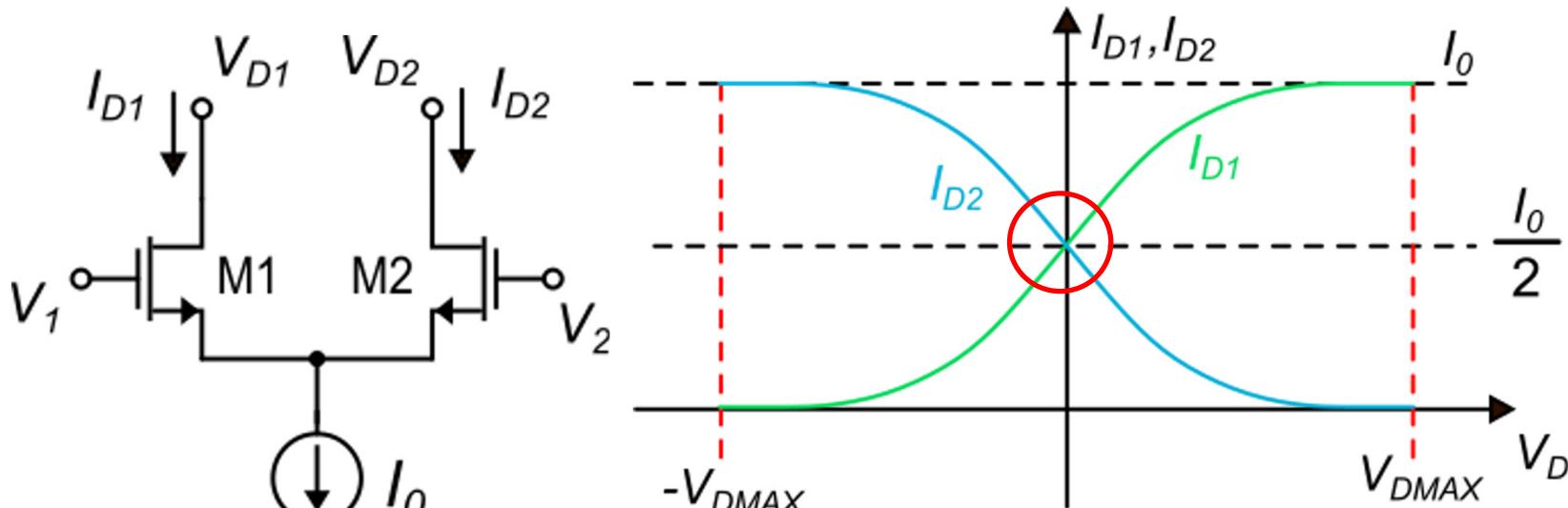
## Small signal behavior

For small variations ( $v_d$ ) of  $V_D$  around 0:




$$\left\{ \begin{array}{l} I_{D1} \approx \frac{I_0}{2} + v_d \left. \frac{dI_{D1}}{dV_D} \right|_{V_D=0} = \frac{I_0}{2} + \frac{g_m}{2} v_d \\ I_{D2} \approx \frac{I_0}{2} + v_d \left. \frac{dI_{D2}}{dV_D} \right|_{V_D=0} = \frac{I_0}{2} - \frac{g_m}{2} v_d \end{array} \right.$$

$$g_m = \sqrt{2\beta I_{DQ}} = \sqrt{\beta I_0}$$

But also:

$$g_m = \beta(V_{GS} - V_t) = \frac{I_{DQ}}{V_{TE}}$$

## Differential output current

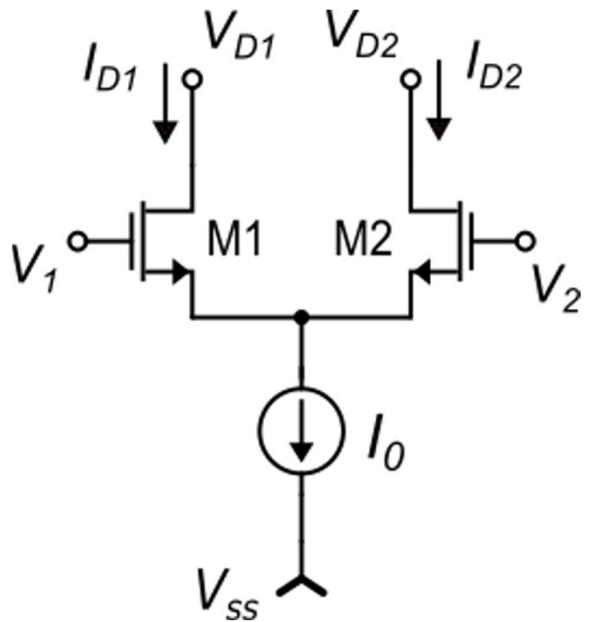


$$I_{D1} - I_{D2} = I_0 \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2}$$


$$i_d = i_{d1} - i_{d2} = g_m v_d$$

$$I_{D1} = \frac{I_0}{2} + \frac{I_0}{2} \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2}$$
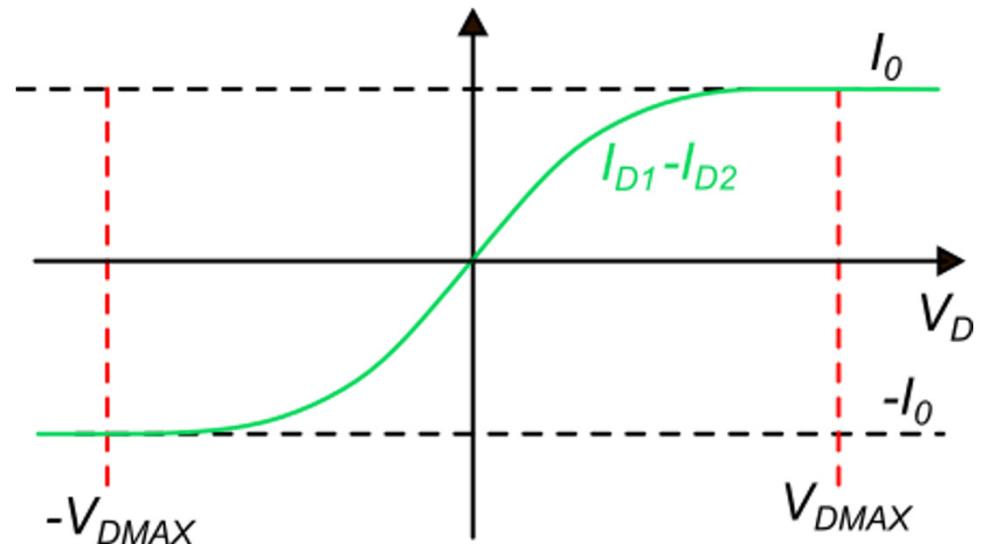
$$I_{D2} = \frac{I_0}{2} - \frac{I_0}{2} \left( \frac{V_D}{V_{DMAX}} \right) \sqrt{2 - \left( \frac{V_D}{V_{DMAX}} \right)^2}$$


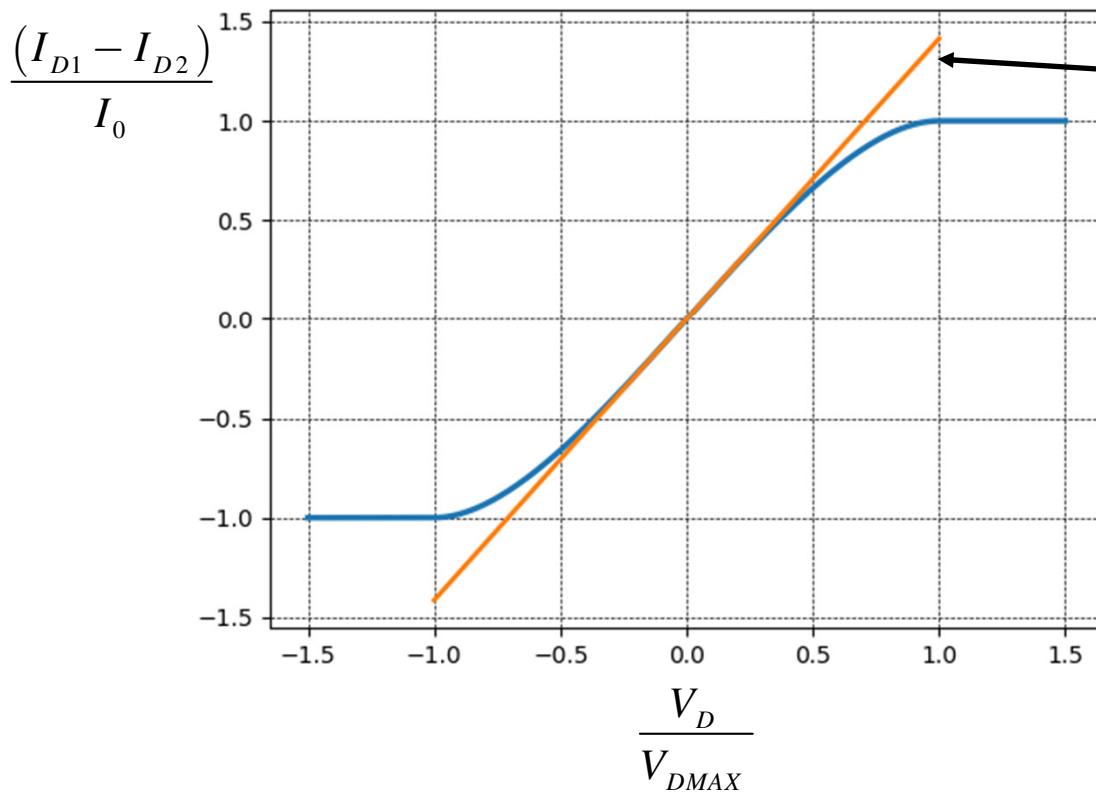
# Mosfet differential pair: real curves (calculated) and linearity



linear approximation  
calculated around origin

Non-linearity error:


$$|V_D| < \frac{V_{DMAX}}{5} : e_R < 1\%$$

$$|V_D| < \frac{V_{DMAX}}{2\sqrt{2}} = \frac{V_{GS} - V_t}{2} : e_R < 3\%$$



$$|V_D| < \frac{V_{DMAX}}{2} : e_R < 7\%$$

$$|V_D| < \frac{V_{DMAX}}{\sqrt{2}} = (V_{GS} - V_t) : e_R < 15\%$$
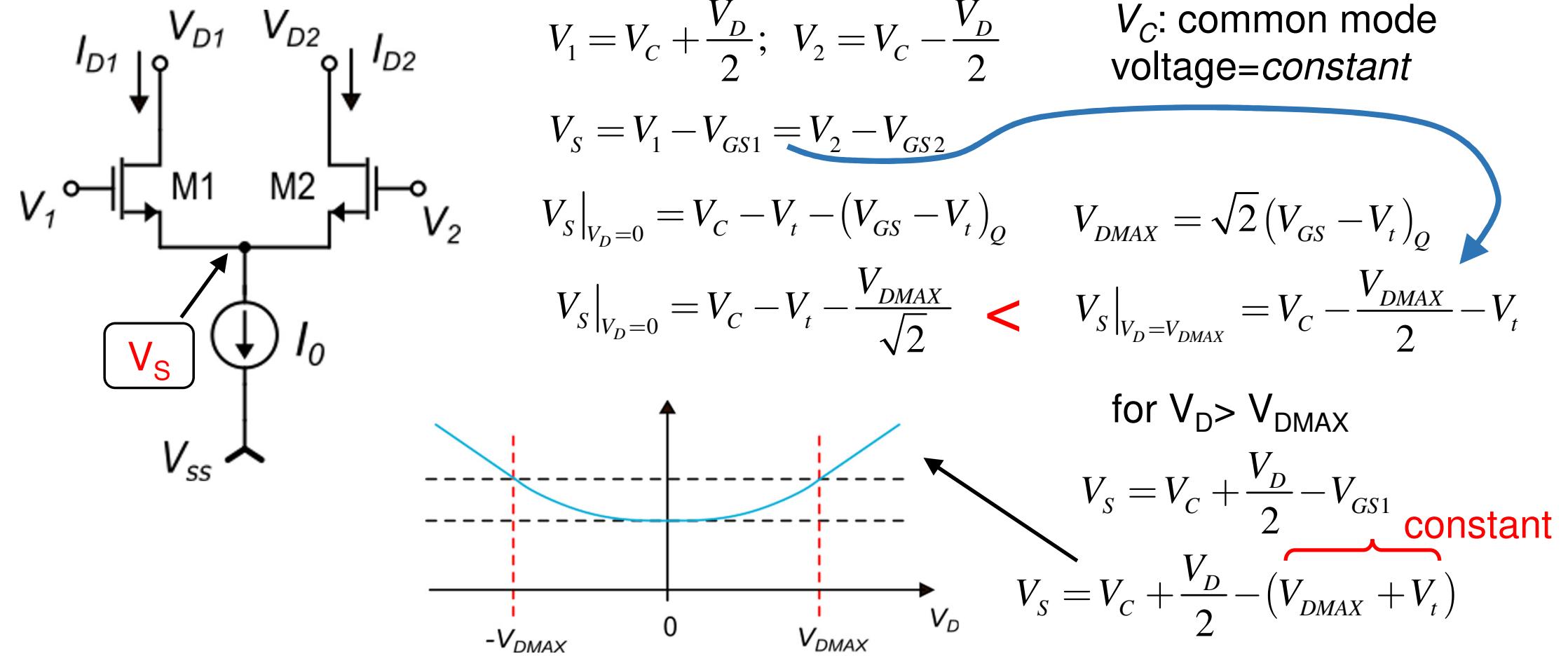
# Large-signal dependence of the source voltage on $V_D$



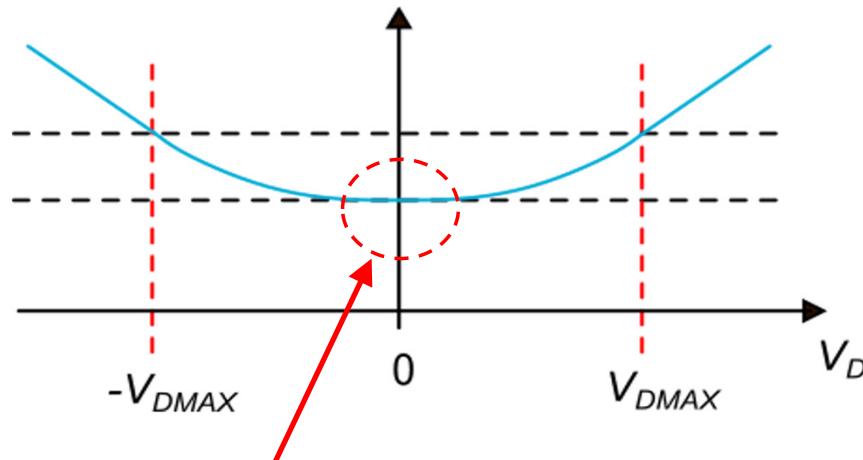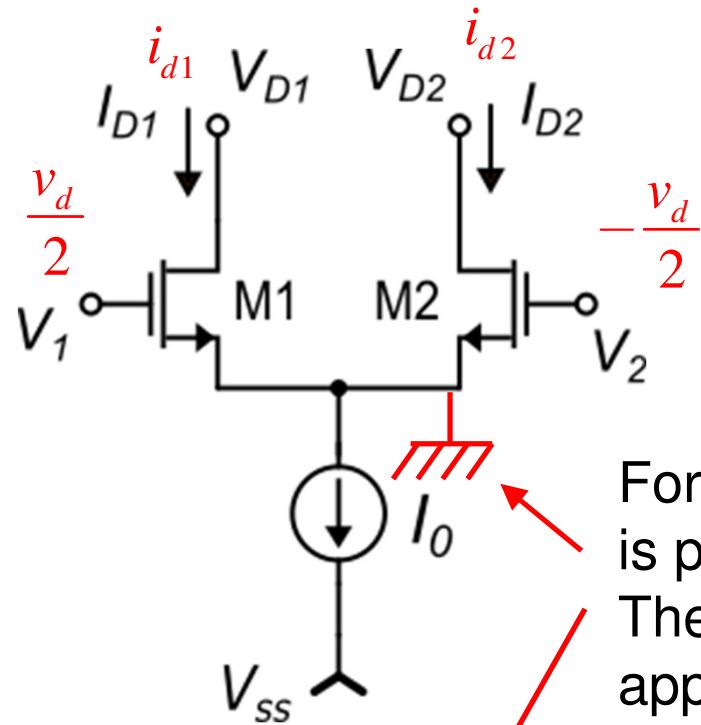
## Small-signal dependence of the source voltage on $V_D$



For small differential voltages ( $v_d \ll V_{DMAX}$ ), the source potential is practically constant.  
Therefore, in a small signal analysis, for only differential signal applied,  $v_S$  can be considered zero (i.e. the source is at gnd).

$$v_{gs1} = \frac{v_d}{2}; v_{gs2} = -\frac{v_d}{2} \rightarrow i_{d1} = g_m v_{gs1} = g_m \frac{v_d}{2}; i_{d2} = g_m v_{gs2} = -g_m \frac{v_d}{2}$$

## BJT differential pair

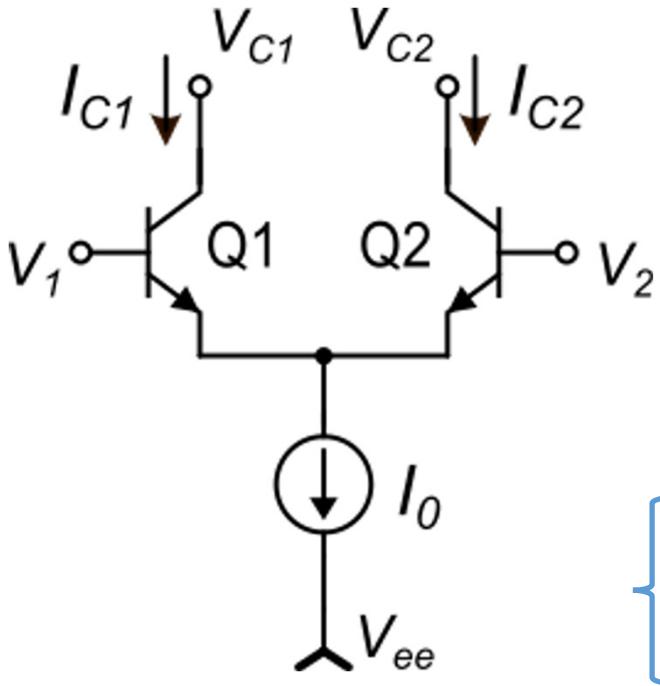

$$I_{E1} + I_{E2} = I_0 \quad \Rightarrow \quad \frac{\beta+1}{\beta} I_{C1} + \frac{\beta+1}{\beta} I_{C2} = I_0$$

$$V_D = V_{BE1} - V_{BE2} \quad I_{C1} + I_{C2} = \frac{\beta}{\beta+1} I_0 \cong I_0$$


$$\begin{cases} I_{C1} = I_S e^{\frac{V_{BE1}}{V_T}} \\ I_{C2} = I_S e^{\frac{V_{BE2}}{V_T}} \end{cases}$$

$$\frac{I_{C2}}{I_{C1}} = e^{\frac{V_{BE2}-V_{BE1}}{V_T}} = e^{\frac{-V_D}{V_T}}$$


$$I_{C1} \left( 1 + e^{\frac{-V_D}{V_T}} \right) = I_0$$

$$\begin{cases} I_{C1} = \frac{I_0}{1 + e^{\frac{-V_D}{V_T}}} \\ I_{C2} = \frac{I_0 e^{\frac{-V_D}{V_T}}}{1 + e^{\frac{-V_D}{V_T}}} \end{cases}$$

## BJT differential pair

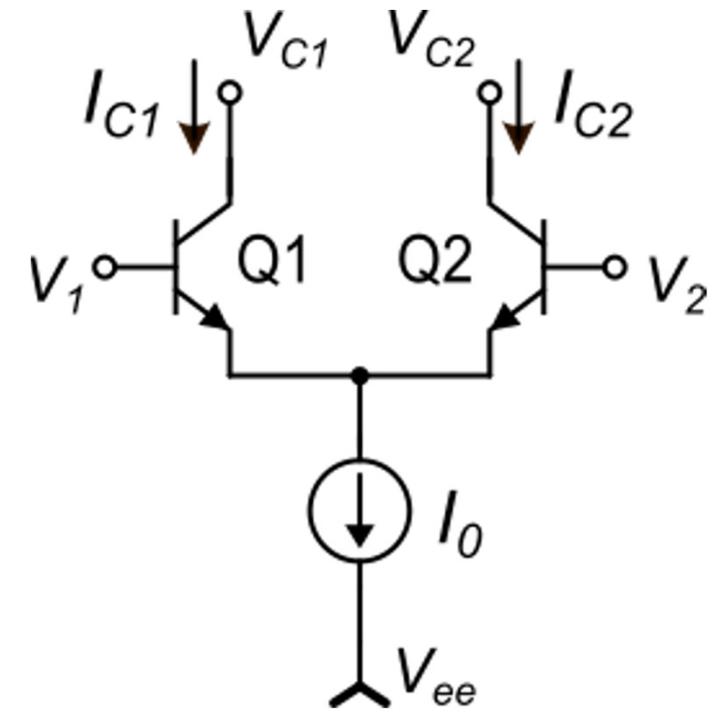

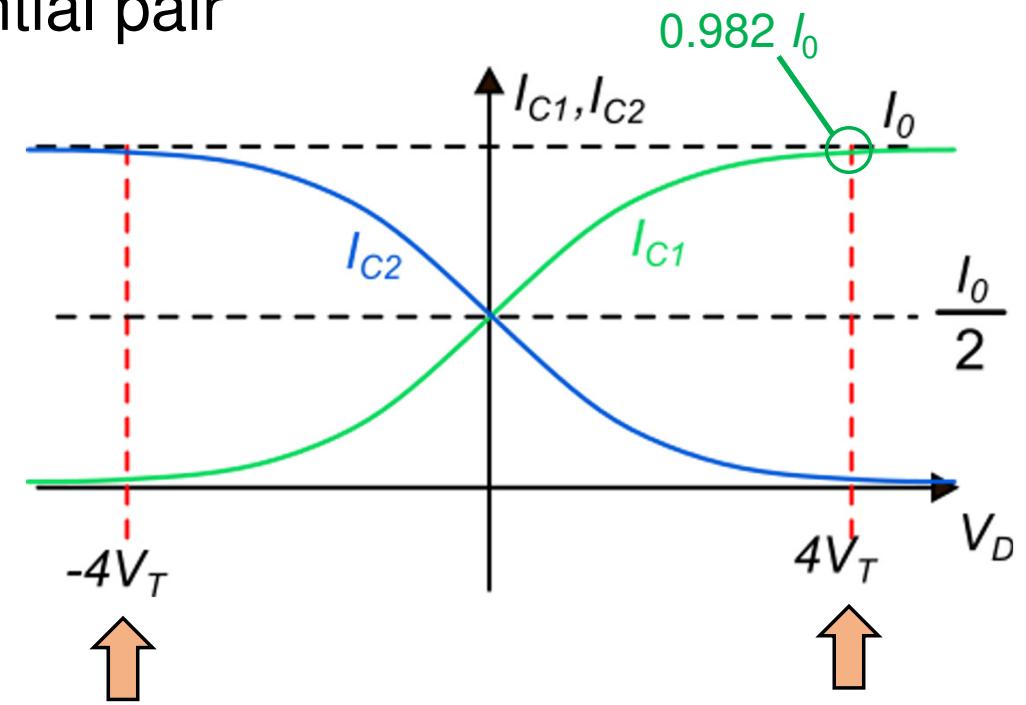
$$\left. \begin{array}{l} I_{C1} = \frac{I_0 e^{\frac{-V_D}{V_T}}}{1 + e^{\frac{-V_D}{V_T}}} \\ I_{C2} = \frac{I_0 e^{\frac{-V_D}{V_T}}}{1 + e^{\frac{-V_D}{V_T}}} \end{array} \right\}$$



$$I_{C1} - I_{C2} = I_0 \frac{1 - e^{\frac{-V_D}{V_T}}}{1 + e^{\frac{-V_D}{V_T}}}$$

$$I_{C1} - I_{C2} = I_0 \frac{e^{\frac{-V_D}{2V_T}} (e^{\frac{V_D}{2V_T}} - e^{-\frac{V_D}{2V_T}})}{e^{\frac{-V_D}{2V_T}} (e^{\frac{V_D}{2V_T}} + e^{-\frac{V_D}{2V_T}})} = I_0 \tanh\left(\frac{V_D}{2V_T}\right)$$
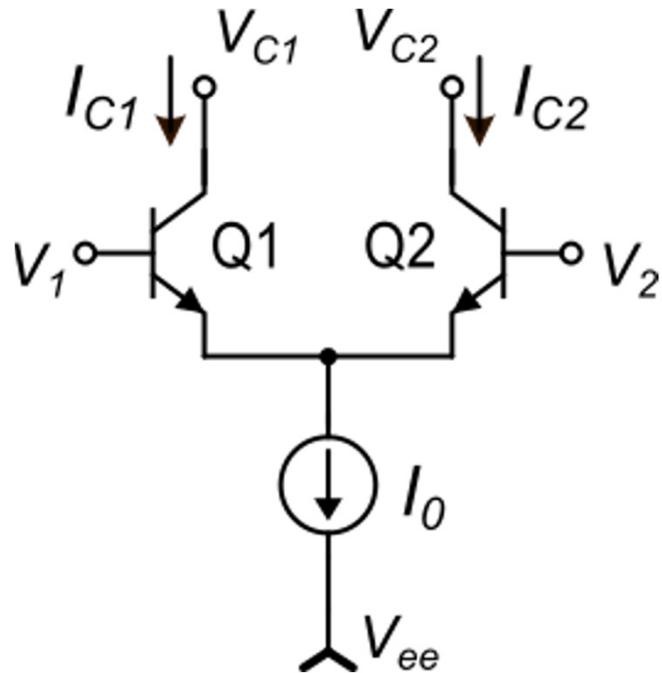
## BJT differential pair - small signal currents






$$I_{C1} = \frac{I_0}{2} + \frac{g_m}{2} v_d$$

$$I_{C2} = \frac{I_0}{2} - \frac{g_m}{2} v_d$$

$$I_{C1} - I_{C2} = g_m v_d$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{I_0}{2V_T}$$
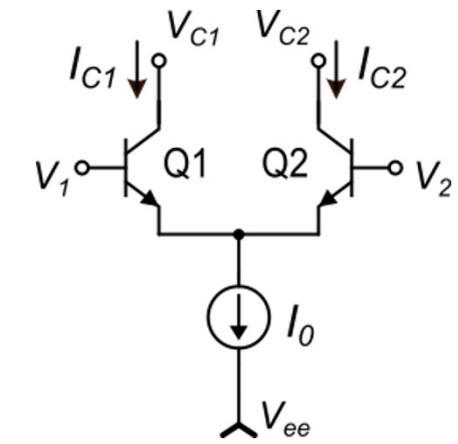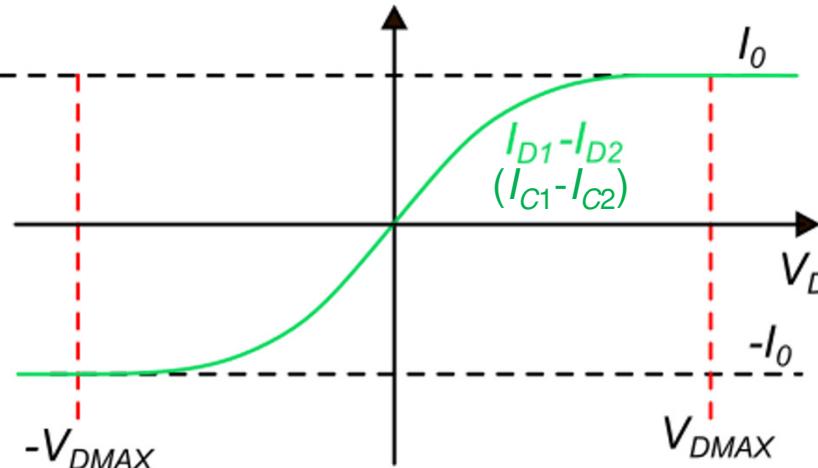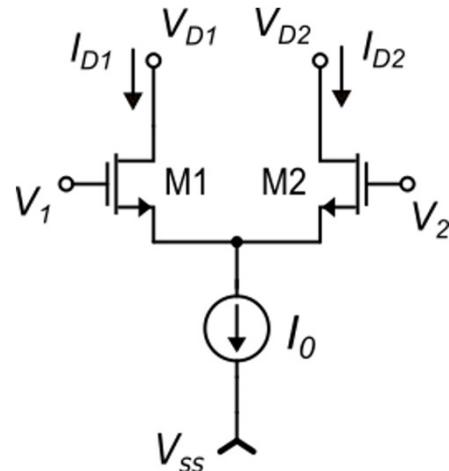
## MOSFET and BJT differential pairs compared



In the mosfet pair,  $V_{DMAX}$  can be varied by modifying  $\beta$  and  $I_0$

Parameter  $g_m$  depends on both  $I_0$  and  $\beta$ :

$$g_m = \sqrt{\beta I_0} \quad V_{DMAX} = \sqrt{\frac{2I_0}{\beta}}$$

Note: a mosfet pair in subthreshold region behaves like a BJT pair with the substitution:


$$mV_T \rightarrow V_T$$

In the BJT pair,  $V_{DMAX}$  is fixed to around  $4V_T$

Parameter  $g_m$  depends only on  $I_0$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{I_0}{2V_T}$$
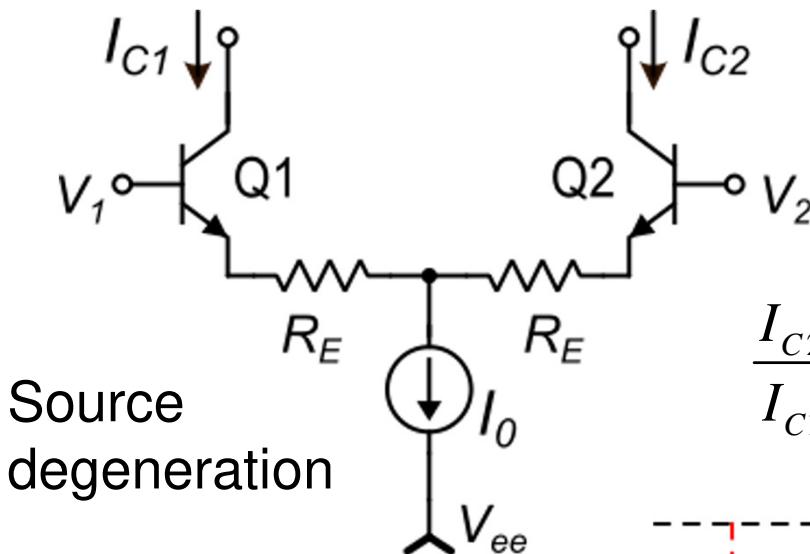
## How to increase the $V_{DMAX}$ of a BJT pair



$$g_{m-rid} = \left. \frac{d(I_{C1} - I_{C2})}{dV_D} \right|_{V_D=0}$$

$$g_{m-rid} = \frac{g_m}{1 + g_m R_E} < g_m$$

$$V_{DMAX} = V'_{DMAX} + I_0 R_E$$




$$\cong 4V_T$$

To demonstrate this,  
let us write  $V_D$ :

$$V_D = V_{BE1} + I_{C1} R_E - (V_{BE2} + I_{C2} R_E)$$
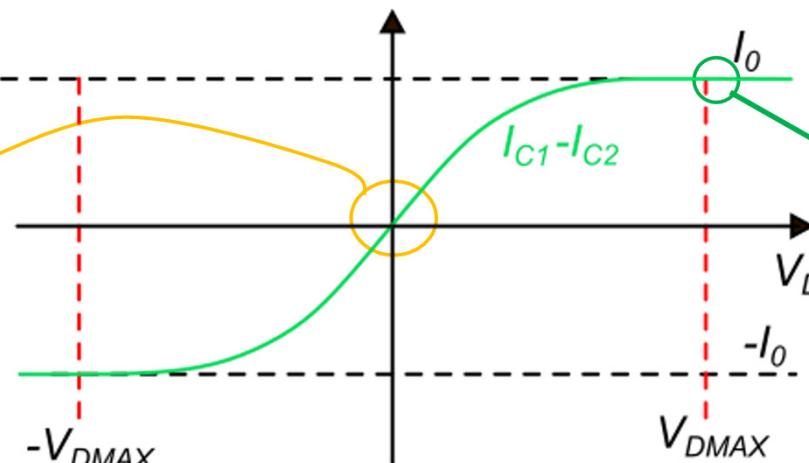
$$V_D = V_{BE1} - V_{BE2} + R_E (I_{C1} - I_{C2})$$



$$V_{BE1} - V_{BE2} \cong 4V_T$$

$$I_{D1} - I_{D2} \cong I_{D1} \cong I_0$$