
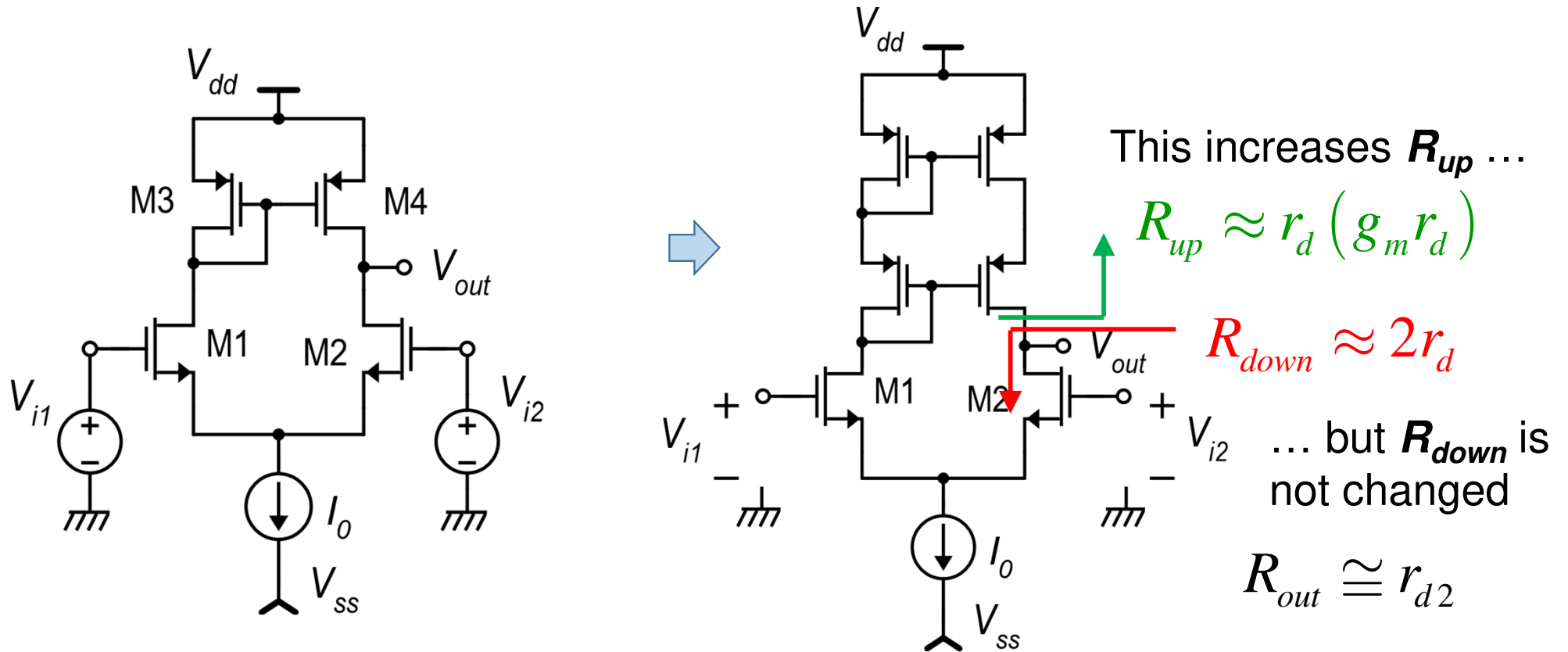


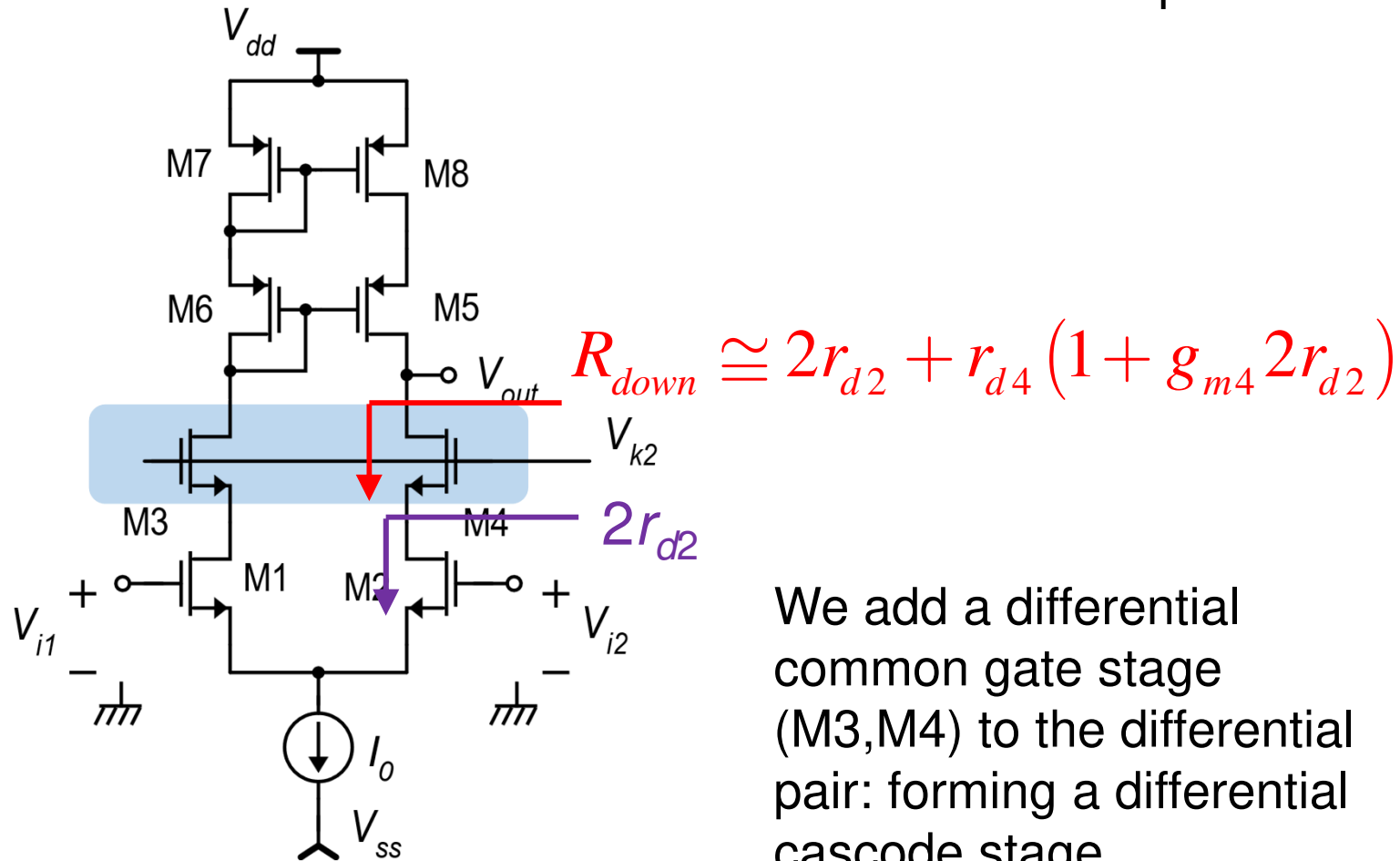Fist step: replace the simple current mirror with a cascode mirror




R_{out} passes from $r_d/2$ to r_d and the gain is only doubled

Second step: add a common-gate also to the differential pair:
The cascode differential amplifier



We add a differential common gate stage (M3, M4) to the differential pair: forming a differential cascode stage

Cascode differential amplifier

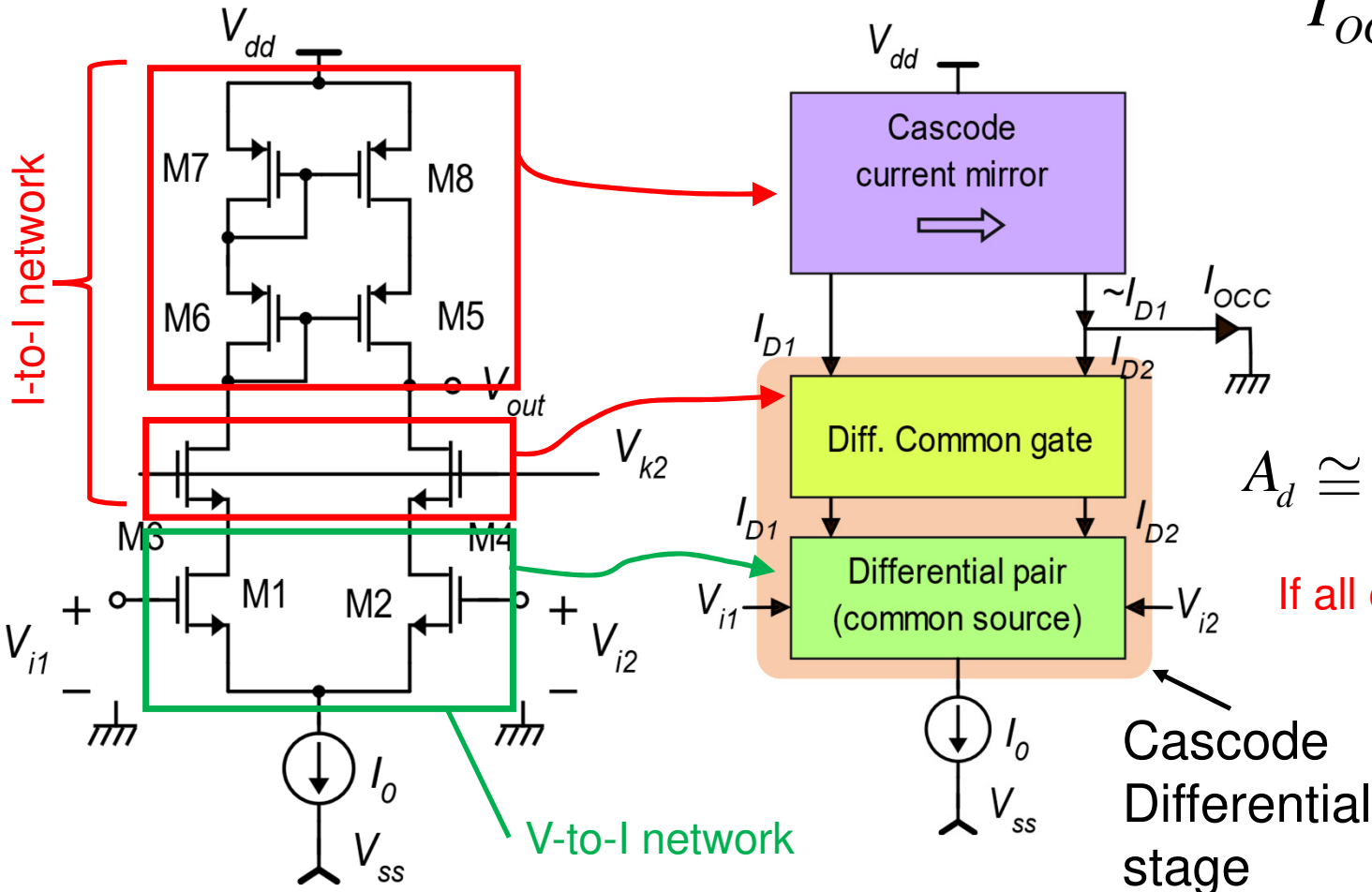

$$I_{OCC} \cong I_{D1} - I_{D2} \cong g_{m1} v_d$$

$$I_{OCC} = G_m v_d$$

$$G_m = g_{m1}$$


$$A_d = G_m R_{out}$$

$$A_d \cong g_{m1} \left[(r_{d2} g_{m4} r_{d4}) // (r_{d8} g_{m5} r_{d5}) \right]$$

If all devices have the same r_d and g_m :

$$A_d \cong \frac{(g_m r_d)^2}{2}$$

CMOS cascode amplifier: output range

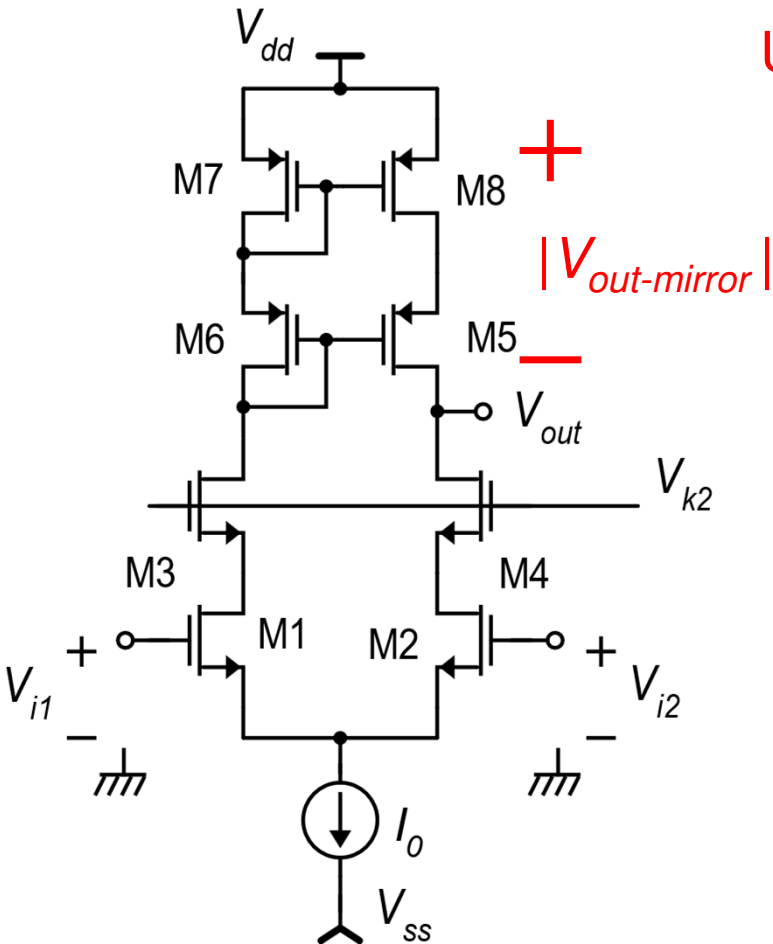

Upper limit

$$|V_{out-mirror}| = V_{dd} - V_{out} \geq V_{MIN-cascode}$$

$$V_{dd} - V_{MIN-cascode} \geq V_{out}$$

$$\max(V_{out}) = V_{dd} - V_{MIN-cascode}$$

As V_{out} gets higher than $\max(V_{out})$, R_{up} decreases making the gain decrease

CMOS cascode amplifier: output range

Lower limit

$$V_{DS4} = V_{out} - V_{S4} \geq V_{DSAT4}$$


$$V_{S4} = V_{k2} - V_{GS4}$$

$$V_{out} - V_{k2} + V_{GS4} \geq V_{DSAT4}$$

$$\min(V_{out}) = V_{k2} - V_{GS4} + V_{DSAT4}$$

In strong inversion: $\min(V_{out}) = V_{k2} - V_{t4}$

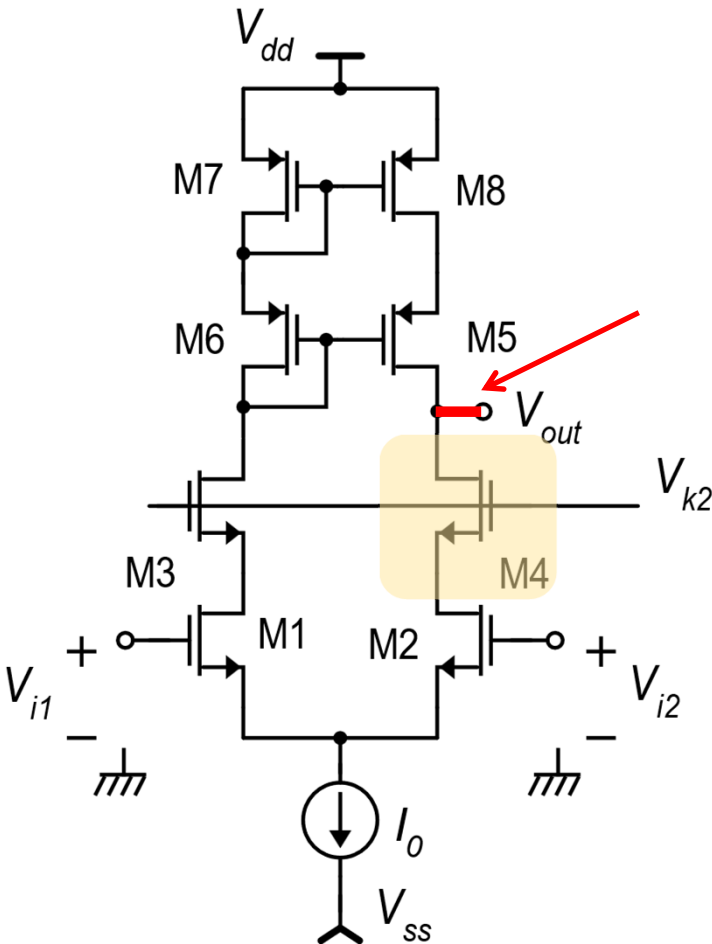For an approximation of $\min(V_{out})$ in weak inversion just add 100 mV



Input common mode range

$$\min(V_{iC}) = V_{SS} + V_{MIN-tail} + V_{GS1}$$


$$V_{DS1} = V_{D1} - V_{S1} \geq V_{DSAT1}$$

$$\begin{cases} V_{D1} = V_{k2} - V_{GS3} \\ V_{S1} = V_{iC} - V_{GS1} \end{cases}$$



$$V_{k2} - V_{GS3} - V_{iC} + V_{GS1} \geq V_{DSAT1}$$

$$\max(V_{iC}) = V_{k2} - \underline{V_{GS3} + V_{GS1}} - V_{DSAT1}$$
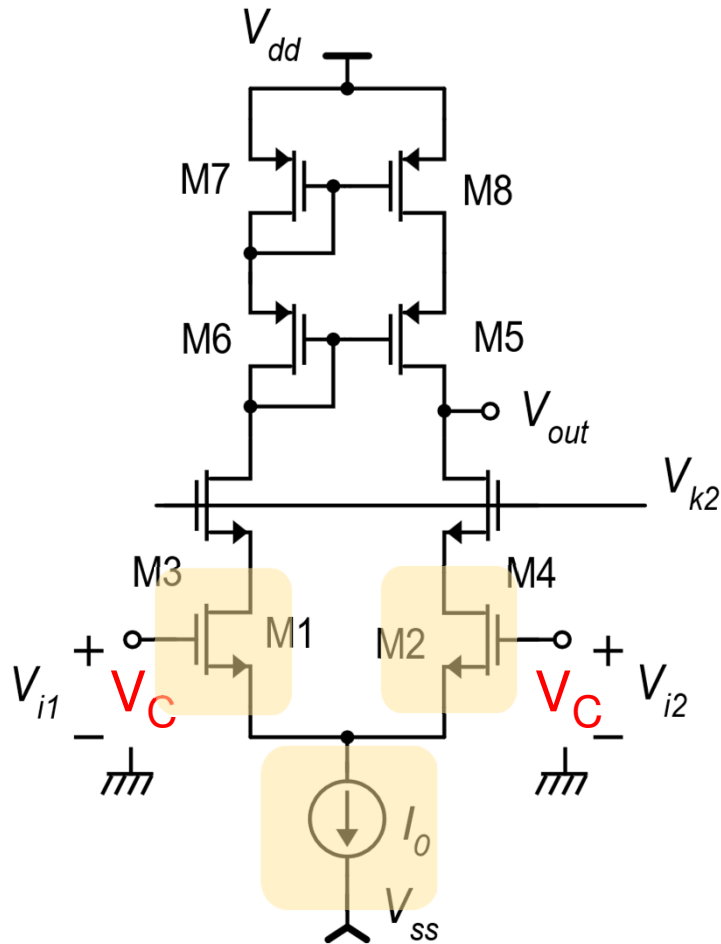
$$\max(V_{iC}) \cong V_{k2} - V_{DSAT1}$$




Cascode amplifier: all ranges

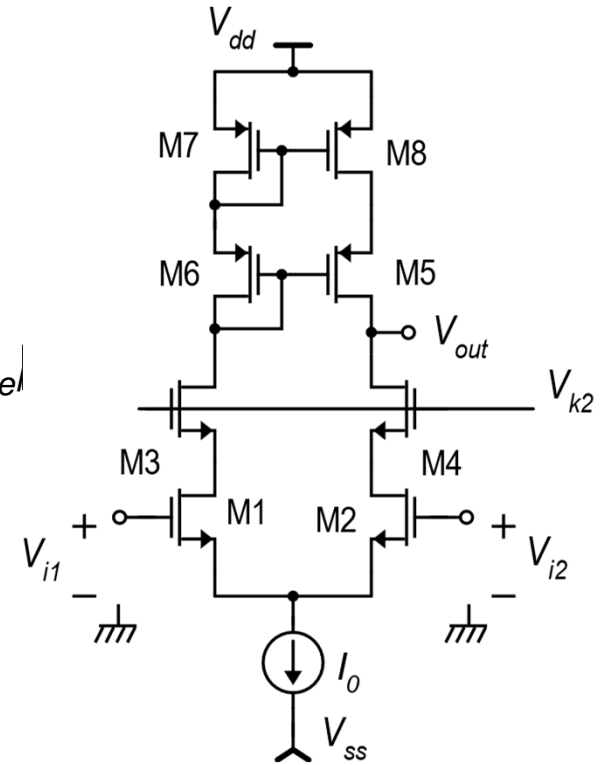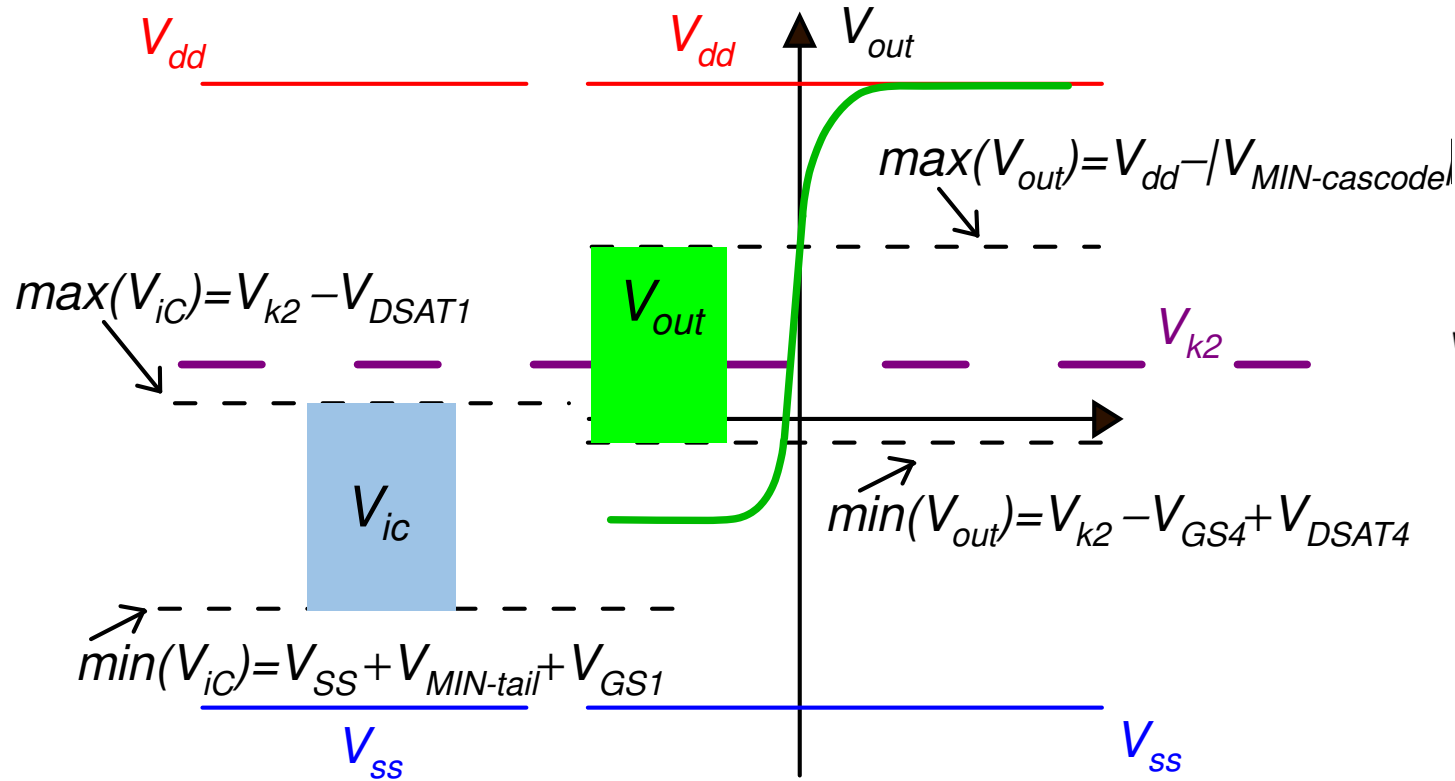

V_{k2} determines a trade-off between the input common mode range and the output swing

Adaptive V_{k2}

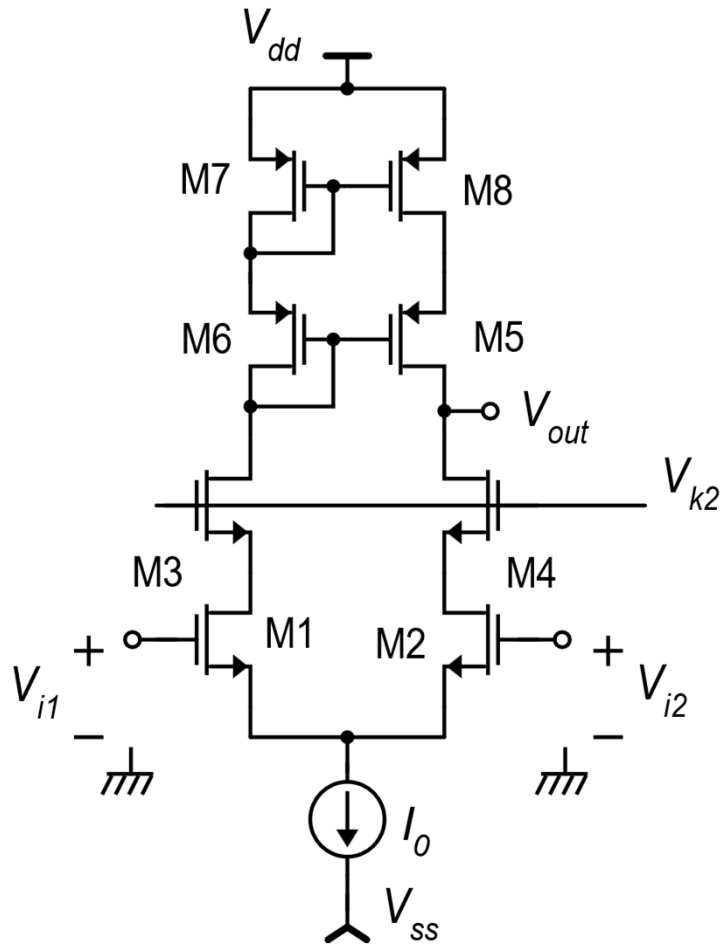


$$V_{k2} - V_{GS3} - V_{iC} + V_{GS1} \geq V_{DSAT1}$$


$$V_{k2} \geq \underbrace{V_{iC} - V_{GS1}}_{V_{S1}} + V_{GS3} + V_{DSAT1}$$

$$V_{k2} = V_{S1} + \underbrace{V_{GS3} + V_{DSAT1}}$$

$$V_{k2} = V_{S1} + V_{GS10}$$

$$V_{GS10} = V_{GS3} + V_{DSAT1}$$

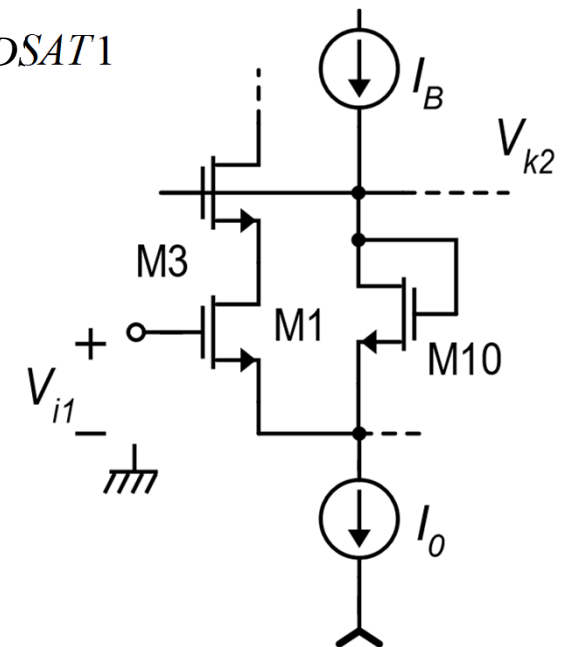

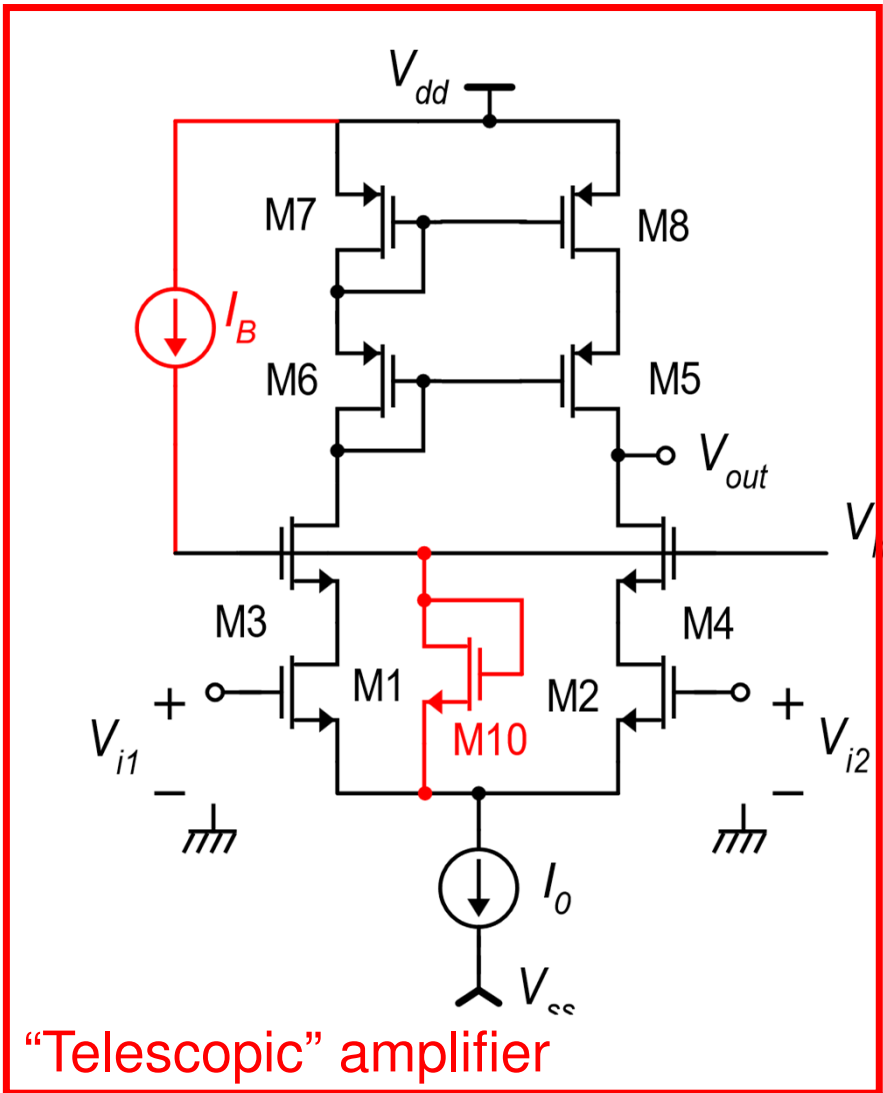

Adaptive V_{k2}

Same as in the case of a general cascode structure

$$V_{GS10} = V_{GS3} + V_{DSAT1}$$




$$(V_{GS} - V_t)_{10} = m_3 V_{DSAT1} + (V_{GS} - V_t)_3$$

$$I_{0-eff} = I_0 - I_B$$

The adaptive V_{k2} does not solve the problem that, as V_{iC} increases, the output swing gets smaller. The advantage is that the amplifier is more flexible and no trade-off on V_{k2} should be made in the design phase.

Removing the interaction between input and output range: The Folded Cascode

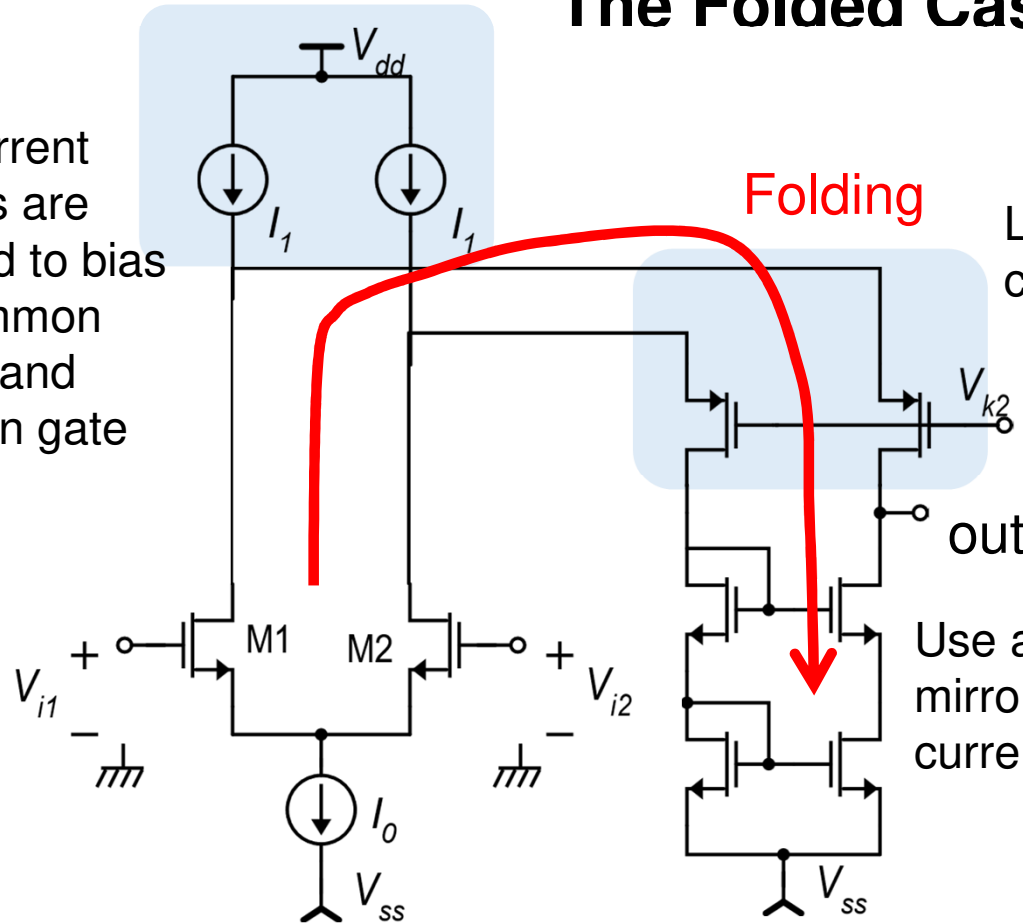Two current sources are required to bias the common source and common gate



Folding


Let us introduce a type-p common gate stage

Use an n-type current mirror to subtract the currents

According to the folding mechanism, the signal (variations) initially travels from one rail to the other and then invert direction and goes back to the initial rail

Folded cascode: setting the correct I_1 value

with: $I_1 = I_0$

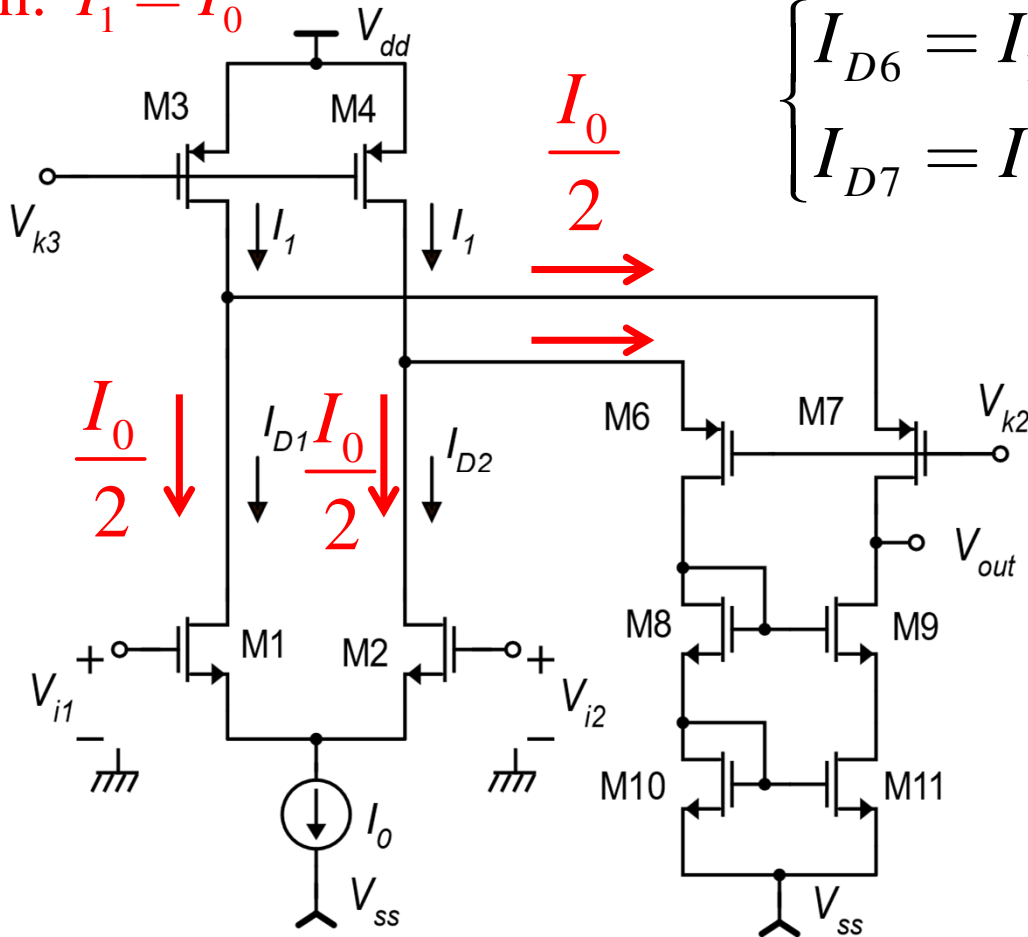

$$\begin{cases} I_{D6} = I_1 - I_{D2} \geq 0 \\ I_{D7} = I_1 - I_{D1} \geq 0 \end{cases}$$

Quiescent point:

$$I_{D1} = I_{D2} = \frac{I_0}{2}$$

$$I_1 > \frac{I_0}{2}$$

With a large input signal ($|V_{id}| > V_{DMAX}$):


$$V_{id} > V_{DMAX} : I_{D1} = I_0$$

$$V_{id} < -V_{DMAX} : I_{D2} = I_0$$

$$I_1 \geq I_0 \quad \text{usually: } I_1 = I_0$$

Folded cascode: differential mode gain

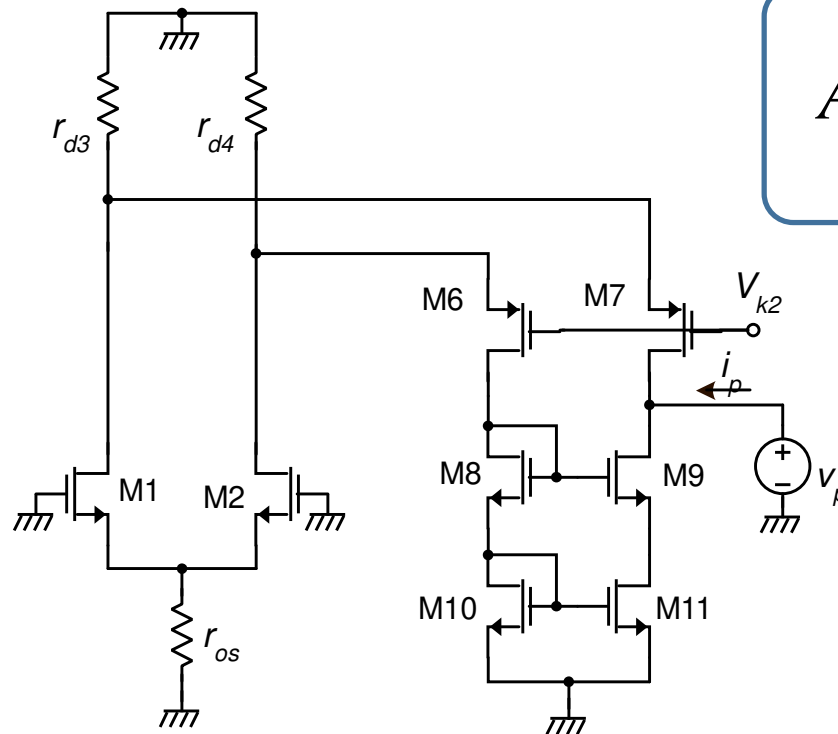Using a Norton equivalent circuit of the output port




$$A_d = G_m R_{out} \quad G_m = \frac{i_{occ}}{v_d}$$

$$I_{occ} \cong -g_{m1} v_d \Rightarrow G_m = -g_{m1}$$


$$A_d = -g_{m1} R_{out}$$

$$R_{out} = \frac{v_p}{i_p}$$

Folded cascode: output resistance (2)

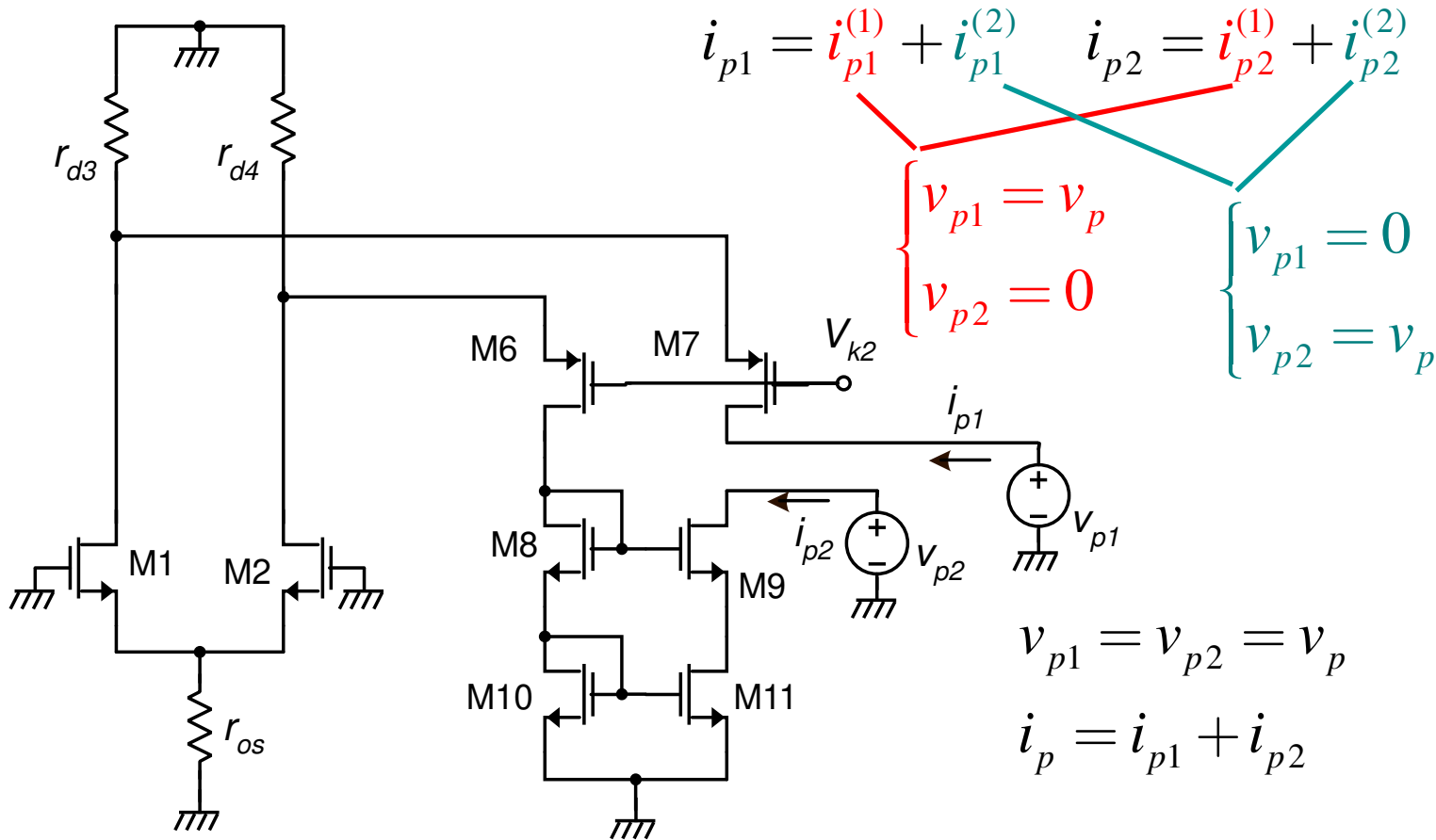

Folded cascode: output resistance (2)

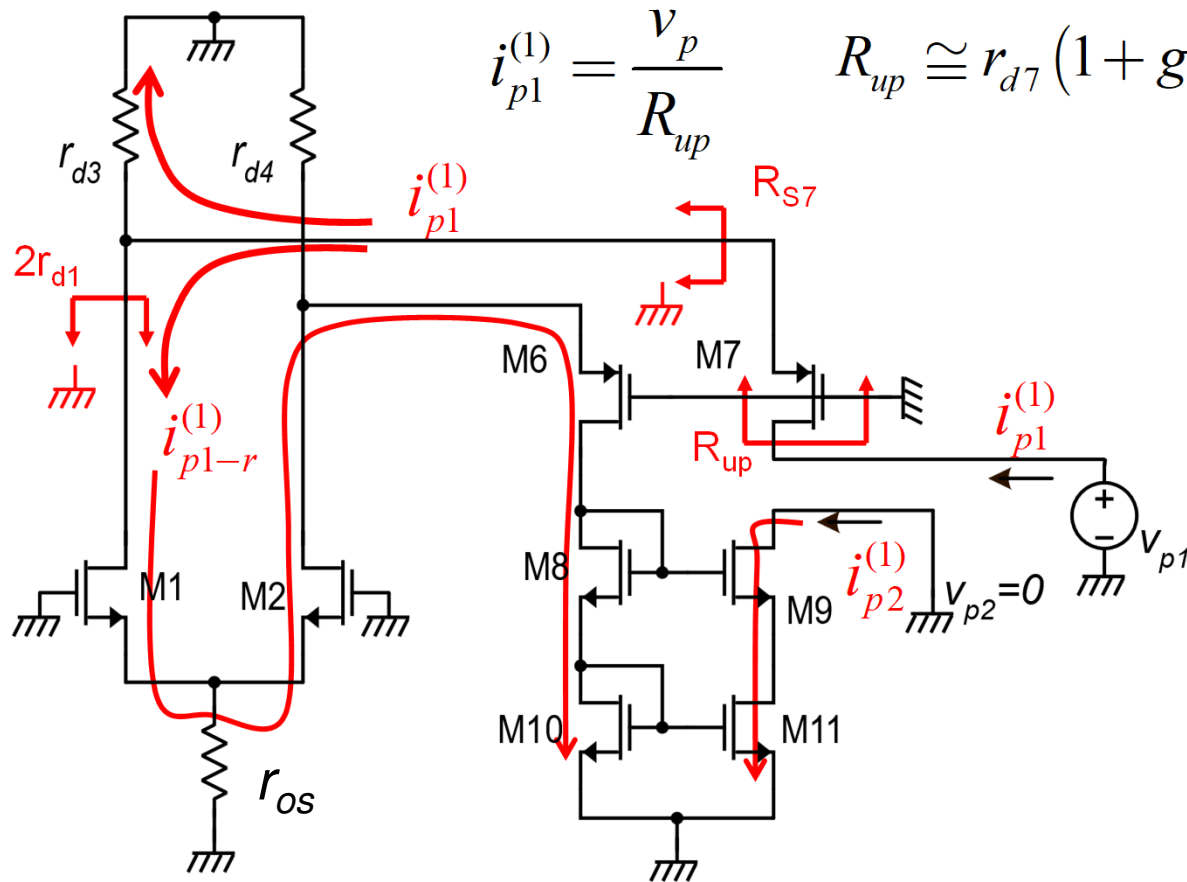

$$i_{p1}^{(1)} = \frac{V_p}{R_{up}}$$


$$R_{up} \cong r_{d7} (1 + g_{m7} R_{S7}) \quad R_{S7} = r_{d3} // 2r_{d1}$$

$$R_{up} \cong r_{d7} g_{m7} (r_{d3} // 2r_{d1})$$

$$i_{p1-r}^{(1)} = i_{p1}^{(1)} \frac{r_{d3}}{r_{d3} + 2r_{d1}}$$

$$i_{p2}^{(1)} = i_{p1-r}^{(1)} = i_{p1}^{(1)} \frac{r_{d3}}{r_{d3} + 2r_{d1}}$$

Folded cascode: output resistance (2)

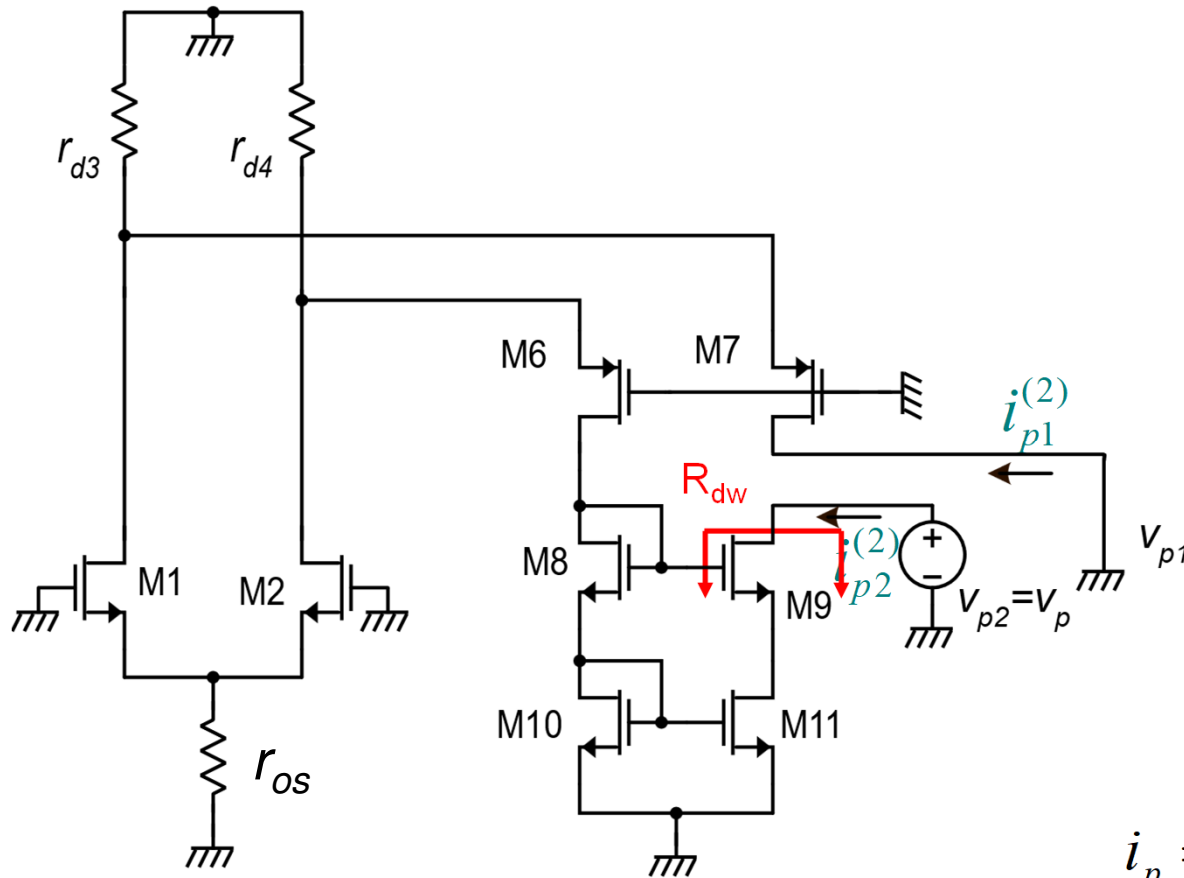

$$R_{dw} \cong r_{d9} g_{m9} r_{d11}$$

$$i_{p2}^{(2)} = \frac{v_p}{R_{dw}}$$

$$i_{p1}^{(2)} = 0$$

$$i_{p1}^{(1)} = \frac{v_p}{R_{up}}$$

$$i_{p2}^{(1)} = i_{p1}^{(1)} \frac{r_{d3}}{r_{d3} + 2r_{d1}}$$

$$i_p = \frac{v_p}{R_{up}} \left(1 + \frac{r_{d3}}{r_{d3} + 2r_{d1}} \right) + \frac{v_p}{R_{dw}}$$

Folded cascode: output resistance (3)

$$i_p = v_p \left(\frac{1}{R_{up}} \left(1 + \frac{r_{d3}}{r_{d3} + 2r_{d1}} \right) + \frac{1}{R_{dw}} \right)$$

$$R_{out} = \left(\frac{1}{R_{up}} \left(1 + \frac{r_{d3}}{r_{d3} + 2r_{d2}} \right) + \frac{1}{R_{dw}} \right)^{-1}$$

$$R_{out} = \left(\frac{1}{\frac{R_{up}}{\left(1 + \frac{r_{d3}}{r_{d3} + 2r_{d1}} \right)}} + \frac{1}{R_{dw}} \right)^{-1}$$

If $r_{d2}=r_{d3}=r_{d7}=r_{d9}=r_{d11} = r_d$
 $g_{m7}=g_{m9}=g_m$

$$R_{out} = R_{dw} // R_{up-r}$$

$$R_{dw} = r_{d9} g_{m9} r_{d11}$$

$$R_{up-r} = \frac{r_{d7} g_{m7} (r_{d3} // 2r_{d1})}{\left(1 + \frac{r_{d3}}{r_{d3} + 2r_{d1}} \right)}$$

$$\frac{2}{3} r_d$$

$$\frac{4}{3}$$

$$R_{dw} = r_d (g_m r_d)$$

$$R_{up-r} = \frac{r_d (g_m r_d)}{2}$$

$$R_{out} = \frac{r_d (g_m r_d)}{3}$$

Folded cascode: differential mode gain

$$A_d = -g_{m1} R_{out}$$

If $r_{d2}=r_{d3}=r_{d7}=r_{d9}=r_{d11} = r_d$
 $g_{m7}=g_{m9} = g_{m1} = g_m$

$$A_d = -g_m \frac{r_d (g_m r_d)}{3} = -\frac{(g_m r_d)^2}{3}$$

Compare with the
“Telescopic” amplifier


$$A_d = \frac{(g_m r_d)^2}{2}$$

... and with the simple
amplifier with mirror
load (non-cascode)

$$A_d = \frac{(g_m r_d)}{2}$$

Ac, CMRR

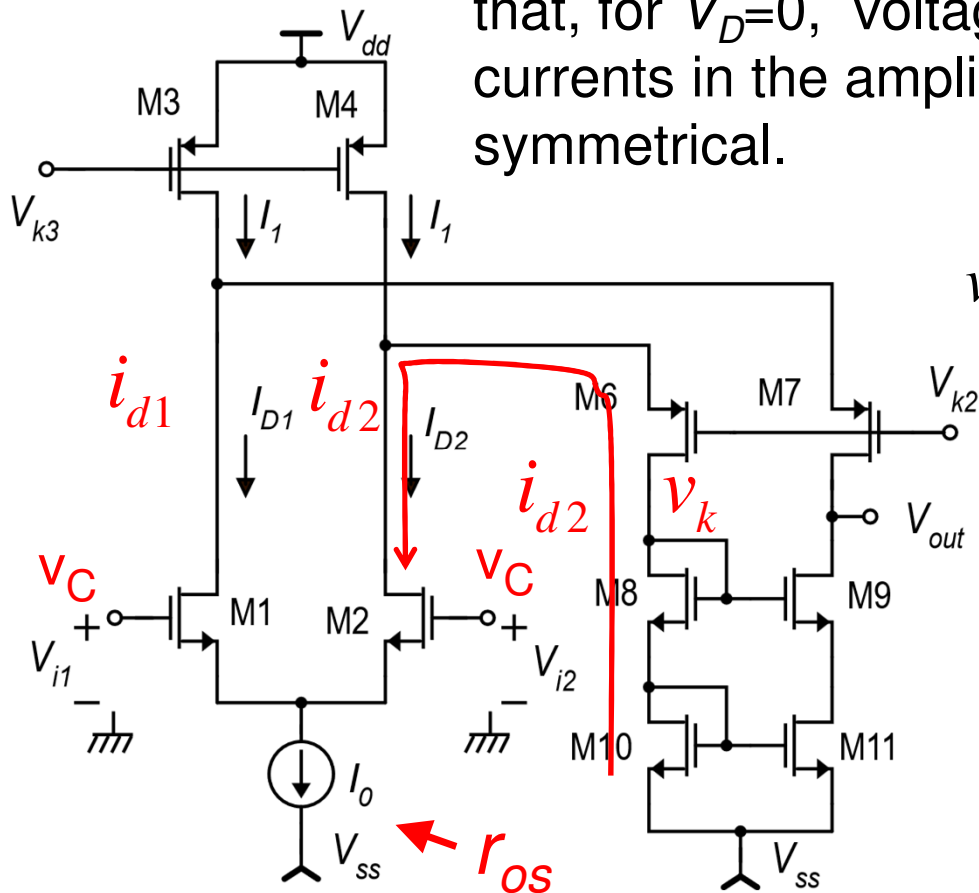It is possible to demonstrate that, for $V_D=0$, voltage and currents in the amplifiers are symmetrical.



Then:

$$\begin{cases} i_{d1} = i_{d2} \approx \frac{v_c}{2r_{os}} \\ v_{out} = v_k \end{cases}$$

$$v_{out} = v_k = -i_{d2} \left(\frac{1}{g_{m8}} + \frac{1}{g_{m10}} \right)$$

$$v_{out} = -\frac{v_c}{2r_{os}} \left(\frac{1}{g_{m8}} + \frac{1}{g_{m10}} \right) = -\frac{v_c}{g_m r_{os}}$$

for $g_{m8} = g_{m10} = g_m$

$$A_C = -\frac{1}{g_m r_{os}}$$

$$CMRR \approx \frac{(g_m r_d)^2}{3} g_m r_{os}$$

Folded cascode: output range

$$\min(V_{out}) = V_{SS} + V_{MIN-cascode} \quad \text{Lower limit}$$

$$\min(V_{out}) = \underline{V_{SS} + V_{GS11} + V_{DSAT9}}$$

Upper limit

$$|V_{DS7}| = V_{S7} - V_{D7} = V_{k2} + |V_{GS7}| - V_{out} \geq |V_{DSAT7}|$$


$$V_{k2} + |V_{GS7}| - |V_{DSAT7}| \geq V_{out}$$

$$\max(V_{out}) = \underline{V_{k2} + |V_{GS7}| - |V_{DSAT7}|}$$


In strong inversion:

$$|V_{DSAT7}| = |V_{GS7}| - |V_{t7}|$$

$$\max(V_{out}) = V_{k2} + |V_{t7}|$$

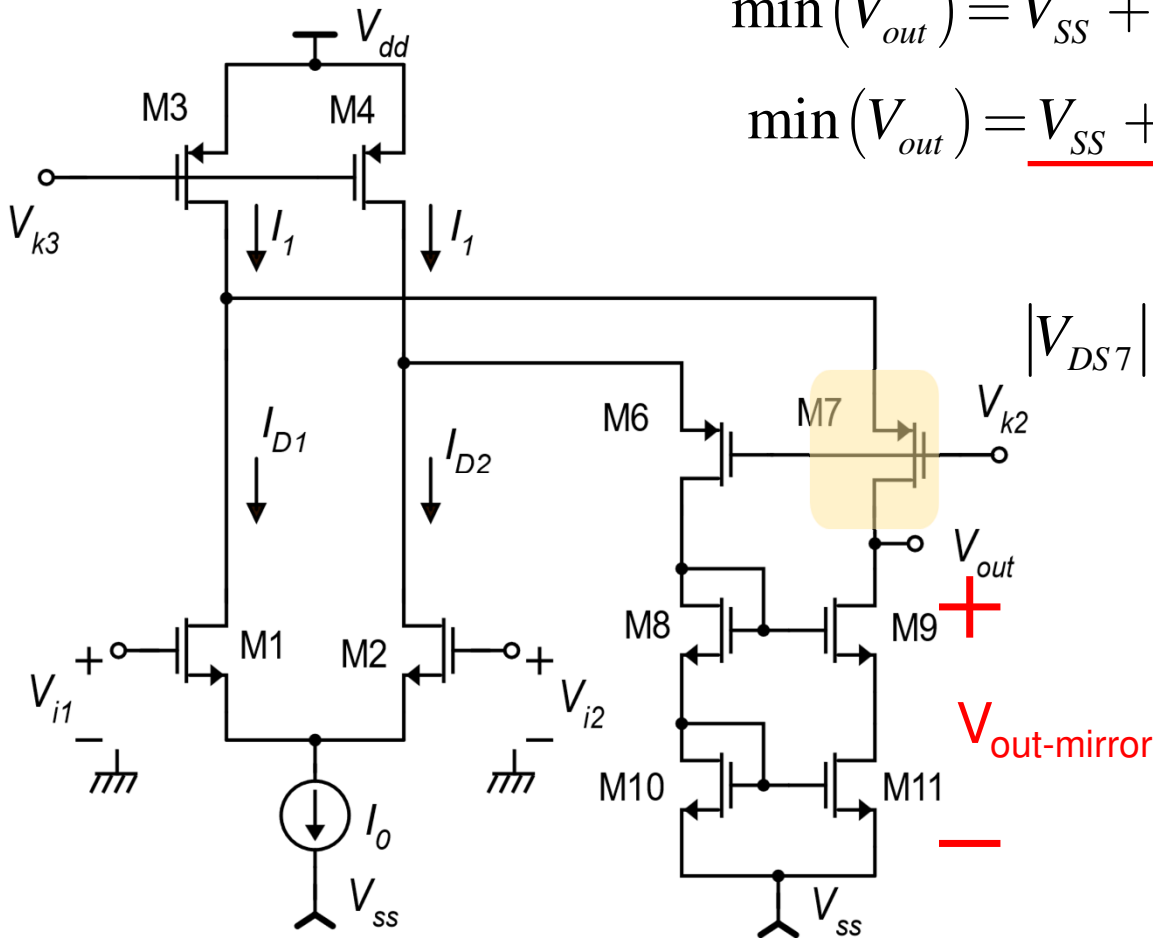

Maximum V_{k2}

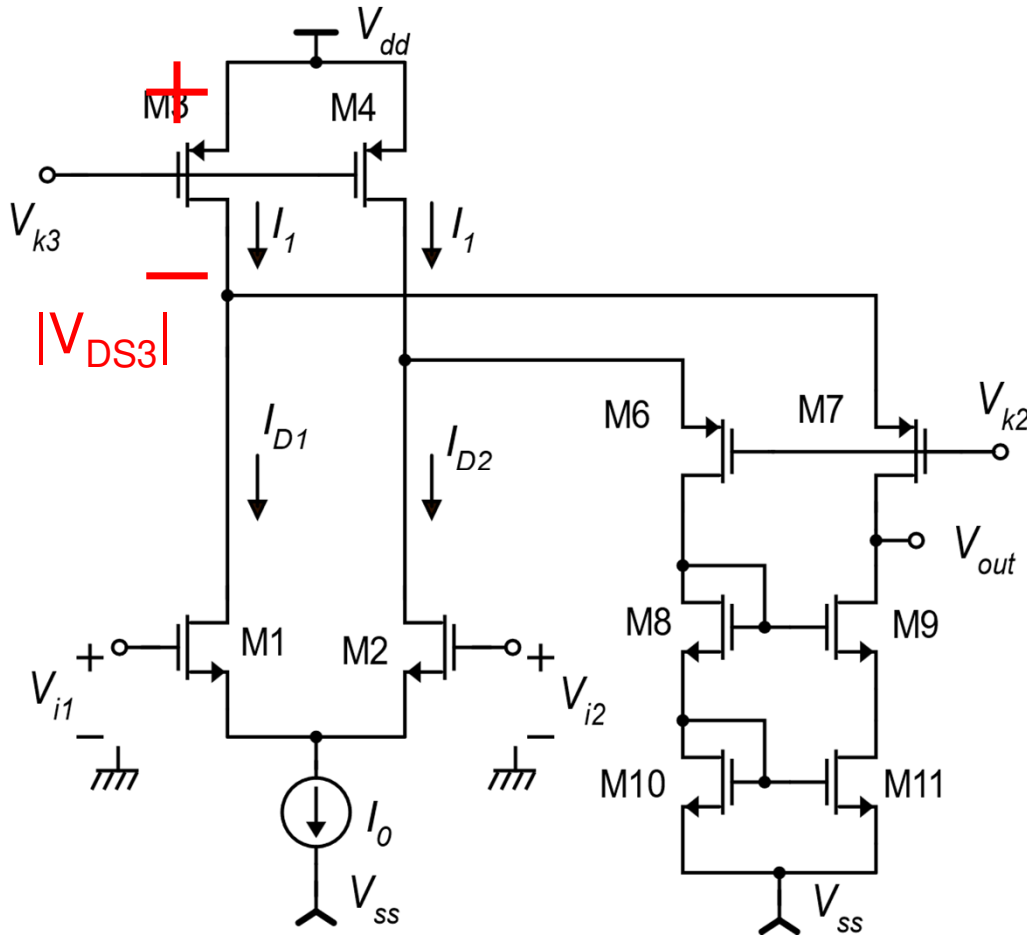

$$\max(V_{out}) = V_{k2} + |V_{GS7}| - |V_{DSAT7}|$$

$$V_{D3} = V_{D1} = V_{k2} + |V_{GS7}|$$

V_{k2} sets the voltage of M1-M3 and M2-M4 drains


$$|V_{DS3}| = V_{dd} - V_{D3} = V_{dd} - V_{k2} - |V_{GS7}| \geq |V_{DSAT3}|$$

$$\max(V_{k2}) = V_{dd} - |V_{DSAT3}| - |V_{GS7}|$$

$$\max(V_{out}) = V_{dd} - |V_{DSAT3}| - |V_{DSAT7}|$$

Input common mode range

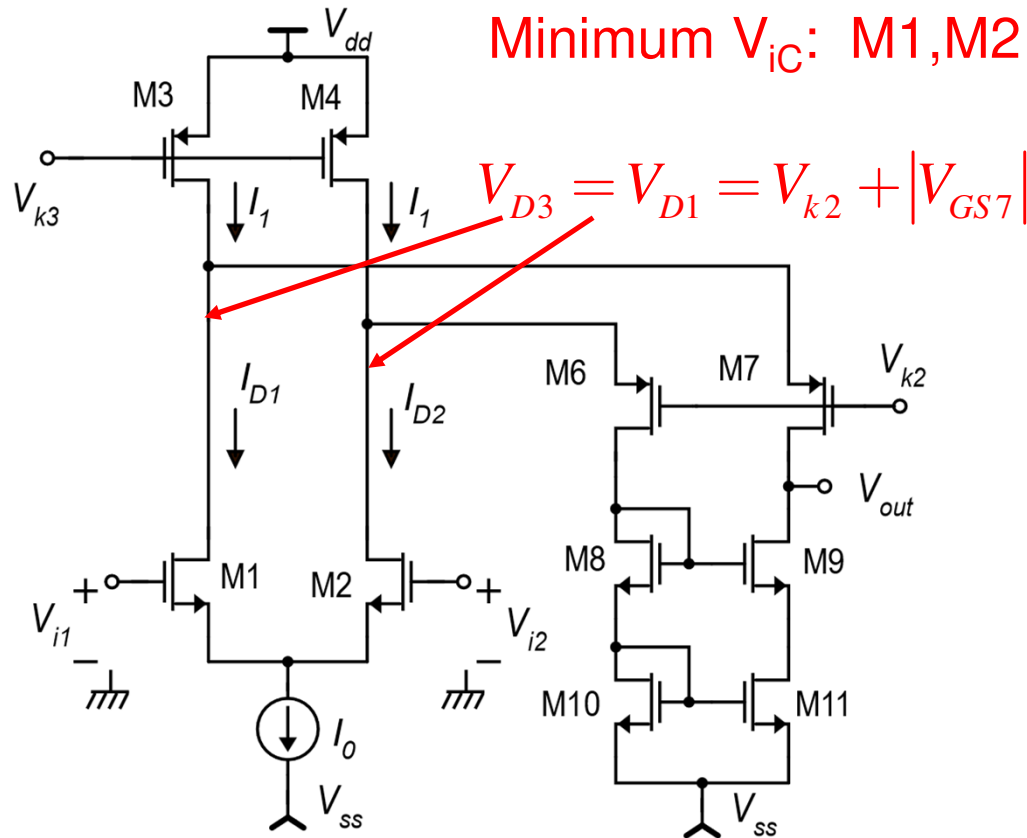Minimum V_{iC} : M1,M2 pair $\Rightarrow \min(V_{iC}) = V_{SS} + V_{MIN-tail} + V_{GS1}$



$$V_{D3} = V_{D1} = V_{k2} + |V_{GS7}|$$

Maximum V_{iC} :

M1 (M2) has the drain at a fixed voltage. If the gate voltage increases, M1 (M2) will eventually leave saturation


$$\begin{aligned} V_{DS1} &= V_{D1} - V_{S1} = \\ &= V_{k2} + |V_{GS7}| - (V_C - V_{GS1}) \geq V_{DSAT1} \end{aligned}$$

$$\max(V_{iC}) = V_{k2} + |V_{GS7}| + V_{GS1} - V_{DSAT1}$$

$$\max(V_{k2}) = V_{dd} - |V_{DSAT3}| - |V_{GS7}|$$

$$\max(V_{iC}) \Big|_{V_{k2-\max}} = V_{dd} - |V_{DSAT3}| + V_{GS1} - V_{DSAT1}$$

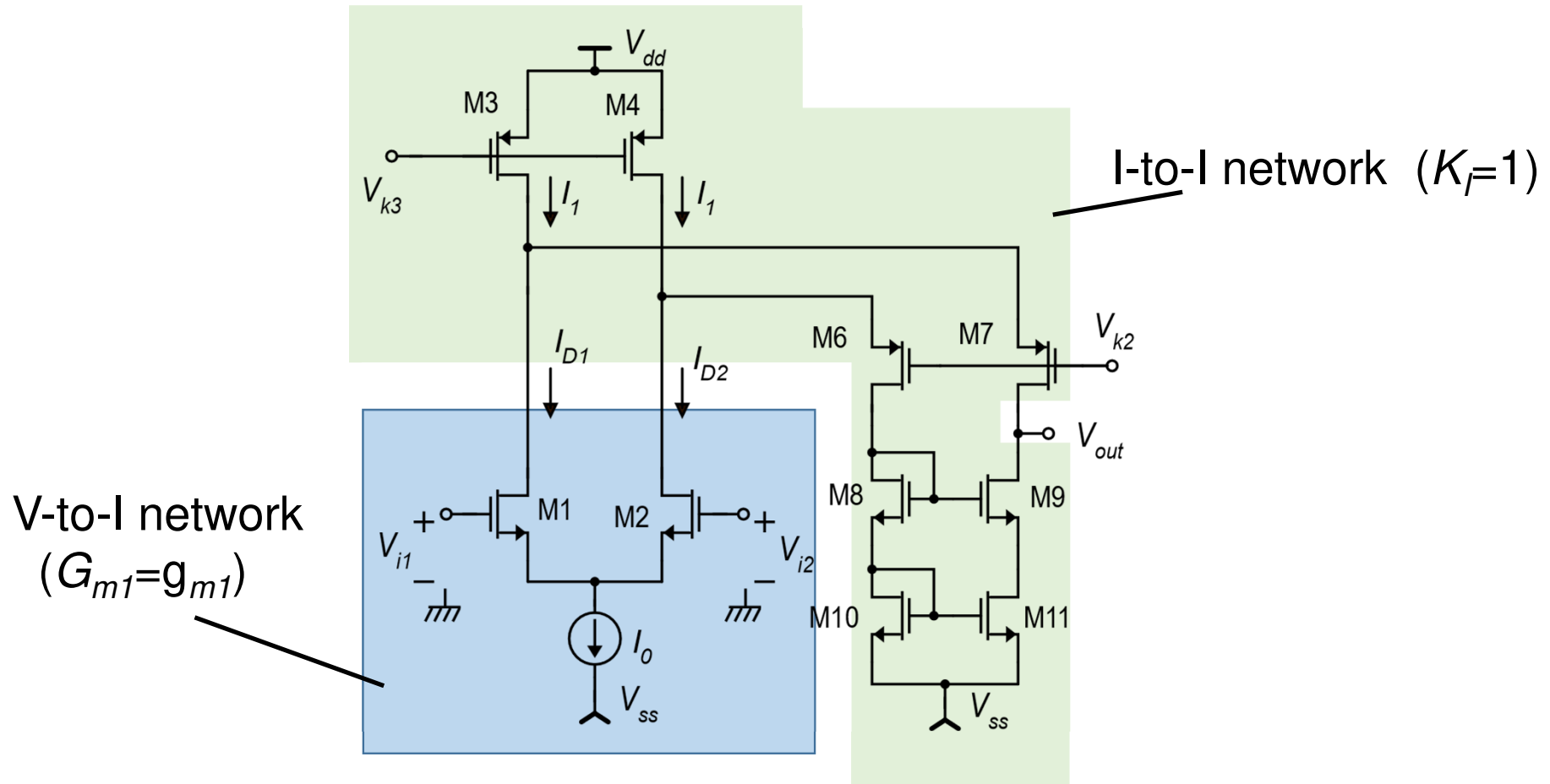The folded cascode as a single stage amplifier



Folded cascode: summary of properties


DC Gain: Slightly smaller than the telescopic amplifier (non-folded cascode) gain. May reach several thousands or even 10^4 (80 dB) with long mosfets. Larger than the gain of the cascade of two common source stages.

Ranges: In the the Folded cascode, the output range is not affected by the input common mode voltage. As a result, the input CM range and output range are much wider than in the telescopic amplifier.

Output range: (swing) $\left\{ \begin{array}{l} \max(V_{out}) = V_{dd} - |V_{DSAT3}| - |V_{DSAT7}| \leftarrow \text{Approaches the } V_{dd} \text{ rail} \\ \min(V_{out}) = V_{SS} + V_{GS11} + V_{DSAT9} \leftarrow \text{May approach the } V_{SS} \text{ rail if a wide swing mirror is used} \end{array} \right.$

Input CM range: $\left\{ \begin{array}{l} \min(V_{iC}) = V_{SS} + V_{MIN-tail} + V_{GS1} \leftarrow \text{The only critical limit} \\ \max(V_C) = V_{dd} - |V_{DSAT3}| + V_{GS1} - V_{DSAT1} \leftarrow \text{Goes over the } V_{dd} \text{ rail} \end{array} \right.$

Example: Analog Devices ADA4530

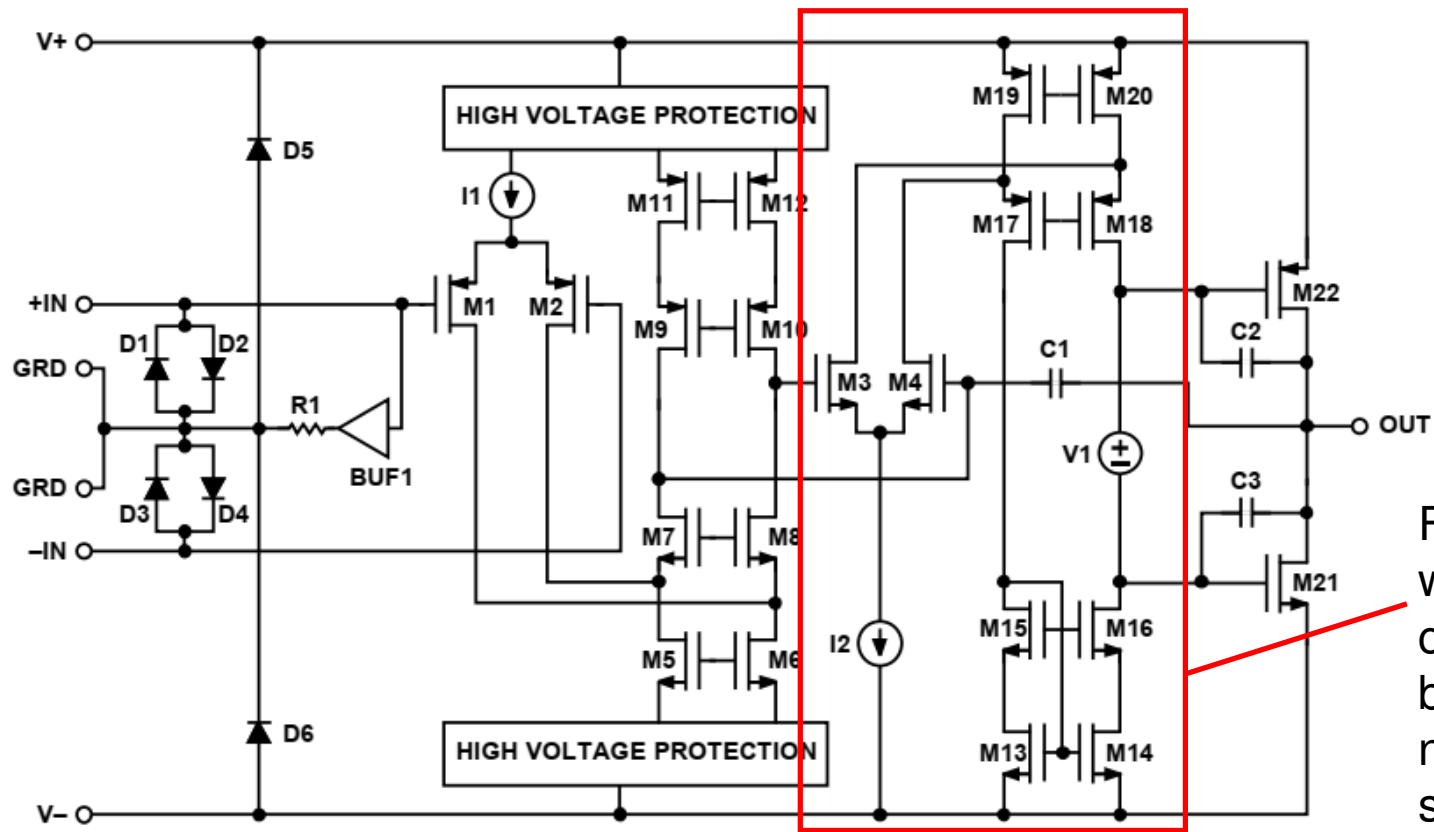

Folded cascode with wide-swing current mirror (gate bias voltages are not indicated for simplicity)

Figure 99. Simplified Schematic
Rev. B | Page 29 of 52

Example of BJT Op-Amp with a single folded cascode gain stage

THS4031-EP
THS4032-EP



SLOS810-NOVEMBER 2008


www.ti.com

APPLICATION INFORMATION

THEORY OF OPERATION

The THS403x is a high-speed operational amplifier configured in a voltage feedback architecture. It is built using a 30-V, dielectrically isolated, complementary bipolar process with NPN and PNP transistors possessing f_T s of several GHz. This results in an exceptionally high-performance amplifier that has wide bandwidth, high slew rate, fast settling time, and low distortion. A simplified schematic is shown in Figure 51.

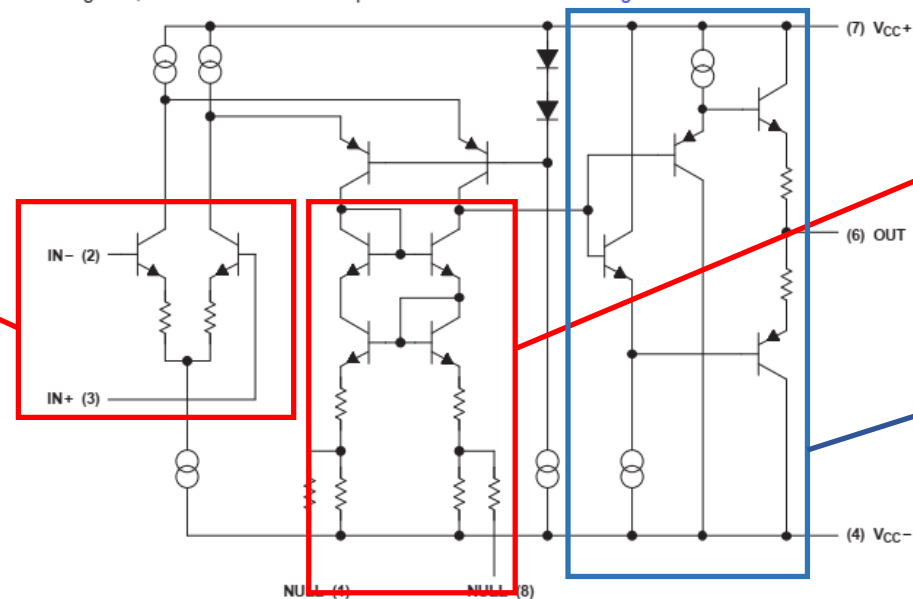Emitter-degenerated input pair (improves input differential range, with benefits in terms of Slew-Rate)



Wilson current mirror with emitter degeneration.

Class-AB emitter follower (gain $\cong 1$)

Figure 51. THS4031 Simplified Schematic