

# Voltage references

Voltage references are blocks that produce an output voltage that is independent of **PVT** variations:

**V**: Supply voltage

**T**: Temperature


**P**: Process errors

Voltage references are used for:

- Providing an absolute reference voltage for ADCs and DACs
- Providing an absolute reference voltage for stimulating sensors or other external devices that require precise control voltages and/or currents.
- Creating constant bias voltages (and currents) when required

## Possible reference voltage sources

- Zener Diodes

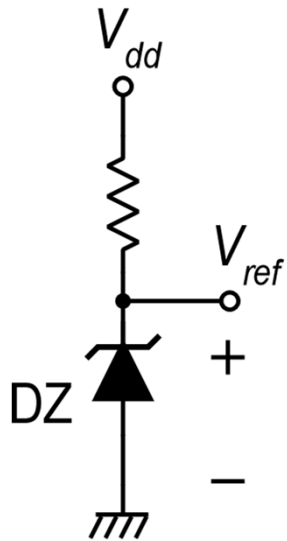

Problems:


- **Require additional process steps**, but only a small number of components are required for each chip (not convenient)
- **Available voltages are  $> 3\text{ V}$**
- Temperature stability is poor for  $V_Z \neq 5\text{-}6\text{ V}$
- The reference voltage generated by a Zener diode is noisy (very wide band noise)

In present days, zener diodes are available only in high voltage processes and are used more for protection than for voltage references

- Band-gap circuits ← solution

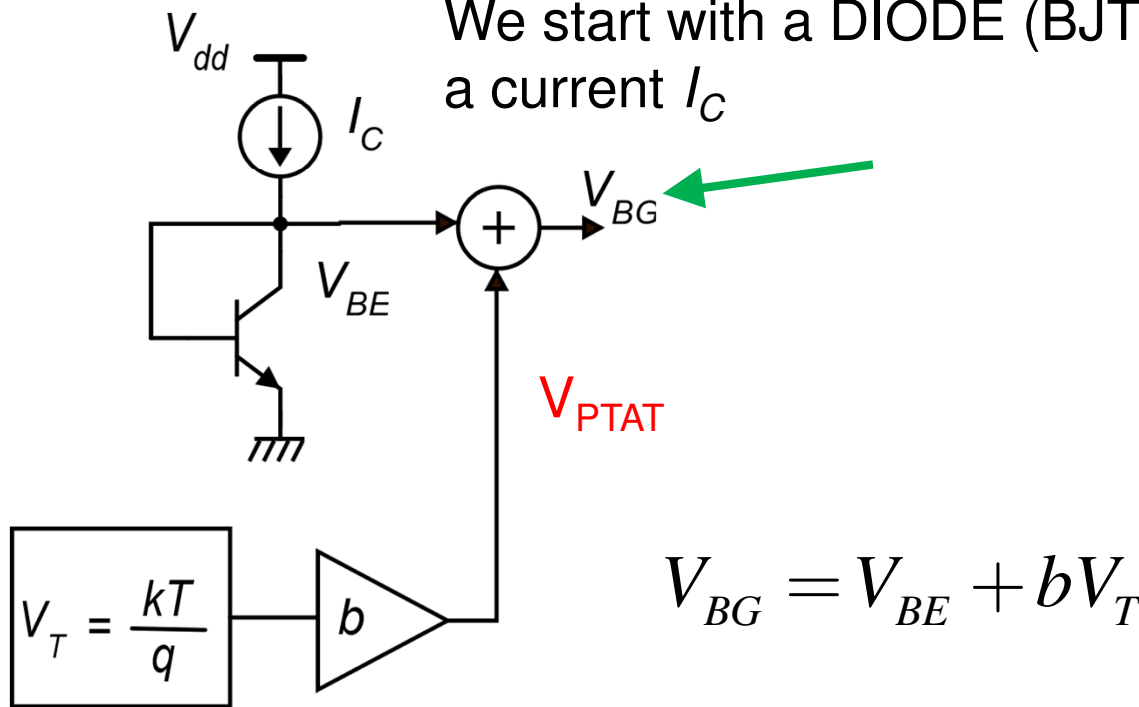
# Band-gap voltage reference: principle of operation

We start with a DIODE (BJT) biased with a current  $I_C$



$$V_{BG} = V_{BE} + bV_T$$
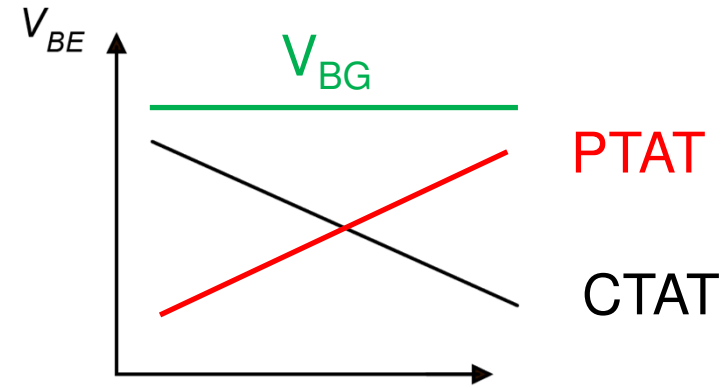
$$\frac{dV_{BE}}{dT} \cong -2 \text{ mV/K} \dots -3 \text{ mV/K}$$



CTAT: Complementary To Absolute Temperature

PTAT: Proportional To Absolute Temperature

## Band-gap voltage reference: determination of parameter $b$ and estimate of the output voltage

$$V_{BG} = V_{BE} + bV_T \quad \text{We have to determine the value of } b, \text{ for which: } \frac{dV_{BG}}{dT} = 0$$

$$\frac{dV_{BG}}{dT} = \frac{dV_{BE}}{dT} + b \frac{dV_T}{dT} = 0$$

$$b = \frac{-\frac{dV_{BE}}{dT}}{\frac{dV_T}{dT}}$$


Good news!  
This voltage is compatible with low-supply voltage circuits

$$\frac{dV_T}{dT} = \frac{k}{q} \cong 8.56 \times 10^{-5} \text{ V / K}$$

Example:

$$\frac{dV_{BE}}{dT} \cong -2 \text{ mV/K} \Rightarrow b \cong 23 \quad V_{BG} \cong 0.65 + 0.025 \times 23 = 1.225 \text{ V}$$

$V_{BE}$   $V_T$  (290 K)

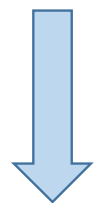

# Band-Gap voltage reference: theory

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$$

$$I_S = \frac{qA_E n_i^2 D_n}{Q_B} = F \cdot n_i^2 D_n$$

constant

$$\frac{E_{g0}}{kT} = \frac{E_{g0}}{q} \frac{q}{kT} = \frac{V_{G0}}{V_T}$$


$V_{G0}$

$$I_S = BT^\gamma e^{-\frac{V_{G0}}{V_T}} \quad \gamma = 4 - \alpha_\mu$$

constant

$\alpha_\mu \cong 1.5$
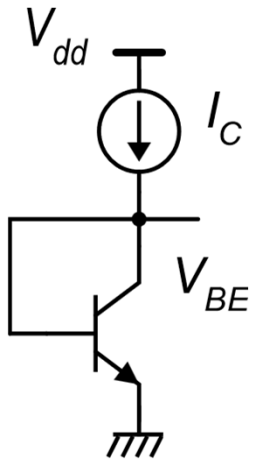
$$\left\{ \begin{array}{l} n_i^2 \propto T^3 e^{-\frac{E_{g0}}{kT}} \\ D_n = \mu_n \frac{kT}{q} \\ \mu_n \propto T^{-\alpha_\mu} \end{array} \right.$$



$$I_C = GT^\alpha$$

constant

It is not necessary that  $I_C$  is temperature-independent

$$V_{BE} = V_T \ln\left(\frac{GT^\alpha}{BT^\gamma \exp\left(\frac{-V_{G0}}{V_T}\right)}\right)$$

$\frac{G}{B} T^{-(\gamma-\alpha)}$

$$= V_{G0} + V_T \left[ \ln(G \cdot E) - (\gamma - \alpha) \ln(T) \right]$$

$E = \frac{1}{B}$

Gray, Hurst, Lewis, Meyer, "Analysis and design of analog integrated circuits" 4th edition, 2001 J.Wiley & Sons

## Band-Gap voltage reference: theory

$$V_{BE} = V_{GO} + V_T \left[ \ln(G \cdot E) - (\gamma - \alpha) \ln(T) \right] \quad V_{BG} = V_{BE} + bV_T$$

$$V_{BG} = V_{GO} + V_T \left[ \ln(G \cdot E) + b - (\gamma - \alpha) \ln(T) \right] = V_{GO} + \frac{kT}{q} \left[ \ln(G \cdot E) + b - (\gamma - \alpha) \ln(T) \right]$$

The name "**band-gap**" of this reference voltage comes from  $V_{GO}$ , which is the dominant part

$$V_{GO} = \frac{E_{g0}}{q} \quad V_{GO} \text{ is numerically equivalent to } E_{g0} \text{ measured in eV}$$

Let us calculate the derivative of  $V_{BG}$  with respect to temperature

$$E_{g0} \cong 1.2 \text{ eV} \Rightarrow V_{GO} \cong 1.2 \text{ V}$$

$$\frac{dV_{BG}}{dT} = \frac{k}{q} \left[ \ln(G \cdot E) + b - (\gamma - \alpha) \ln(T) \right] - (\gamma - \alpha) \frac{kT}{q} \frac{1}{T}$$

$$\frac{dV_{BG}}{dT} = \frac{k}{q} \left[ \ln(G \cdot E) + b - (\gamma - \alpha) - \underline{\underline{(\gamma - \alpha) \ln(T)}} \right]$$

The derivative of  $V_{BG}$  depends on temperature

## Band-Gap voltage reference: theory

We impose that the derivative of  $V_{BG}$  is zero at a given temperature  $T_0$ . This is possible, since  $b$  is a free parameter that can be chosen to obtain this result.

$$\frac{k}{q} \left[ \ln(G \cdot E) + \overset{\downarrow}{b} - (\gamma - \alpha) - (\gamma - \alpha) \ln(T_0) \right] = 0$$

$$\ln(G \cdot E) + b = (\gamma - \alpha) + (\gamma - \alpha) \ln(T_0)$$

$$V_{BG} = V_{G0} + V_T \left[ \ln(G \cdot E) + b - (\gamma - \alpha) \ln(T) \right]$$

$$V_{BG} = V_{G0} + V_T \left[ (\gamma - \alpha) + (\gamma - \alpha) \ln(T_0) - (\gamma - \alpha) \ln(T) \right]$$


Typically:  $\alpha=1$

$$V_{BG} = V_{G0} + V_T (\gamma - \alpha) \left( 1 + \ln\left(\frac{T_0}{T}\right) \right)$$

$$V_{BG}(T_0) = V_{G0} + \frac{kT_0}{q} (\gamma - \alpha) \cong 1.24 \text{ V}$$

$$\gamma \cong 2.5$$
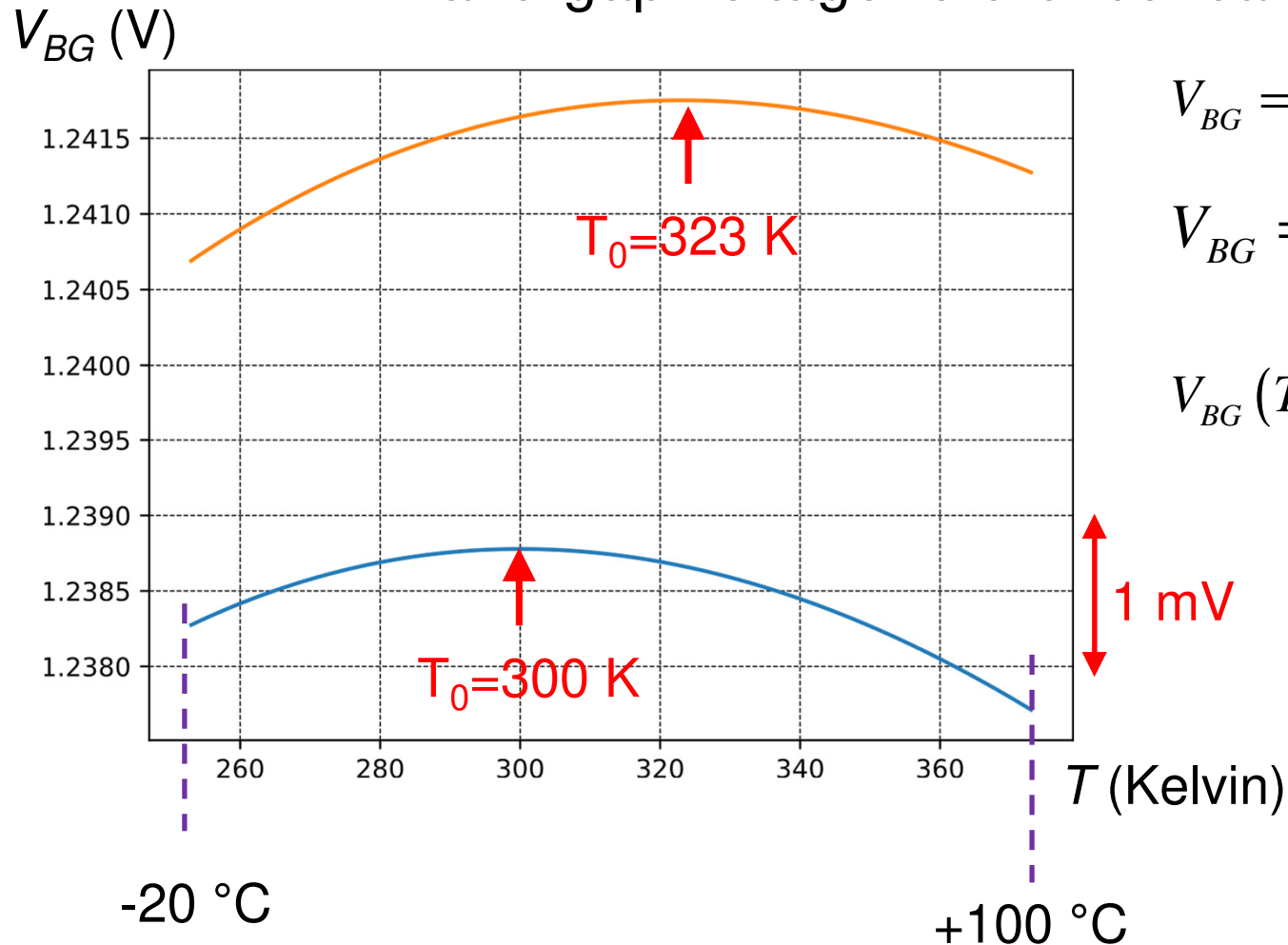
## Band-gap voltage reference: calculation result



$$V_{BG} = V_{BE} + bV_T$$

$$V_{BG} = V_{G0} + V_T (\gamma - \alpha) \left( 1 + \ln \left( \frac{T_0}{T} \right) \right)$$

$$V_{BG}(T_0) = V_{G0} + \frac{kT_0}{q} (\gamma - \alpha)$$


Even if the derivative is zero only at  $T_0$ , the total voltage variation is only a few mV for a wide range

A bandgap voltage reference designed for a higher  $T_0$ , will also have a higher output voltage.




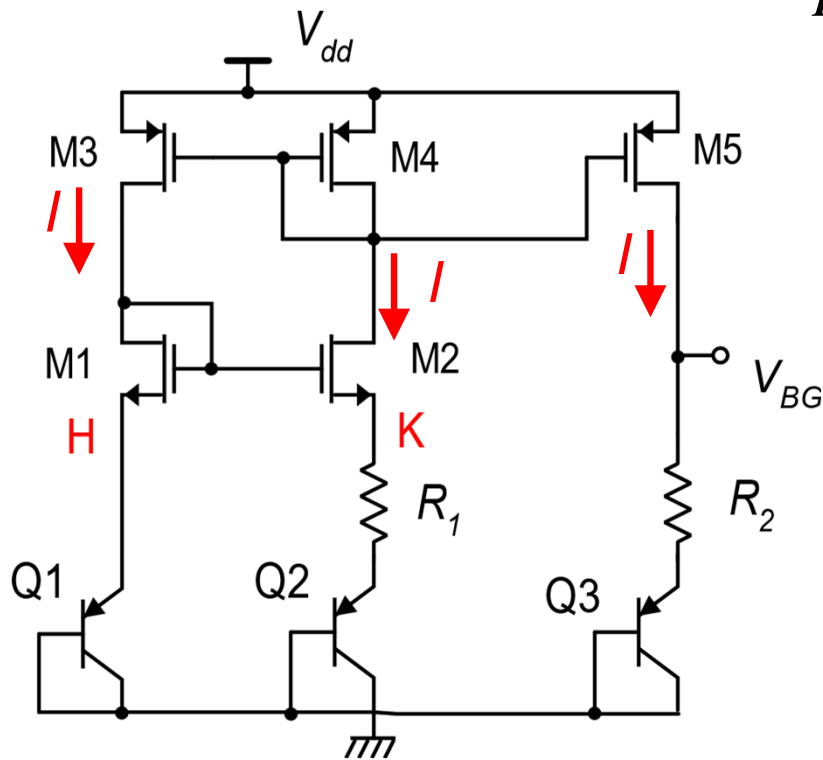
# Band-Gap voltage: a CMOS compatible Circuit



$$I = \frac{1}{R_1} \frac{kT}{q} \ln(n)$$

$$V_{BG} = |V_{BE3}| + IR_2$$


Biased with  $I$   
 $\alpha=1$

$$V_{BG} = |V_{BE3}| + \frac{R_2}{R_1} \frac{kT}{q} \ln(n)$$

$$V_{BG} = |V_{BE3}| + V_T \frac{R_2}{R_1} \ln(n)$$

$$V_{BG} = V_{BE} + bV_T$$
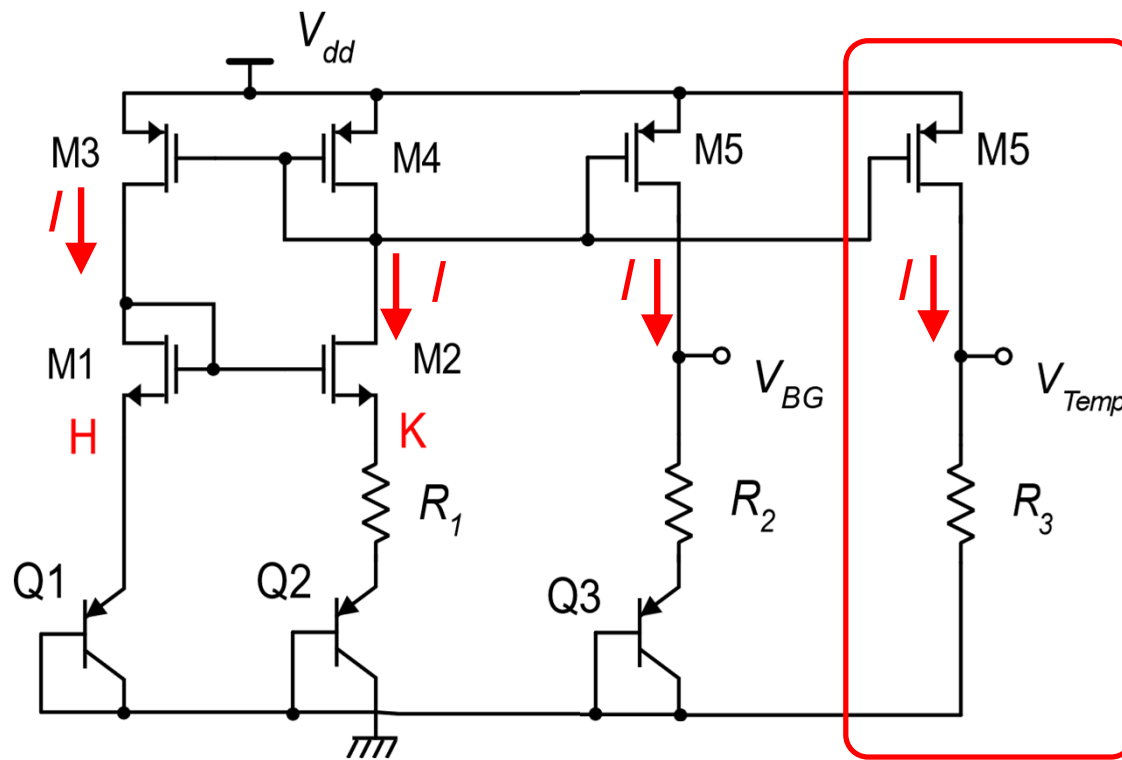
## Deriving a temperature sensor from the Band-Gap circuit




Adding this branch, we can obtain a voltage proportional to the absolute temperature, which can be conveniently used to monitor the chip temperature.

$$V_{Temp} = R_3 I = \frac{R_3}{R_1} \frac{kT}{q} \ln(n)$$



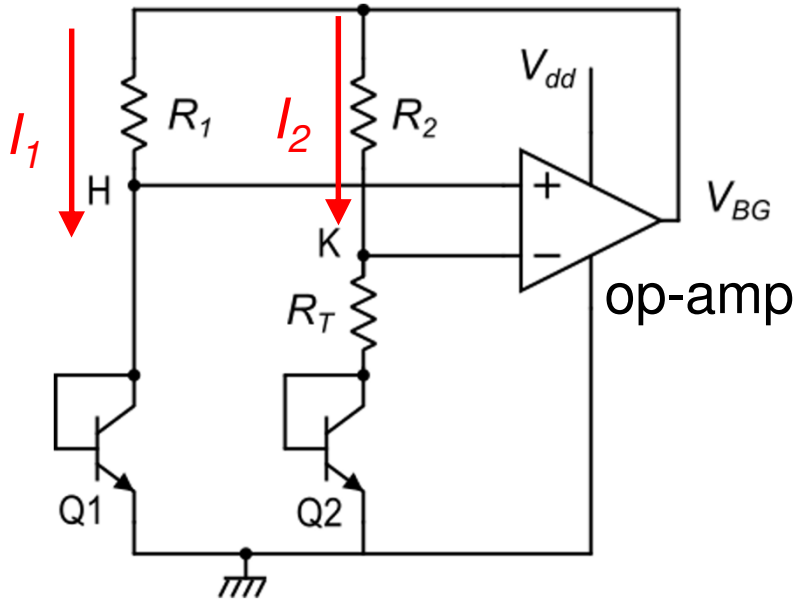Mention to another very popular bandgap circuit



Due to virtual short circuit:

$$V_H = V_K \Rightarrow V_{R1} = V_{R2} \quad (\text{voltages across } R_1 \text{ and } R_2)$$

$$\text{We choose } R_1 = R_2 \Rightarrow I_1 = I_2$$

$$V_H = V_K \Rightarrow V_{BE1} = V_{BE2} + I_2 R_T$$

$$I_2 R_T = V_{BE1} - V_{BE2} = V_T \ln \left( \frac{I_{C1} I_{S2}}{I_{S1} I_{C2}} \right)$$

$$\begin{aligned} I_{C1} &\cong I_1 \\ I_{C2} &\cong I_2 \\ n &= \frac{I_{S2}}{I_{S1}} \end{aligned}$$


$$I_2 = I_1 = \frac{V_T \ln(n)}{R_T}$$

$$V_{BG} = V_{BE1} + I_1 R_1 = V_{BE1} + \frac{V_T \ln(n)}{R_T} R_1^b$$

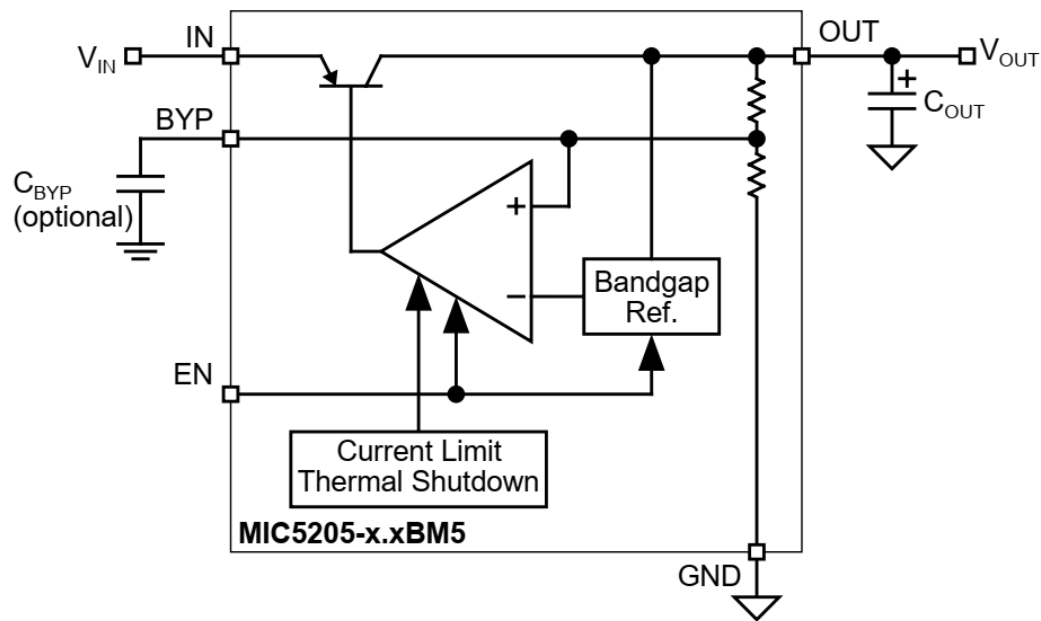
# The bandgap voltage reference in voltage regulators



**MIC5205**  
150mA Low-Noise LDO Regulator  
Final Information



**Ultra-Low-Noise Fixed Regulator**

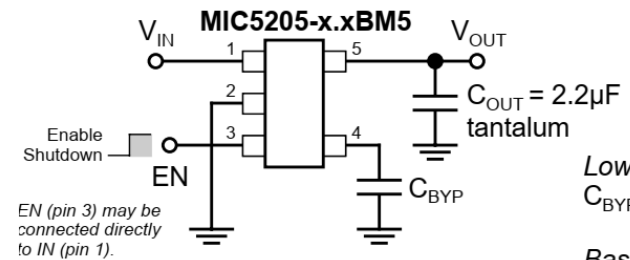

*Low-Noise Operation:*  
 $C_{BYP} = 470\text{pF}$ ,  $C_{OUT} \geq 2.2\mu\text{F}$

*Basic Operation:*  
 $C_{BYP} = \text{not used}$ ,  $C_{OUT} \geq 1\mu\text{F}$