

1 Considerations on the cascode topology

A simple cascode architecture involving two n-MOSFETs is shown in Fig. 1.1.

Let us consider the effects of variations applied to V_{out} , when V_k and V_{in} are constant. In terms of variations:

$$v_{out} = v_{ds1} + v_{ds2} \tag{1.1}$$

Using the small signal equations of M_1 and M_2 , we find:

$$i_{d1} = \frac{v_{ds1}}{r_{d1}} \tag{1.2}$$

$$i_{d2} = g_{m2}v_{gs2} + g_{mB2}v_{bs2} + \frac{v_{ds2}}{r_{d2}} \tag{1.3}$$

where g_{mb2} is M_2 body transconductance, given by:

$$g_{mB2} = (m-1) \cdot g_{m2} \tag{1.4}$$

where m is a coefficient generally varying in the range 1.2-1.3 (see chapter on MOSFET models).

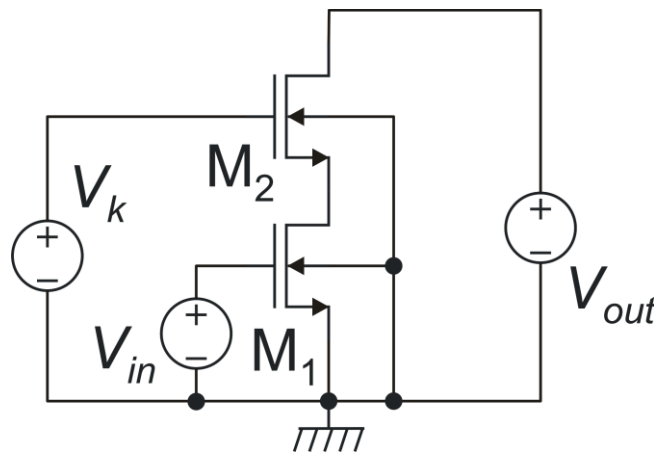


Fig. 1.1. Cascode topology with main voltages indicated.

Since:

$$i_{d2} = i_{d1} \quad v_{gs2} = v_{bs2} = -v_{ds1} \tag{1.5}$$

We find the following equations that ties v_{ds1} and v_{ds2} :

$$\frac{v_{ds1}}{r_{d1}} = -g_{m2}v_{ds1} - g_{mB2}v_{ds1} + \frac{v_{ds2}}{r_{d2}} \quad (1.6)$$

from which we find:

$$v_{ds1} \left(\frac{1}{r_{d1}} + g_{m2} + g_{mB2} \right) = \frac{v_{ds2}}{r_{d2}} \quad (1.7)$$

and finally:

$$v_{ds1} = \frac{v_{ds2}}{r_{d2} (g_{m2} + g_{mB2}) + \frac{r_{d2}}{r_{d1}}} \quad (1.8)$$

As far as M_2 is in saturation, $g_{m2}r_{d2} \gg 1$, therefore the following approximation applies:

$$v_{ds1} \cong \frac{v_{ds2}}{r_{d2} (g_{m2} + g_{mB2})} = \frac{v_{ds2}}{m \cdot g_{m2}r_{d2}} \quad \text{with } m > 1 \quad (1.9)$$

Then, as v_{out} varies the effects on M_1 and M_2 are such that $v_{ds1} \ll v_{ds2}$. As a result, considering (1.1):

$$v_{out} \cong v_{ds2} \quad (1.10)$$

Equations (1.9) and (1.10) are well representative of the mechanisms that produces the typically high output resistance of cascode structures. In fact, M_2 “absorbs” the largest part of V_{out} variations and “protects” M_1 . More precisely, v_{out} variations are transmitted to M_1 through an attenuation of the order of $g_{m2}r_{d2}$. Therefore, as V_{out} varies, V_{DS1} is practically kept constant. Since $V_{GS1}=V_{in}=\text{constant}$ in this analysis and $V_{BS1}=0$, I_{D1} is controlled only by V_{DS1} . If the latter is nearly constant, then also $I_{out} (=I_{D1})$ is nearly constant confirming the high output resistance. As V_{out} is progressively reduced, V_{DS2} diminishes at same pace. When eventually V_{DS2} gets lower than V_{DSAT2} , and M_2 gets into triode region, $g_{m2}r_{d2}$ starts getting progressively smaller and M_2 is no more effective in protecting M_1 from V_{out} variations. From this point on, also V_{DS1} start decreasing and the output current variations becomes more and more important, so that the output resistance enhancement produced by the cascode structure is disrupted.

The V_{out} value at which the output resistance starts increasing significantly is then given by:

$$\min(V_{out}) \equiv V_{MIN} = V_{DS1} + V_{DSAT2} \quad (1.11)$$

Note that:

$$V_{DS1} = V_K - V_{GS2} \quad (1.12)$$

V_{DS1} is determined by V_K and by V_{GS2} , which are both under control of the designer. Depending on the circuit used to produce V_K , V_{DS1} can be significantly higher than V_{DSAT1} .