
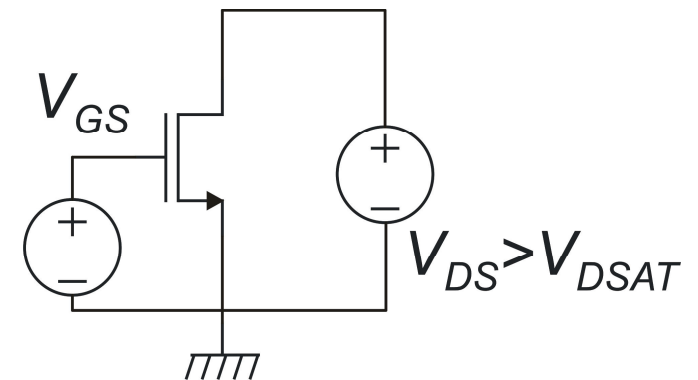


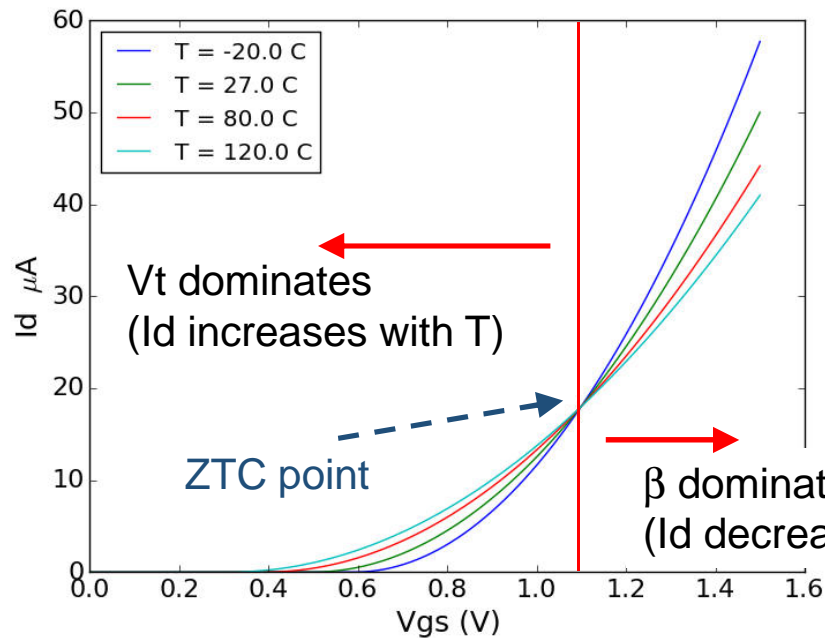
## Temperature effects on MOSFET characteristics

$$\beta_n(T) = \beta_n(T_0) \left( \frac{T}{T_0} \right)^{-\alpha_\mu} \quad \alpha_\mu = 1.2 - 2.4 \text{ (typical 1.5)}$$

$$V_t(T) = V_t(T_0) - \alpha_{VT} (T - T_0) \quad 1 \text{ mV/K} \leq \alpha_{VT} \leq 4 \text{ mV/K}$$



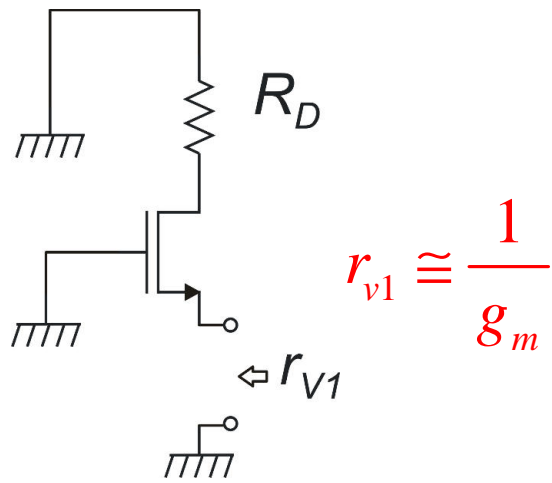
# The six basic (small signal) resistances: MOSFETS




$$r_{v1} = \frac{R_D + r_d}{1 + g_m r_d} \quad \text{exact result}$$

Conditions for approximation
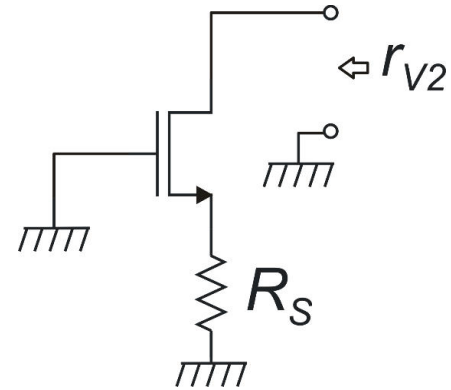
$$g_m r_d \gg 1 \quad \text{and} \quad R_D \ll r_d \Rightarrow r_{v1} \cong \frac{1}{g_m}$$




$$r_{v2} = R_S + r_d (1 + g_m R_S)$$

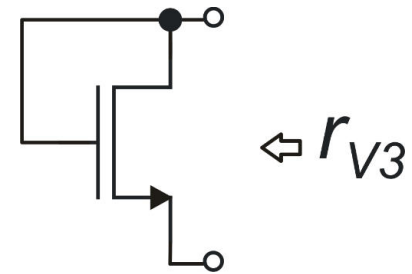

$$r_{v3} = r_D // \frac{1}{g_m} \cong \frac{1}{g_m}$$

Diode-connected MOSFET
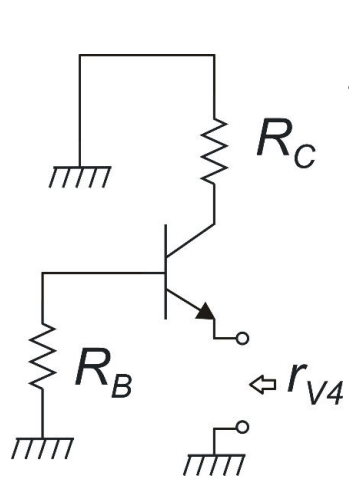
# The six basic (small signal) resistances: BJTs



$$g_{meq} \equiv \frac{r_{be}}{R_B + r_{be}} g_m = \frac{h_{fe}}{R_B + r_{be}}$$


$$r_{v4} \cong \frac{1}{g_{meq}}$$

exact result

$$r_{v4} = \frac{R_C + r_o}{1 + g_{meq} r_o} \parallel (r_{be} + R_B)$$

Conditions for approximation
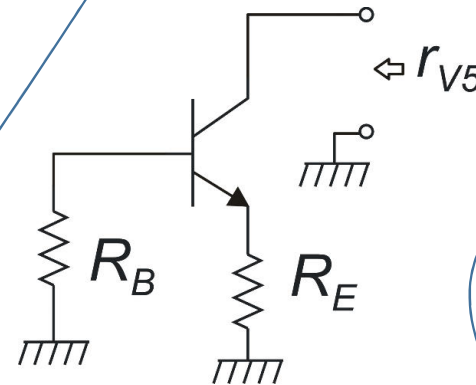
$$g_{meq} r_o \gg 1 \quad \text{and} \quad R_C \ll r_o$$



exact result


$$r_{v5} = R_{Eeq} + r_o (1 + g_{meq} R_{Eeq})$$

$$R_{Eeq} = (R_B + h_{ie}) \parallel R_E$$

approximations

$$1) \quad R_E \ll (r_{be} + R_B) \Rightarrow r_{v5} \cong r_o (1 + g_{meq} R_E)$$

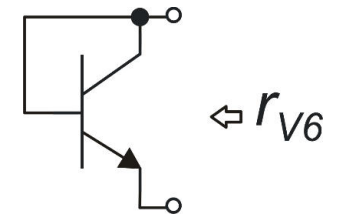
$$2) \quad R_E \gg (r_{be} + R_B) \Rightarrow r_{v5} \cong r_o (1 + h_{fe})$$



$$r_{v6} = r_o \parallel \frac{1}{g_m} \parallel h_{ie} \cong \frac{1}{g_m}$$
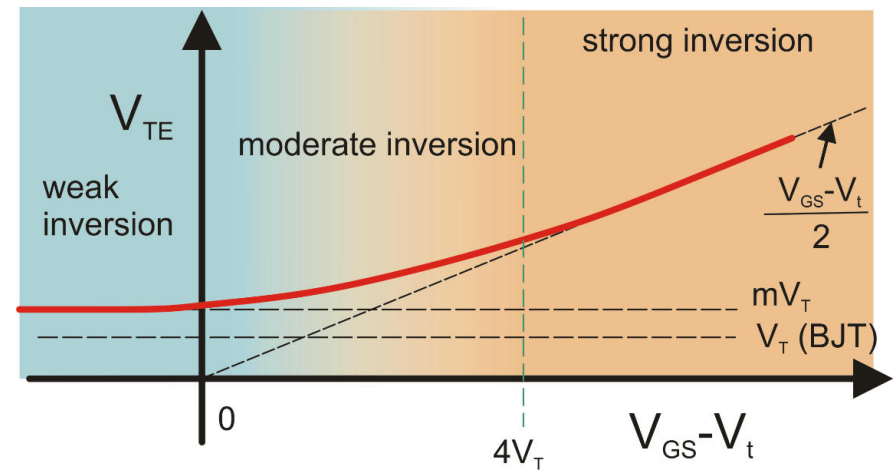
## The $g_m r_d$ product (in saturation region)

$$r_d = \frac{1}{g_{ds}} = \frac{1}{\lambda I_D} = \frac{\lambda^{-1}}{I_D} \quad \left. \begin{array}{l} g_m = \frac{I_D}{V_{TE}} \\ \end{array} \right\} g_m r_d = \frac{1}{V_{TE}} \cdot \frac{1}{\lambda}$$



$$\frac{1}{\lambda} \propto L_{eff}$$

Large  $g_m r_d$  products are obtained for small  $V_{GS} - V_t$  and large  $L$


$g_m r_d$  is generally of the order of 100

## $g_m r_o$ for BJTs in active zone


$$\left. \begin{aligned} g_m &= \frac{I_C}{V_T} \\ r_o &= \frac{V_A}{I_C} \end{aligned} \right\} g_m r_o = \frac{V_A}{V_T}$$

$g_m r_o$  may easily reach 1000 (e.g. for  $V_A=25$  V)

## Source / Emitter degeneration

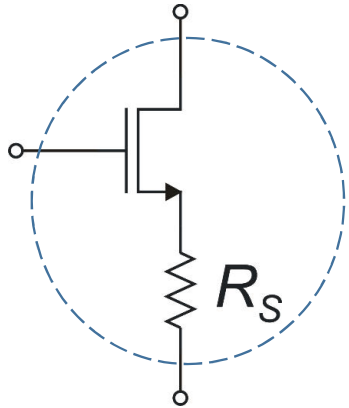

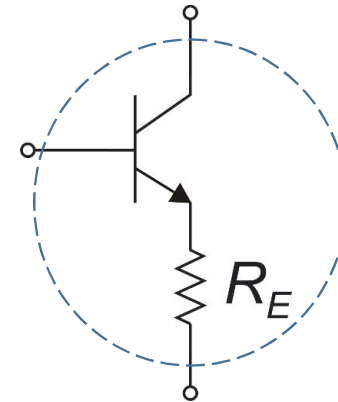- Lower effective  $g_m$  for the same  $I_D$  ( $I_C$ )
- Higher equivalent  $r_o$
- Higher input impedance



$$g_{mrid} = \frac{g_m}{1 + g_m R_S}$$

← reduced gm →

$$g_{mrid} \cong \frac{g_m}{1 + g_m R_E}$$

$$\frac{g_{mrid}}{I_D} = \frac{1}{V_{TE}} \cdot \frac{1}{1 + g_m R_S}$$

$$\frac{g_{mrid}}{I_D} \cong \frac{1}{V_T} \cdot \frac{1}{1 + g_m R_E}$$

$$g_m R_S = \frac{I_D R_S}{V_{TE}}$$

$$g_m R_E = \frac{I_C R_E}{V_T}$$