
 


 
Voltage amplifiers: number of inputs and outputs



Unipolar:
single input
single output (single-ended, S/E)




 Differential:
differential input,
single output (single-ended, S/E)




Fully Differential:
differential input,
differential output

Voltage Amplifiers: gains

 

$$v_{id} = v_{i1} - v_{i2}$$

$$v_{ic} = \frac{v_{i1} + v_{i2}}{2}$$

 

$$v_{od} = v_{o1} - v_{o2}$$

$$v_{oc} = \frac{v_{o1} + v_{o2}}{2}$$


$$A_{dd} = \left. \frac{v_{od}}{v_{id}} \right|_{v_{ic}=0}$$

$$A_{cd} = \left. \frac{v_{od}}{v_{ic}} \right|_{v_{id}=0}$$

$$A_{dc} = \left. \frac{v_{oc}}{v_{id}} \right|_{v_{ic}=0}$$

$$A_{cc} = \left. \frac{v_{oc}}{v_{ic}} \right|_{v_{id}=0}$$

$$CMRR = \left| \frac{A_{dd}}{A_{cd}} \right|$$

 


$$A_d = \left. \frac{v_{out}}{v_d} \right|_{v_c=0}$$

$$A_c = \left. \frac{v_{out}}{v_c} \right|_{v_d=0}$$


$$v_d = v_{i1} - v_{i2}$$

$$v_c = \frac{v_{i1} + v_{i2}}{2}$$

$$CMRR = \left| \frac{A_d}{A_c} \right|$$

 

Differential amplifiers: parameters

 

$$V_{out} = A_d (V_{id} - V_{io})$$

Linear response
(with input offset voltage)

Input voltage ranges:

Input differential range
(maximum V_{ID} (V_D) to
maintain an acceptable
input-output linearity

$$-V_{DMAX} \leq V_D \leq V_{DMAX}$$

Input common-mode range:

Interval of VC values where
the amplifier behaves as
designed

$$V_{CMIN} \leq V_C \leq V_{CMAX}$$


Output voltage range (Output voltage swing)

$$V_{OMIN} \leq V_{out} \leq V_{OMAX}$$

Outside the output range
the amplifier stop working
correctly (e.g. the output
voltage tends to saturate)

Differential amplifiers: role of the input common mode range

 Example: voltage follower (buffer amplifier)



In the ideal case:

$$V_{io} = 0, A_d \rightarrow \infty$$

We have:

$$V_C = V_{in}$$
$$V_D \cong 0$$




The voltage follower operates correctly only for V_{in} within the CM range

Another condition is clearly that V_{out} is within the output range

Then the conditions for correct operation are:

$$V_{out} = V_{in} \text{ only for } \begin{cases} V_{CMIN} \leq V_{in} \leq V_{CMAX} \\ V_{OMIN} \leq V_{out} \leq V_{OMAX} \end{cases}$$

Single Stage Voltage Amplifiers

 

small-signal output voltage

$$v_{out} = i_{occ} R_{out}$$

The first component converts the input voltage (single or differential) into a current (single or differential)

example

$$I_1 - I_2 = G_{m1} V_{in}$$

The second component is a current processing network, that takes the input currents and applies simple linear operations such as:

- Addition and subtraction
- Addition of constant currents
- Multiplication by a constant gain factor

The processed currents are finally conveyed to an output resistance (R_{out}) and converted back to a voltage (V_{out}). In most cases, R_{out} is not a physical resistor, but is the output differential resistance of the I-to-I network.

For this reason, one of the function of the I-to-I network is increasing the output resistance to increase gain

example


$$I_{occ} = k_I (I_1 - I_2) = G_{m1} k_I V_{in}$$

$$v_{out} = G_{m1} k_I v_{in} R_{out}$$

defining: $G_m = k_I G_{m1}$

$$\underline{\underline{A = G_m R_{out}}}$$

 Differential amplifier with resistive loads



$$V_{ID} = V_{i1} - V_{i2} \quad V_{OD} = V_{o1} - V_{o2}$$

$$V_{O1} = V_{DD} - R_{D1}I_{D1} \quad V_{O2} = V_{DD} - R_{D2}I_{D2} \quad V_{OD} = R_{D2}I_{D2} - R_{D1}I_{D1}$$

Small signal analysis

$$v_{o1} = -R_{D1}i_{d1} \quad v_{o2} = -R_{D2}i_{d2} \quad v_{od} = i_{d2}R_{D2} - i_{d1}R_{D1}$$

$$\text{Differential mode: } i_{d1} = \frac{g_m}{2}v_{id} \quad i_{d2} = -\frac{g_m}{2}v_{id}$$

Single-ended case:

$$v_{out} = v_{o1} = -R_{D1} \frac{g_m}{2} v_{id}$$


$$A_d = -R_{D1} \frac{g_m}{2}$$

Fully-differential case:

$$v_{out} = v_{od} = -\frac{g_m}{2} (R_{D1} + R_{D2}) v_{id}$$

$$A_{dd} = -g_m \frac{(R_{D1} + R_{D2})}{2}$$

Common mode Analysis

 

$$v_{id} = 0 \Rightarrow i_{d1} = i_{d2}$$

$$v_{i1} = v_{i2} = v_c$$

$$i_0 = i_{d1} + i_{d2} = \frac{v_s}{r_{os}}$$

$$v_s = v_{i1} - v_{gs1} = v_c - v_{gs1}$$

$$i_{d1} \cong g_m v_{gs1}$$

$$v_{GS} \cong \text{constant}$$

$$v_{gs1} = \frac{i_{d1}}{g_m}$$

$$v_s = v_c - \frac{i_{d1}}{g_m}$$

$$i_{d1} + i_{d2} = 2i_{d1} = i_0$$

$$i_{d1} = \frac{i_0}{2} = \frac{v_s}{2r_{os}}$$

$$v_s = v_c - \frac{v_s}{2r_{os}g_m}$$


$$v_s = v_c \frac{1}{1 + \frac{1}{2g_m r_{os}}} \cong v_c$$

This, actually, is not an ideal current source. It has a finite output resistance = r_{os} . If it is implemented by a simple current mirror, $r_{os} = r_d$ otherwise it can be even higher

The source voltage practically follows the common mode variations. V_s is V_c shifted by V_{GS}

Common mode gain and CMRR

output voltages

 

$$i_{d1} = i_{d2} \cong \frac{i_0}{2}$$

$$v_{o1} = -R_{D1}i_{d1} \quad v_{o2} = -R_{D2}i_{d2} \quad v_{od} = i_{d2}R_{D2} - i_{d1}R_{D1}$$

Single-ended case

$$v_{out} = v_{o1} = -R_{D1}i_{d1} \quad v_{out} - R_{D1} \frac{i_0}{2} \cong -R_{D1} \frac{v_c}{2r_{os}}$$

$$A_c = \left. \frac{v_{out}}{v_c} \right|_{v_d=0} \cong -\frac{R_{D1}}{2r_{os}}$$

$$CMRR = \frac{A_d}{A_c} = \frac{g_m R_{D1}}{2} \frac{2r_{os}}{R_{D1}} \quad |A_d|$$

$$v_{i1} = v_{i2} = v_c$$

$$v_s \cong v_c$$


$$i_0 = \frac{v_s}{r_{os}} \cong \frac{v_c}{r_{os}}$$

$$CMRR = \left| \frac{A_d}{A_c} \right| = g_m r_{os}$$

Considering that generally I_o is produced by a simple current mirror, $r_{os} = r_d$, then $CMRR \sim 40$ dB,

This CMRR is not sufficient for many applications

Common mode gain and CMRR

 

$$i_{d1} = i_{d2} \cong \frac{i_0}{2} \quad v_{o1} = -R_{D1}i_{d1} \quad v_{o2} = -R_{D2}i_{d2} \quad v_{od} = i_{d2}R_{D2} - i_{d1}R_{D1}$$

Fully differential case

$$v_{out} = v_{od} = \frac{i_0}{2}R_{D2} - \frac{i_0}{2}R_{D1} = \frac{i_0}{2}(R_{D2} - R_{D1})$$

$$v_{out} = \frac{v_c}{2r_{os}}(R_{D2} - R_{D1}) \quad A_{cd} = \frac{v_{od}}{v_{ic}} \Big|_{v_{id}=0} = -\frac{1}{2r_{os}}(R_{D1} - R_{D2})$$

$$CMRR = \left| \frac{A_{dd}}{A_{cd}} \right| = \frac{g_m}{2} \frac{(R_{D1} + R_{D2})}{(R_{D1} - R_{D2})} \frac{2r_{os}}{1} = 2g_m r_{os} \left(\frac{\Delta R_D}{\bar{R}_D} \right)^{-1}$$


$\left(\frac{\Delta R_D}{\bar{R}_D} \right)$ is a relative matching error ~ 0.01 $\implies \left(\frac{\Delta R_D}{\bar{R}_D} \right)^{-1} \approx 100$

$CMRR \approx 10^4 = 80 \text{ dB}$
Adequate for most applications


BJT case

In the case of a BJT differential amplifier, the expressions are exactly the same as for the MOSFET case.

 
The only important difference is the presence of a base current that is drawn from the voltage sources that provide V_{i1} and V_{i2} . In terms of small signal analysis, this base current is the cause of a finite input resistance that may result in an input attenuation if the signal voltage sources (V_{i1} , V_{i2}) have a significant internal resistance.



 Equivalent circuit of the input terminals



Maximum gain for a given supply voltage

 

$$\left. \begin{array}{l} \text{single ended} \quad A_d = -R_{D1} \frac{g_m}{2} \quad \left| A_d \right| = \frac{g_m R_D}{2} \\ \text{fully-differential} \quad A_{dd} = -g_m \frac{(R_{D1} + R_{D2})}{2} \quad \left| A_{dd} \right| = g_m R_D \end{array} \right\} \text{nominal case: } R_{D1} = R_{D2} = R_D$$

$$\text{using: } g_m = \frac{I_D}{V_{TE}} \quad \left| A_{dd} \right| = \frac{R_D I_D}{V_{TE}}$$

$R_D I_D$ is the static voltage drop across resistors R_D . It cannot exceed the total supply voltage $V_{DD} - V_{SS}$


$$R_D I_D < (V_{DD} - V_{SS})$$

$$\left| A_{dd} \right| < \frac{(V_{DD} - V_{SS})}{V_{TE}}$$

Example: $V_{TE} = 50 \text{ mV}$, $V_{DD} - V_{SS} = 3 \text{ V}$: $\left| A_{dd} \right| < 60$


With a BJT: $V_{TE} = V_T = 25 \text{ mV}$: $\left| A_{dd} \right| < 120$

 To get the highest gain for a given supply voltage it is convenient to bias the MOSFETS with the smallest V_{TE} .



Offset voltage of differential amplifiers with resistive load

 MOSFET case - fully-differential - Strong inversion



Nominally identical circuits

$$v_{io} = V_D \Big|_{V_{out}=0}$$

$$V_{out} = V_{o1} - V_{o2}$$

$$V_D = V_{GS1} - V_{GS2} \triangleq \Delta V_{GS}$$

We can consider the difference of V_{GS} as the matching error between two nominally identical circuits: M1, R_{D1} and M2, R_{D2}

$$V_{GS} = V_t + \sqrt{\frac{2I_D}{\beta}}$$

$$V_{GS} = A + B$$

$$\Delta A = \Delta V_t$$

$$A = V_t \quad B = \sqrt{\frac{2I_D}{\beta}} = \sqrt{2} \cdot I_D^{\frac{1}{2}} \beta^{-\frac{1}{2}}$$


$$\Delta V_{GS} = \Delta A + \Delta B$$

$$\Delta B = B \cdot \frac{\Delta B}{B} = B \cdot \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta \beta}{\beta} \right)$$

posynomial form

Offset voltage of differential amplifiers with resistive load

MOSFET case - fully-differential

 

$$V_D = \Delta V_{GS} = \Delta A + \Delta B$$

$$V_{GS} = V_t + \sqrt{\frac{2I_D}{\beta}}$$

A ↓ B

$$\Delta A = \Delta V_t \quad \Delta B = B \cdot \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta \beta}{\beta} \right)$$


$$V_D = \Delta V_{GS} = \Delta V_t + \sqrt{\frac{2I_D}{\beta}} \cdot \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta \beta}{\beta} \right)$$

This is a generic expression of V_D , corresponding to a given value of $\frac{\Delta I_D}{I_D}$

This expression gives V_{io} for the particular $\frac{\Delta I_D}{I_D}$ value that results in $V_{out}=0$

Offset voltage of differential amplifiers with resistive load

MOSFET case - fully-differential

 

$$V_{out} = V_{OD} = \underbrace{R_{D2}I_{D2} - R_{D1}I_{D1}}$$

defining: $Z = R_D I_D \quad \Delta Z = V_{out}$

Imposing $V_{out}=0$
is the same as
imposing $\Delta Z=0$

$$\Delta Z = \frac{\Delta Z}{Z} Z = \left(\frac{\Delta R_D}{R_D} + \frac{\Delta I_D}{I_D} \right) R_D I_D = 0$$


$R_D I_D$ is the average
value and cannot
be zero

$$\frac{\Delta I_D}{I_D} = -\frac{\Delta R_D}{R_D} \quad \leftarrow \quad = 0 \quad V_D = \Delta V_{GS} = \Delta V_t + \sqrt{\frac{2I_D}{\beta}} \cdot \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta \beta}{\beta} \right)$$

$$V_{io} = \Delta V_t + \sqrt{\frac{2I_D}{\beta}} \cdot \left(-\frac{1}{2} \frac{\Delta R_D}{R_D} - \frac{1}{2} \frac{\Delta \beta}{\beta} \right)$$

Offset voltage of differential amplifiers with resistive load

MOSFET case - fully-differential

 


$$V_{io} = \Delta V_t + \sqrt{\frac{2I_D}{\beta}} \cdot \left(-\frac{1}{2} \frac{\Delta R_D}{R_D} - \frac{1}{2} \frac{\Delta \beta}{\beta} \right)$$

$$V_{io} = \Delta V_t - \frac{(V_{GS} - V_t)}{2} \left(\frac{\Delta R_D}{R_D} + \frac{\Delta \beta}{\beta} \right)$$

$$\sigma_{V_{io}} = \sqrt{\sigma_{V_t}^2 + \left[\sigma_{\frac{\Delta \beta}{\beta}} \frac{(V_{GS} - V_t)}{2} \right]^2 + \left[\sigma_{\frac{\Delta R_D}{R_D}} \frac{(V_{GS} - V_t)}{2} \right]^2}$$

Role of the design parameters

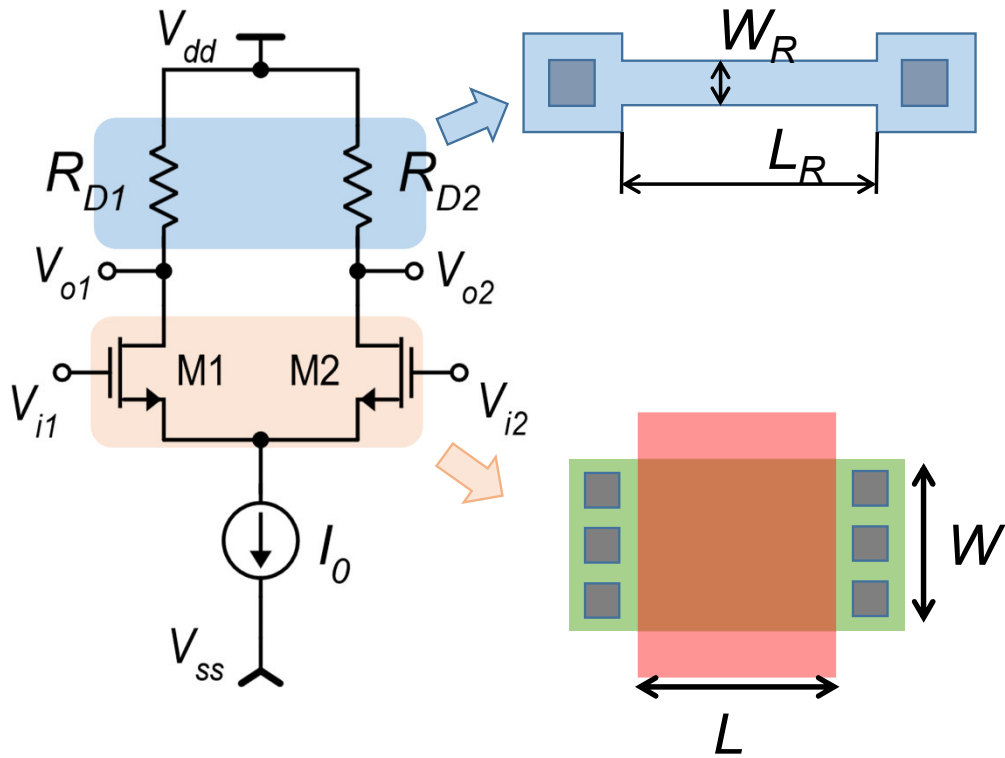

$$\sigma_{V_{io}} = \sqrt{\sigma_{V_t}^2 + \left[\sigma_{\frac{\Delta\beta}{\beta}} \frac{(V_{GS} - V_t)}{2} \right]^2 + \left[\sigma_{\frac{\Delta R_D}{R_D}} \frac{(V_{GS} - V_t)}{2} \right]^2}$$

$$\frac{L_R}{W_R} \rightarrow R_D \quad W_R L_R \rightarrow \sigma_{\frac{\Delta R_D}{R_D}} = \frac{C_R}{\sqrt{W_R L_R}}$$


To be made as small as possible, to reduce $\sigma_{V_{io}}$

$$I_0 \rightarrow (V_{GS} - V_t) \quad \begin{cases} \sigma_{V_t} = \frac{C_{vt}}{\sqrt{WL}} \\ \sigma_{\frac{\Delta\beta}{\beta}} = \frac{C_\beta}{\sqrt{WL}} \end{cases}$$

$$\frac{W}{L} \rightarrow \beta$$

Small offset means large silicon area

 Offset voltage of a BJT differential amplifier with resistor load



$$\underline{v_{io} = V_{id} \Big|_{V_{od}=0}} \quad \underline{V_{od} = V_{o1} - V_{o2} = R_{C2}I_{C2} - R_{C1}I_{C1}}$$


$$V_{id} = V_{i1} - V_{i2} = V_{BE1} - V_{BE2} = \Delta V_{BE}$$

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) \quad V_{id} = \Delta V_{BE} = V_T \left(\frac{\Delta I_C}{I_C} - \frac{\Delta I_S}{I_S} \right)$$

$$\underline{V_{od} = 0} \Rightarrow \Delta(R_C I_C) = 0 \Rightarrow \frac{\Delta I_C}{I_C} = -\frac{\Delta R_C}{R_C}$$

$$v_{io} = V_T \left(-\frac{\Delta R_C}{R_C} - \frac{\Delta I_S}{I_S} \right)$$

 Offset voltage of a BJT differential amplifier with resistor load



$$v_{io} = V_T \left(-\frac{\Delta R_C}{R_C} - \frac{\Delta I_S}{I_S} \right)$$

$$\sigma_{vio} = \sqrt{\left(V_T \sigma \frac{\Delta R_C}{R_C} \right)^2 + \left(V_T \sigma \frac{\Delta I_S}{I_S} \right)^2}$$

$$V_T \sigma \frac{\Delta I_S}{I_S} = \sigma_{\Delta V_{BE}^*}$$

$$\sigma_{\frac{\Delta R_C}{R_C}} = \frac{C_R}{\sqrt{W_R L_R}}$$

Minimum size BJT (elemental BJT) of the process


$$\sigma_{\Delta V_{BE-e}^*}$$

$$\sigma_{\Delta V_{BE}^*} = \frac{\sigma_{\Delta V_{BE-e}^*}}{\sqrt{\text{area}}}$$

$$\sigma_{vio} = \sqrt{\left(V_T \sigma \frac{\Delta R_C}{R_C} \right)^2 + \sigma_{\Delta V_{BE}^*}^2}$$

Small offset means large silicon area

 Temperature drift of the input offset voltage: BJT case




$$v_{io} = \frac{kT}{q} \left(-\frac{\Delta R_C}{R_C} - \frac{\Delta I_S}{I_S} \right)$$

$$\frac{dv_{io}}{dT} = \frac{k}{q} \left(-\frac{\Delta R_C}{R_C} - \frac{\Delta I_S}{I_S} \right)$$

$$\frac{dv_{io}}{dT} = \frac{kT}{q} \left(-\frac{\Delta R_C}{R_C} - \frac{\Delta I_S}{I_S} \right) \frac{1}{T} = \frac{v_{io}}{T}$$

These terms are practically temperature independent (ratios of homogeneous quantities)

 A method to reduce the offset voltage and its drift



$$\frac{dv_{io}}{dT} = \frac{v_{io}}{T}$$

Example: $v_{io}=1$ mV
 $T=300$ K


$$\frac{dv_{io}}{dT} = \frac{1.0 \times 10^{-3}}{300} = 3.3 \mu\text{V/K}$$

By trimming the resistors, I can null the offset. In this way, also the temperature drift is nulled.

This is an advantage of the BJT amplifier. Trimming the offset of a MOSFET differential amplifier does not null the drift.

Example: the OP07

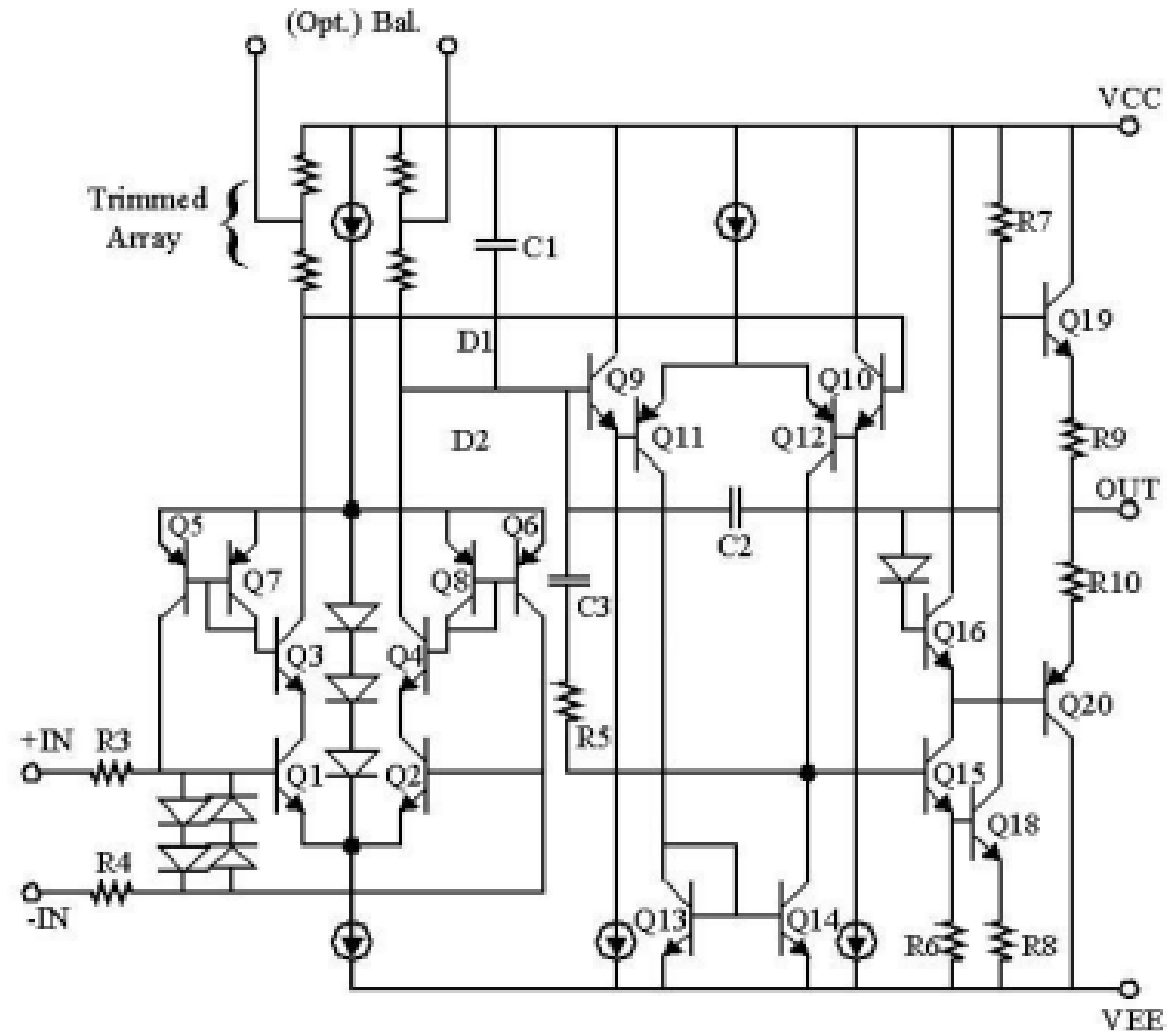1. Resistors are varied by laser trimming to null the offset
2. In this way, also the offset drift is strongly reduced
3. The base currents of the input devices (Q1, Q2) are reproduced by Q3 and Q4 and then fed back to the input terminals by mirrors Q8, Q6 and Q7, Q5. This approach allows to reduce the input bias currents.



OP07 vs μ A741

OP07

Table 1.


Parameter	Symbol	Conditions	Min	Typ	Max	Unit
INPUT CHARACTERISTICS						
T_A = 25°C						
Input Offset Voltage ¹	V _{OS}			30	75	μV
Long-Term V _{OS} Stability ²	V _{OS} /Time			0.3	1.5	μV/Month
Input Offset Current	I _{OS}			0.5	3.8	nA
Input Bias Current	I _B			±1.2	±4.0	nA
0°C ≤ T_A ≤ 70°C						
Input Offset Voltage ¹	V _{OS}			45	130	μV
Voltage Drift Without External Trim ⁴	TCV _{OS}			0.3	1.3	μV/°C
Voltage Drift with External Trim ³	TCV _{OSN}	R _P = 20 kΩ		0.3	1.3	μV/°C

μA741

at specified virtual junction temperature, V_{CC±} = ±15 V (unless otherwise noted)

PARAMETER		TEST CONDITIONS ⁽¹⁾		MIN	TYP	MAX	UNIT
V _{IO}	Input offset voltage	V _O = 0	25°C		1	6	mV
			Full range			7.5	
ΔV _{IO(adj)}	Offset voltage adjust range	V _O = 0	25°C		±15		mV
I _{IO}	Input offset current	V _O = 0	25°C		20	200	nA
			Full range			300	
I _{IB}	Input bias current	V _O = 0	25°C		80	500	nA
			Full range			800	

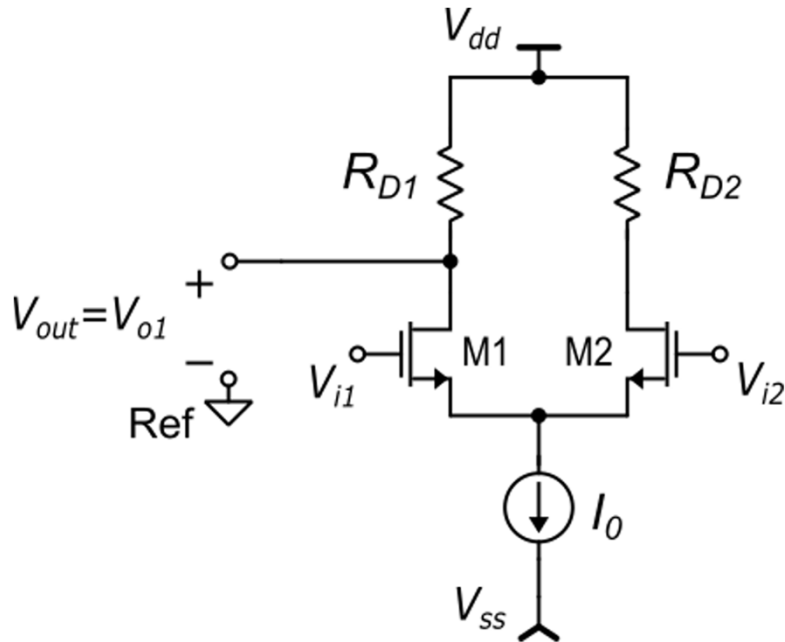How is the amplifier offset when the single ended option is chosen?



$$V_{out} = V_{O1} = V_{dd} - \underline{\underline{R_1 I_{D1}}}$$

Single ended (S/E): device parameters do not appear as differences: the output voltage is affected mainly by global errors

The single ended case is subjected to a much larger offset!

Compare with the fully-differential case:
the output voltage depends only on matching differences

$$V_{od} = R_{D2} I_{D2} - R_{D1} I_{D1}$$