
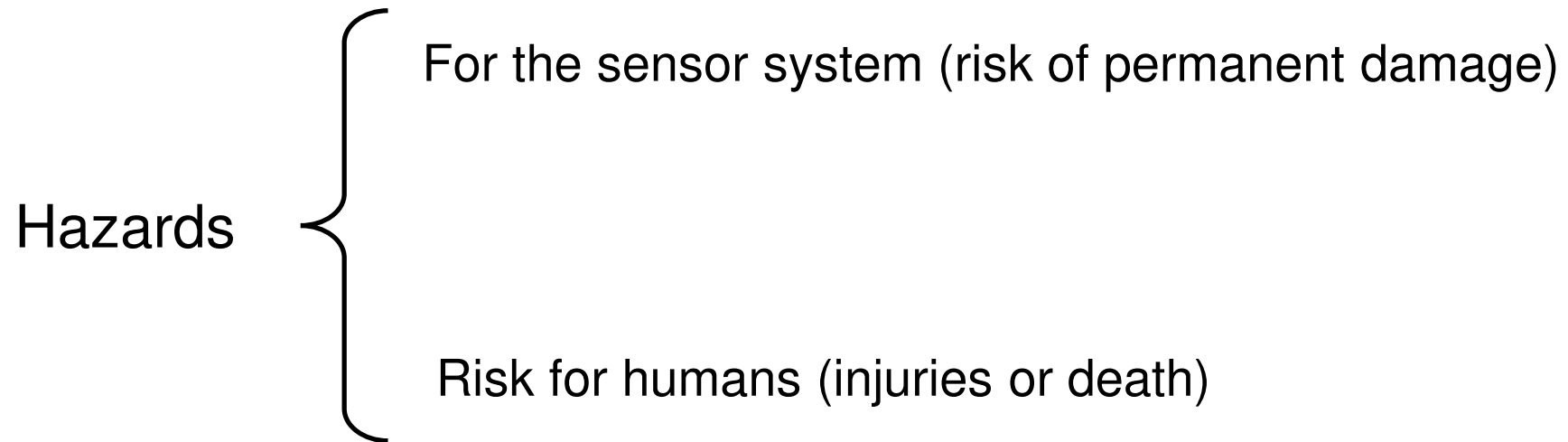


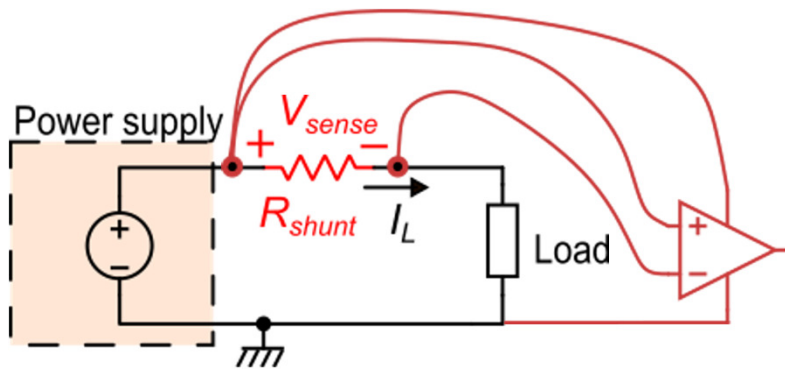Hazards due to unwanted coupling with high voltage sources



Premise: resistive current sensing in power systems

High-side current sensing



$$V_{sense} = I_L R_{shunt}$$


For negligible power loss:

$$V_{sense} \sim \text{mV}$$

Amplification is needed

Input $V_{CM} \cong V_{sup}$
Very high CMRR is required if V_{sup} has large variations


Low-side current sensing

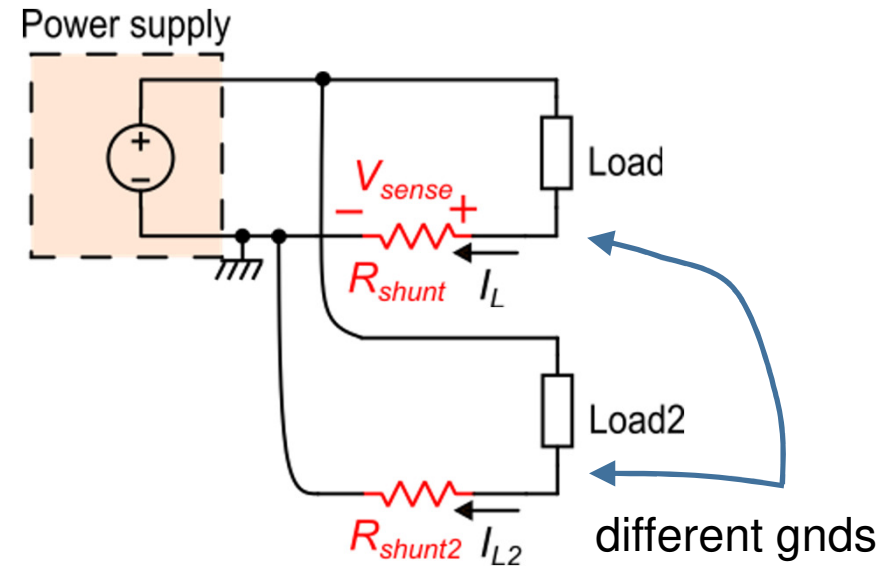

- +) Amplifier input $V_{CM} \cong 0$
-) Load gnd is not power supply *gnd*
-) Current sensing of independent loads cause gnd voltage differences

Risk for the sensor system

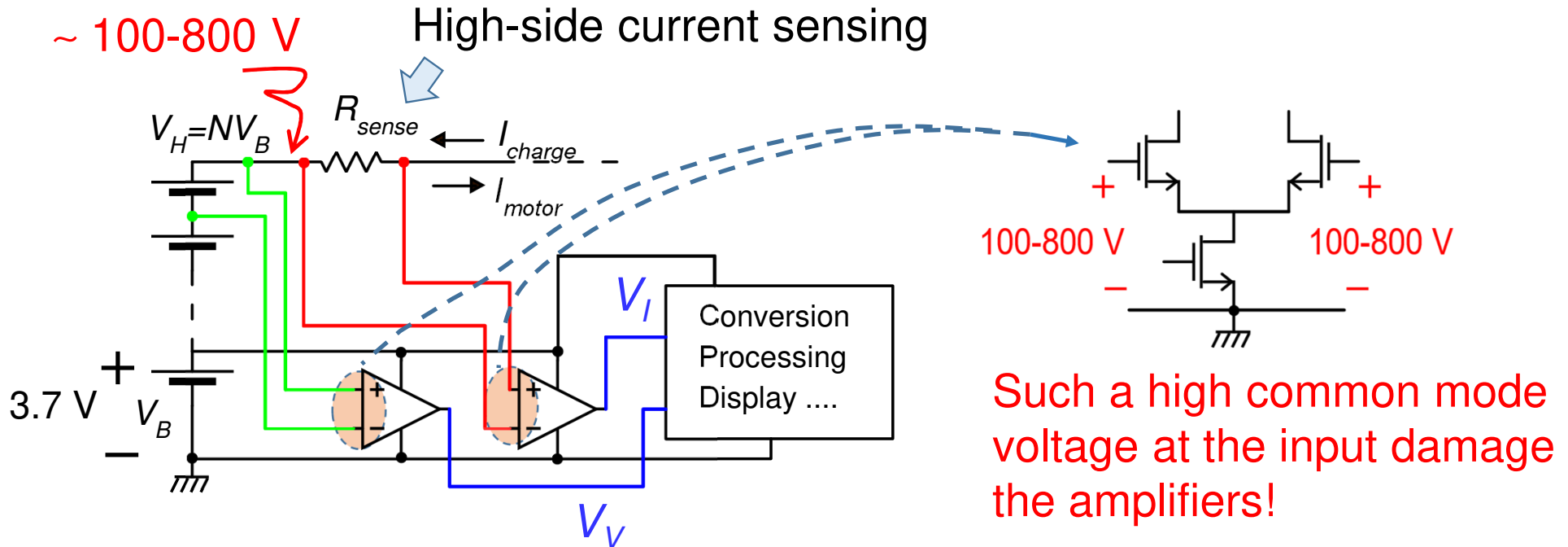Voltage and current sensing in battery packs for e-vehicles




Goal: monitor the current through the battery and the voltage of individual cells for State-of-Charge estimation.

Hazards to humans

Case 1: AC powered biomedical apparatus, electrically connected to the patient.

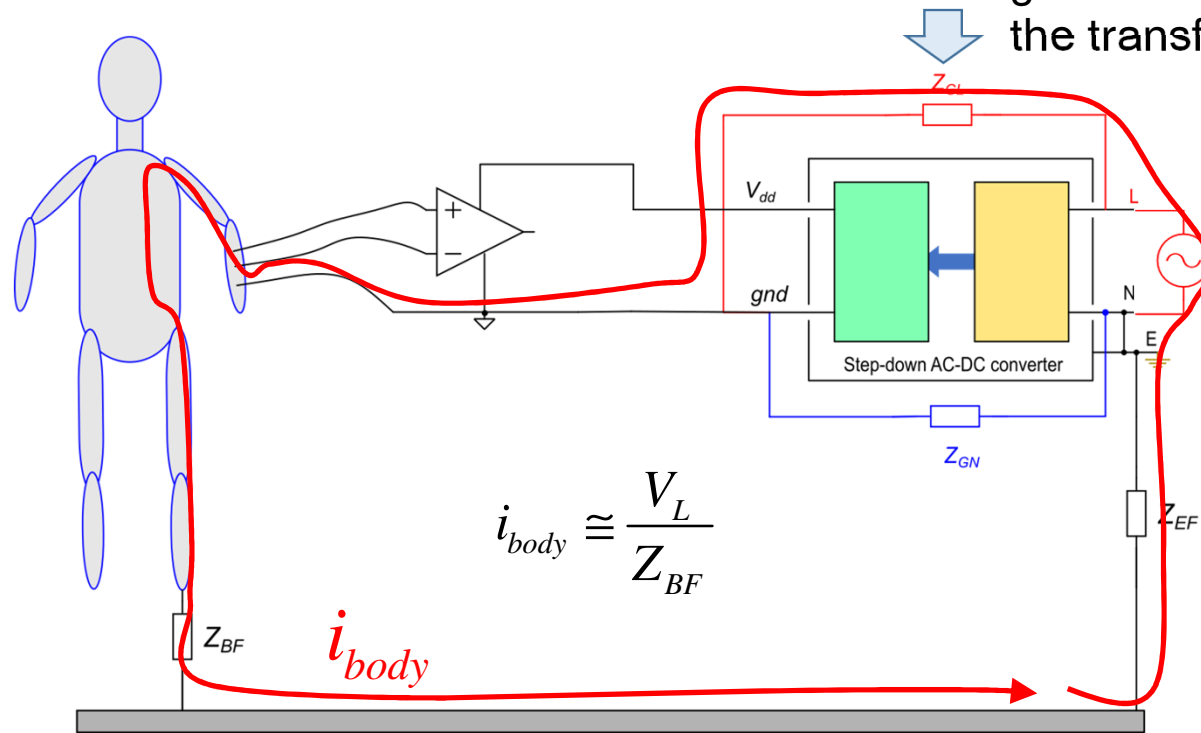Let us suppose that this impedance gets much smaller due to a failure in the transformer insulation.



$$i_{body} = \frac{V_L}{Z_{BF} + Z_{GL} + Z_{EF}}$$


$$i_{body} \cong \frac{V_L}{Z_{BF}}$$

Depending on Z_{BF} , a large current may pass through the body. A current that passes through the heart is potentially fatal.

Hazards to humans

Case 2: Sensing systems with possible continuity with a high voltage domain.

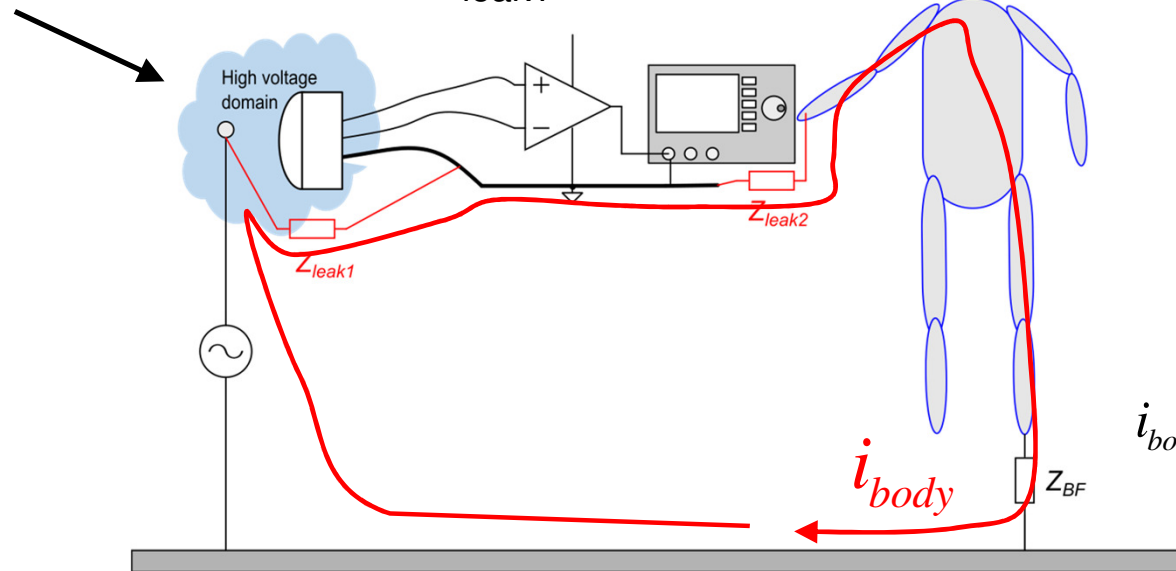
The sensor is isolated from conductors of the high voltage domain, but a leakage impedance may originate from dielectric failure or an unwanted contact (Z_{leak1}).



From the operator side, the front panel control may lose insulation due to wearing or presence of moisture / accidental liquid pouring

$$i_{body} = \frac{V_L}{Z_{BF} + Z_{leak1} + Z_{leak2}}$$

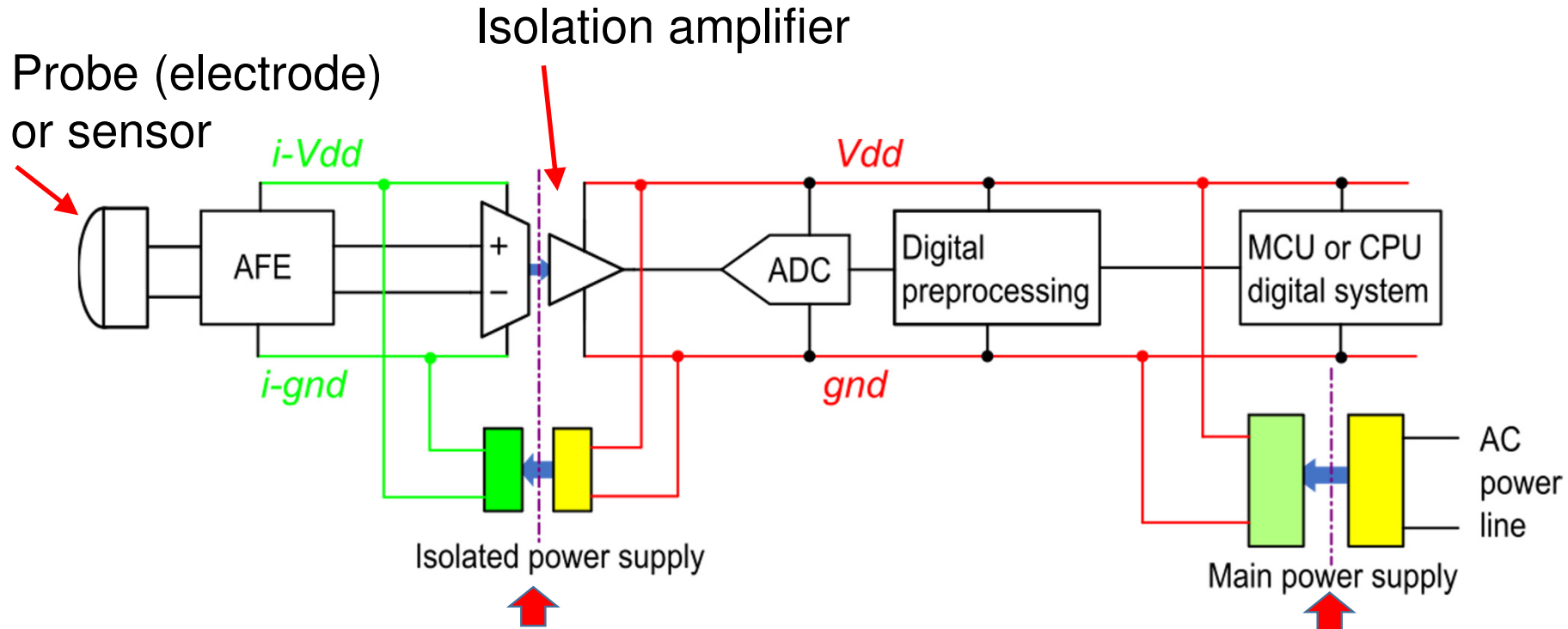Isolation approach 1: Isolation Amplifier



Double protection concept: this is a strict requisite in biomedical instrumentation

Techniques for analog signal insulation

- ❑ Transformer coupling
- ❑ Optical Coupling
- ❑ Capacitive Coupling


Example of transformer coupling: the AD210

FEATURES


High CMV Isolation: 2500 V rms Continuous
 ± 3500 V Peak Continuous
Small Size: 1.00" \times 2.10" \times 0.350"
Three-Port Isolation: Input, Output, and Power
Low Nonlinearity: $\pm 0.012\%$ max
Wide Bandwidth: 20 kHz Full-Power (-)
Low Gain Drift: ± 25 ppm/ $^{\circ}$ C max
High CMR: 120 dB (G = 100 V/V)
Isolated Power: ± 15 V @ ± 5 mA
Uncommitted Input Amplifier

APPLICATIONS

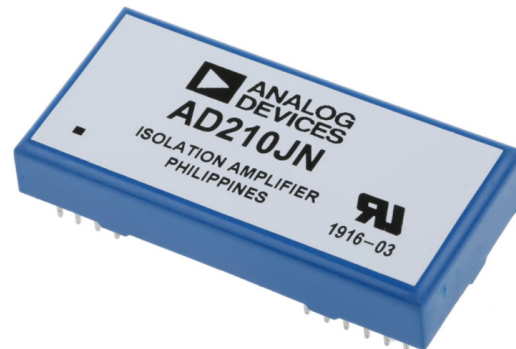
Multichannel Data Acquisition
High Voltage Instrumentation Amplifier
Current Shunt Measurements
Process Signal Isolation



FUNCTIONAL BLOCK DIAGRAM

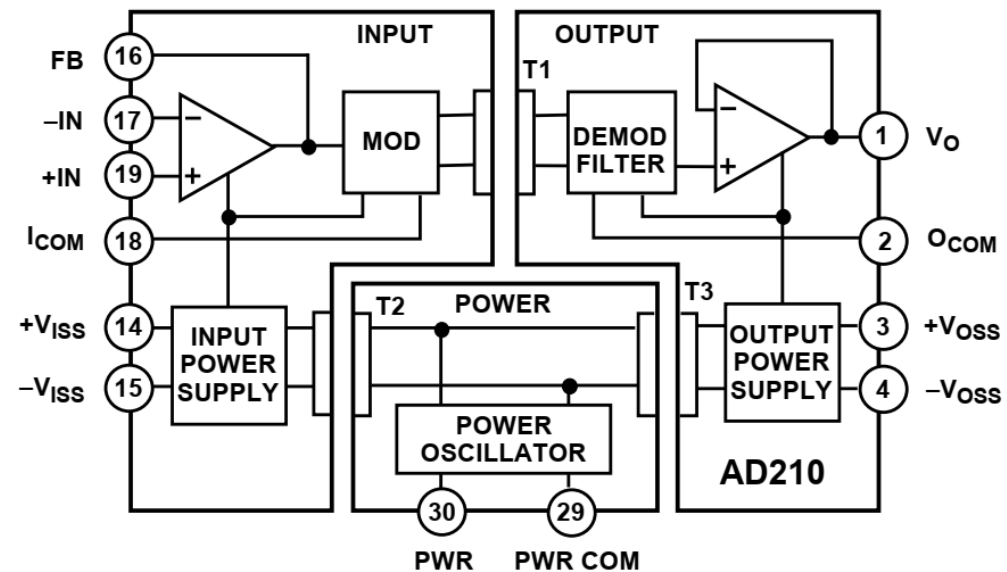

Principle of analog optical coupling

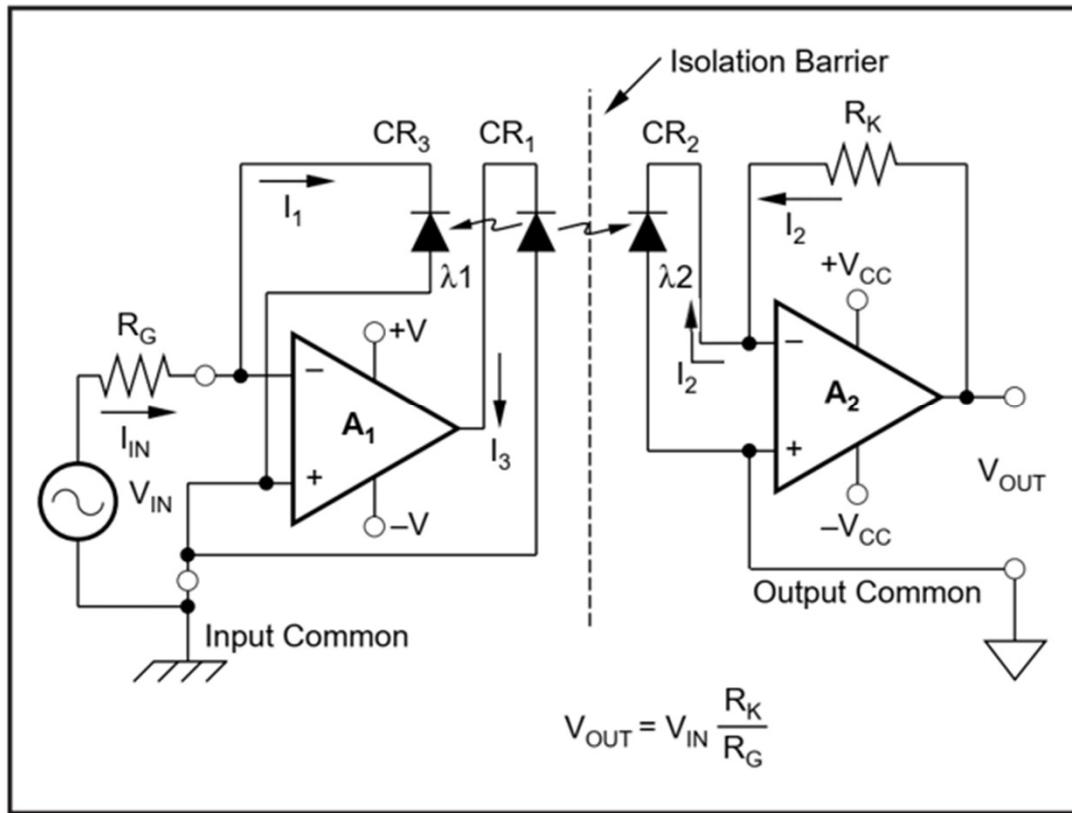

Example: Broadcom ACNT-H79A

An optical link is marked by strong non-linearity. It can be used in an open-loop scheme only to transmit digital signals.

For analog signals, a feedback scheme can be used, as in the figure. The LED CR₁ is coupled in a symmetrical way to photodetectors CR₃ and CR₂, thus:

$$I_1 = I_2 \quad (\text{photocurrents})$$

$$I_1 = I_{IN} = \frac{V_{IN}}{R_G} \quad \text{virtual short circuit due to optical feedback at } A_1.$$

$$V_{OUT} = I_2 R_K = V_{IN} \frac{R_K}{R_G}$$


Isolation amplifier with capacitive coupling

Data that cross the barrier are digital (bitstream).
Differential data links are used

Data are converted back to analog by filtering.



AMC1302-Q1

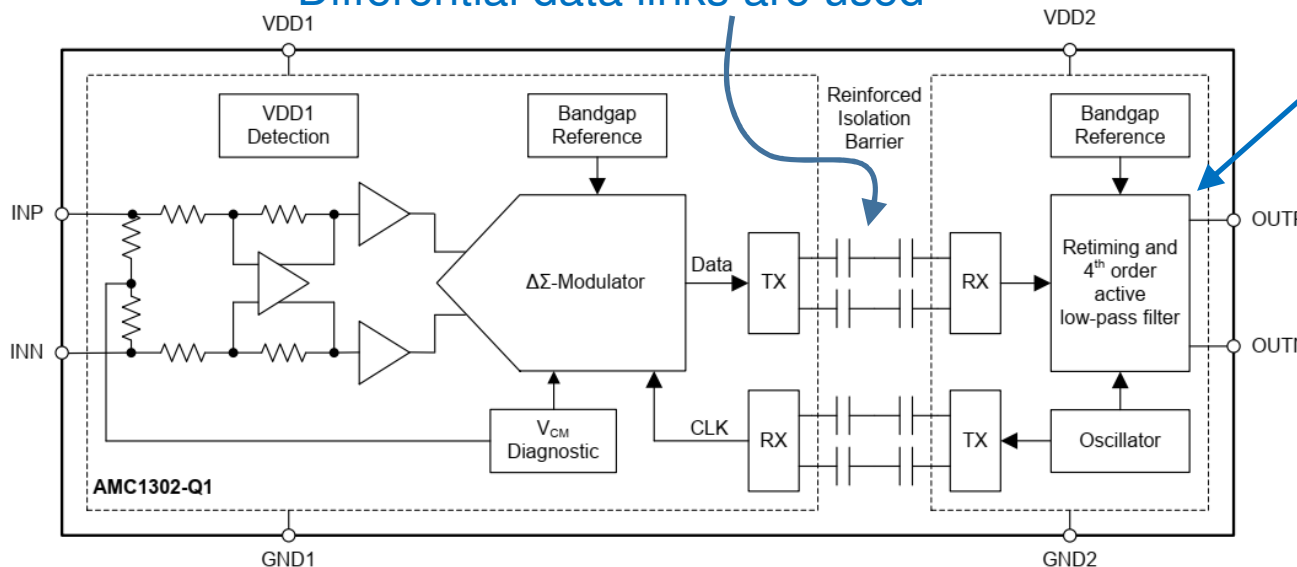


2 Applications

- Shunt-Resistor-Based Current Sensing In:
 - Onboard Chargers (OBC)
 - DC/DC Converters
 - Traction Inverters
 - Battery Management Systems (BMS)

DIN V VDE V 0884-11 (VDE V 0884-11): 2017-01⁽²⁾

V_{IORM}	Maximum repetitive peak isolation voltage	At AC voltage	2121	V_{PK}
V_{IOWM}	Maximum-rated isolation working voltage	At AC voltage (sine wave); see Figure 4	1500	V_{RMS}
		At DC voltage	2121	V_{DC}

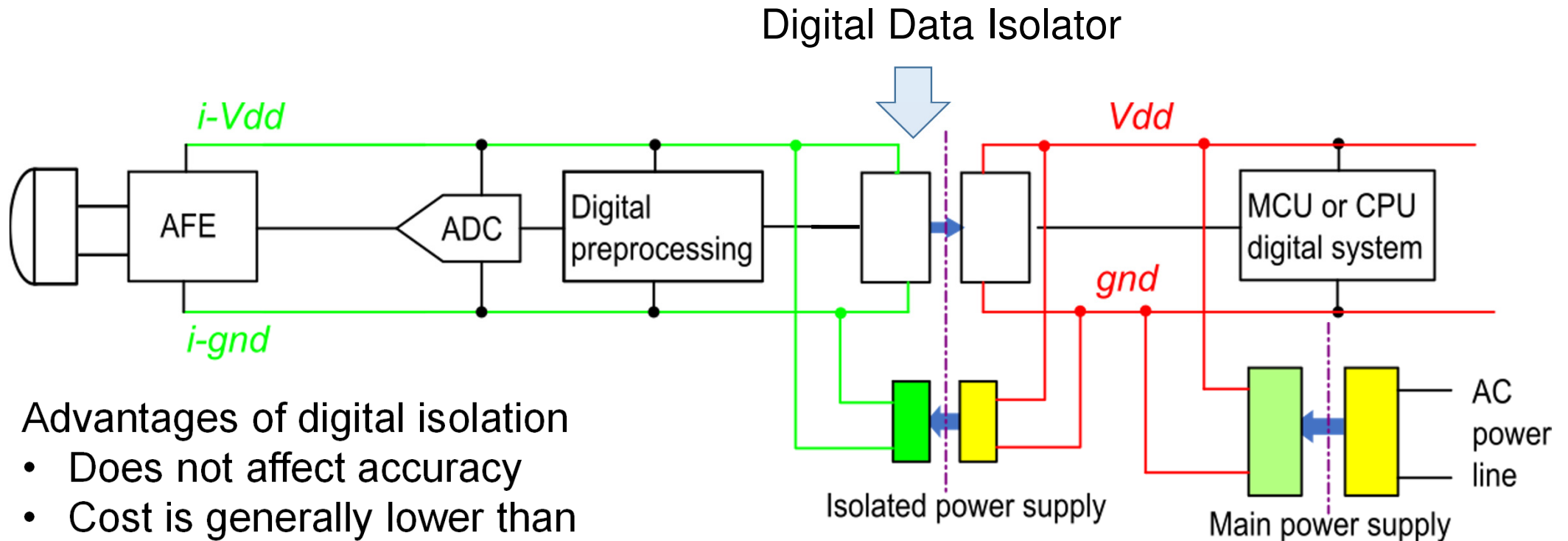Isolation approach 2: Isolated Digital Link



Advantages of digital isolation

- Does not affect accuracy
- Cost is generally lower than analog
- Size is also generally smaller

Digital isolators are based on two principles:
(1) Optical (photocouplers) (2) Capacitive

Example of digital data isolator: I2C isolator

4 channels are necessary because each one of the two I2C lines is bidirectional

Texas Instrument **ISO1640**,

Digital data are modulated by a high frequency carrier (on-off modulation (on-off keying, OOK) and transmitted across the barrier through a capacitive barrier.


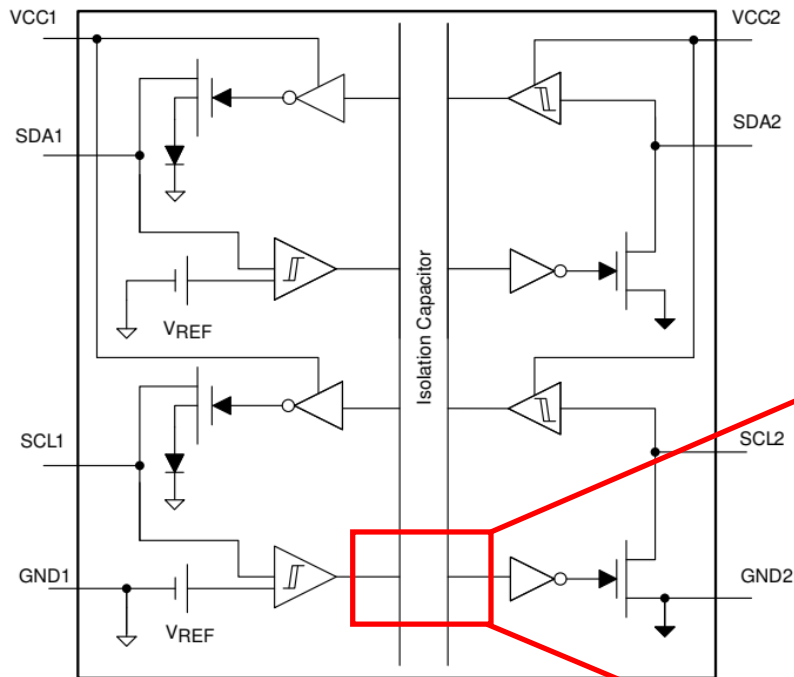



Figure 8-1. ISO1640 Block Diagram

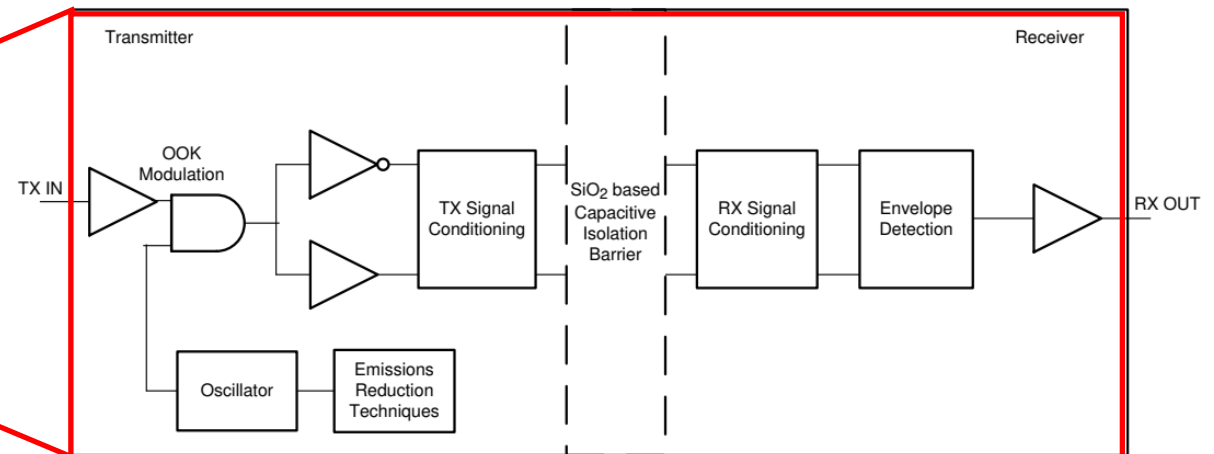

Example of isolated power supply

RECOM REM10 (10 W)
Medical compliant



Isolation voltage: 5 kV

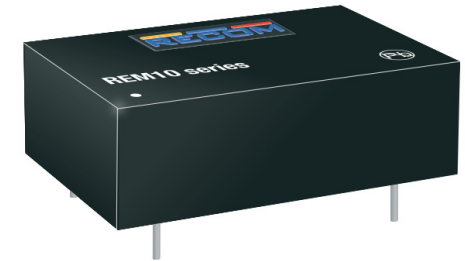

Pin Connections

Pin #	Single	Dual
1	CTRL*	CTRL*
2	-Vin	-Vin
11	NC	-Vout
14	+Vout	+Vout
16	-Vout	Com
22	+Vin	+Vin
23	+Vin	+Vin

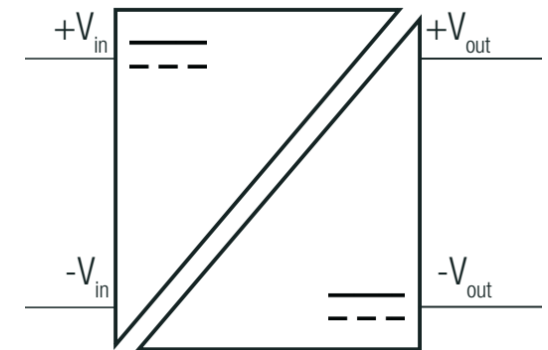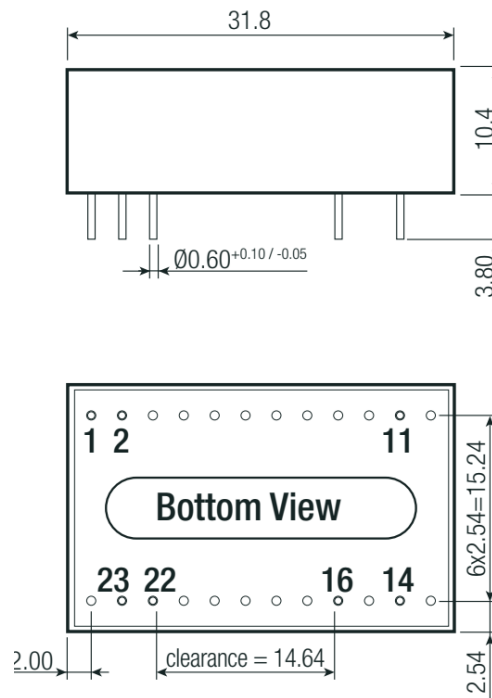* If the CTRL option is not chosen, Pin 1 will be absent



Simbolo

For standby mode