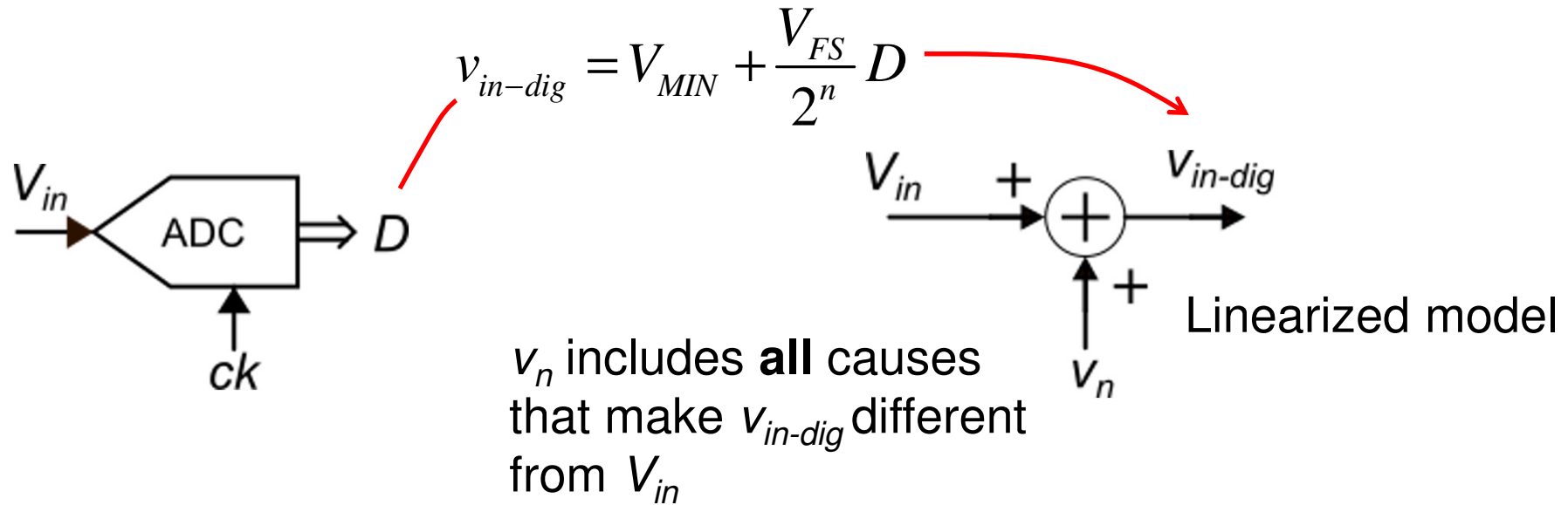



## ADC linearized model



The error due to quantization can be represented by a component of  $v_n$ : the quantization noise:


$$\langle v_{nq}^2 \rangle = \frac{\Delta^2}{12}$$
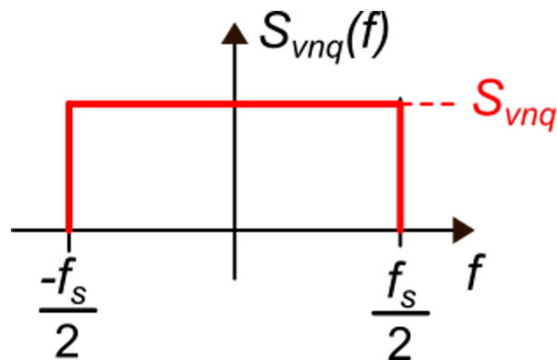
## Uniform quantization noise PSD: properties



Total  $v_{nq}$  power:  $\langle v_{nq}^2 \rangle = \frac{\Delta^2}{12}$        $S_{vnq} = \frac{\Delta^2}{12} \frac{1}{f_s}$

Increasing the sampling frequency:

 


$$S'_{vnq} = \frac{\Delta^2}{12} \frac{1}{f'_s} = \frac{\Delta^2}{12} \frac{1}{f'_s} \frac{f_s}{f_s} = S_{vnq} \frac{f_s}{f'_s}$$

For the same ADC, increasing the sampling frequency proportionally reduces the PSD of the quantization noise

# Oversampling ADCs

Nyquist  
rate sampling

 


$$f_s = 2B_s = \text{"Nyquist rate"}$$

$$\langle v_{nq-NR}^2 \rangle = \frac{\Delta^2}{12} = f_s \cdot S_{nq-NR} = 2B_s \cdot S_{nq-NR}$$

$$r_{OS} = \frac{f'_s}{2B_s} > 1$$

 $r_{OS} = \text{OSR}$   
OverSampling Ratio



Oversampling case

$$f'_s = r_{OS} \cdot 2B_s \quad S_{nq-OS} = S_{nq-NR} \frac{2B_s}{f'_s} = \frac{S_{nq-NR}}{r_{OS}}$$

$$\langle v_{nq-OS}^2 \rangle = 2B_s \cdot S_{nq-OS} = \frac{2B_s \cdot S_{nq-NR}}{r_{OS}} = \frac{1}{r_{OS}} \langle v_{nq-NR}^2 \rangle$$

# Resolution increment in a pure oversampling ADC

## Premise


Considering two ADCs with same  $V_{FS}$   $\left\{ \begin{array}{l} \text{ADC}_1: \text{SQNR}_1, n_1 \\ \text{ADC}_2: \text{SQNR}_2, n_2 \end{array} \right.$

$$\text{SQNR} = \frac{P_{MAX}}{\langle v_{nq}^2 \rangle} = \frac{3}{2} \cdot 2^{2n} \quad P_{MAX} = \frac{V_{FS}^2}{8} \Rightarrow P_{MAX1} = P_{MAX2}$$

$$\frac{\text{SQNR}_2}{\text{SQNR}_1} = \underline{2^{2(n_2 - n_1)}} = \frac{P_{MAX2}}{\langle v_{nq2}^2 \rangle} \frac{\langle v_{nq1}^2 \rangle}{P_{MAX1}} = \frac{\langle v_{nq1}^2 \rangle}{\langle v_{nq2}^2 \rangle}$$

$$n_2 - n_1 = \frac{1}{2} \log_2 \left( \frac{\langle v_{n1}^2 \rangle}{\langle v_{n2}^2 \rangle} \right)$$
 
# Resolution increment in a pure oversampling ADC



$$\langle v_{nq1}^2 \rangle = \langle v_{nq-NR}^2 \rangle$$

$$\langle v_{nq2}^2 \rangle = \langle v_{nq-OS}^2 \rangle = \frac{1}{r_{OS}} \langle v_{nq-NR}^2 \rangle$$

$$n_2 - n_1 = \frac{1}{2} \log_2 \left( \frac{\langle v_{n1}^2 \rangle}{\langle v_{n2}^2 \rangle} \right) = \frac{1}{2} \log_2 \left( \frac{\langle v_{nq-NR}^2 \rangle}{\langle v_{nq-OS}^2 \rangle} \right) = \frac{1}{2} \log_2 (r_{OS})$$


Resolution improvement

## Pure oversampling ADCs: limits


A minor limit:

The oversampling approach is based on the assumption that the quantization noise respects the uniform PSD model

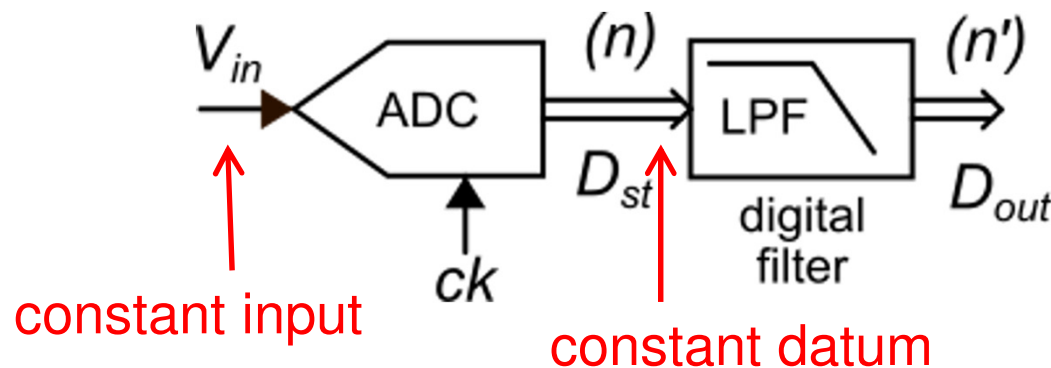If the input signal is a dc, the quantization noise superimposed on the data stream will be constant and then will be unaffected by the LPF. A similar problem occurs with signals that are slowly-varying and/or have a small magnitude.



## Signal dithering

 


Dithering


Dithering consists in adding noise to the signal.

The added noise must have spectral components out of the signal band so that it is rejected by the LPF

 Noise makes the ADC switch across the two adjacent levels closer to  $V_{in}$


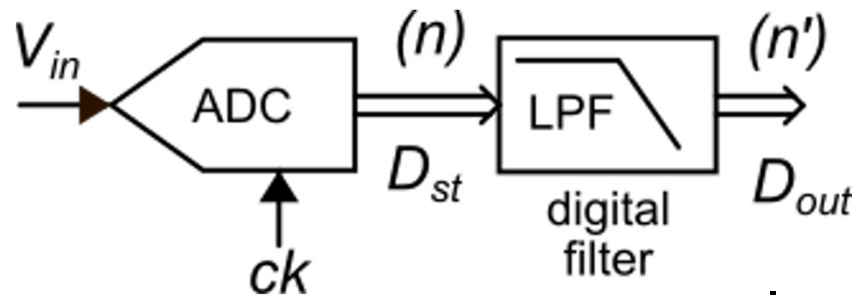
## The real limitation of the pure oversampling approach



$$n_{OS} - n_{NR} = \frac{1}{2} \log_2(r_{OS})$$

In order to obtain a resolution increment of a single bit, the sampling frequency must be incremented by a factor of 4

Example:

To obtain 16 bits of resolution from a 12 bit ADC:

$$n_{OS} - n_{NR} = 4 \text{ (bits)}$$

$$r_{OS} = \frac{f_s}{2B_s} = 4^4 = 256$$

The pure oversampling approach is highly inefficient !



# The Delta-Sigma ( $\Delta$ – $\Sigma$ ) ADC

The Delta-Sigma converter combines two principles:

- Oversampling:  $f_s \gg 2B_s$
- Noise shaping



It was introduced in 1960

The term "Sigma-Delta ( $\Sigma$ – $\Delta$ )" ADC is simply a synonym.

# Delta-Sigma principle


## Response to a DC voltage
 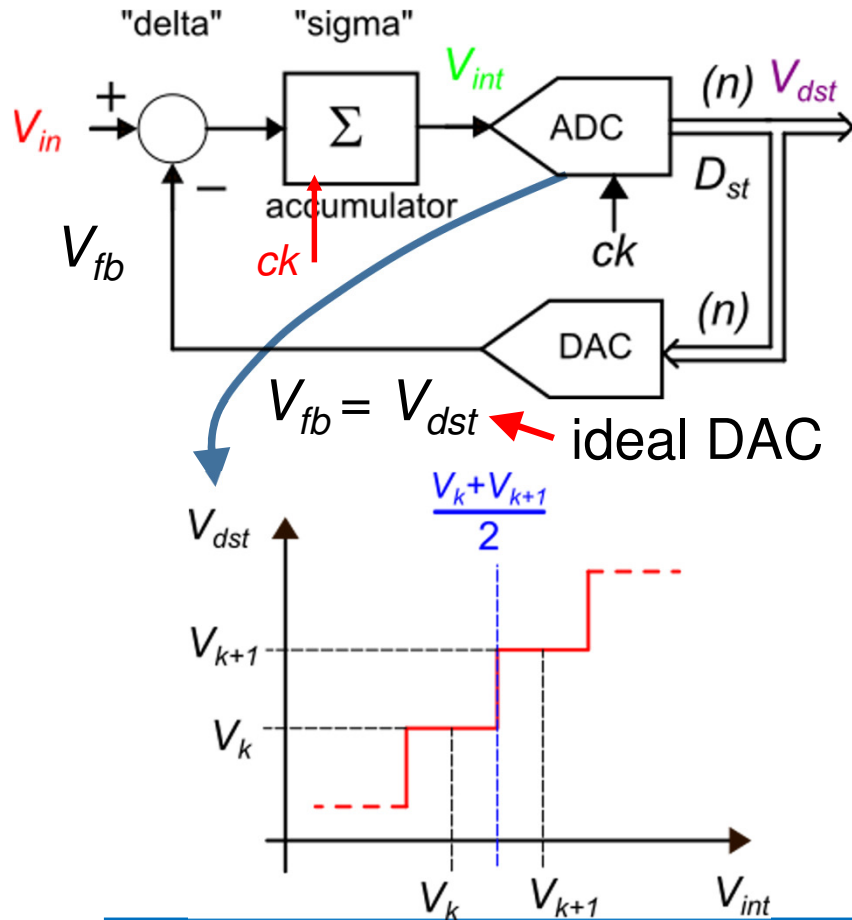
### The Delta-Sigma modulator (1st order)



## Delta-Sigma principle

### Response to a DC voltage

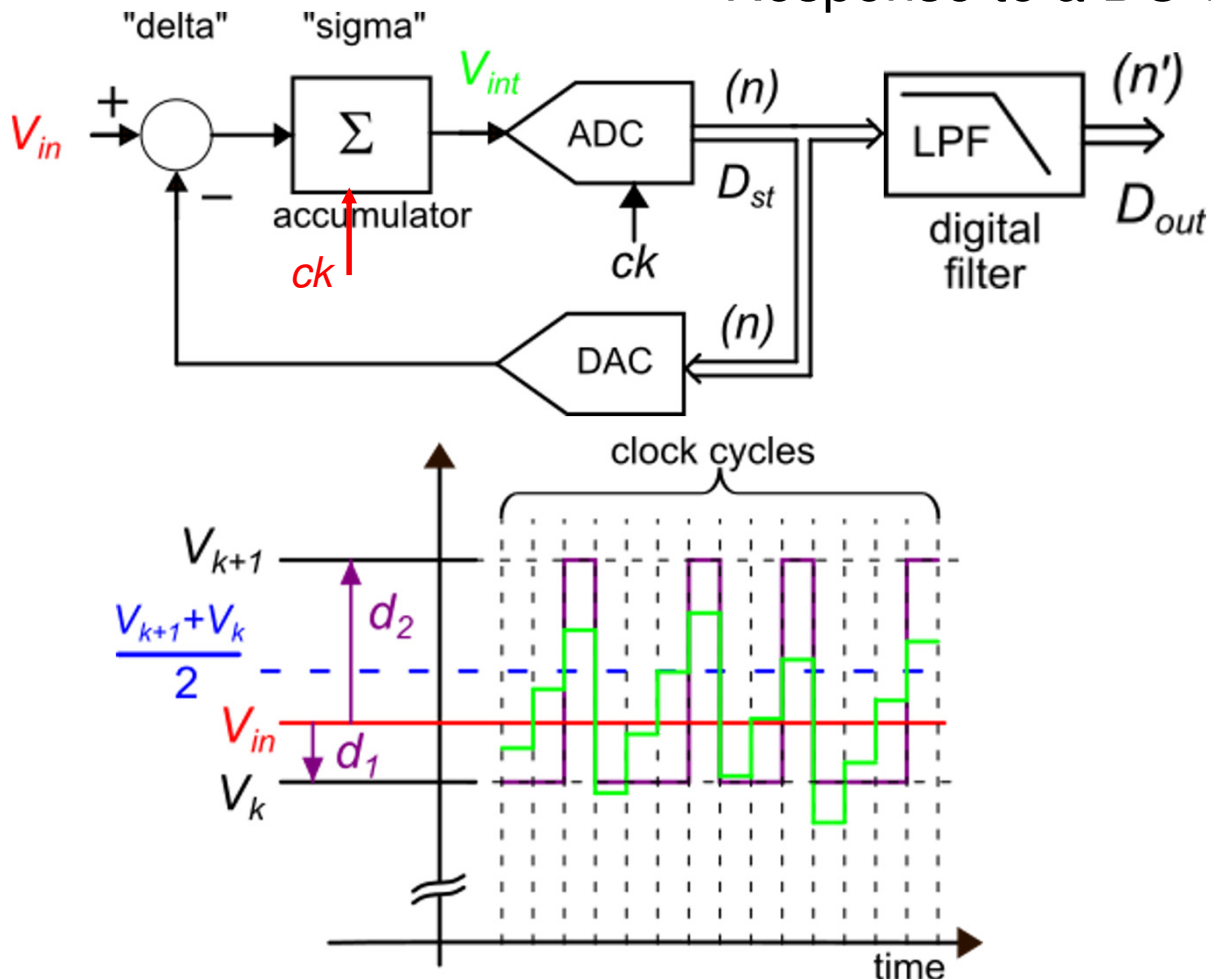


The digital filter averages the data stream that, in the example, contains only  $V_k$  and  $V_{k+1}$  levels.

The average will be a value between the two levels and will be closer to  $V_{in}$  than both  $V_k$  and  $V_{k+1}$

In this example, value  $V_k$  appears more frequently than  $V_{k+1}$ . Then the average will be closer to  $V_k$ , as actually  $V_{in}$  is.

## Delta-Sigma principle

### Response to a DC voltage

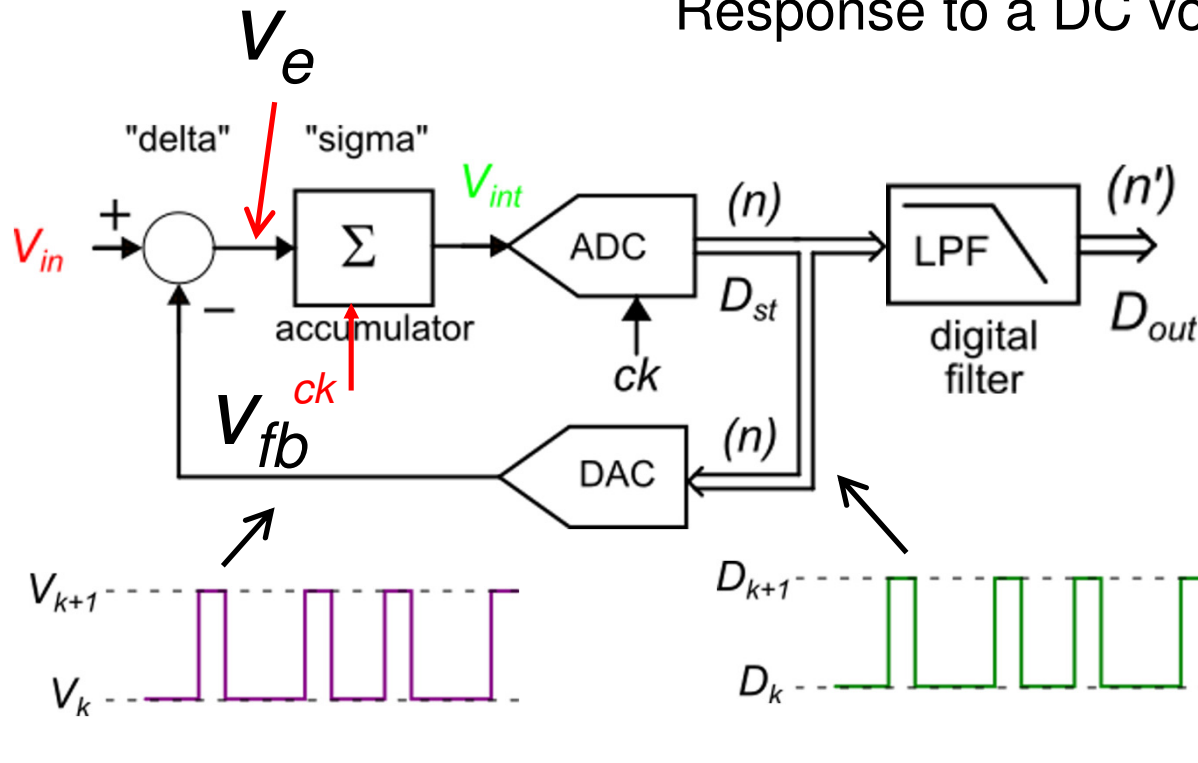

The average of  $V_e$ , performed over a very long time, must be zero, otherwise the output of the accumulator would diverge.

$$\langle V_e \rangle = \langle V_{in} - V_{fb} \rangle = 0$$

$$\langle V_{fb} \rangle = \langle V_{in} \rangle$$

If the LPF filter has a bandwidth small enough, it can extract the average of the data stream  $D_k$  with arbitrary accuracy. If the DAC is ideal (no distortion), then the average of  $D_k$  gives  $V_{in}$  with an arbitrary resolution.


## Delta-Sigma principle

What we have seen so far suggests that the delta-sigma modulator can produce a data stream that, once properly filtered, can yield  $V_{in}$  with a higher resolution than the original ADC.

Differently from the pure oversampling ADC, the delta-sigma is capable of producing the alternation of two adjacent codes ( $V_k, V_{k+1}$ ) even with a dc signal without dithering. In the case of an input dc signal, the constant error  $v_n$  is modulated (this is the origin of the name) and can be filtered out.

As in the oversampling approach, it is necessary to filter the output data stream, reducing the bandwidth to the minimum required by the signal spectrum. We will show that high resolution increments can be obtained with moderate oversampling ratios.

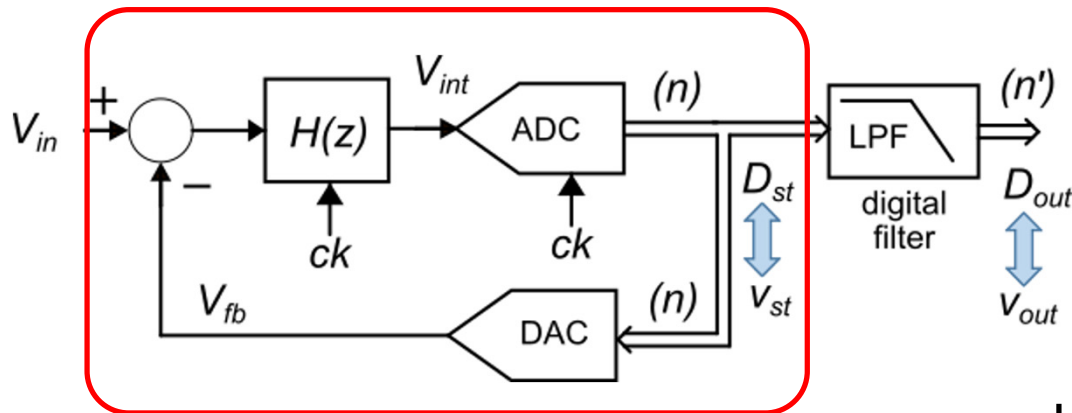
## Analysis of a first order delta-sigma modulator




$\Delta$ - $\Sigma$  modulator

$H(z)$  is a discrete time transfer function, properly represented with its z-transform.

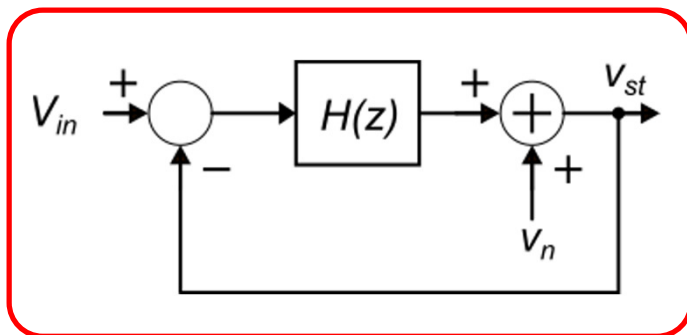Linearized model of the modulator. The DAC is considered ideal; thus, it simply translates the voltage representation of  $D_{st}$  ( $v_{st}$ ) in an exactly corresponding analog voltage ( $v_{fb}=v_{st}$ )


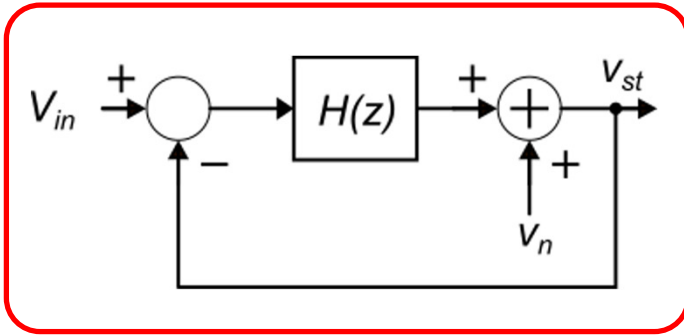
## Analysis of a first order delta-sigma modulator



$$v_{st} = (v_{in} - v_{st}) H(z) + v_n$$

$$v_{st} [1 + H(z)] = v_{in} H(z) + v_n$$


$$v_{st} = v_{in} \frac{H(z)}{1 + H(z)} + v_n \frac{1}{1 + H(z)}$$

$$v_{st} = v_{in} \cdot STF(z) + v_n \cdot NTF(z)$$

$$STF(z) = \text{Signal Transfer Function} = \frac{H(z)}{1 + H(z)}$$


$$NTF(z) = \text{Noise Transfer Function} = \frac{1}{1 + H(z)}$$
 
# Analysis of a first order delta-sigma modulator



$$v_{st} = v_{in} \cdot STF(z) + v_n \cdot NTF(z)$$
 
$$STF(z) = \frac{H(z)}{1 + H(z)} \quad NTF(z) = \frac{1}{1 + H(z)}$$



$$v_s(nT) = v_a(nT - T) + v_s(nT - T)$$

$$v_s(z) = v_a(z) z^{-1} + v_s(z) z^{-1}$$

$$v_s(z) = v_a(z) \frac{z^{-1}}{1 - z^{-1}}$$

$$H(z) = \frac{z^{-1}}{1 - z^{-1}}$$



## Analysis of a first order delta-sigma modulator

$$H(z) = \frac{z^{-1}}{1 - z^{-1}} = \frac{1}{z - 1} \quad (\text{forward Euler integrator})$$

$$STF(z) = \frac{H(z)}{1 + H(z)} = \frac{\frac{z^{-1}}{1 - z^{-1}}}{1 + \frac{z^{-1}}{1 - z^{-1}}} = \frac{\frac{z^{-1}}{1 - z^{-1}}}{\frac{1 - z^{-1} + z^{-1}}{1 - z^{-1}}} = \frac{z^{-1}}{1} = z^{-1}$$

A simple delay of one clock cycle

$$NTF(z) = \frac{1}{1 + H(z)} = \frac{1}{1 + \frac{z^{-1}}{1 - z^{-1}}} = \frac{1}{\frac{1 - z^{-1} + z^{-1}}{1 - z^{-1}}} = \frac{1}{1 - z^{-1}} = 1 - z^{-1}$$

This is the equivalent of the derivative in the DT domain

## NTF in the frequency domain

$$STF(z) = z^{-1}$$

$$NTF(z) = 1 - z^{-1} \quad z \Leftarrow e^{j\omega T} \quad \text{where: } T = \frac{1}{f_s}$$

$$NTF(j\omega) = 1 - e^{-j\omega T} = e^{-\frac{j\omega T}{2}} \left( e^{\frac{j\omega T}{2}} - e^{-\frac{j\omega T}{2}} \right)$$


$$NTF(j\omega) = e^{-\frac{j\omega T}{2}} \cdot 2j \sin\left(\frac{\omega T}{2}\right) \quad \omega = 2\pi f$$

$$NTF(j\omega) = e^{-j\pi f T} \cdot 2j \sin(\pi f T)$$

 
## Output spectral density of the quantization noise

The uniform PSD model of the quantization noise is acceptable because the modulator continuously changes the input of the original ADC, sweeping across the whole range  $[-\Delta/2, +\Delta/2]$  of the quantization noise.

For more accurate analysis of second order effects, the limits of the uniform PSD model should be taken into account.


 
# Quantization noise PSD at the output of the $\Delta$ - $\Sigma$ modulator




$$NTF(j\omega) = e^{-j\pi fT} \cdot 2j \sin(\pi fT)$$


$$S_{n-DS}(f) = S_{n-OS} |NTF(f)|^2$$

$$\text{Recall: } T = \frac{1}{f_s}$$


 
$$S_{n-DS}(f) = S_{n-OS} \cdot 4 \sin^2 \left( \pi \frac{f}{f_s} \right)$$


 
## Quantization noise PSD at the output of the $\Delta$ - $\Sigma$ modulator


 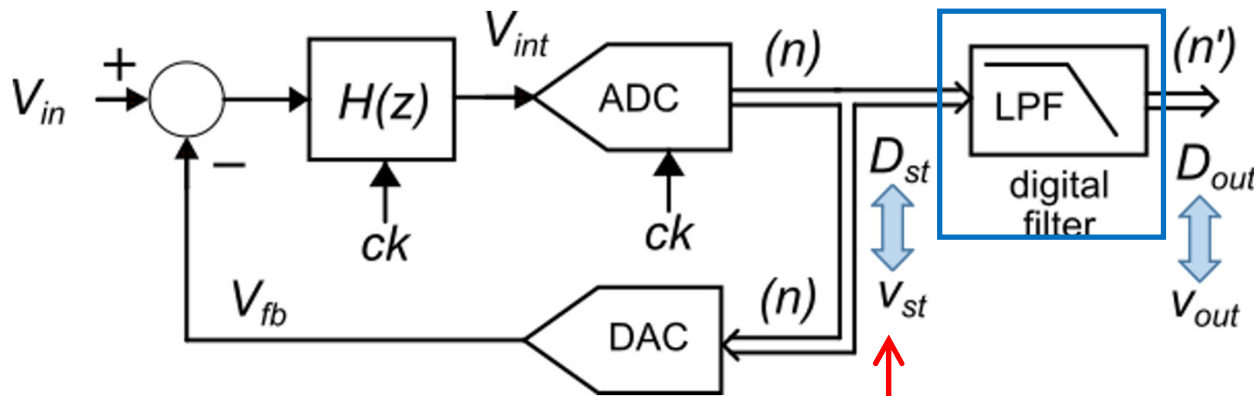
# Output noise power in the Delta-Sigma ADC



$$S_{n-DS}(f) = S_{n-OS} \cdot 4 \sin^2 \left( \pi \frac{f}{f_s} \right)$$

$$\langle v_{n-out}^2 \rangle = \int_{-B_s}^{B_s} S_{n-DS}(f) df$$

$$\langle v_{n-out}^2 \rangle = S_{n-OS} \int_{-B_s}^{B_s} 4 \sin^2 \left( \pi \frac{f}{f_s} \right) df$$

$$\sin \left( \pi \frac{f}{f_s} \right) \cong \pi \frac{f}{f_s} \quad f \ll f_s$$

$$\langle v_{n-out}^2 \rangle \cong S_{n-OS} \int_{-B_s}^{B_s} 4 \left( \pi \frac{f}{f_s} \right)^2 df$$

## Output noise power in the Delta-Sigma ADC

$$\langle v_{n-out}^2 \rangle \cong S_{n-OS} \int_{-B_S}^{B_S} 4 \left( \pi \frac{f}{f_S} \right)^2 df = S_{n-OS} 4\pi^2 \frac{1}{f_S^2} \int_{-B_S}^{B_S} f^2 df = S_{n-OS} \frac{4\pi^2}{f_S^2} \left[ \frac{f^3}{3} \right]_{-B_S}^{B_S}$$

$$\langle v_{n-out}^2 \rangle \cong \underline{S_{n-OS}} 4\pi^2 \frac{1}{f_S^2} \frac{2}{3} B_S^3 \quad \underline{S_{n-OS}} = \frac{S_{n-NR}}{r_{OS}} \quad \left( r_{OS} = \frac{f_S}{2B_S} \right)$$


$$\langle v_{n-out}^2 \rangle \cong \frac{S_{n-NR}}{r_{OS}} \underbrace{4\pi^2 \frac{1}{f_S^2} \frac{2}{3} B_S^3}_{8B_S^3 = 2B_S \cdot (2B_S)^2}$$

$$\langle v_{n-out}^2 \rangle \cong \frac{\boxed{S_{n-NR} \cdot 2B_S}}{r_{OS}} \frac{\pi^2}{3} \left( \boxed{\frac{2B_S}{f_S}} \right)^2 \cdot \frac{1}{r_{OS}^2}$$

$\langle v_{nq-NR}^2 \rangle$

$$\langle v_{n-out}^2 \rangle \cong \langle v_{nq-NR}^2 \rangle \frac{\pi^2}{3} \frac{1}{r_{OS}^3}$$
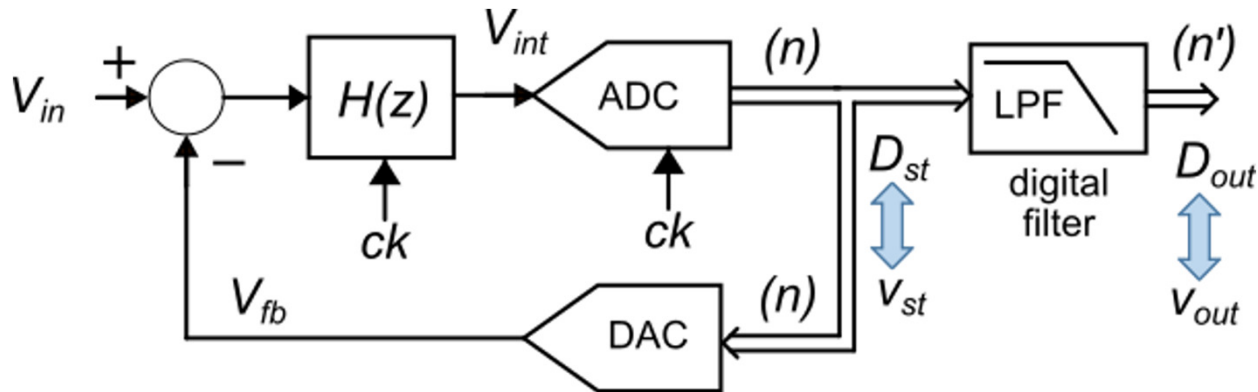
## Resolution increment in the first-order $\Delta$ - $\Sigma$ ADC



$$n_2 - n_1 = \frac{1}{2} \log_2 \left( \frac{\langle v_{n1}^2 \rangle}{\langle v_{n2}^2 \rangle} \right)$$

$$\left( \frac{\langle v_{n1}^2 \rangle}{\langle v_{n2}^2 \rangle} \right) = \frac{\langle v_{nq-NR}^2 \rangle}{\langle v_{nq-NR}^2 \rangle \frac{\pi^2}{3} \frac{1}{r_{OS}^3}} = r_{OS}^3 \frac{3}{\pi^2}$$

$$n' - n = \frac{1}{2} \log_2 \left( r_{OS}^3 \frac{3}{\pi^2} \right)$$

$$n' - n = \frac{3}{2} \log_2 (r_{OS}) - 0.86$$

$$\frac{1}{2} \log_2 \left( \frac{3}{\pi^2} \right)$$




## Resolution increment in the first order $\Delta$ - $\Sigma$ ADC

$$n' - n = \frac{3}{2} \log_2 (r_{OS}) - 0.86$$


Every increment of  $r_{OS}$  by a factor of 2 produces a resolution gain of 1.5 bits.

This gain was only 1/2 bit in the pure oversampling ADC
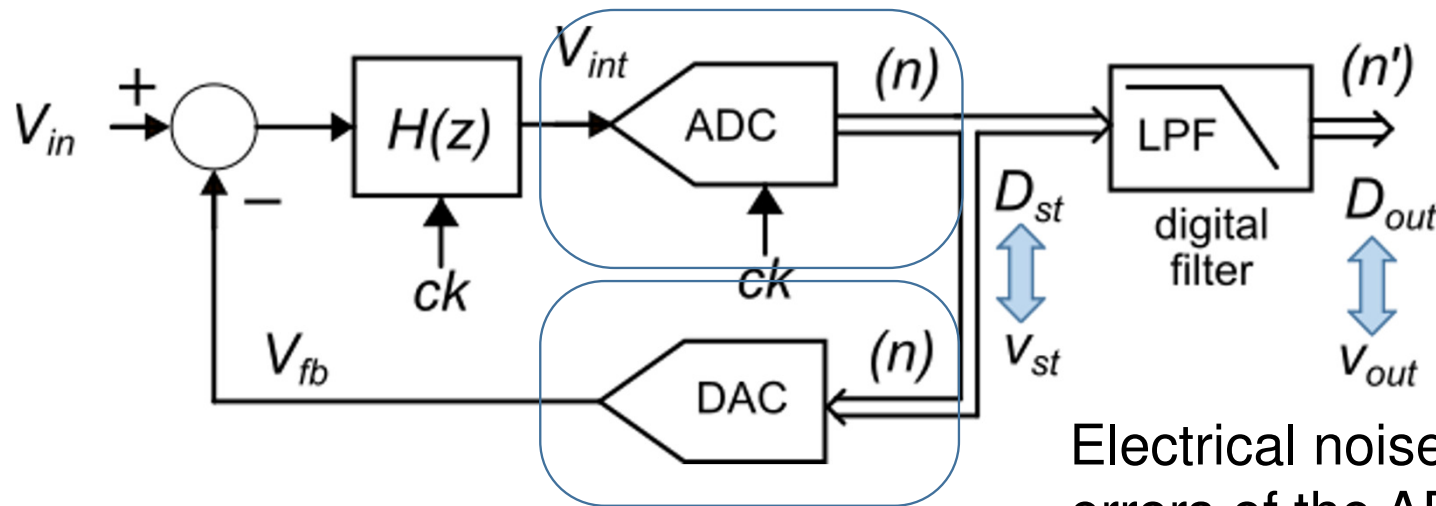
## ADC and DAC non idealities in $\Delta$ - $\Sigma$ ADC



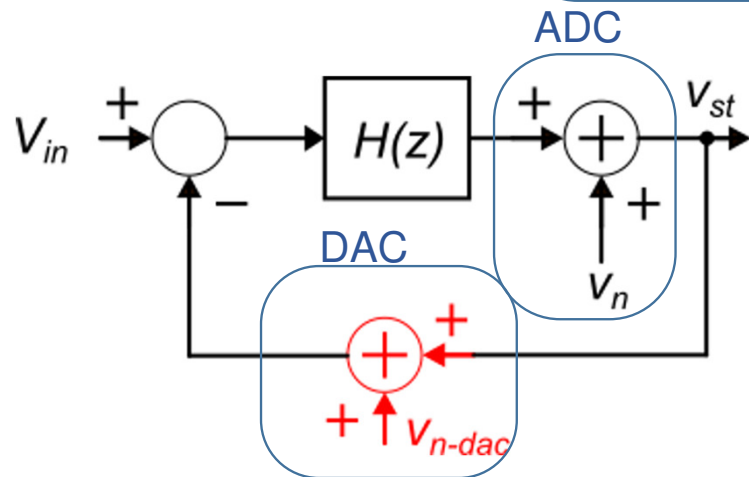Electrical noise, offset and non-linearity errors of the ADC are shaped by the high pass NTF of the modulator, then the effect on the signal BW is negligible.




The **DAC** should be linear because it is in the feedback path. The DAC noise (that includes also non-linearity errors) are simply summed-up to the input signal.

## Single-bit $\Delta$ - $\Sigma$ ADC


As we have seen, the DAC linearity is a main issue of the  $\Delta$ - $\Sigma$  approach

A very elegant and widely used solution is the single bit  $\Delta$ - $\Sigma$  ADC

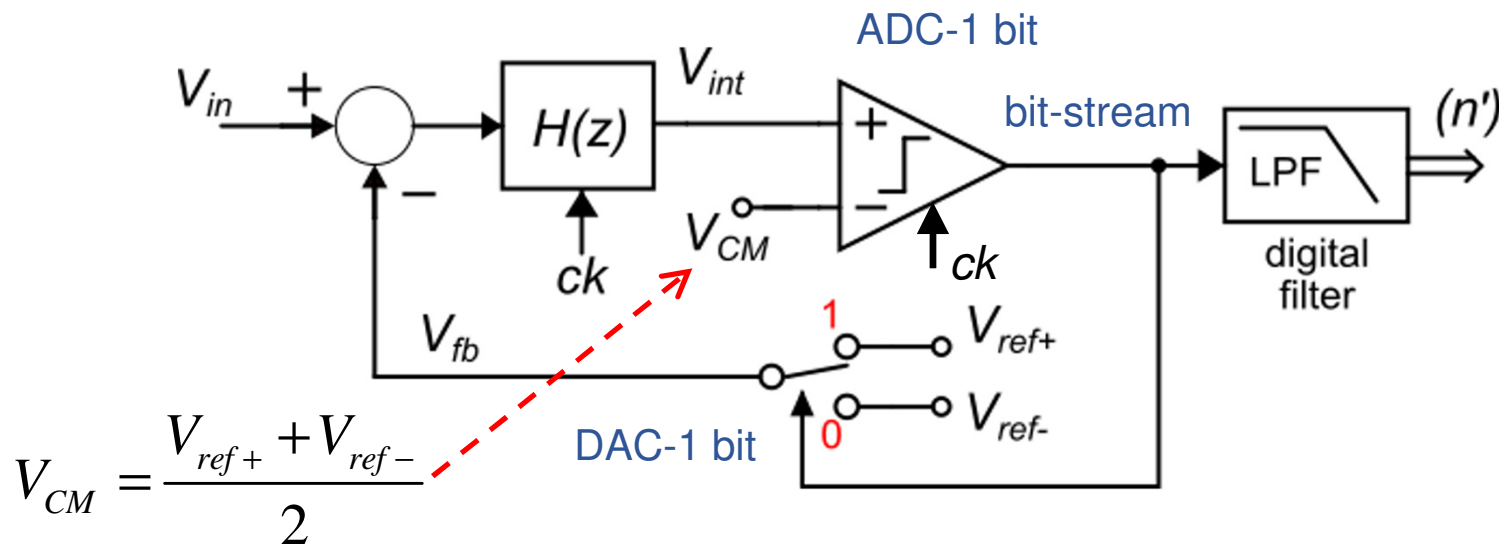In the single bit D-S ADC the internal Nyquist-rate ADC is a single bit quantizer, i.e., a comparator



# Single-bit $\Delta$ - $\Sigma$ ADC

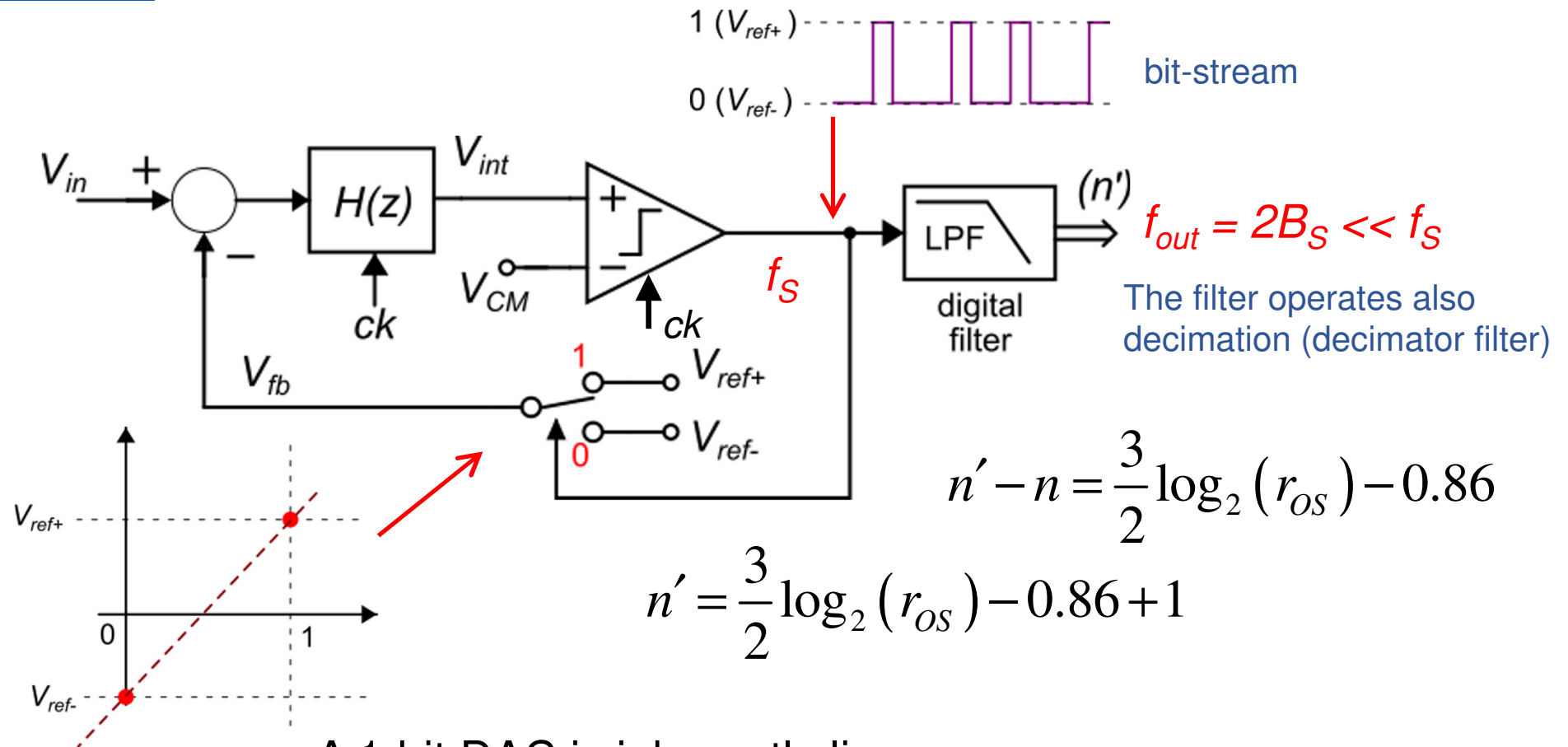

A 1-bit DAC is inherently linear

## Example of DS ADC with 1-bit quantizer


$$n' = \frac{3}{2} \log_2(r_{OS}) - 0.86 + 1$$

$$r_{OS} = \text{OSR} = 128$$

$$n' = \frac{3}{2} \times 7 - 0.86 + 1 = 10.8 \text{ bits}$$

 
## H(z) implementation (Single ended)

Classical, "parasitic insensitive" Switched Capacitor Integrator




Note: electrical noise and distortion of the DT integrator are not shaped by the NTF: careful design of the integrator is required.
 
$$V_{int}^{(2)} = V_{int}^{(1)} + \frac{C_1}{C_2} (V_{in}^{(1)} - V_{fb}^{(2-p)})$$



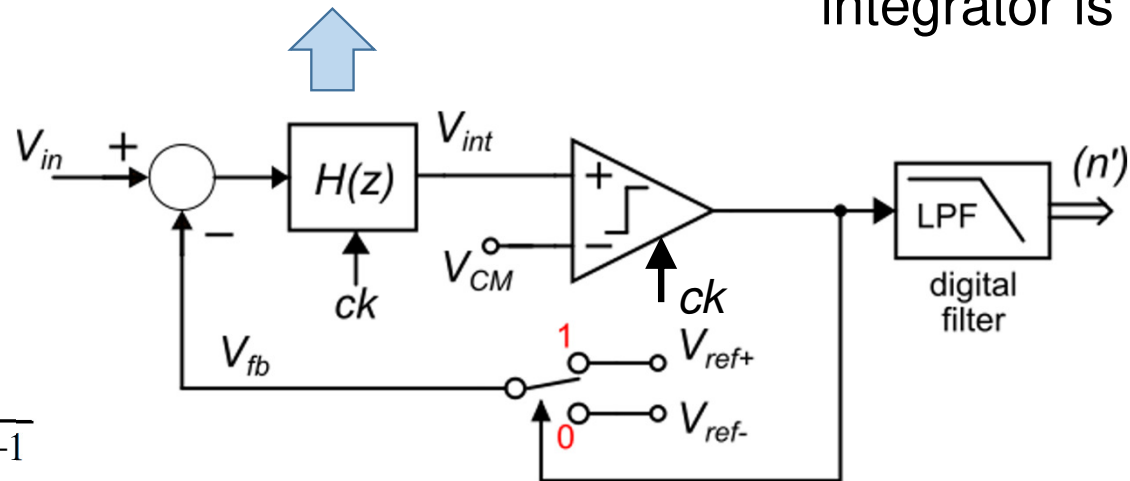
$$H(z) = \frac{C_1}{C_2} \frac{z^{-1}}{1 - z^{-1}}$$



## Higher order $\Delta$ - $\Sigma$ ADCs

$$n' - n \approx \frac{5}{2} \log_2(r_{os})$$

Example: second-order ADC

 

Advantage: 2.5 bits are gained doubling the OSR (instead of 1.5 bits).  
Same final resolution with a much smaller OSR  
The 2nd order D-S ADC is a very popular converter for sensor interfaces.