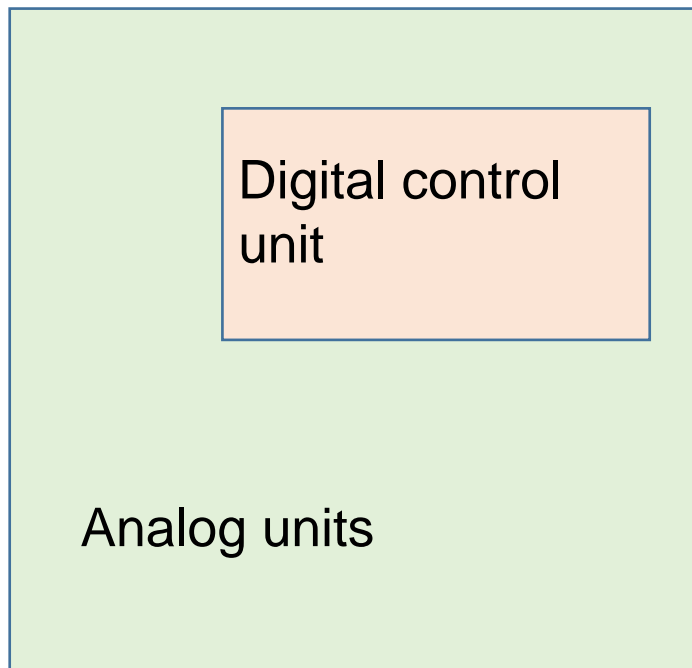


Mixed-Signal Design Flow and Example of SAR ADC Design


Dr. Alessandro Catania and Dr. Michele Dei

Mixed Signal Design Flow

Traditional mixed circuit system
(e.g. interface for a MEMS sensor)




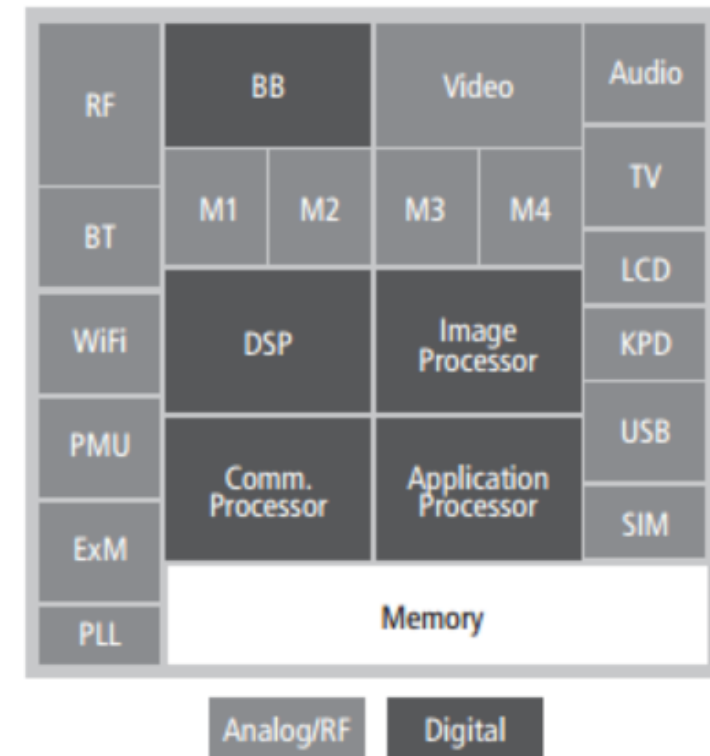System on a chip with distribution
of analog and digital units




Both are examples of Mixed Signal integrated circuits

Possible design flows

 


- **Analog centric (or analog on top):** the analog and digital units are designed with their proper tools and integration is performed using the analog tool.
- **Digital centric (or digital on top):** the analog and digital units are designed with their proper tools and integration is performed using the (highly automated) digital tool.

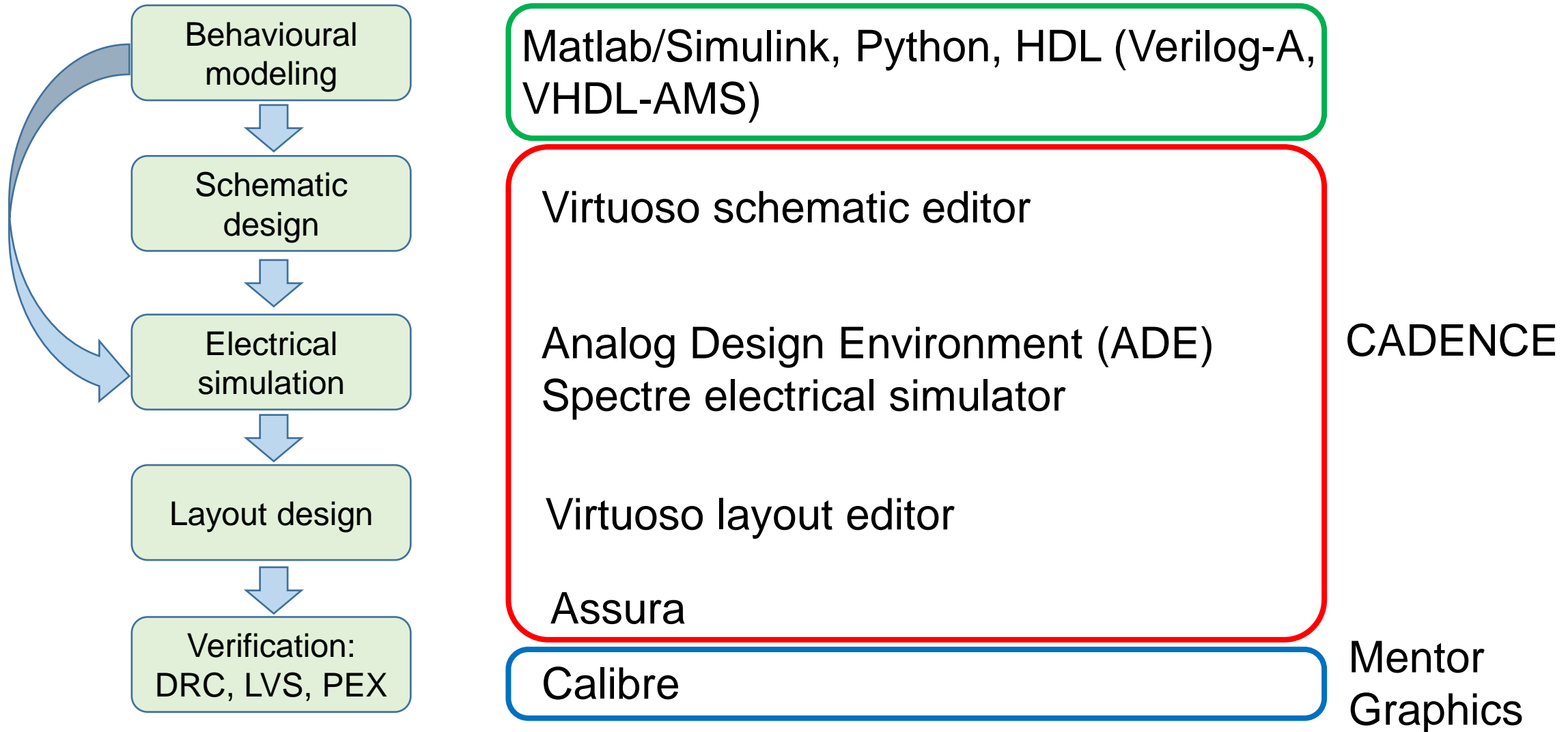Analog Design Flow and examples of CAD tools




PEX: Parasitic extraction (for post-layout simulations)

Digital Design Flow and CADENCE tools

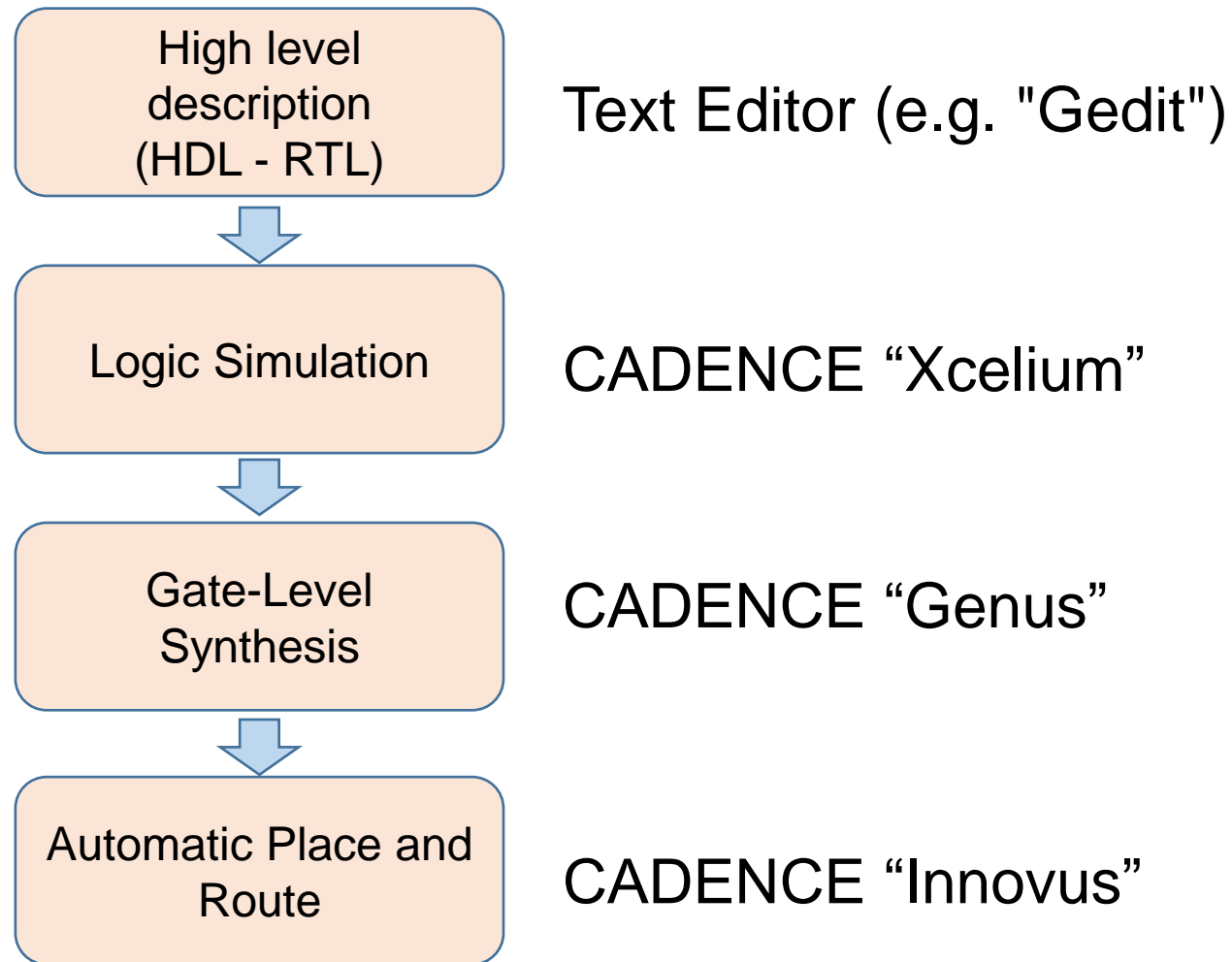


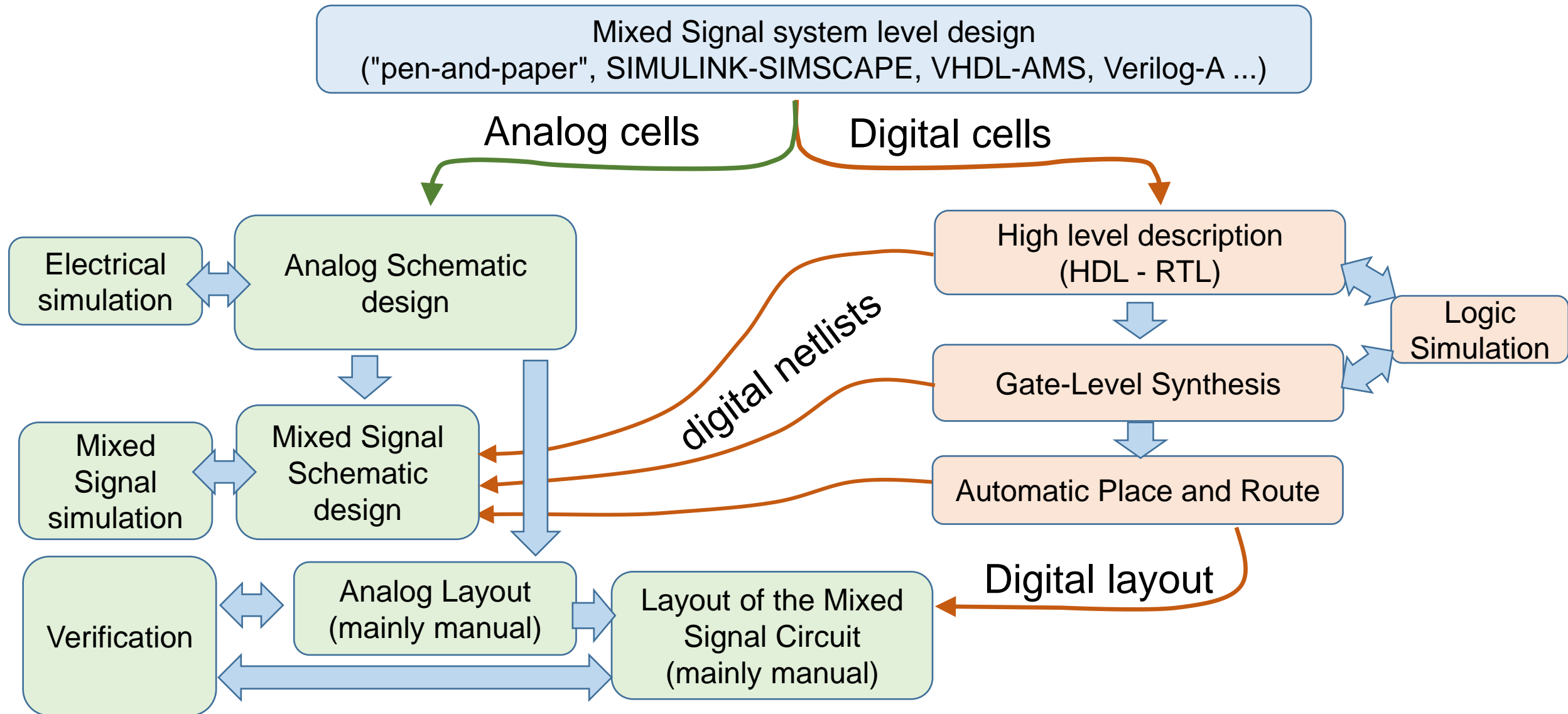Mixed Signal Design Flow: Analog Centric Approach





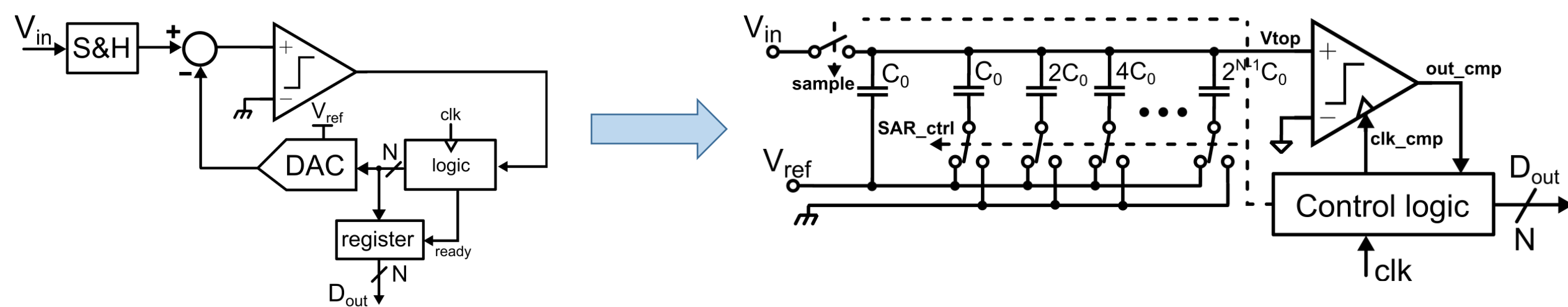Example: Design of an SAR ADC



- High-level behavioural description of the SAR algorithm (e.g. MATLAB, python)
- Transistor-level design and simulations of the comparator and the DAC
- HDL description and digital simulations of the SAR control logic
- Mixed-signal simulations of the whole ADC
- Layout of the analog blocks / synthesis and place-and-route of the SAR logic



 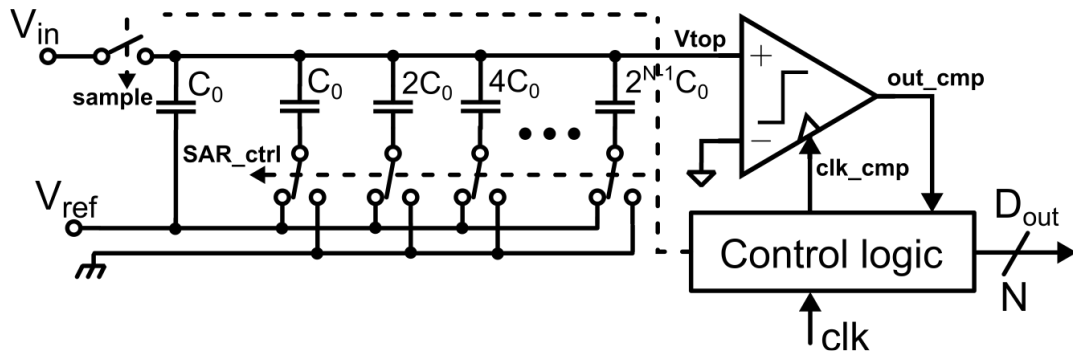Successive Approximation Register ADC (6 bit)


  
$$\begin{aligned}
 V_{top} &= V_{in} \quad \Rightarrow \quad \Delta V_{top} = \Delta V \frac{2^{N-1}C_0}{C_{tot}} \\
 &= -V_{ref} \frac{2^{N-1}C_0}{2^N C_0} \\
 &= -\frac{V_{ref}}{2}
 \end{aligned}$$



$$\begin{cases}
 V_{in} = 82.7 \text{ mV} \\
 V_{ref} = 500 \text{ mV}
 \end{cases}$$

Clock cycle

A/D (N = 6)

$D_{out} = 001010$
(10 in decimale)


Behavioural description of the SAR algorithm

SAR algorithm:



- Signal sampling
- SAR conversion (N phases)

SAR phase:

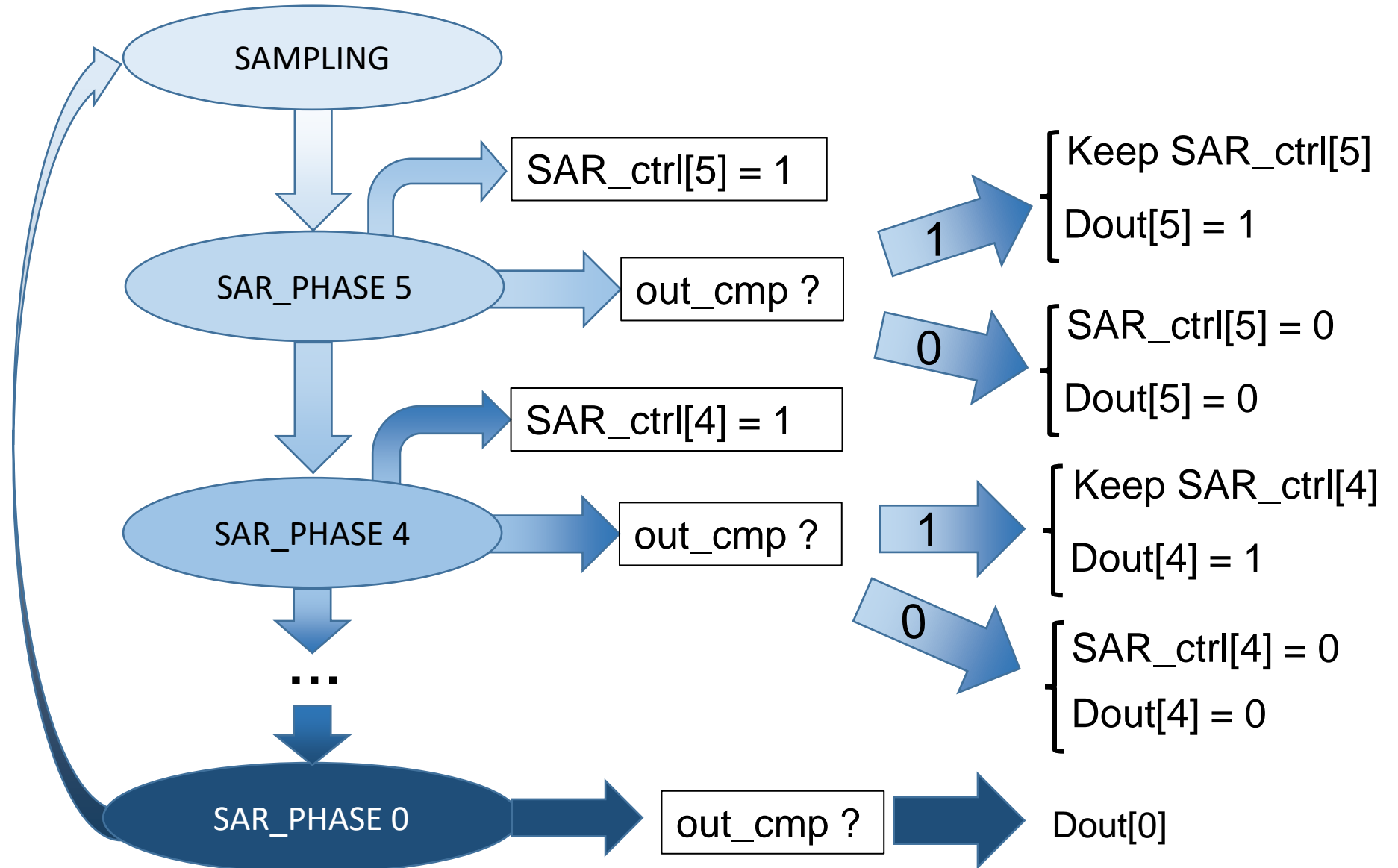1. DAC update (initial guess)
2. Verify the comparator output
3. DAC correction (if needed)



 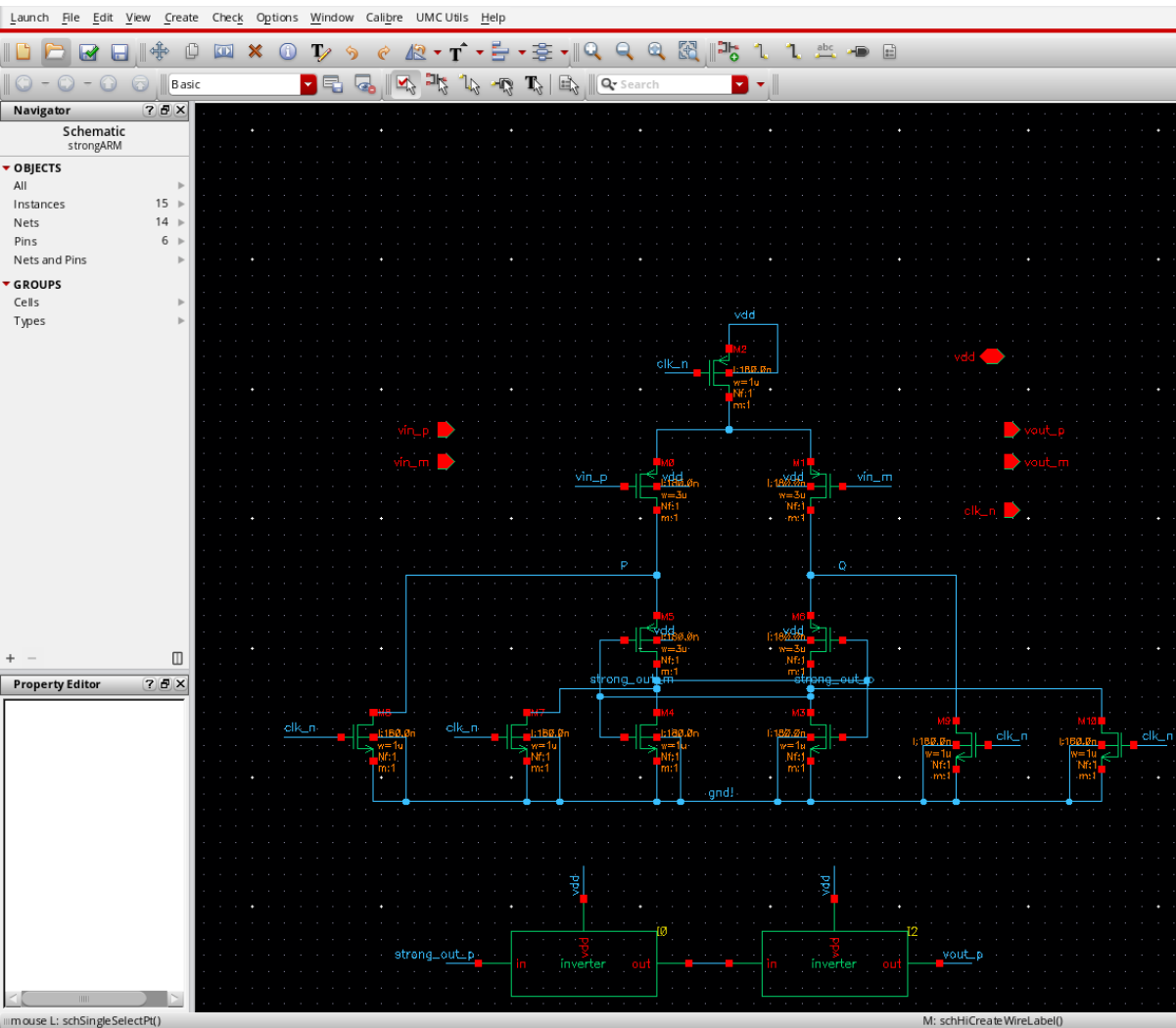Analog Design and Simulations (Spectre simulator)



VHDL description of the SAR digital control block

VHDL Code


```
Open SAR_ctrl_block.vhd Save
Library IEEE;
use IEEE.numeric_std.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.std_logic_1164.all;

entity SAR_ctrl_block is
  port(
    clk_in: in std_logic;
    cmp_out: in std_logic;
    reset_n: in std_logic;
    sample: out std_logic;
    clk_cmp: out std_logic;
    SAR_ctrl: out std_logic_vector (5 downto 0);
    output_word: out std_logic_vector (5 downto 0)
  );
end SAR_ctrl_block;


architecture fsm of SAR_ctrl_block is
  type T_STATE is (RESET, SAMPLING, SAR_PHASE_5, SAR_PHASE_4, SAR_PHASE_3, SAR_PHASE_2, SAR_PHASE_1, SAR_PHASE_0, FINISH);
  signal state: T_STATE := RESET;
  signal aux_word: std_logic_vector (5 downto 0) := (others => '0');
  signal SAR_ctrl_1: std_logic_vector (5 downto 0) := (others => '1');
  signal SAR_ctrl_2: std_logic_vector (5 downto 0) := (others => '1');
  signal aux_clk: std_logic := '0';
  signal clk_aux: std_logic := '0';
begin
  SAR_ctrl_1 <= SAR_ctrl_1 and SAR_ctrl_2;
  clk_aux <= clk_in and aux_clk;
  clk_cmp <= inertial clk_aux after 1ns;

  process (clk_in, reset_n)
  begin
    if (reset_n='0') then
      sample <= '0';
      SAR_ctrl_1 <= (others => '0');
      state <= RESET;
      aux_clk <= '0';
    elsif rising_edge(clk_in) then
      case state is
        when RESET =>
          sample <= '0';
          SAR_ctrl_1 <= (others => '0');
          state <= SAMPLING;
          aux_clk <= '0';
        when SAMPLING =>
          sample <= '1';
          SAR_ctrl_1 <= (others => '0');
          aux_clk <= '1';
          state <= SAR_PHASE_5;
      end case;
    end if;
  end process;
end fsm;
```

Digital simulations (XCELIUM)

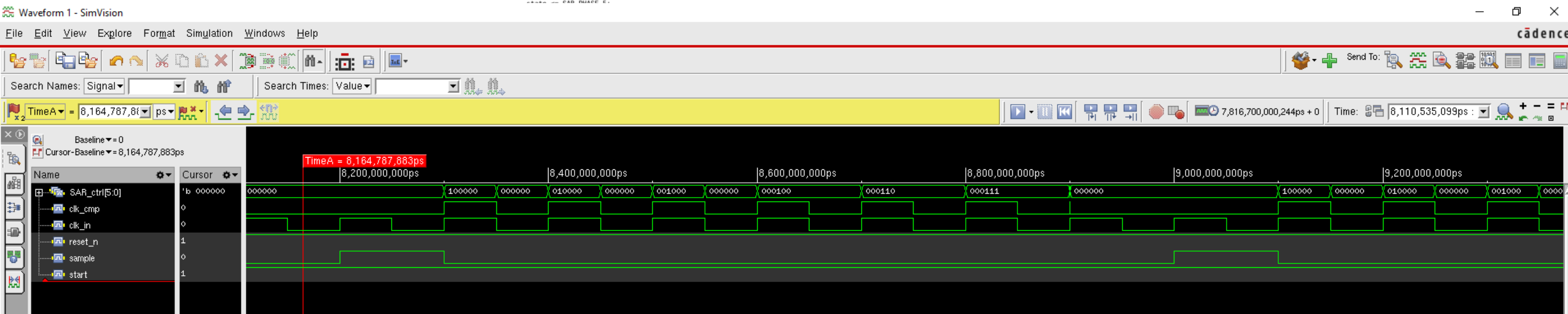

Digital synthesis (GENUS)

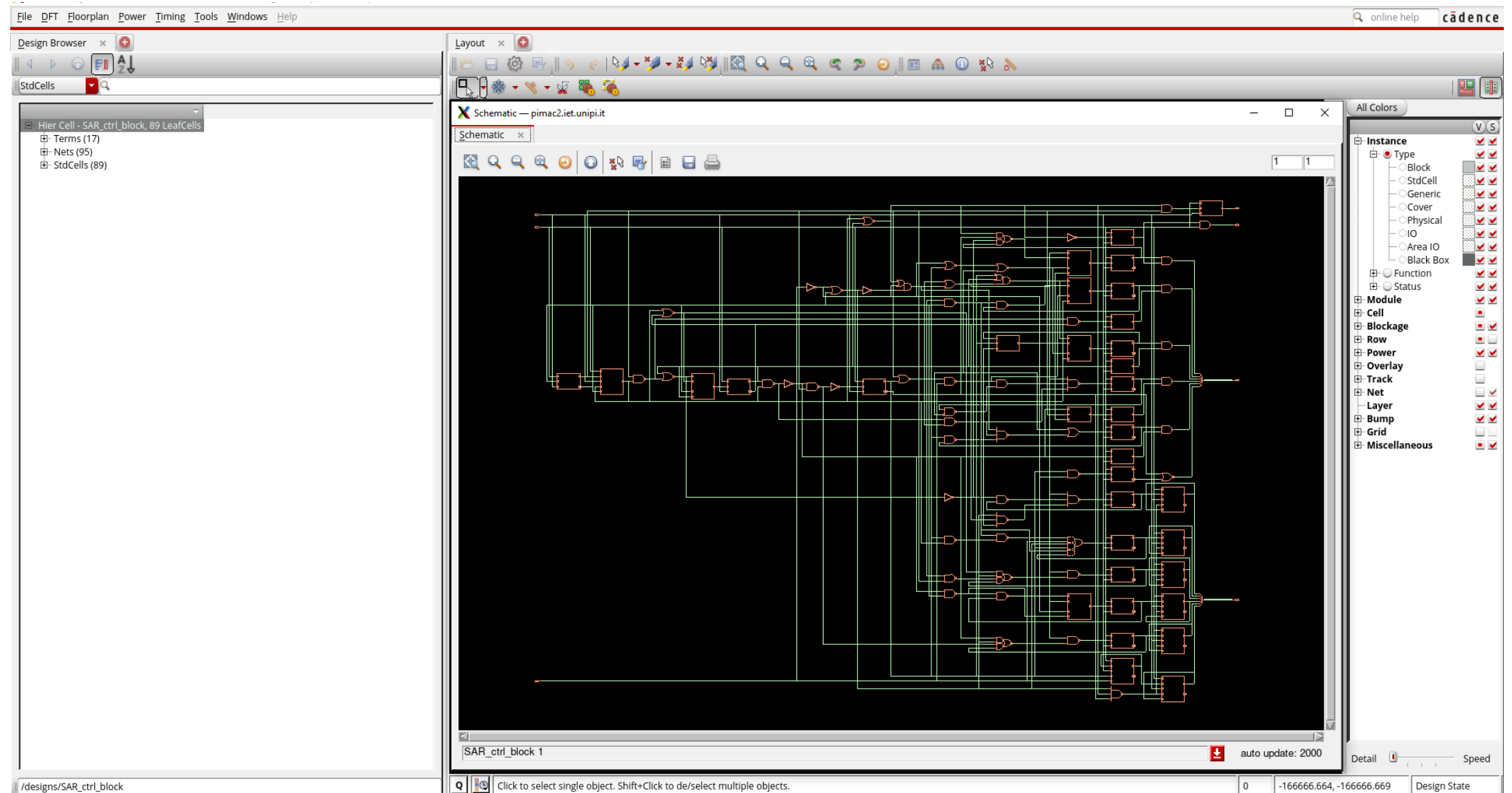

Digital synthesis (GENUS)

RTL (Register Transfer Level) Description (GENUS input)

```
library IEEE;
use IEEE.numeric_std.all;
use IEEE.STD_LOGIC_UNSIGNED.all;
use IEEE.std_logic_1164.all;

entity SAR_ctrl_block is
    port(
        clk_in: in std_logic;
        cmp_out: in std_logic;
        reset_n: in std_logic;
        sample: out std_logic;
        clk_cmp: out std_logic;
        SAR_ctrl: out std_logic_vector (5 downto 0);
        output_word: out std_logic_vector (5 downto 0)
    );
end SAR_ctrl_block;

architecture fsm of SAR_ctrl_block is

    type T_STATE is (RESET, SAMPLING, SAR_PHASE_5, SAR_PHASE_4, SAR_PHASE_3, SAR_PHASE_2, SAR_PHASE_1, SAR_PHASE_0, FINISH);
    signal state: T_STATE := RESET;
    signal aux_word: std_logic_vector (5 downto 0) := (others => '0');
    signal SAR_ctrl_1: std_logic_vector (5 downto 0) := (others => '1');
    signal SAR_ctrl_2: std_logic_vector (5 downto 0) := (others => '1');
    signal aux_clk: std_logic := '0';
    signal clk_aux: std_logic := '0';
begin

    SAR_ctrl <= SAR_ctrl_1 and SAR_ctrl_2;
    clk_aux <= clk_in and aux_clk;
    clk_cmp <= inertial clk_aux after 1ns;


    process (clk_in, reset_n)
    begin
        if (reset_n='0') then
            sample <= '0';
            SAR_ctrl_1 <= (others => '0');
            state <= RESET;
            aux_clk <= '0';
        elsif rising_edge(clk_in) then
            case state is
                when RESET =>
                    sample <= '0';
                    SAR_ctrl_1 <= (others => '0');
                    state <= SAMPLING;
                    aux_clk <= '0';
                when SAMPLING =>
                    sample <= '1';
                    SAR_ctrl_1 <= (others => '0');
                    state <= SAR_PHASE_5;
            end case;
        end if;
    end process;
end architecture;
```



Gate Level Description (GENUS output)


```
module SAR_ctrl_block(clk_in, cmp_out, reset_n, sample, clk_cmp,
    SAR_ctrl, output_word);
    input clk_in, cmp_out, reset_n;
    output sample, clk_cmp;
    output [5:0] SAR_ctrl, output_word;
    wire clk_in, cmp_out, reset_n;
    wire sample, clk_cmp;
    wire [5:0] SAR_ctrl, output_word;
    wire [5:0] SAR_ctrl_2;
    wire [5:0] aux_word;
    wire [3:0] state;
    wire [5:0] SAR_ctrl_1;
    wire UNCONNECTED, UNCONNECTED0, UNCONNECTED1, UNCONNECTED2,
        UNCONNECTED3, UNCONNECTED4, UNCONNECTED5, UNCONNECTED6;
    wire UNCONNECTED7, UNCONNECTED8, UNCONNECTED9, UNCONNECTED10,
        UNCONNECTED11, UNCONNECTED12, UNCONNECTED13, UNCONNECTED14;
    wire UNCONNECTED15, UNCONNECTED16, n_0, n_1, n_2, n_3, n_5, n_6;
    wire n_7, n_8, n_9, n_10, n_11, n_12, n_13, n_14;
    wire n_15, n_16, n_18, n_19, n_20, n_21, n_23, n_24;
    wire n_27, n_29, n_31, n_32, n_33, n_34, n_35, n_36;
    wire n_37, n_38, n_39, n_40, n_41, n_42, n_43, n_44;
    wire n_45, n_46, n_47, n_48, n_50, n_51, n_52, n_53;
    wire n_55, n_56, n_57, n_58, n_59, n_60, n_61, n_62;
    wire n_63, n_64, n_68;
    DBFRBN \SAR_ctrl_2_reg[2] (.RB (reset_n), .CKB (clk_in), .D (n_64),
        .Q (SAR_ctrl_2[2]), .QB (UNCONNECTED));
    DBFRBN \SAR_ctrl_2_reg[4] (.RB (reset_n), .CKB (clk_in), .D (n_62),
        .Q (SAR_ctrl_2[4]), .QB (UNCONNECTED0));
    DBFRBN \SAR_ctrl_2_reg[3] (.RB (reset_n), .CKB (clk_in), .D (n_60),
        .Q (SAR_ctrl_2[3]), .QB (UNCONNECTED1));
    DBFRBN \aux_word_reg[4] (.RB (reset_n), .CKB (clk_in), .D (n_58), .Q
        (aux_word[4]), .QB (UNCONNECTED2));
    DBFRBN \SAR_ctrl_2_reg[1] (.RB (reset_n), .CKB (clk_in), .D (n_63),
        .Q (SAR_ctrl_2[1]), .QB (UNCONNECTED3));
    ND3S g1595_2398(.I1 (n_56), .I2 (n_51), .I3 (n_52), .O (n_64));
    DBFRBN \SAR_ctrl_2_reg[5] (.RB (reset_n), .CKB (clk_in), .D (n_57),
        .Q (SAR_ctrl_2[5]), .QB (UNCONNECTED4));
    OR2S g1601_5107(.I1 (n_42), .I2 (n_53), .O (n_63));
    OAI112HS g1590_6260(.A1 (n_59), .B1 (n_21), .C1 (n_50), .C2
        (state[1]), .O (n_62));
    DBZRBN \output_word_reg[1] (.RB (reset_n), .CKB (clk_in), .D
        (aux_word[1]), .TD (output_word[1]), .SEL (n_61), .Q
        (output_word[1]), .QB (UNCONNECTED5));
end module;
```

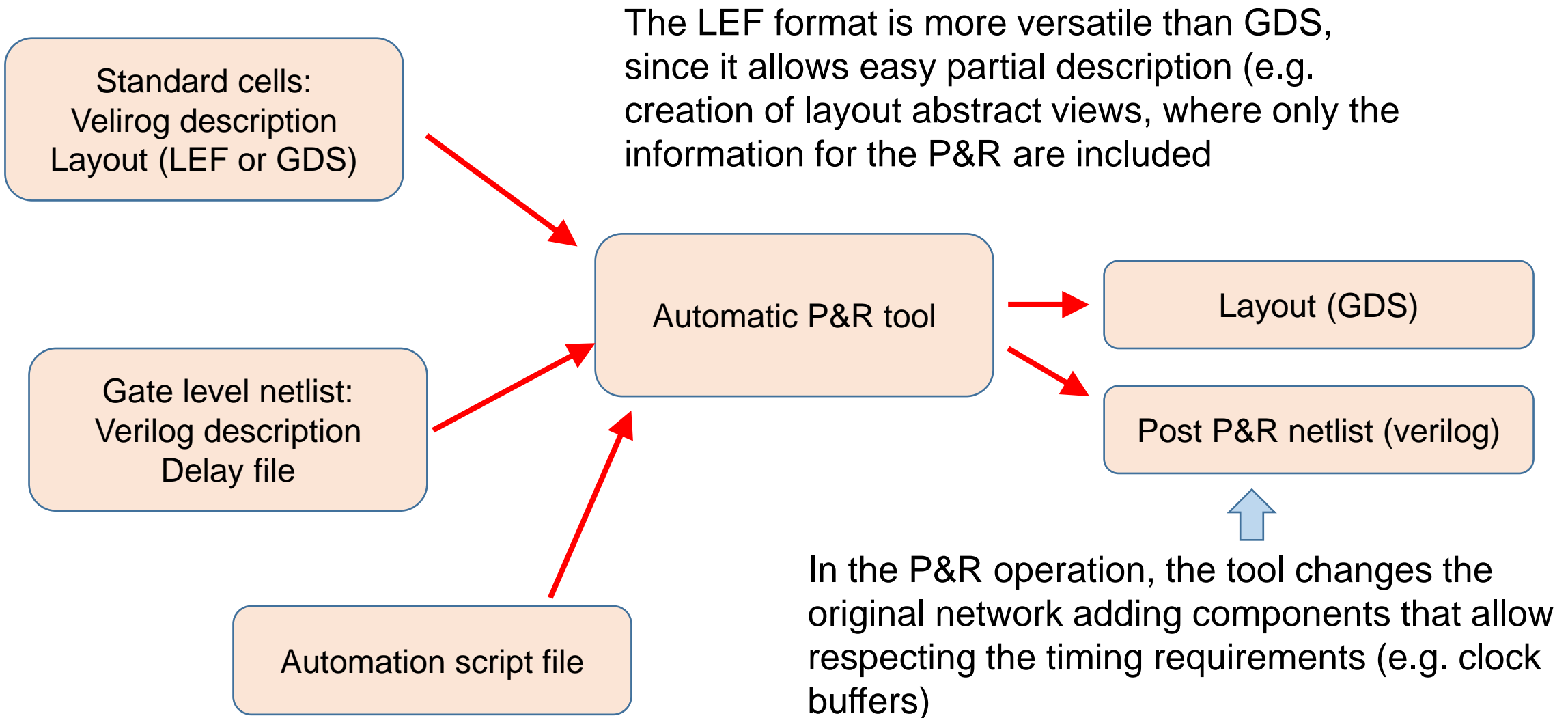Automatic layout generation (Automatic Place and Route, P&R)





Automatic Place-and-Route (INNOVUS)

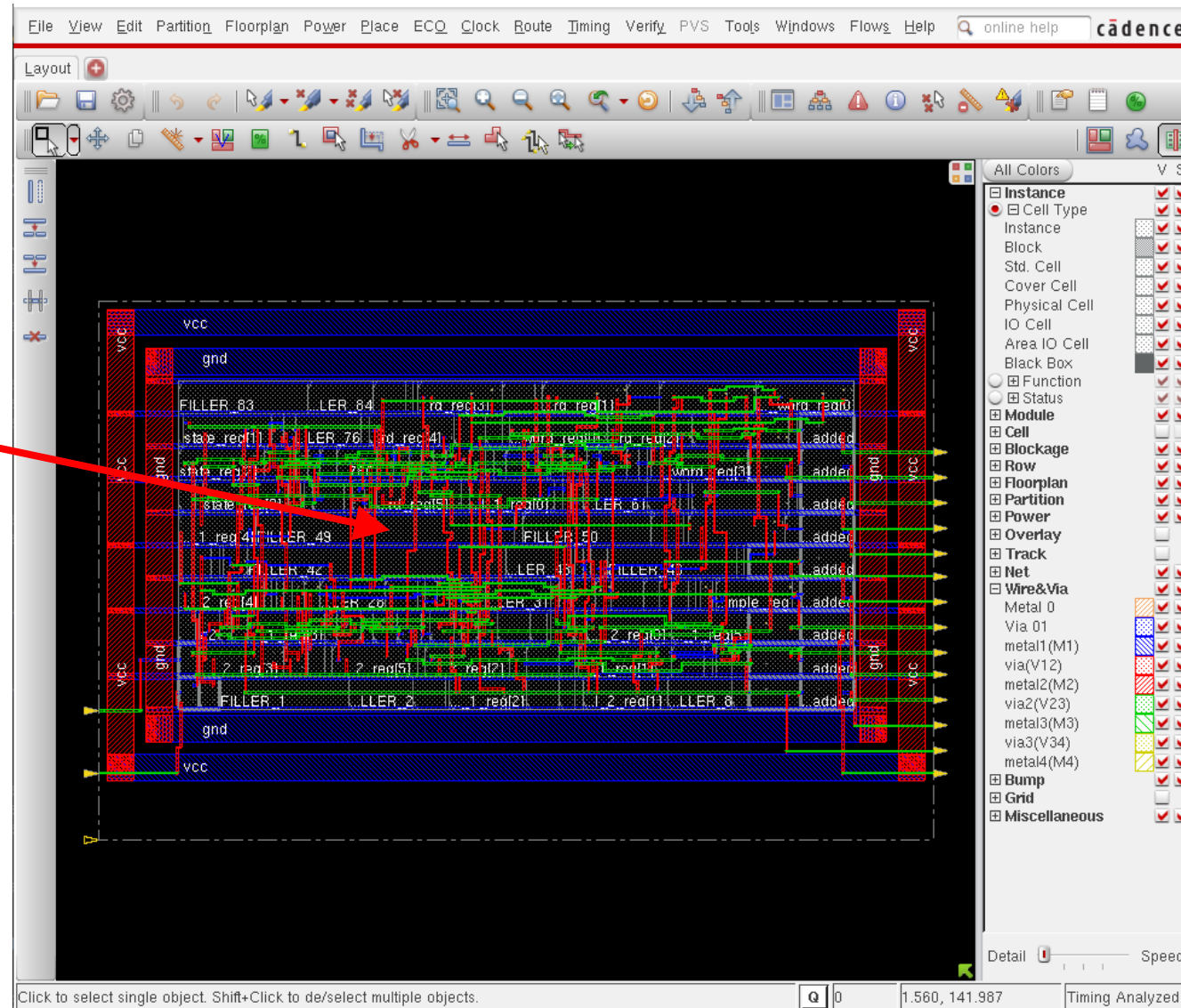Empty spaces between cells are covered by "filler" elements in the final layout. Fillers include n-wells and other layers that improve continuity between cells




Layout imported in Virtuoso

 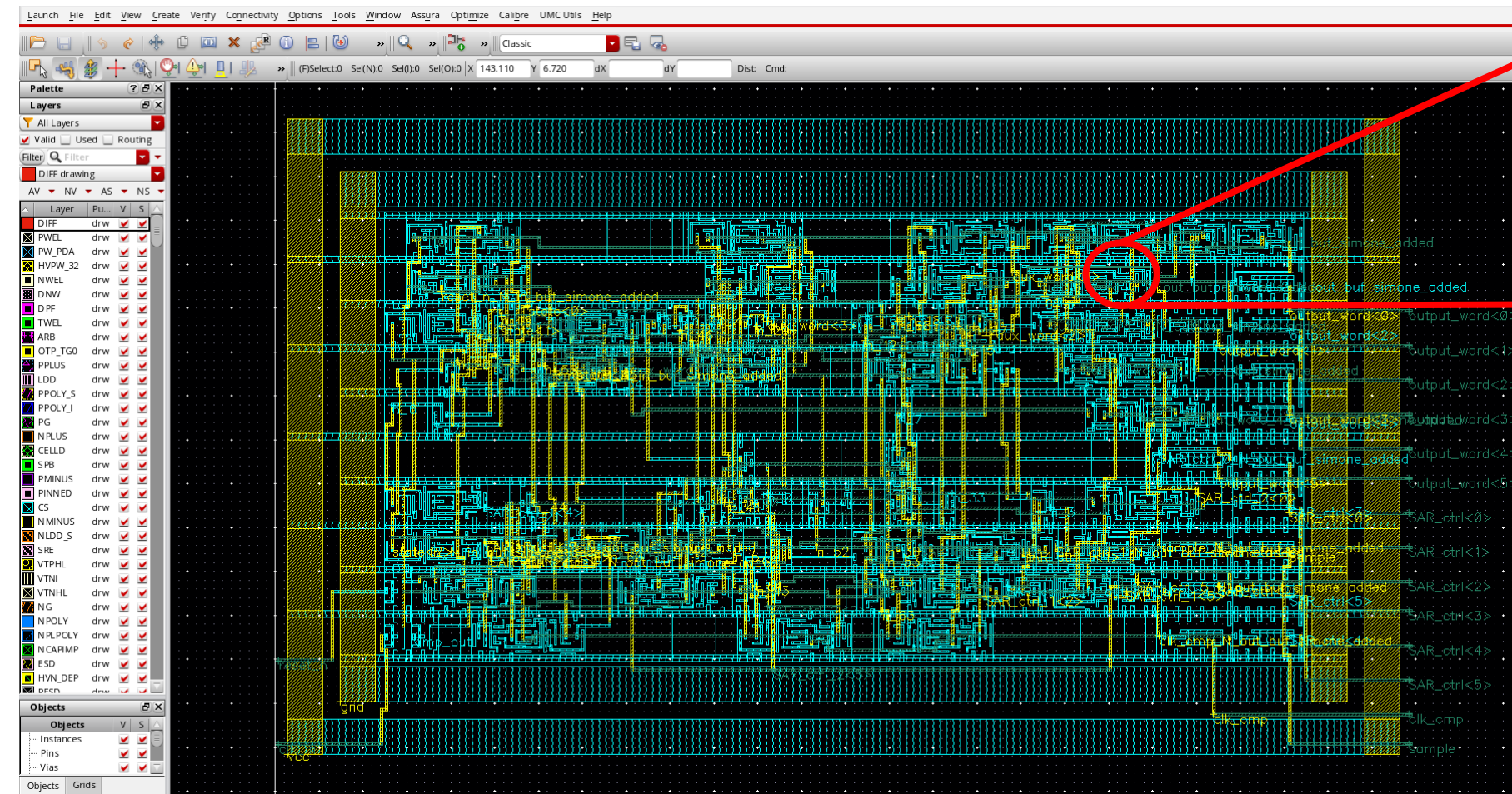


Abstract view of
D Flip-Flop

Mixed-Signal Simulations (ams simulator)

Config view of the testbench

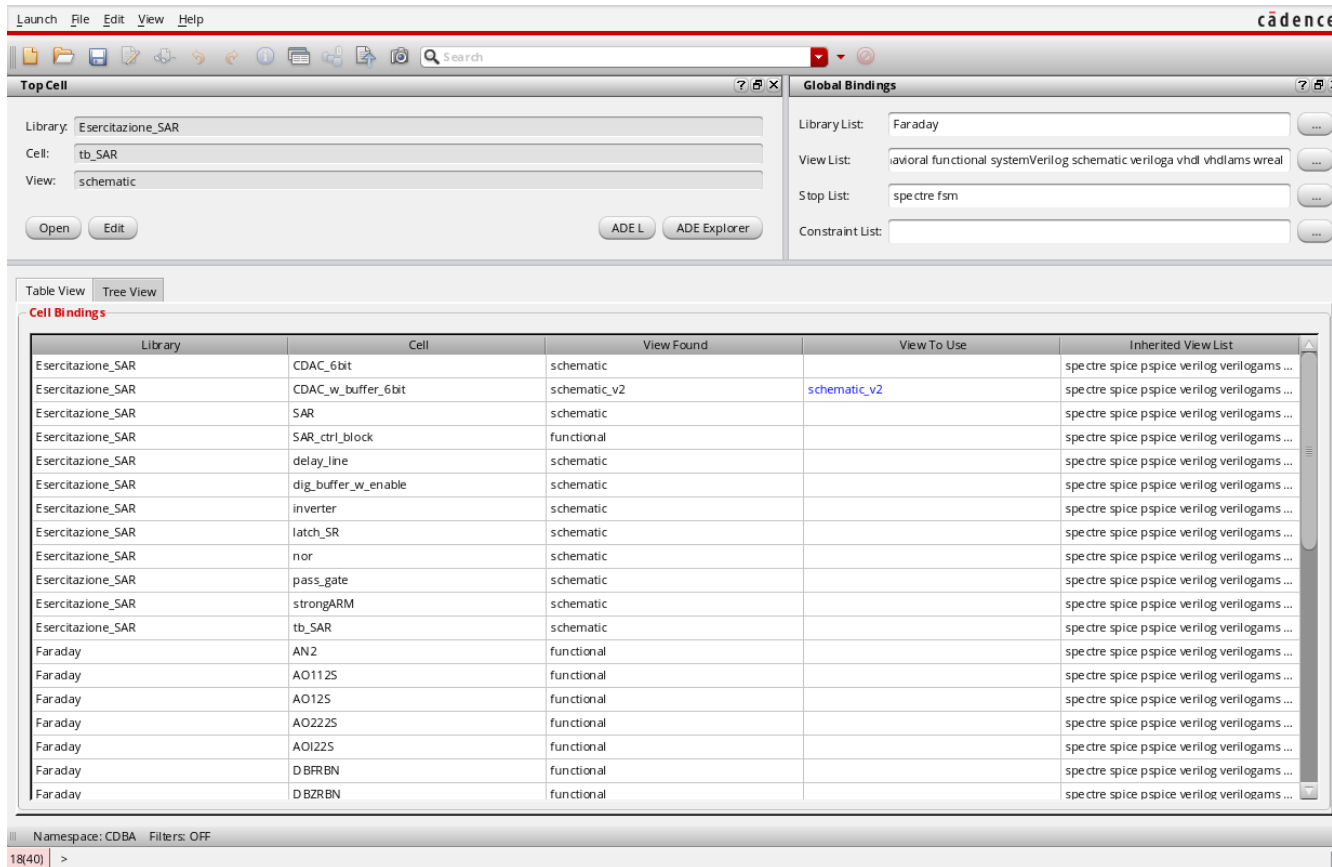

Connect rules

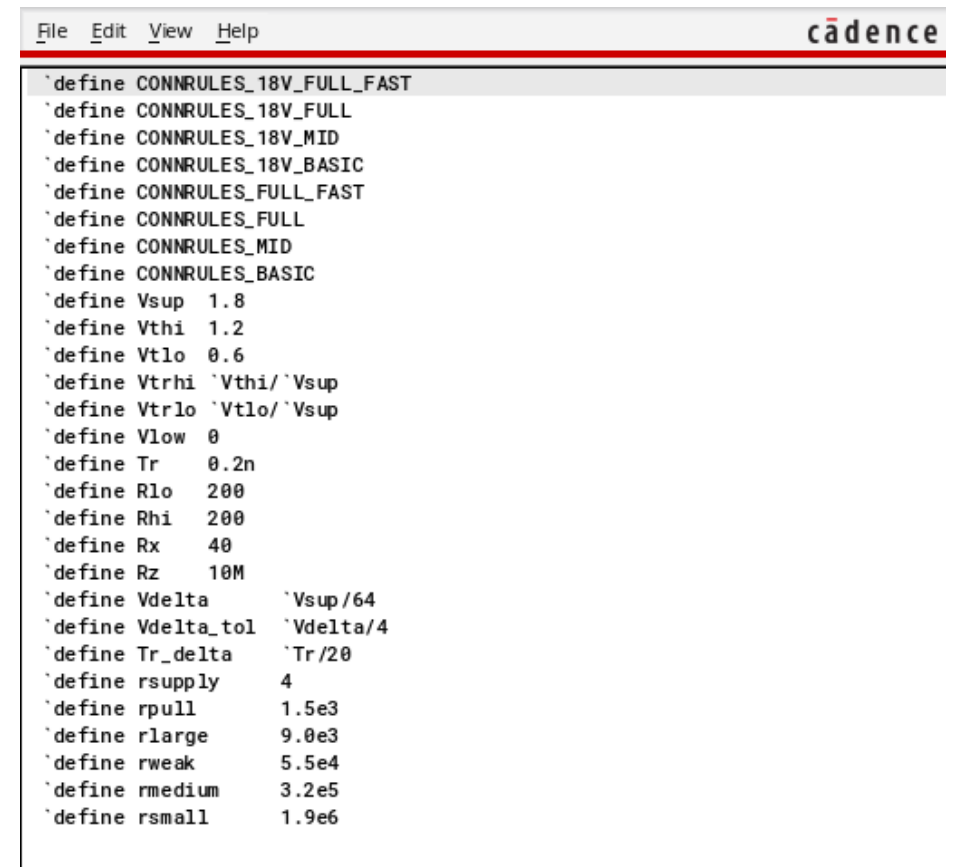

Mixed-Signal Simulations

