SISTEMI EMBEDDED AA 2013/2014


SOPC DE2 Basic Computer
Parallel port

Federico Baronti

DE2 Basic Computer


- Nios II configuration provided by Altera University Program
 - Core: Nios II/e
 - Memory: SDRAM, RAM, On-chip memory
 - Parallel ports: Red_LEDs, Green_LEDs,
 HEX3_HEX0, HEX7_HEX4, Slider_switches,
 Pushbuttons, etc.
 - Other peripherals: JTAG UART, Serial_port,
 Interval_timer, sysid

DE2 Basic Computer (cont.)

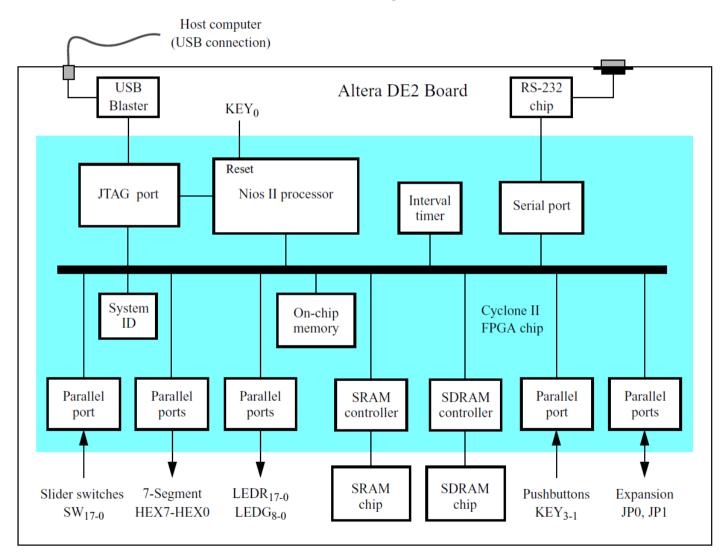

Parallel port (1)

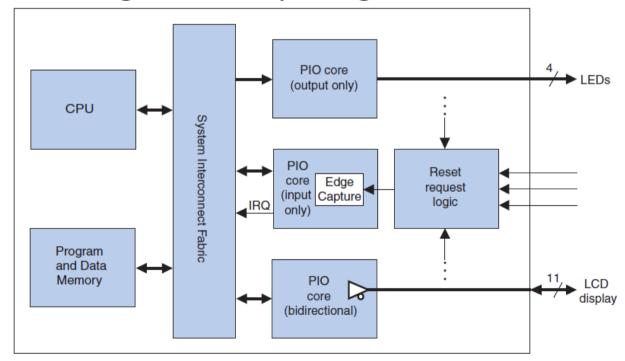- Interface for general purpose I/O
 - Based on Altera's PIO core customized for DE-series boards
 - Controlling LEDs, acquiring data from Switches, etc.




Parallel port (2)

- 4 32-bit memory-mapped registers
- n actual number of I/O pins

Table 2. Parallel Port register map				
Offset in bytes	Register name		Read/Write	Bits $(n-1)0$
0	data	Input	R	Data value currently on Parallel Port inputs.
		Output	W	New value to drive on Parallel Port outputs.
4	direction		R/W	Individual direction control for each I/O port.
				A value of 0 sets the direction to input; 1 sets
				the direction to output.
8	interruptmask		R/W	IRQ enable/disable for each input port. Set-
				ting a bit to 1 enables interrupts for the corre-
				sponding port.
12	edgecapture		R/W	Edge detection for each input port.

Parallel port (3)

Managing PIO in C program:

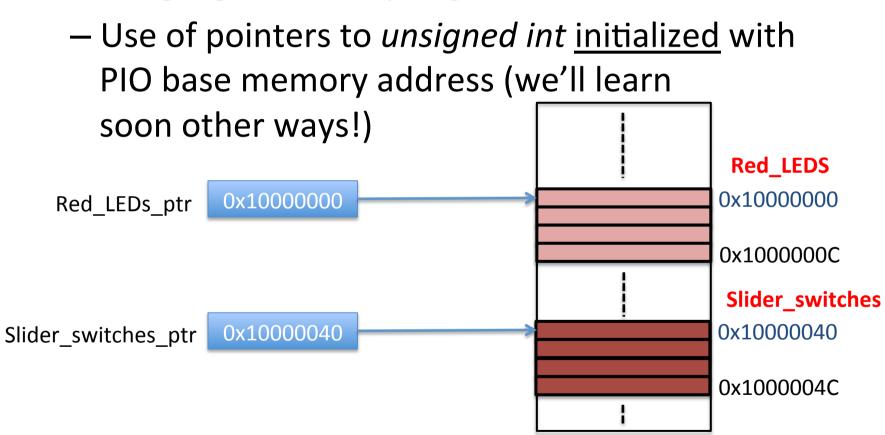

Parallel port (4)

- Why volatile attribute?
 - I/O registers may change even if the program does not modify them!
 - The peripheral hardware may modify their contents
 - Volatile tell the compiler do not make any optimization to the code involving an object declared with the volatile attribute

Parallel port (5)

Reading/Writing I/O registers:


```
*red_LED_ptr = *Slider_switches_ptr;
```

Putting into practice (1)

- Let's start our first program with Nios II processor
 - Control each DE2 red LED status through the corresponding slider switch (LEDR $_i$ = Sw $_i$)

Putting into practice (2)

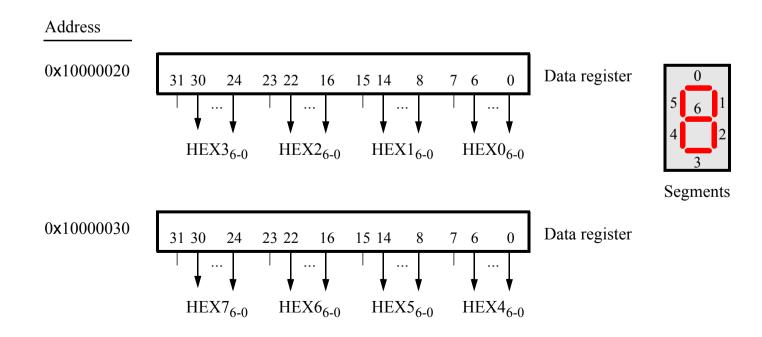- To go on:
 - 1. Show on the 4x 7-Seg HEX3_HEX0 display the 4 <u>hexadecimal</u> digits of the 16-bit <u>unsigned</u> number $(Sw_{15}-Sw_0)$



Putting into practice (3)

- To go on:
 - 2. Show on the 4x 7-Seg HEX3_HEX0 display the 4 decimal digits of the 16-bit unsigned number $(Sw_{15}-Sw_0)$ if the number can be represented; **E** otherwise
 - 3. Allow the user to choice the representation between hexadecimal and decimal by the slider Sw_{17}

Putting into practice (4)

• To go on:

- 4. Show on the 4x 7-Seg HEX3_HEX0 display the module of the 16-bit signed number (Sw_{15} - Sw_0) and on LEDG₈ the sign of the number (LEDG₈ is ON if and only if the number is negative). Show the module using hexadecimal and decimal digits as before
- 5. Allow the user to choice if $(Sw_{15}-Sw_0)$ code an <u>unsigned</u> or <u>signed</u> number by the slider Sw_{16}
- 6. Combine all the features in a single program

References

- Altera "Basic Computer System for the Altera DE2 Board"
- Altera "Parallel Port for Altera DE-Series Boards"